

EECS150 - Digital Design

Lecture 25 – Shifters and Counters

Nov. 21, 2013
 Prof. Ronald Fearing
 Electrical Engineering and Computer
 Sciences
 University of California, Berkeley

(slides courtesy of Prof. John Wawrzynek)

<http://www-inst.eecs.berkeley.edu/~cs150>


Fall 2013

EECS150 - Lec25-shift-count


Page 1

Recap


- Carry Look-ahead Adder

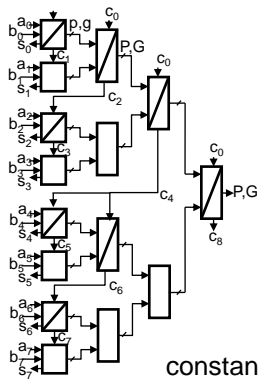


constant coefficient multiplication

 

- Carry save adder

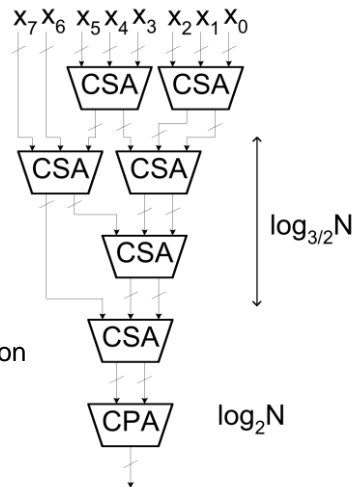

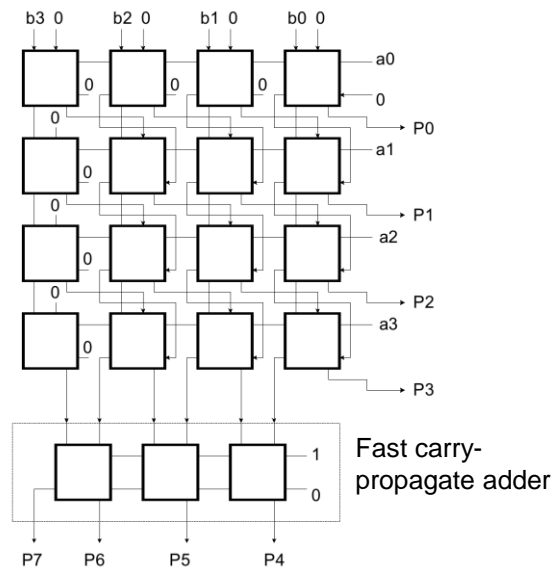
Recap: multiply using carry save addition



3


Recap “Constant Coefficient Multiplication” (KCM)

 Binary multiplier: $Y = 231 * X = (2^7 + 2^6 + 2^5 + 2^2 + 2^1 + 2^0) * X$




- CSD helps, but the multipliers are limited to shifts followed by adds.

 - CSD multiplier: $Y = 231 * X = (2^8 - 2^5 + 2^3 - 2^0) * X$



- How about shift/add/shift/add ...?

 - KCM multiplier: $Y = 231 * X = 7 * 33 * X = (2^3 - 2^0) * (2^5 + 2^0) * X$




- No simple algorithm exists to determine the optimal KCM representation.
- Most use exhaustive search method.

Outline


- *Shifters*
- *Counters*

5


Fixed Shifters / Rotators

 

Logical
Shift

 


Rotate

 

Arithmetic
Shift

Variable Shifters / Rotators

 - Example: $X \gg S$, where S is unknown when we synthesize the circuit.
- Uses: shift instruction in processors (ARM includes a shift on every instruction), floating-point arithmetic, division/multiplication by powers of 2, etc.
- One way to build this is a simple shift-register:
 - a) Load word, b) shift enable for S cycles, c) read word.



- Worst case delay $O(N)$, not good for processor design.
- Can we do it in $O(\log N)$ time and fit it in one cycle?


Fall 2013

EECS150 - Lec25-shift-count

Page 7

Log Shifter / Rotator

- $\log(N)$ stages, each shifts (or not) by a power of 2 places, $S=[s_2;s_1;s_0]$:

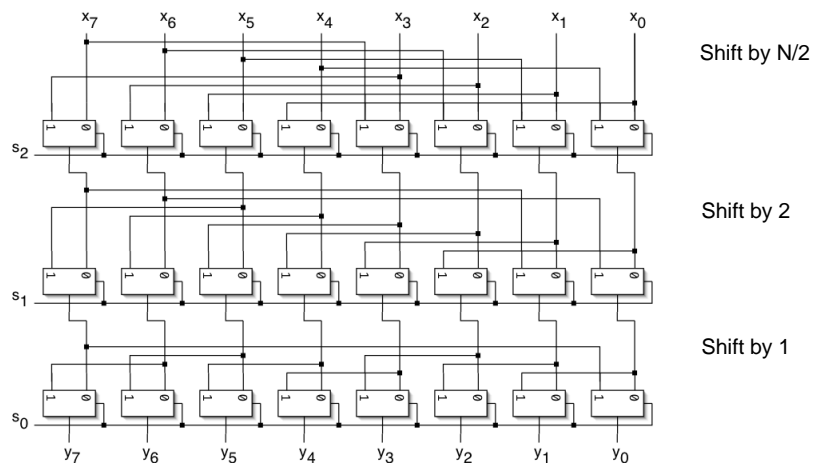


Fall 2013

EECS150 - Lec25-shift-count

Page 8



LUT Mapping of Log shifter

 

Efficient with 2to1 multiplexors, for instance, 3LUTs.

Virtex5 has 6LUTs. Naturally makes 4to1 muxes:


Reorganize shifter to use 4to1 muxes.

  

Final stage uses F7 mux


“Improved” Shifter / Rotator

 - How about this approach? Could it lead to even less delay?




- What is the delay of these big muxes?
- Look at transistor-level implementation?


Barrel Shifter

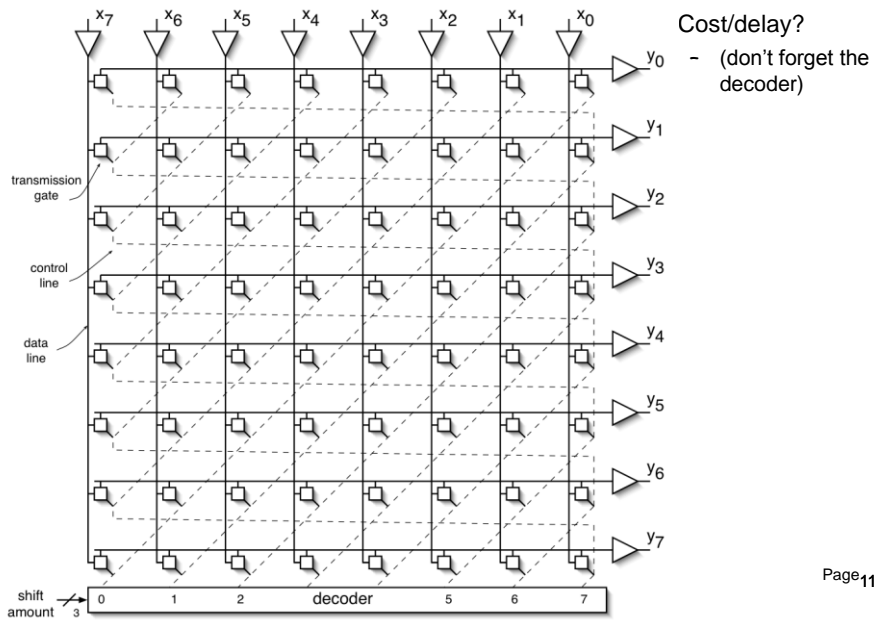

Connection Matrix

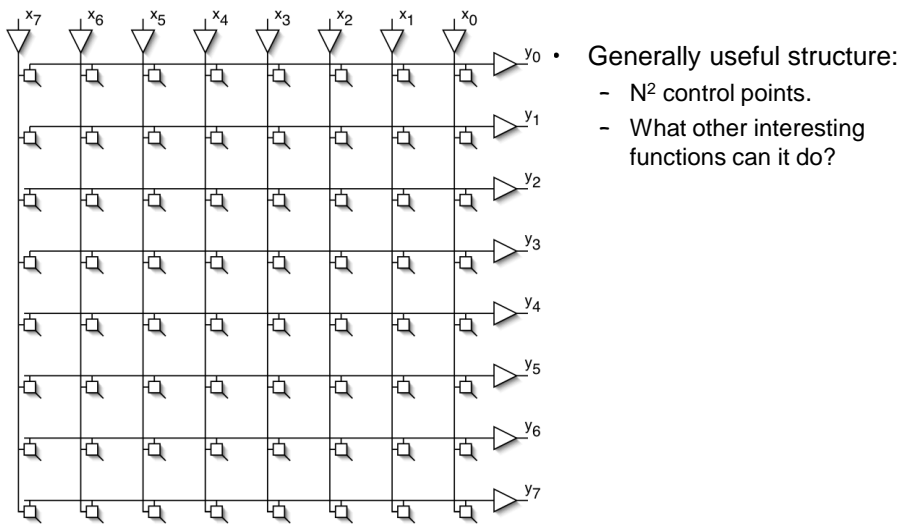

Cross-bar Switch

 

$N \log(N)$ control signals.

Supports all interesting permutations

- All one-to-one and one-to-many connections.

Commonly used in communication hardware (switches, routers).

Page13

Outline


- Shifters
- Counters

Counters

- Special sequential circuits (FSMs) that repeatedly sequence through a set of outputs.
- Examples:
 - binary counter: 000, 001, 010, 011, 100, 101, 110, 111, 000,
 - gray code counter: 000, 010, 110, 100, 101, 111, 011, 001, 000, 010, 110, ...
 - one-hot counter: 0001, 0010, 0100, 1000, 0001, 0010, ...
 - BCD counter: 0000, 0001, 0010, ..., 1001, 0000, 0001
 - pseudo-random sequence generators: 10, 01, 00, 11, 10, 01, 00, ...
- Moore machines with “ring” structure in State Transition Diagram:


Fall 2013

EECS150 - Lec25-shift-count

 Page₁₅

What are they used for?

 - Counters are commonly used in hardware designs because most (if not all) computations that we put into hardware include iteration (looping). Examples:
 - Shift-and-add multiplication scheme.
 - Bit serial communication circuits (must count one “words worth” of serial bits).
- Other uses for counter:
 - Clock divider circuits



- Systematic inspection of data-structures
 - Example: Network packet parser/filter control.
- Counters simplify “controller” design by:
 - providing a specific number of cycles of action,
 - sometimes used with a decoder to generate a sequence of timed control signals.
 - Consider using a counter when many FSM states with few branches.


Fall 2013

EECS150 - Lec25-shift-count

Page₁₆

Controller using Counters

 - Example, Bit-serial multiplier (n^2 cycles, one bit of result per n cycles):



- Control Algorithm:

```

repeat n cycles { // outer (i) loop
  repeat n cycles{ // inner (j) loop
    shiftA, selectSum, shiftHI
  }
  shiftB, shiftHI, shiftLOW, reset
}

```

Note: The occurrence of a control signal x means $x=1$. The absence of x means $x=0$.

Fall 2013


EECS150 - Lec25-shift-count

Page₁₇

Controller using Counters

- **State Transition Diagram:**

- Assume presence of two binary counters. An “i” counter for the outer loop and “j” counter for inner loop.

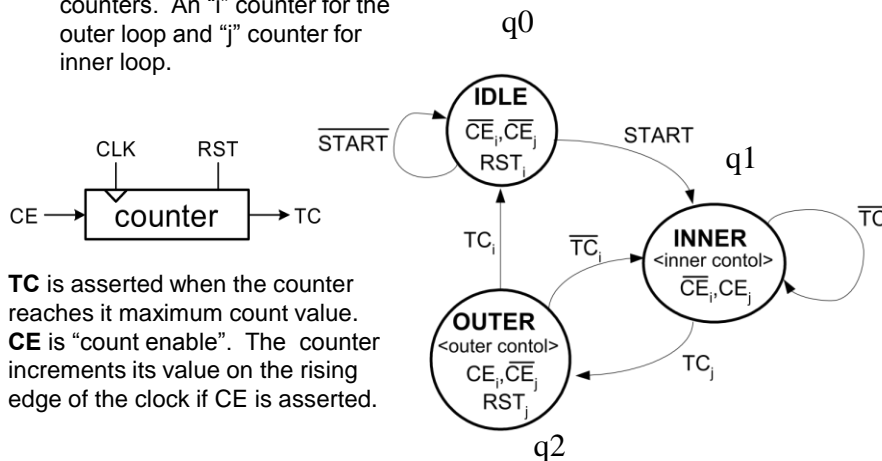


Fall 2013

EECS150 - Lec25-shift-count

Page₁₈

Controller using Counters

- **Controller circuit implementation:**

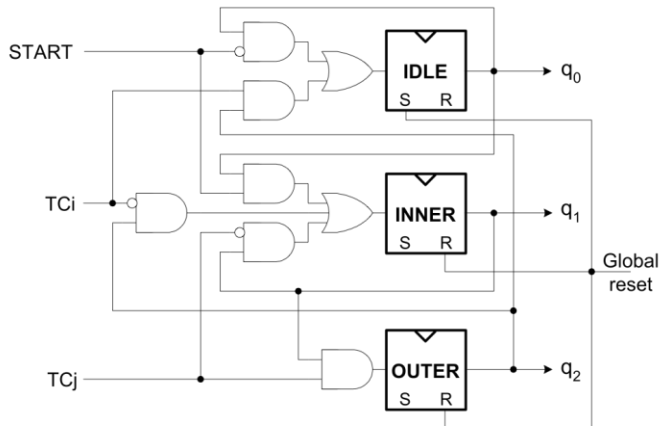

- **Outputs:**

$$\begin{aligned} CE_i &= q_2 \\ CE_j &= q_1 \\ RST_i &= q_0 \\ RST_j &= q_2 \end{aligned}$$

$$\begin{aligned} \text{shiftA} &= q_1 \\ \text{shiftB} &= q_2 \\ \text{shiftLOW} &= q_2 \\ \text{shiftHI} &= q_1 + q_2 \\ \text{reset} &= q_2 \\ \text{selectSUM} &= q_1 \end{aligned}$$


Fall 2013

EECS150 - Lec25-shift-count

Page19

How do we design counters?

 - For binary counters (most common case) incremter circuit would work:



- In Verilog, a counter is specified as: $x = x + 1$;
 - This does *not* imply an adder
 - An incremter is simpler than an adder
 - And a counter might be simpler yet.
- In general, the best way to understand counter design is to think of them as FSMs, and follow general procedure, however some special cases can be optimized.

Fall 2013

EECS150 - Lec25-shift-count

Page20

Synchronous Counters

All outputs change with clock edge.


- Binary Counter Design:
Start with 3-bit version and generalize:

c	b	a	c ⁺	b ⁺	a ⁺
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

$$a^+ = a'$$

$$b^+ = a \text{ xor } b$$

$$\begin{aligned} c^+ &= abc' + a'b'c + ab'c + a'bc \\ &= a'c + abc' + b'c \\ &= c(a'+b') + c'(ab) \\ &= c(ab)' + c'(ab) \\ &= c \text{ xor } ab \end{aligned}$$

 


Fall 2013

EECS150 - Lec25-shift-count


Page21

Synchronous Counters

 - How do we extend to n-bits?
- Extrapolate c⁺: d⁺ = d xor abc, e⁺ = e xor abcd



 - Has difficulty scaling (AND gate inputs grow with n)




- CE is "count enable", allows external control of counting,
- TC is "terminal count", is asserted on highest value, allows cascading, external sensing of occurrence of max value.

Fall 2013


EECS150 - Lec25-shift-count

Page22

Synchronous Counters

 

- How does this one scale?
- ⊕ Delay grows $\sim n$
- Generation of TC signals very similar to generation of carry signals in adder.
- "Parallel Prefix" circuit reduces delay:

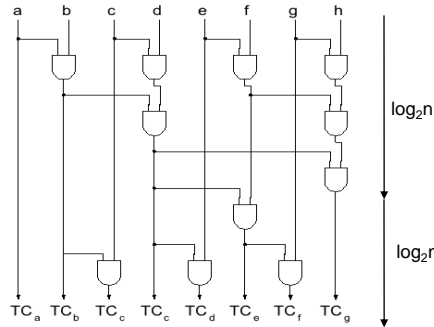


Fall 2013

EECS150 - Lec25-shift-count

Page23

Up-Down Counter

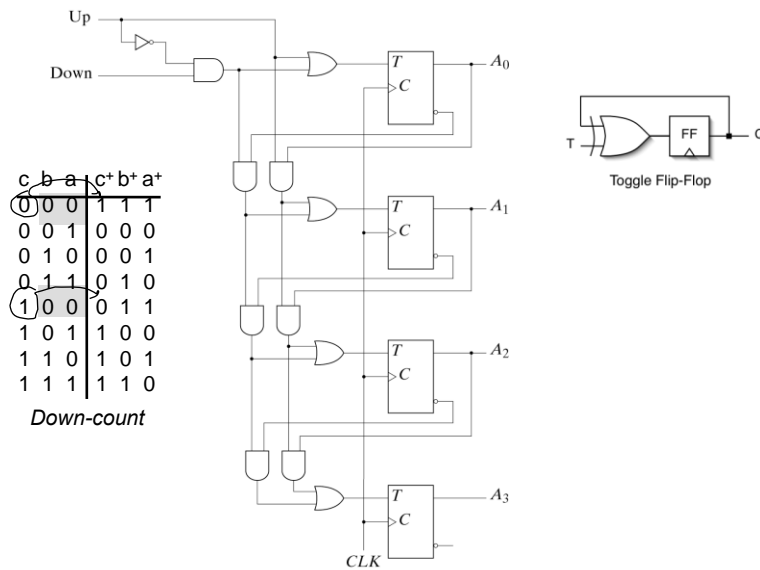



Fall 2013

Fig. 6-13 4-Bit Up-Down Binary Counter

Page24

Odd Counts

- Extra combinational logic can be added to terminate count before max value is reached:
- Example: **count to 12**
- Alternative:

  


Fall 2013

EECS150 - Lec25-shift-count


Page25

Ring Counters

 - “one-hot” counters
0001, 0010, 0100, 1000, 0001, ...
- What are these good for?



“Self-starting” version:

 


Fall 2013

EECS150 - Lec25-shift-count

Page26

Johnson Counter

 

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	AB'
3	1	1	0	0	BC'
4	1	1	1	0	CE'
5	1	1	1	1	AE
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding

Fall 2013

Fig. 6-18 Construction of a Johnson Counter

Page27

Asynchronous "Ripple" counters

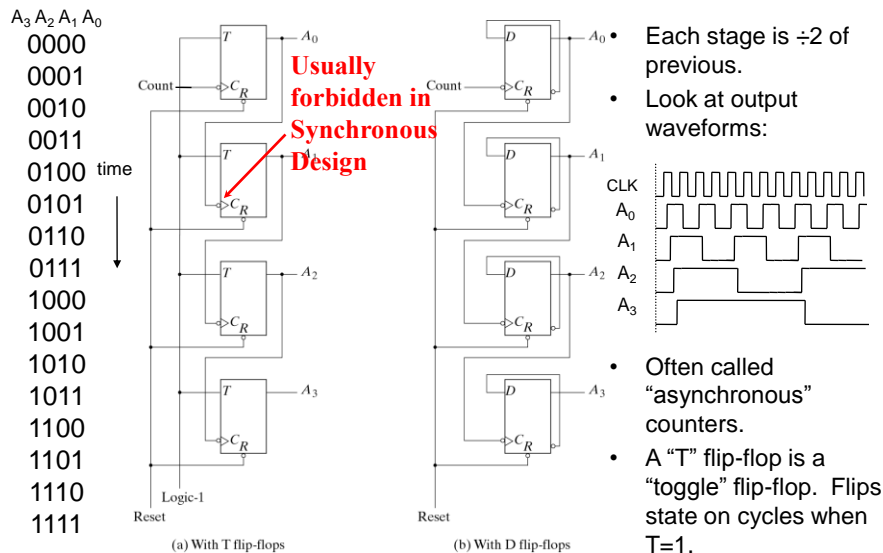



Fig. 6-8 4-Bit Binary Ripple Counter
EECS150 - Lec25-shift-count

Fall 2013



Page28

Summary

- Shifters

 

- Counters

  

29