
 


(Vers 1.1)



Problem 1: Adders.

For each part, use 4 bit blocks, 2 input gates only. Estimate number of 2 input gates used (assume AND, NAND, OR, NOR, and that inverters can be considered part of 2 input gates). Also estimate worst case delay.

a. A 16 bit ripple carry adder.

 


  XOR has 3 2-input gates. 1-bit FA has 9 gates when not using P,G and the carry or 8 gates when using P,G but not the carry.



Gate delay through first FA to carry out is 4 unit delays. Then 2 unit delays from carry in to carry out of the other FAs. Thus, first 4 bit FA has $4+2*3=10$ delay. All others have 8 (just carry propagation). Therefore 16-bit FA has $10+8*3= \sim 34$ unit delay.

1b. A 16 bit carry look ahead adder.

 


- 4x8 gates FA with P&G (no Cout from the 1 bit FA) [32 gates]
- $C_1 = G_0 + C_{in}P_0$ [2 gates]
- $C_2 = G_1 + C_1P_1 = G_1 + P_1G_0 + C_{in}P_1P_0 = (G_1 + P_1G_0) + C_{in}(P_1P_0)$ [5 gates]
- $C_3 = G_2 + P_2C_2 = G_2 + P_2G_1 + P_2P_1C_1 = G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_{in} = ((G_2 + G_1P_2) + G_0(P_1P_2)) + C_{in}((P_0P_1)P_2)$ [9 gates]
- $P = (P_0P_1)(P_2P_3)$ [3 gates]
- $G = G_3 + G_2P_3 + G_1P_2P_3 + G_0P_1P_2P_3 = ((G_3 + G_2P_3) + (G_1P_2)P_3) + (G_0P_1)(P_2P_3)$ [9 gates]
- $C_{out} = G + C_{in}P$ [2 gates]

Total: 62 gates

- Delays for 4 bit CLA: $\{A,B\} \rightarrow \{P_i, G_i\}$ 1 delay
- $\{A,B\} \rightarrow P$ 3 delays
- $\{A,B\} \rightarrow G$ 5 delays
- $\{P,G,C_{in}\} \rightarrow C_{out}$ 2 delays

 Thus for a single 4 bit CL adder, delay from C_{in} to C_{out} will be 6 unit delays.



For 16 bit adder, need 4X62 gates for each 4 bit block, then 30 for P-G network, Total = 278 gates.



After 1 delay, all FA P-G are settled. After 4 more delay, all 4LA P,G out are settled. Then, for the main P-G network, need another 2, 3, 4, and 4 delay for the C1, C2, C3, and Cout signals to settle. (Note that for highest level P-G block, C1 out is C4in for the [7:4] adder, C3 out is C12in for [15:12] adder.) Thus, highest 4LA will be the one on the critical path and have its C12in settle by delay 1+4+4=9. Need another 2 delays to generate C15in from C12in:

$$[C15 = ((G2 + G1P2) + G0(P1P2)) + C12in((P0P1)P2)]$$

Inside the P-G network for the [15:12] 4LA block. And then 2 unit delays to incorporate the C15 carry input into the FA S[15] output. Thus, have a total of 9+2+2=13 delay.

1c. A 16 bit carry select adder.

  From part 1a, we had 10 unit delay from {A0,B0,Cin} to Cout, with 4 delays to first carry out, and 2 for each additional delay. If we consider two different 4 bit adders, one with Cin=0, and one with Cin=1, we can make it faster. Now first carry out will have one delay from {A0,B0}, so total will be 7 delays instead of 10.



$\sim 8 \cdot 36 + 4 \cdot 3 + 4 \cdot 4 \cdot 3 = 348 \text{ gates}$

16-bit carry select adder

Note, each 1-bit 2:1 mux requires 3 gates and has delay of 2. Also, note that if Cin is ready near beginning of cycle, can convert carry-select adder for bits 3:0 to ripple-carry adder and save 48 gates. Looking at carry propagation, need 10 delays for each FA to output a carry. Then, 8 delays for that carry to ripple through the muxes. Thus, this **requires 18 delay (16 if the lowest adder is simplified)**. If we use the FA optimized with carry in tied to zero or one, we have 7 adder delays + 2 mux delays to get C8 select + 2 delays to get C12 select + 2 delays to get Cout select = 15 delays.


2. (35 pts) Multiplier

Design an unsigned combinational multiplier (no flip-flops or controller) for multiplying the unsigned constant value $199 = 0xC7$ by the 4 bit variable $Z[3:0]$. Using only full-adder cells and inverters, draw a circuit that implements the multiplier using carry-save addition. Estimate delay from input to output. How many full-adder cells are needed?

$$\begin{aligned}
 2. \quad A \cdot 0xC7 &= A \cdot 0b11000111 = A \cdot (0b11000000 + 0b1000 - 0b1) \\
 &= A \cdot (1\ll 7 + 1\ll 6 + 1\ll 3 - 1\ll 0) \\
 &= A \cdot (\underbrace{1\ll 7 + 1\ll 3}_{\text{concatenation}}) + (\underbrace{1\ll 6 - 1\ll 0}_{\text{concatenation + carry}})
 \end{aligned}$$


recall: $-A = \sim A + 1$

highly optimized solution:

 

(11-bit FA can be reduced to 5 FA and 6 HA)

simpler solution

 

Note that constant shifters just append 0s to the input value. Optimized solution has delay only associated with the 11-bit FA. From analysis in 1, this will have delay of around $4 + 2 \cdot 10 = 24$ (if using ripple carry) or 13 (if using carry lookahead). For the simpler solution, each carry-save level adds about 4-gate delay (2 if willing to spend more area).

Problem 3:

The charts with the logical values substituted in after interpreting the table and voltage specifications are as follows:

Determine the Boolean functions for the following:

a. $Z.H = f(X.H, Y.H)$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

b. $C.L = f(X.H, Y.H)$

X	Y	C
0	0	0
0	1	1
1	0	1
1	1	1

c. $C.L = f(A.L, B.L)$

A	B	C
1	1	0
1	0	1
0	1	1
0	0	1

d. $Z.H = f(X.H, A.L)$

X	A	Z
0	1	1
0	0	0
1	1	0
1	0	0

Thus:

- A. $Z = !(X+Y)$
- B. $C = X+Y$
- C. $C = !(AB)$
- D. $Z = (!X)A$