

**Due at 10 am, Thu. Sep. 12 (location tbd)**

Reading Harris and Harris: 1.1-1.6, 2.1-2.6, 4.1-4.3, 4.5, 4.8

1. (10 pts) Perform the following number system conversions (assume unsigned binary):

- a.  $0010\ 0011\ 1001_2 = ?_8 = ?_{10} = ?_{16}$     b.  $111.1001_2 = ?_8 = ?_{10} = ?_{16}$   
 c.  $?_2 = ?_8 = ?_{10} = 1A0_{16}$     d.  $?_2 = ?_8 = ?_{10} = 3.133_{16}$   
 e.  $?_2 = ?_8 = 232.5_{10} = ?_{16}$

2. (15 pts) Arithmetic:

- a. Showing your calculations, add  $108_{10}$  and  $117_{10}$  in base 2, 10, and sixteen.  
 b. Showing your calculations, multiply  $123_4$  and  $231_4$  in base 2, 10, and sixteen.  
 c. Showing your calculations, use long division to find  $1110\ 0010_2$  divided by  $1001_2$ .

3. (15 pts) DC Transfer Characteristics

Harris & Harris exercise 1.78.

4. (10 pts) 2-input Mux

Using a minimum number of 2:1 muxes, draw a diagram showing designs for NOT, and 2-input AND, OR, and XOR functions. You may use static inputs “0” and “1” to the muxes in addition to the function inputs.

5. (10 pts) Look-up Tables

You are given a look-up table (LUT) with 2 binary addresses and one input. Show how these 2 input LUTs can be combined to perform ANY 4 input logic function.

6. (10 pts) Boolean algebra

Reduce the following Boolean expressions using theorems and identities and express in Sum-of-Products form (luckily now done by synthesis tools):

- a.  $F = A(B + \overline{C})D$   
 b.  $F = \overline{A} \cdot \overline{B} \cdot \overline{C}$   
 c.  $F = (A + \overline{B})(\overline{A} + B + C)(\overline{A} + B + \overline{C})$

7. (15 pts) Verilog

Write a Verilog module (with correct syntax) called `majority`. It receives three inputs `a`, `b`, and `c`. It produces one output `y` which is TRUE if 2 or more of the inputs are TRUE.

8. (15 pts) Verilog

Write a Verilog module (with correct syntax) called `PriorityEncoder` with 8 inputs `A[7:0]`, 3 bit output `Y[2:0]`, and binary output `None`. `Y` encodes the most significant “1” input bit in `A`. Output `None` is TRUE if all inputs `A[7:0]` are “0”. For example if `A = 0110 11112` then `Y = 1102`. (This is a priority encoder.)