
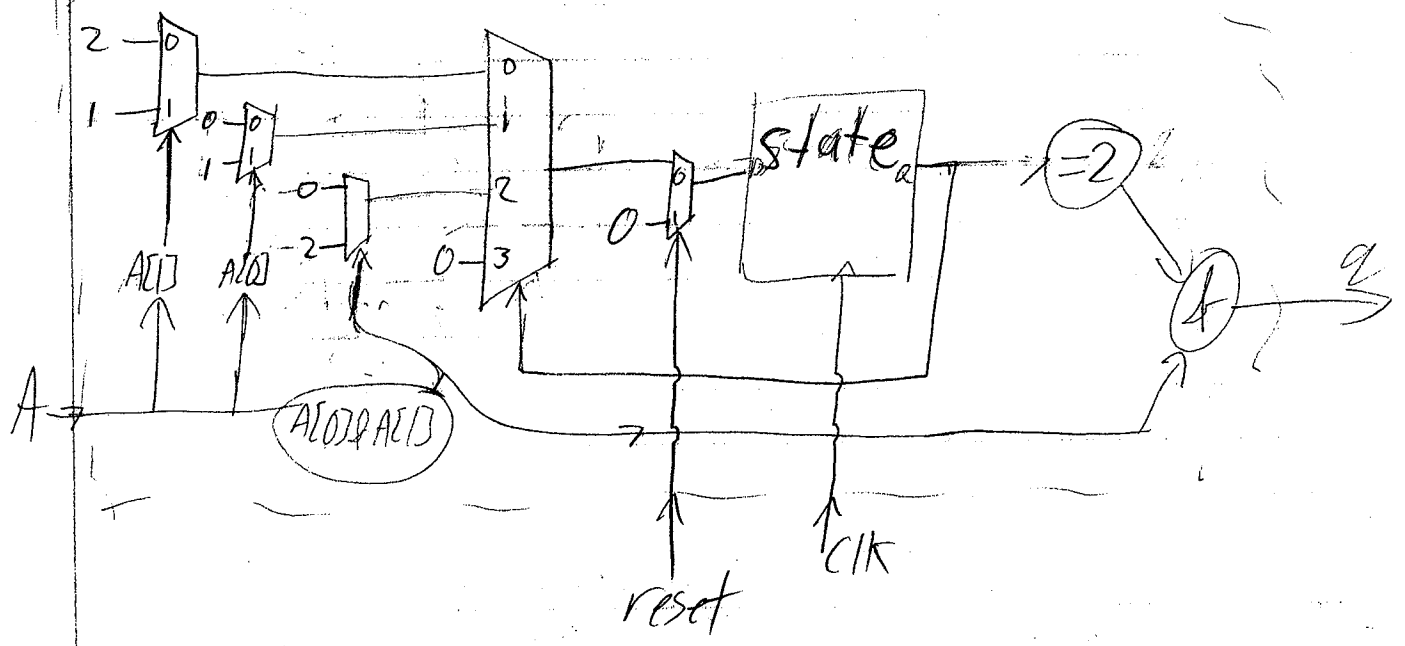


Problem 1.


a.

 

b.





c.


 


Problem 2

a)

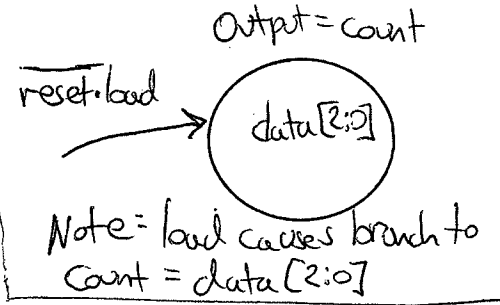 

b)

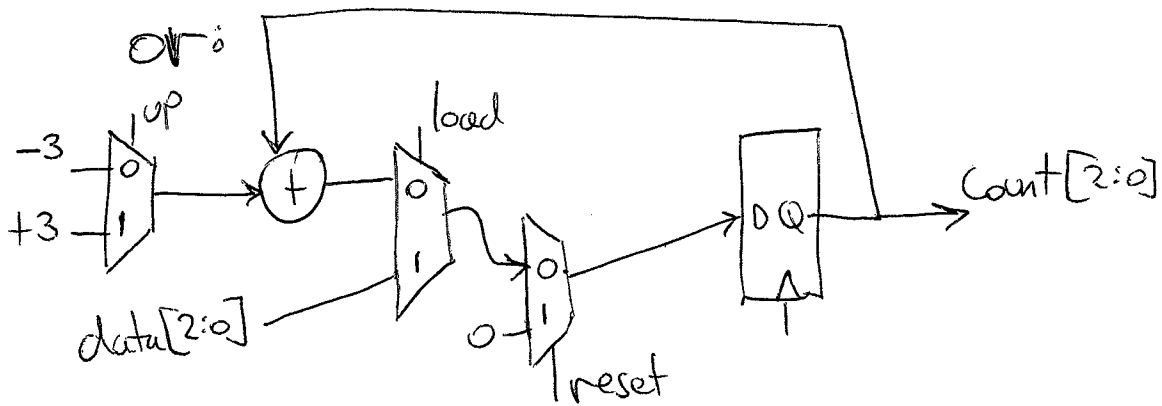 

Problem 2c

```
module hw2_2FSM_v1(  
    input clk, input reset,  
    input up, input load, input [2:0] data,  
    output [2:0] count  
);  
reg [2:0] state;  
  
always @(posedge clk)  
begin  
    if(reset)  
        state <= 0;  
    else if(load)  
        state <= data;  
    else if(up)  
        state <= state + 3;  
    else  
        state <= state - 3;  
end  
  
assign count = state;  
  
endmodule
```

Version 1

```
module hw2_2FSM_v2(  
    input clk, input reset,  
    input up, input load, input [2:0] data,  
    output [2:0] count  
);  
reg [2:0] state, nextstate;  
  
always @(posedge clk)  
begin  
    if(reset) state <= 0;  
    else state <= nextstate  
end  
  
always @(*)  
begin  
    nextstate <= state  
    if(load)  
        nextstate <= data;  
    else if(up)  
        nextstate <= state + 3;  
    else  
        nextstate <= state - 3;  
end  
  
assign count = state;  
  
endmodule
```

Version 2

} State update


} Next State
Decode

Problem 3

```
module summer(  
    input clk, input rst,  
    output [7:0] total, output done  
);  
    reg [3:0] addr_counter;  
    reg [7:0] accumulator;  
    wire [3:0] mem_out;  
  
    always @(posedge clk)  
    begin  
        if(rst) addr_counter <= 0;  
        else addr_counter <= addr_counter + 1;  
    end  
  
    RAM16x4S #(  
        // These constants can be anything but this part should be here.  
        .INIT_00(16'hffff), // INIT for bit 0 of RAM  
        .INIT_01(16'h0000), // INIT for bit 1 of RAM  
        .INIT_02(16'h0000), // INIT for bit 2 of RAM  
        .INIT_03(16'h0000), // INIT for bit 3 of RAM  
    ) RAM16x4S_inst (  
        .O0(mem_out[0]),  
        .O1(mem_out[1]),  
        .O2(mem_out[2]),  
        .O3(mem_out[3]),  
        .A0(addr_counter[0]),  
        .A1(addr_counter[1]),  
        .A2(addr_counter[2]),  
        .A3(addr_counter[3]),  
        .D0(0), // can be whatever  
        .D1(0), // can be whatever  
        .D2(0), // can be whatever  
        .D3(0), // can be whatever  
        .WCLK(0), // can be whatever  
        .WE(0) // THIS MUST BE HERE  
    );  
  
    always @(posedge clk)  
    begin  
        if(rst) accumulator <= 0;  
        else accumulator <= accumulator + mem_out;  
    end  
  
    assign total = accumulator;  
    assign done = addr_counter == 4'b1111;  
  
endmodule
```

} optional

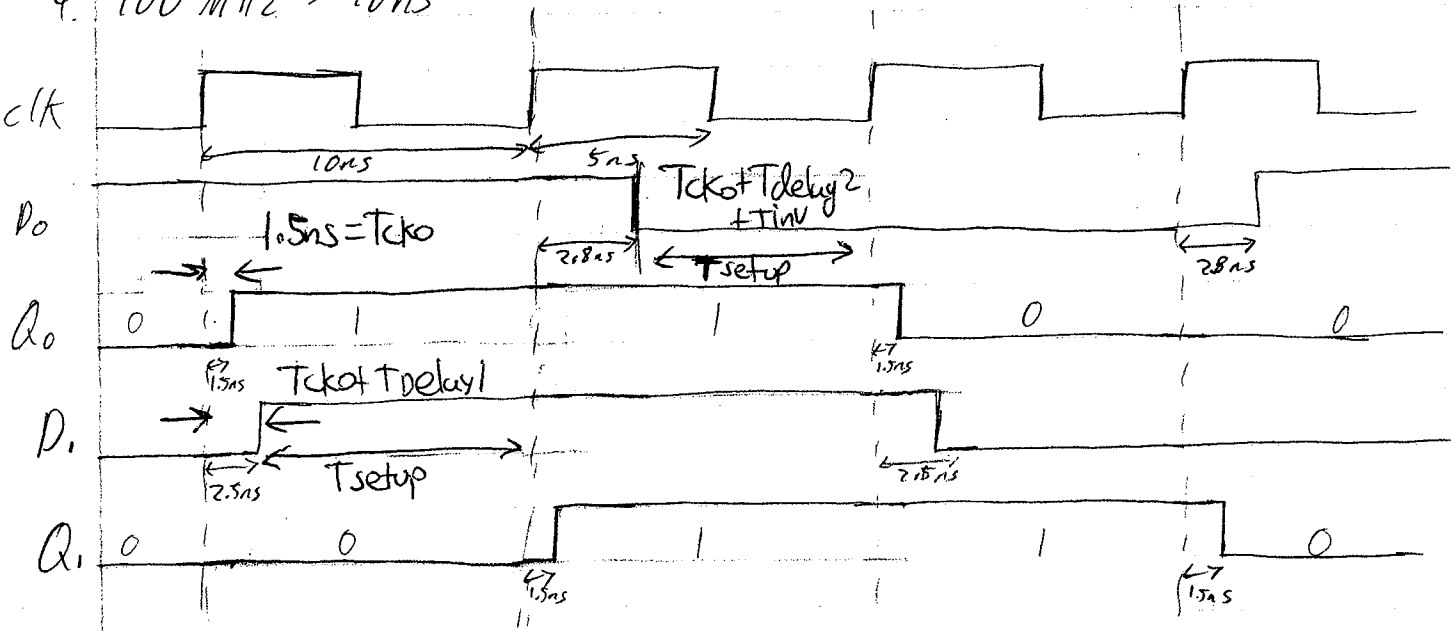4. $100 \text{ MHz} \rightarrow 10 \text{ ns}$



b. $2.8 \text{ ns} + 1.0 \text{ ns} = 3.8 \text{ ns}$ minimum clock period

$$b. \text{ min period} = \max \left\{ T_{ck0} + T_{delay1} + T_{setup}, T_{ck0} + T_{delay2} + T_{inv} + T_{setup} \right\}$$

$$= \max \left\{ 3.5, 3.8 \text{ ns} \right\}$$