


1. **(20 pts) Datapath and control I.** For the datapath below, determine a sequence of operations which will exchange the contents of `Acc` and `Sum`. (Contents of register `A` can be discarded). The data path is 8 bits wide. Φ is the clock.

a. Describe the necessary operations using a Register Transfer Level (RTL) description. How many clock cycles are required?


```
A ← Acc ;
Sum ← 0, Acc ← Sum ;
Sum ← Sum + A ;
```

3 clock cycles are required.

 b. Draw a functional timing diagram for the circuit including Φ , `LoadA`, `LoadSum`, `EnAdd`, `LoadAcc`, `ClearA`, `ClearSum` which shows the RTL operation of part a.



 c. Draw a state diagram for a controller which starting in `Idle`, when given a `Start` signal, will swap `Acc` and `Sum` and then go back to the `Idle` state.



Signals are only listed if asserted (i.e. set to 1).


2. **(30 pts) Datapath and control II.** For the datapath below, determine a sequence of operations which will perform the operation $z = 4 * x + 2 * y$, where initial values are `Acc = x`, `Sum = y` and answer `z` is stored in `Sum`.

a. Describe the necessary operations using a Register Transfer Level description. What is the minimum number of clock cycles required?


```
A ← Acc ;
Sum ← Sum + A ;
Sum ← Sum + A ;
A ← Sum ;
Sum ← Sum + A ;
```

5 clock cycles are required.

 - b. Draw a functional timing diagram for the circuit including Φ , LoadA, LoadSum, EnAdd, LoadAcc, ClearA, ClearSum which shows the RTL operation of part a.



 - c. Draw a state diagram for a controller which given a Start signal, will perform the operation, and then go back to the Idle state.



- d. Implement the control FSM and data path as separate Verilog modules.

```

module Q2_DP(
    input Phi, LoadA, LoadSum, EnAdd,
    LoadAcc, ClearA, ClearSum);

    localparam x=2, y=3; //Initialization values optional
    reg [7:0] A, Sum=y, Acc=x;
    wire [7:0] DataBus;

    assign DataBus = EnAdd ? Sum : Acc;

    always @(posedge Phi) begin
        if(ClearA) A <= 0;
        else if(LoadA) A <= DataBus;

        if(ClearSum) Sum <= 0;
        else if(LoadSum) Sum <= A + DataBus;

        if(LoadAcc) Acc <= DataBus;
    end
endmodule

module Q2_FSM(
    input Phi, Start,
    output LoadA, LoadSum, EnAdd,
    LoadAcc, ClearA, ClearSum);

    // Should either initialize state, or include a Reset
    localparam IDLE=3'd7;
    reg [2:0] State = IDLE, NextState;

    assign LoadA = (State==0) | (State==3);
  
```

```

assign LoadSum = (State==1) | (State==2) | (State==4);
assign EnAdd   = (State==1) | (State==2) | (State==3) | (State==4);
assign LoadAcc = 0;
assign ClearA  = 0;
assign ClearSum = 0;


always @(posedge Phi) State <= NextState;

always @(*)begin
    if(State==IDLE) NextState = Start ? 0 : IDLE;
    else if(State==4) NextState = IDLE;
    else NextState = State + 1;
end
endmodule

```


3. (25 Points) **FSM Design.** Design a Moore type FSM for a sequence recognizer. The FSM should assert Output for every sequence “110” detected in the synchronized serial input stream Z.

 a. Show state diagram for sequence recognizer.



 - b. Show timing diagram (Clock, Z, Q[2:0], Output) for the input sequence “01011011101”, with left most bit arriving first.

For the following, the state encoding matches the state index (S0 = 2'b00, ...,S3=2'b11).



- c. Implement the FSM in Verilog.

```

module Q3_FSM(
    input Clock, Z, Reset,
    output Output,
    output reg [1:0] State);

    reg [1:0] NextState;

    always@(posedge Clock) begin
        if(Reset) State <= 0;
        else State <= NextState;
    end

    assign Output = State==3;

```

```

always@(*) begin
  case(State)
    0: NextState = Z ? 1 : 0;
    1: NextState = Z ? 2 : 0;
    2: NextState = Z ? 2 : 3;
    3: NextState = Z ? 1 : 0;
  endcase
end
endmodule

```

4. (25 pts) **Verilog Testbench** Write a Verilog test bench for the FSM in question 3, making sure that all state transitions are covered.

```

`timescale 1ns/1ps
module Q4_Test();

  reg Clock=0, Reset=1;
  reg [11:0] Z          = 12'b010011011100;
  reg [11:0] ExpOutAll  = 12'b000100100000;
  reg [23:0] ExpStateAll = 24'b00_01_00_11_10_01_11_10_10_01_00_00;
  wire Output, ExpOut;
  wire [1:0] State, ExpState;
  integer idx;

  Q3_FSM dut(
    .Clock(Clock),
    .Reset(Reset),
    .Z(Z[idx]),
    .State(State),
    .Output(Output));

  always #5 Clock = ~Clock;

  // Select the current expected values from list of all expected values
  assign ExpOut = ExpOutAll[idx];
  assign ExpState = {ExpStateAll[2*idx+1], ExpStateAll[2*idx]};

  initial #10 Reset = 0;

  initial begin
    idx = 0;
    repeat(12) begin
      #6 $display("idx:%d_0:%b_1E0:%b_1S:%b_1ES:%b",
        idx, Output, ExpOut, State, ExpState);
      if(Output != ExpOut | State != ExpState)
        $display("FAIL: _Output_or_state_mismatch_at_idx:%d", idx);
      #4 idx = idx + 1;
    end
    $stop();
  end
endmodule

```