
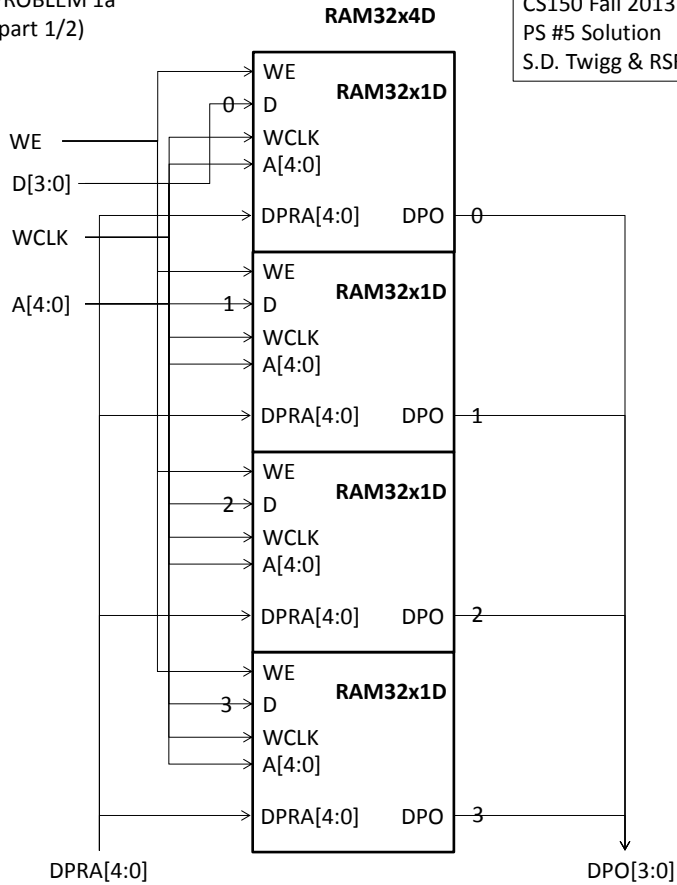



PROBLEM 1a
(part 1/2)

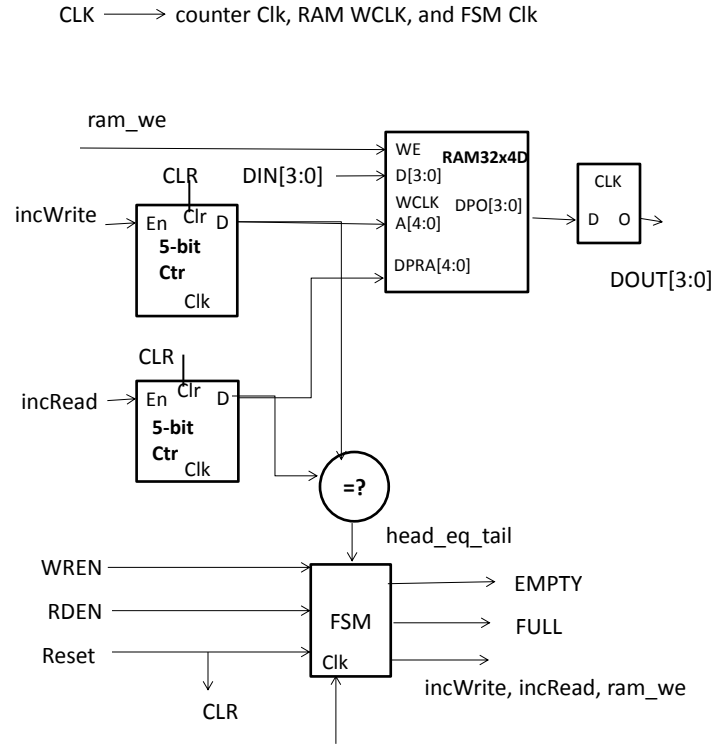

CS150 Fall 2013
PS #5 Solution
S.D. Twigg & RSF

PROBLEM 1a
(part 2/2)




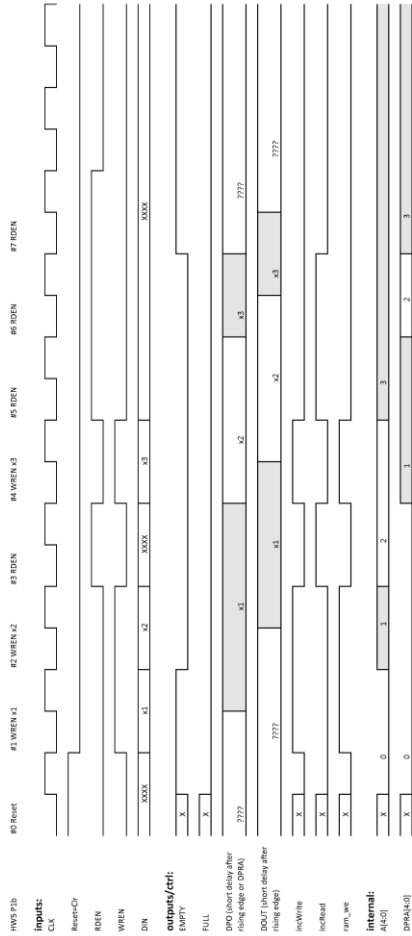

PROBLEM 1b

Note: Delay is exaggerated to 0.5 clock cycle from rising edge of clock for all signals except DPO and DOUT

PROBLEM 1c

 


FULL = (Maybe Full) && head_eq_tail
 EMPTY = (Maybe Empty) && head_eq_tail

incRead = !EMPTY && RDEN
 incWrite, ram_we = !FULL && WREN


PROBLEM 2a

RAM32x8S

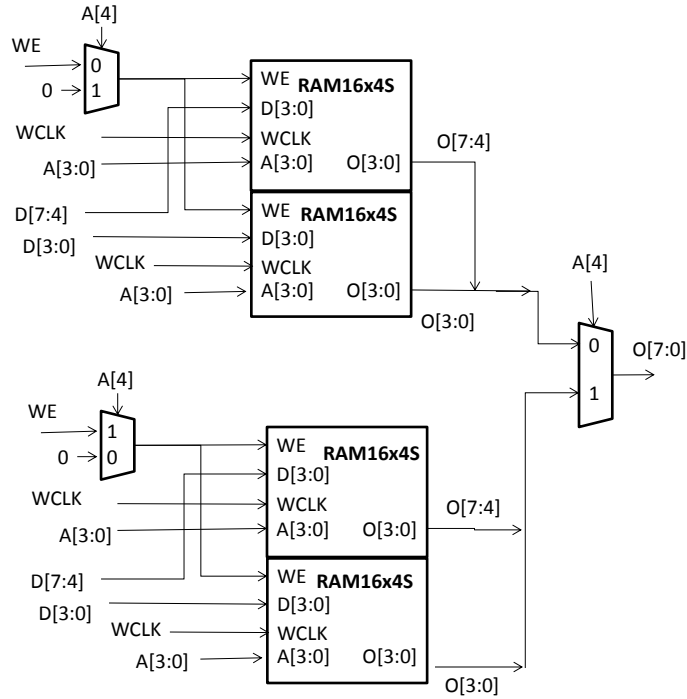


PROBLEM 2b
(part 1/2)

RAM32x2D

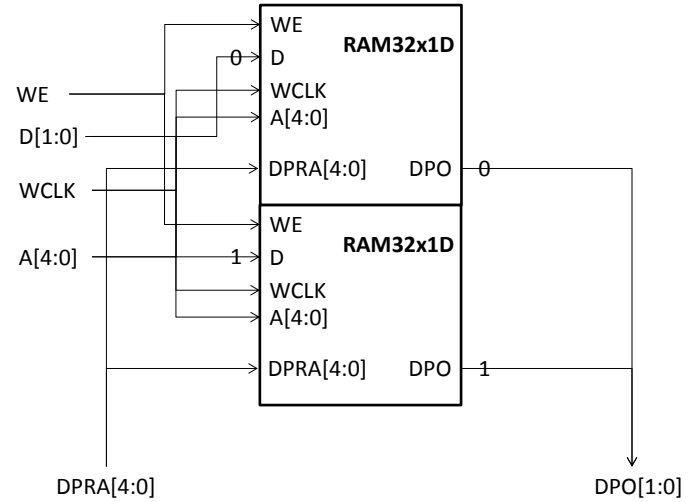


PROBLEM 2b
(part 2/2)

RAM32x2D w 4 asynch read ports

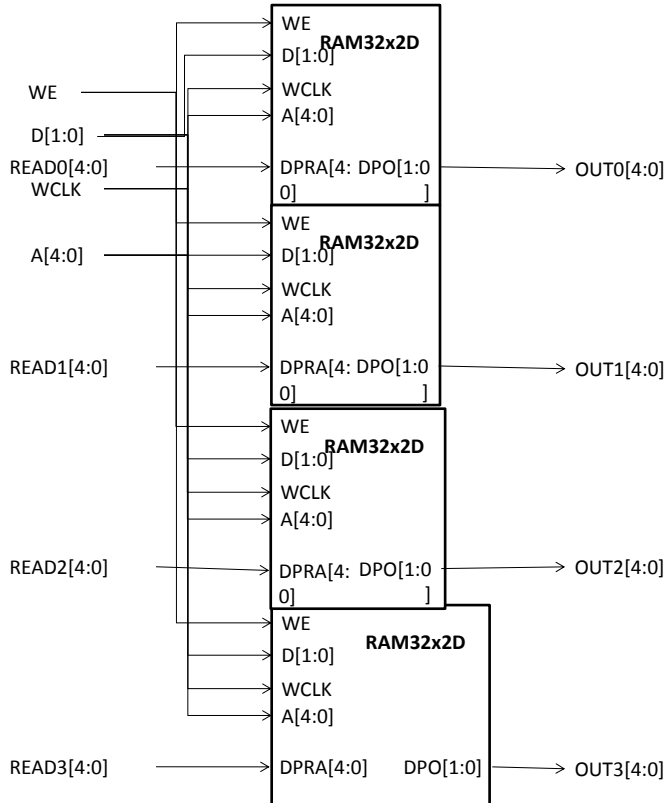

PROBLEM 2c

RAM16x4S w 4 sync read, sync write

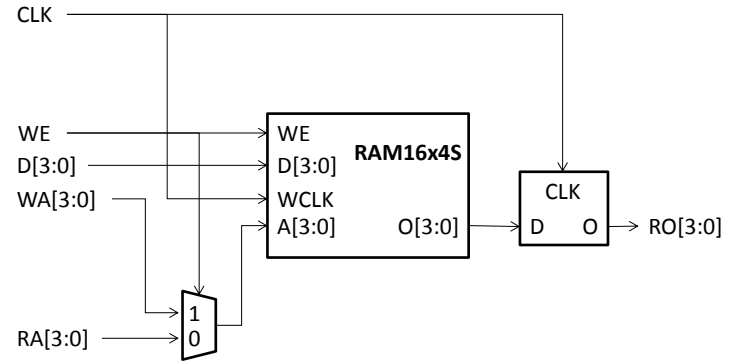

Problem 3.

Note: $MTBF = T_c / (N * T_o) * \exp((T_c - t_{setup}) / \tau)$

Where N is the number of changes per second (100 million).

MTBF= 100 years = 3.15 billion seconds

$T_o = 20 \text{ ps}$

$T_{setup} = 50 \text{ ps}$

$\tau = 30 \text{ ps}$

T_c is clock period to find = $1950 \text{ ps} = 1.95 \text{ ns}$