

EECS 150 Spring 2004

Lab Lecture 3 *Verilog Simulation Mapping* 2/6/2004

Michael Liao
Greg Gibeling
Sandro Pintz

Today

- Lab Motivation
- Overall Design
- Practical Verilog
- Think Hardware
- Behavioral vs Structural Verilog
- Lab #2

Motivation

- Basic Introduction to HDL Design Entry (Covered in Main Lecture)
- Architectural Definition and Modularization (Partitioning)
- What are "Good Verilog Techniques"
- Behavioral vs Structural Verilog


Top Down Architecture (1)

- Top Down Refinement Process
- Start Here:



Top Down Architecture (2)

- End Here:

 

Partitioning

- Define modules that:
 - Have clean, well defined interfaces to other modules
 - Are manageable in size
 - Can be verified independently
 - Might be designed by different people
 - Functionally makes sense

Practical Verilog (1)

- Remember :
 - “Think Hardware” as you write
 - Meaningful Signal Names:
 - clockEnable, busSync (good)
 - A, B&*_ (not good)
 - Choose a naming style and STICK TO IT
 - Match modules and filenames, 1 module per file

Practical Verilog (2)

- Clear Comments:
 - Comment a whole section
 - Comment for special cases (exceptions)
 - Comments for special signals
- Choose a Code Structure and STICK TO IT
 - State machine style
 - Special section for flops
 - Special section for structural stuff (instantiations)

Think Hardware (1)

- You are NOT programming
 - Easiest way to waste time
 - Programming will only confuse you
- You are describing hardware
 - You should have a circuit in mind
 - Know what you want BEFORE YOU WRITE IT
 - Don't try to hack it together
 - You will not be happy with the results

Think Hardware (2)

- Hardware isn't like software
 - Things happen all at once
 - There is no sequential execution model
 - You are not writing a set of instructions
 - You are basically creating a schematic in text form
- ALWAYS REMEMBER THIS!

Example


```

// Module Description, Company Information
// Copyright Notice, Log of Changes
// Cvs version
module lab2_cir (IN, E, R, CLK, OUT);
// Inputs
input [7:0] IN; // comment
input E, R, CLK; // comment
// Outputs
output [7:0] OUT; // comment
// Declarations
reg [7:0] OUT; // comment
// Behavioral Code
// Module Instantiations (Structural)
// Flip flops
always @(posedge CLK) begin
  if (R)
    OUT <= 0;
  else if (E)
    OUT <= OUT + IN;
end
endmodule
```

Behavioral vs Structural (1)


- Rule of thumb:
 - Behavioral doesn't have sub-components
 - Structural has sub-components:
 - Instantiated Modules
 - Instantiated Gates
 - Instantiated Primitives
- Most levels are mixed

Behavioral vs Structural (2)

 


Lab #2 Part I

- Behavioral Only
- No Instantiations

 


Lab #2 Part II

 - Behavioral:
 - Adder
 - Register
- Structural:
 - Top
 - Two Instantiations



Lab #2 Part III

 

Lab #2 Part IV

- Half Adder
- Full Adder

