

Lab Lecture 4
Verilog Design Synthesis
 2/13/2003

Greg Gibeling
 (Original By Sandro Pintz,
 Adaptions from John Wawryznek)

Today


- "Think Hardware"
 - Tips for making EECS150 an easy class
- Simulation
- Blocking vs Non-Blocking
- The Combo Lock
- FSMs in Verilog
- Kramnik!

MOTIVATION


- Finite State Machine Design
- Design Partitioning
- Design Entry
- Synthesis
- Mapping, Placing and Routing

"Think Hardware" (1)
 
```
always @ (**/)
    if (a) Z = A+B;
    Else Z = A+C;
```



 
```
always @ (**/) begin
    if (a) aux = B;
    else aux = C;
    Z = A + aux;
end
```




"Think Hardware" (2)

```
assign B = 3;
assign Z = A * B;
```

 

 
```
assign Z = A + (2 * A);
Or
assign Z = A + (A << 1);
Or
assign Z = A + {A, 1'b0};
```



"Think Hardware" (3)
 
```
assign aux = {1'b0, A[n-1:1]} + A;
assign Z = {aux, A[0]};
```



Simulation (1)

- Event Driven Simulation
- Order of execution in time tick is not fixed
- Simulator dependent (ouch!)
- Deadlocks can happen in perfectly good design
- **Simulation and Synthesis can differ functionally**

Simulation (2)

- When an event happens put in queue
- When bored get next event
- Figure out the consequences
- This means non-blocking assignments really are executed in any old order, but the results are as-if they were executed in parallel

Administrativa

- Midterm!
 - Thursday 2/19/2004 in class
 - ALL LECTURE MATERIAL COVERED
 - Emphasis on material 2/12 and before
 - TA Review Session
- Monday is a holiday
 - Come to any other lab/discussion

Blocking vs Non-Blocking (1)

```
always @ (b) begin
```

```
  a = b;
```

```
  c = a;
```

```
end
```

■ Result

■ c = a = b

```
always @ (posedge Clock) begin
```

```
  a <= b;
```

```
  c <= a;
```

```
end
```

■ Result:

■ a = (old?) b

■ c = old a

Blocking vs Non-Blocking (2)

- Use Non-Blocking for FlipFlop Inference:
 - posedge/negedge require nonblocking
 - Otherwise synthesis and simulation will not match
- Use "#1" to visual causality!

```
always @ (posedge Clock) begin
  b <= #1 a; /* b and c will be flip flops */
  c <= #1 b;
end
```

Blocking vs Non-Blocking (3)

- If you use Blocking for FlipFlops:
You will not get what you want

```
always @ (posedge Clock) begin
  b = a; /* Only c will be a flip flop, */
  c = b; /* b will go away after synthesis. */
end
/* 'b' is not needed at all */
```

```
always @ (posedge Clock) begin
  c = b; /* c and b will be flip flops */
  b = a;
end
```

Blocking vs Non-Blocking (4)

Race Conditions

```

file xyz.v:
module XYZ(A, B, Clock);
  input  B, Clock;
  output A;
  reg   A;
  always @ (posedge Clock)
    A = B;
endmodule

file abc.v:
module ABC(B, C, Clock);
  input  C, Clock;
  output B;
  reg   B;
  always @ (posedge Clock)
    B = C;
endmodule
    
```

THIS IS WRONG!!

Blocking vs Non-Blocking (5)

Race Conditions


```

file xyz.v:
module XYZ(A, B, Clock);
  input  B, Clock;
  output A;
  reg   A;
  always @ (posedge Clock)
    A <= B;
endmodule

file abc.v:
module ABC(B, C, Clock);
  input  C, Clock;
  output B;
  reg   B;
  always @ (posedge Clock)
    B <= C;
endmodule
    
```

THIS IS CORRECT!!

Combination Lock (1)

 


- Used to allow entry to a locked room:

2-bit serial combination. Example 01,11:


- Set switches to 01, press ENTER
- Set switches to 11, press ENTER
- OPEN is asserted (OPEN=1).
If wrong code, ERROR is asserted (after second combo word entry).
Press Reset at anytime to try again.

Combination Lock (2)


| Input Signal | Description |
|---------------|---|
| Reset | Clear any entered numbers |
| Enter | Read the switches (enter a number in the combination) |
| Code[1:0] | Two binary switches |
| Output signal | Description |
| Open | Lock opens |
| Error | Incorrect combination |

 

Combination Lock (3)

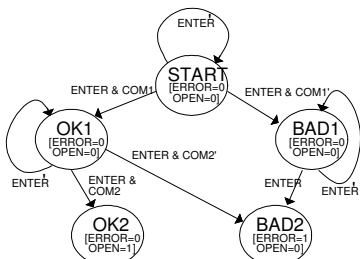


Combination Lock (4)

 

FSM Implementation Notes

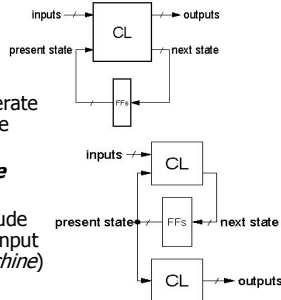- General FSM form:
- All examples so far generate output based only on the present state:
- Commonly name **Moore Machine**
(If output functions include both present state and input then called a *Mealy Machine*)



FSMs in Verilog (1)

- Two always blocks
 - One is **CurrentState** register (clocked)
 - Other is combinational
 - Generates **NextState**
 - Generates Outputs
- USE MOORE MACHINES
 - Avoid combinational loops

FSMs in Verilog (2)

```

module MyFSM(In, Out, Clock, Reset);
  input    In, Clock, Reset;
  output   Out;

  parameter IDLE = 1'b0,
            RUNNING = 1'b1;

  reg      CurrentState, NextState, Out;

  always @ (posedge Clock) begin
    if (Reset) CurrentState <= IDLE;
    else CurrentState <= NextState;
  end
  ...

```

FSMs in Verilog (3)

```

...
always @ (CurrentState or In) begin
  NextState = CurrentState;
  Out = 1'b0;

  // A case block goes here
end
endmodule

```

FSMs in Verilog (4)

```

case (CurrentState)
  IDLE: begin
    if (In) NextState = RUNNING;
    Out = 1'b0;
  end
  RUNNING: begin
    if (In) NextState = IDLE;
    Out = 1'b1;
  end
  default: begin
    NextState = 1'bX;
    Out = 1'bX;
  end
endcase

```

Kramnik

- Windows Terminal Server
- You can log in from home
 - Transfer Files
 - Run Simulations
 - Don't bother with synthesis obviously
- Instructions will be posted
- Server will be available shortly
 - We're still upgrading software