


Sequential Logic

- Sequential Circuits
 - Simple circuits with feedback
 - Latches
 - Edge-triggered flip-flops
- Timing Methodologies
 - Cascading flip-flops for proper operation
 - Clock skew
- Basic Registers
 - Shift registers

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 1

Sequential Circuits


- Circuits with Feedback
 - Outputs = $f(\text{inputs, past inputs, past outputs})$
 - Basis for building "memory" into logic circuits
 - Door combination lock is an example of a sequential circuit
 - State is memory
 - State is an "output" and an "input" to combinational logic
 - Combination storage elements are also memory

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 2

Circuits with Feedback


- How to control feedback?
 - What stops values from cycling around endlessly

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 3

Simplest Circuits with Feedback

 - Two inverters form a static memory cell
 - Will hold value as long as it has power applied




- How to get a new value into the memory cell?
 - Selectively break feedback path
 - Load new value into cell

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 4

Memory with Cross-coupled Gates

 - Cross-coupled NOR gates
 - Similar to inverter pair, with capability to force output to 0 (reset=1) or 1 (set=1)





- Cross-coupled NAND gates
 - Similar to inverter pair, with capability to force output to 0 (reset=0) or 1 (set=0)

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 5

Timing Behavior

  

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 6

State Behavior of R-S latch

Truth table of R-S latch behavior

S	R	Q
0	0	hold
0	1	0
1	0	1
1	1	unstable

Q Q'
0 1

Q Q'
1 0

Q Q'
0 0

Q Q'
1 1


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 7

Theoretical R-S Latch Behavior

State Diagram

- States: possible values
- Transitions: changes based on inputs

possible oscillation between states 00 and 11

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 8

Observed R-S Latch Behavior

Very difficult to observe R-S latch in the 1-1 state


- One of R or S usually changes first
- Ambiguously returns to state 0-1 or 1-0
- A so-called "race condition"
- Or non-deterministic transition

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 9

R-S Latch Analysis

Break feedback path

 

S	R	Q(t)	Q(t+Δ)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

		S	
		0	1
Q(t)	0	0	X
	1	0	X
		R	
		0	1



characteristic equation
 $Q(t+\Delta) = S + R'Q(t)$

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 10

Gated R-S Latch

Control when R and S inputs matter

- Otherwise, the slightest glitch on R or S while enable is low could cause change in value stored

  

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 11


Clocks

Used to keep time

- Wait long enough for inputs (R' and S') to settle
- Then allow to have effect on value stored

Clocks are regular periodic signals


- Period (time between ticks)
- Duty-cycle (time clock is high between ticks - expressed as % of period)

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 12

Clocks (cont'd)


- Controlling an R-S latch with a clock
 - Can't let R and S change while clock is active (allowing R and S to pass)
 - Only have half of clock period for signal changes to propagate
 - Signals must be stable for the other half of clock period

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 13

Cascading Latches


- Connect output of one latch to input of another
- How to stop changes from racing through chain?
 - Need to control flow of data from one latch to the next
 - Advance from one latch per clock period
 - Worry about logic between latches (arrows) that is too fast

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 14

Master-Slave Structure


- Break flow by alternating clocks (like an air-lock)
 - Use positive clock to latch inputs into one R-S latch
 - Use negative clock to change outputs with another R-S latch
- View pair as one basic unit
 - master-slave flip-flop
 - twice as much logic
 - output changes a few gate delays after the falling edge of clock but does not affect any cascaded flip-flops

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 15

The 1s Catching Problem


- In first R-S stage of master-slave FF
 - 0-1-0 glitch on R or S while clock is high "caught" by master stage
 - Leads to constraints on logic to be hazard-free

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 16

D Flip-Flop


- Make S and R complements of each other
 - Eliminates 1s catching problem
 - Can't just hold previous value (must have new value ready every clock period)
 - Value of D just before clock goes low is what is stored in flip-flop
 - Can make R-S flip-flop by adding logic to make $D = S + R'Q$

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 17

Edge-Triggered Flip-Flops


- More efficient solution: only 6 gates
 - sensitive to inputs only near edge of clock signal (not while high)

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 18


Edge-Triggered Flip-Flops (cont'd)

Step-by-step analysis

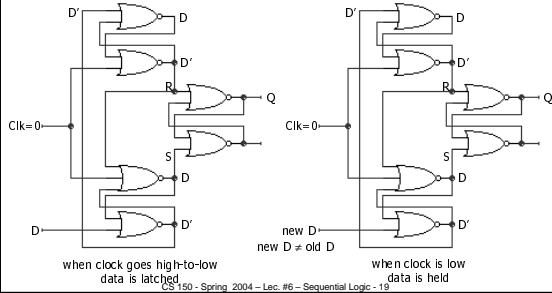


Edge-Triggered Flip-Flops (cont'd)

D = 0, Clk High

 


Edge-Triggered Flip-Flops (cont'd)

D = 1, Clk High

 

Edge-Triggered Flip-Flops (cont'd)

D = 1, Clk LOW

 


Edge-Triggered Flip-Flops (cont'd)

Positive edge-triggered

- Inputs sampled on rising edge; outputs change after rising edge

Negative edge-triggered flip-flops

 - Inputs sampled on falling edge; outputs change after falling edge



Negative Edge Trigger FF in Verilog

```

module d_ff (q, q_bar, data, clk);
  input data, clk;
  output q, q_bar;
  reg q;

  assign q_bar = ~q;

  always @(negedge clk)
  begin
    q <= data;
  end
endmodule

```

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 24


Timing Methodologies

- Rules for interconnecting components and clocks
 - Guarantee proper operation of system when strictly followed
- Approach depends on building blocks used for memory elements
 - Focus on systems with edge-triggered flip-flops
 - Found in programmable logic devices
 - Many custom integrated circuits focus on level-sensitive latches
- Basic rules for correct timing:
 - (1) Correct inputs, with respect to time, are provided to the flip-flops
 - (2) No flip-flop changes state more than once per clocking event

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 25


Timing Methodologies (cont'd)

- Definition of terms
 - clock: periodic event, causes state of memory element to change; can be rising or falling edge, or high or low level
 - setup time: minimum time before the clocking event by which the input must be stable (T_{su})
 - hold time: minimum time after the clocking event until which the input must remain stable (T_h)

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 26

Comparison of Latches and Flip-Flops

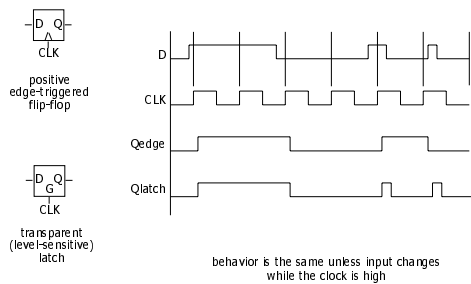

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 27


Comparison of Latches and Flip-Flops (cont'd)

Type	When inputs are sampled	When output is valid
unclocked latch	always	propagation delay from input change
level-sensitive latch	clock high (T_{su}/T_h around falling edge of clock)	propagation delay from input change or clock edge (whichever is later)
master-slave flip-flop	clock high (T_{su}/T_h around falling edge of clock)	propagation delay from falling edge of clock
negative edge-triggered flip-flop	clock hi-to-lo transition (T_{su}/T_h around falling edge of clock)	propagation delay from falling edge of clock

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 28

Typical Timing Specifications

 - Positive edge-triggered D flip-flop
 - Setup and hold times
 - Minimum clock width
 - Propagation delays (low to high, high to low, max and typical)




all measurements are made from the clocking event that is, the rising edge of the clock

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 29

Cascading Edge-triggered Flip-Flops

- Shift register
 - New value goes into first stage
 - While previous value of first stage goes into second stage
 - Consider setup/hold/propagation delays (prop must be > hold)

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 30

Cascading Edge-triggered Flip-Flops (cont'd)

Why this works

- Propagation delays exceed hold times
- Clock width constraint exceeds setup time
- This guarantees following stage will latch current value before it changes to new value

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 31

Clock Skew

The problem

 - Correct behavior assumes next state of all storage elements determined by all storage elements at the same time
- This is difficult in high-performance systems because time for clock to arrive at flip-flop is comparable to delays through logic
- Effect of skew on cascaded flip-flops:



original state: $IN = 0, Q0 = 1, Q1 = 1$
due to skew, next state becomes: $Q0 = 0, Q1 = 0$, and not $Q0 = 0, Q1 = 1$

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 32

Summary of Latches and Flip-Flops

Development of D-FF

- Level-sensitive used in custom integrated circuits
 - can be made with 4 switches
- Edge-triggered used in programmable logic devices
- Good choice for data storage register
- Historically J-K FF was popular but now never used
 - Similar to R-S but with 1-1 being used to toggle output (complement state)
 - Good in days of TTL/SSI (more complex input function: $D = JQ' + K'Q$)
 - Not a good choice for PALs/PLAs as it requires 2 inputs
 - Can always be implemented using D-FF
- Preset and clear inputs are highly desirable on flip-flops
 - Used at start-up or to reset system to a known state

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 33

Flip-Flop Features

Reset (set state to 0) - R

- Synchronous: $D_{new} = R' \cdot D_{old}$ (when next clock edge arrives)
- Asynchronous: doesn't wait for clock, quick but dangerous

Preset or set (set state to 1) - S (or sometimes P)

- Synchronous: $D_{new} = D_{old} + S$ (when next clock edge arrives)
- Asynchronous: doesn't wait for clock, quick but dangerous

Both reset and preset

- $D_{new} = R' \cdot D_{old} + S$ (set-dominant)
- $D_{new} = R' \cdot D_{old} + R' \cdot S$ (reset-dominant)

Selective input capability (input enable/load) - LD or EN

- Multiplexer at input: $D_{new} = LD' \cdot Q + LD \cdot D_{old}$
- Load may/may not override reset/set (usually R/S have priority)

Complementary outputs - Q and Q'

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 34


Registers

Collections of flip-flops with similar controls and logic

- Stored values somehow related (e.g., form binary value)
- Share clock, reset, and set lines
- Similar logic at each stage

Examples

- Shift registers
- Counters

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 35

Shift Register

Holds samples of input

- Store last 4 input values in sequence
- 4-bit shift register:

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 36

Shift Register Verilog

```

module shift_reg (out4, out3, out2, out1, in, clk);
  output out4, out3, out2, out1;
  input in, clk;
  reg out4, out3, out2, out1;

  always @(posedge clk)
  begin
    out4 <= out3;
    out3 <= out2;
    out2 <= out1;
    out1 <= in;
  end
endmodule

```

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 37

Shift Register Verilog

```

module shift_reg (out, in, clk);
  output [4:1] out;
  input in, clk;
  reg [4:1] out;


  always @(posedge clk)
  begin
    out <= {out[3:1], in};
  end
endmodule

```

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 38

Universal Shift Register

 - Holds 4 values
 - Serial or parallel inputs
 - Serial or parallel outputs
 - Permits shift left or right
 - Shift in new values from left or right




clear sets the register contents and output to 0
s1 and s0 determine the shift function

s0	s1	function
0	0	hold state
0	1	shift right
1	0	shift left
1	1	load new input

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 39

Design of Universal Shift Register

- Consider one of the four flip-flops
 - New value at next clock cycle:

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 40

Universal Shift Register Verilog

```

module univ_shift (out, lo, ro, in, li, ri, s, clr, clk);
  output [3:0] out;
  output lo, ro;
  input [3:0] in;
  input [1:0] s;
  input li, ri, clr, clk;
  reg [3:0] out;

  assign lo = out[3];
  assign ro = out[0];


  always @(posedge clk or clr)
  begin
    if (clr) out <= 0;
    else
      case (s)
        3: out <= in;
        2: out <= {out[2:0], ri};
        1: out <= {li, out[3:1]};
        0: out <= out;
      endcase
    end
  end
endmodule

```

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 41

Shift Register Application

- Parallel-to-serial conversion for serial transmission

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 42

Pattern Recognizer

Combinational function of input samples

- In this case, recognizing the pattern 1001 on the single input signal

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 43

Counters


Sequences through a fixed set of patterns

 - In this case, 1000, 0100, 0010, 0001
- If one of the patterns is its initial state (by loading or set/reset)



Mobius (or Johnson) counter

- In this case, 1000, 1100, 1110, 1111, 0111, 0011, 0001, 0000

 


CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 44

Binary Counter

Logic between registers (not just multiplexer)

- XOR decides when bit should be toggled
- Always for low-order bit, only when first bit is true for second bit, and so on

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 45

Binary Counter Verilog

```
module shift_reg (out4, out3, out2, out1, clk);
    output out4, out3, out2, out1;
    input in, clk;
    reg out4, out3, out2, out1;
```

```
always @(posedge clk)
begin
    out4 <= (out1 & out2 & out3) ^ out4;
    out3 <= (out1 & out2) ^ out3;
    out2 <= out1 ^ out2;
    out1 <= out1 ^ 1b'1;
end
endmodule
```

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 46

Binary Counter Verilog

```
module shift_reg (out4, out3, out2, out1, clk);
    output [4:1] out;
    input in, clk;
    reg [4:1] out;
```

```
always @(posedge clk)
    out <= out + 1;
```


```
endmodule
```

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 47

Four-bit Binary Synchronous Up-Counter

Standard component with many applications



- Positive edge-triggered FF's w/ sync load and clear inputs
- Parallel load data from D, C, B, A
- Enable inputs: must be asserted to enable counting
- RCO: ripple-carry out used for cascading counters
 - high when counter is in its highest state 1111
 - implemented using an AND gate

 

CS 150 - Spring 2004 - Lec. #6 - Sequential Logic - 48

Offset Counters

  - Starting offset counters - use of synchronous load
 - ┆ e.g., 0110, 0111, 1000, 1001, 1010, 1011, 1100, 1101, 1111, 0110, ...
- Ending offset counter - comparator for ending value
 - ┆ e.g., 0000, 0001, 0010, ..., 1100, 1101, 0000
- Combinations of the above (start and stop value)



Sequential Logic Summary

- Fundamental building block of circuits with state
 - ┆ Latch and flip-flop
 - ┆ R-S latch, R-S master/slave, D master/slave, edge-triggered D FF
- Timing methodologies
 - ┆ Use of clocks
 - ┆ Cascaded FFs work because prop delays exceed hold times
 - ┆ Beware of clock skew
- Basic registers
 - ┆ Shift registers
 - ┆ Pattern detectors
 - ┆ Counters