


Sequential Logic Implementation

- Models for representing sequential circuits
 - Finite-state machines (Moore and Mealy)
 - Representation of memory (states)
 - Changes in state (transitions)
- Design procedure
 - State diagrams
 - State transition table
 - Next state functions

CS 150 - Spring 2004 - Moore and Mealy Machines - 1

Abstraction of State Elements


- Divide circuit into combinational logic and state
- Localize feedback loops and make it easy to break cycles
- Implementation of storage elements leads to various forms of sequential logic

 

CS 150 - Spring 2004 - Moore and Mealy Machines - 2

Forms of Sequential Logic


- Asynchronous sequential logic - state changes occur whenever state inputs change (elements may be simple wires or delay elements)
- Synchronous sequential logic - state changes occur in lock step across all storage elements (using a periodic waveform - the clock)

 

CS 150 - Spring 2004 - Moore and Mealy Machines - 3

Finite State Machine Representations

 - States: determined by possible values in sequential storage elements
- Transitions: change of state
- Clock: controls when state can change by controlling storage elements




- Sequential Logic
 - Sequences through a series of states
 - Based on sequence of values on input signals
 - Clock period defines elements of sequence

CS 150 - Spring 2004 - Moore and Mealy Machines - 4

Example Finite State Machine Diagram



- Combination lock from first lecture

 

CS 150 - Spring 2004 - Moore and Mealy Machines - 5

Can Any Sequential System be Represented with a State Diagram?

- Shift Register

  


CS 150 - Spring 2004 - Moore and Mealy Machines - 6

Counters are Simple Finite State Machines

Counters

- Proceed thru well-defined state sequence in response to enable
- Many types of counters: binary, BCD, Gray-code
 - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
 - 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...

 

CS 150 - Spring 2004 - Moore and Mealy Machines - 7

Verilog Upcounter

```

module binary_cntr (q, clk)
  inputs  clk;
  outputs [2:0] q;
  reg     [2:0] q;
  reg     [2:0] p;

  always @(q) //Calculate next state
    case (q)
      3'b000: p = 3'b001;
      3'b001: p = 3'b010;
      ...
      3'b111: p = 3'b000;
    endcase

  always @(posedge clk) //next becomes current state
    q <= p;


endmodule
  
```

CS 150 - Spring 2004 - Moore and Mealy Machines - 8

How Do We Turn a State Diagram into Logic?

Counter

- Three flip-flops to hold state
- Logic to compute next state
- Clock signal controls when flip-flop memory can change
 - Wait long enough for combinational logic to compute new value
 - Don't wait too long as that is low performance

 

CS 150 - Spring 2004 - Moore and Mealy Machines - 9

FSM Design Procedure

Start with counters

- Simple because output is just state
- Simple because no choice of next state based on input

State diagram to state transition table

- Tabular form of state diagram
- Like a truth-table

State encoding

- Decide on representation of states
- For counters it is simple: just its value

Implementation

- Flip-flop for each state bit
- Combinational logic based on encoding


CS 150 - Spring 2004 - Moore and Mealy Machines - 10

FSM Design Procedure: State Diagram to Encoded State Transition Table

Tabular form of state diagram

- Like a truth-table (specify output for all input combinations)

 Encoding of states: easy for counters - just use value



	current state	next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

CS 150 - Spring 2004 - Moore and Mealy Machines - 11

Implementation


D flip-flop for each state bit

Combinational logic based on encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

notation to show function represent input to D-FF


$$\begin{aligned}
 N1 &:= C1' \\
 N2 &:= C1C2' + C1'C2 \\
 &:= C1 \text{ xor } C2 \\
 N3 &:= C1C2C3' + C1C3 + C2'C3 \\
 &:= C1C2C3' + (C1' + C2')C3 \\
 &:= (C1C2) \text{ xor } C3
 \end{aligned}$$

 

CS 150 - Spring 2004 - Moore and Mealy Machines - 12

Implementation (cont'd)

- Programmable Logic Building Block for Sequential Logic
 - Macro-cell: FF + logic
 - D-FF
 - Two-level logic capability like PAL (e.g., 8 product terms)


 


CS 150 - Spring, 2004 - Moore and Mealy Machines - 13

Another Example

- Shift Register
 - Input determines next state


In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

  

CS 150 - Spring, 2004 - Moore and Mealy Machines - 14

More Complex Counter Example

 - Complex Counter
 - Repeats five states in sequence
 - Not a binary number representation
- Step 1: Derive the state transition diagram
 - Count sequence: 000, 010, 011, 101, 110
- Step 2: Derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	-	-	-
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	-	-	-
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	-	-	-

note the don't care conditions that arise from the unused state codes

CS 150 - Spring, 2004 - Moore and Mealy Machines - 15

More Complex Counter Example (cont'd)

- Step 3: K-maps for Next State Functions

	C			
0	0	0	X	
A	X	1	X	1
	B			

	C			
1	1	0	X	
A	X	0	X	1
	B			

	C			
0	1	0	X	
A	X	1	X	0
	B			

- $C+ := A$
- $B+ := B' + AC'$
- $A+ := BC'$

CS 150 - Spring, 2004 - Moore and Mealy Machines - 16

Self-Starting Counters (cont'd)


- Re-deriving state transition table from don't care assignment

	C			
0	0	0	0	
A	1	1	1	1
	B			

	C			
1	1	0	1	
A	1	0	0	1
	B			

	C			
0	1	0	0	
A	0	1	0	0
	B			


Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 17

Self-Starting Counters


- Start-up States
 - At power-up, counter may be in an unused or invalid state
 - Designer must guarantee it (eventually) enters a valid state
- Self-starting Solution
 - Design counter so that invalid states eventually transition to a valid state
 - May limit exploitation of don't cares

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 18

State Machine Model



- Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - Next state
 - Function of current state and inputs
 - Outputs
 - Function of current state and inputs (Mealy machine)
 - Function of current state only (Moore machine)

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 19

State Machine Model (cont'd)


- States: S_1, S_2, \dots, S_k
- Inputs: I_1, I_2, \dots, I_m
- Outputs: O_1, O_2, \dots, O_n
- Transition function: $Fs(S_i, I_j)$
- Output function: $Fo(S_i)$ or $Fo(S_i, I_j)$

  

CS 150 - Spring, 2004 - Moore and Mealy Machines - 20


Example: Ant Brain (Ward, MIT)

- Sensors: L and R antennae, 1 if in touching wall
- Actuators: F - forward step, TL/TR - turn left/right slightly
- Goal: find way out of maze
- Strategy: keep the wall on the right

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 21


Ant Behavior

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 22

Designing an Ant Brain

State Diagram

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 23


Synthesizing the Ant Brain Circuit

- Encode States Using a Set of State Variables
 - Arbitrary choice - may affect cost, speed
- Use Transition Truth Table
 - Define next state function for each state variable
 - Define output function for each output
- Implement next state and output functions using combinational logic
 - 2-level logic (ROM/PLA/PAL)
 - Multi-level logic
 - Next state and output functions can be optimized together

CS 150 - Spring, 2004 - Moore and Mealy Machines - 24

Transition Truth Table

- Using symbolic states and outputs

 

state	L	R	next state	outputs
LOST	0	0	LOST	F
LOST	-	1	E/G	F
LOST	1	-	E/G	F
A	0	0	B	TL, F
A	0	1	A	TL, F
A	1	-	E/G	TL, F
B	-	0	C	TR, F
B	-	1	A	TR, F
...

CS 150 - Spring, 2004 - Moore and Mealy Machines - 25

Synthesis

- 5 states : at least 3 state variables required (X, Y, Z)
- State assignment (in this case, arbitrarily chosen)

state	L	R	next state	outputs
X,Y,Z			X', Y', Z'	F TR TL
000	0	0	000	1 0 0
000	0	1	001	1 0 0
...
010	0	0	011	1 0 1
010	0	1	010	1 0 1
010	1	0	001	1 0 1
010	1	1	001	1 0 1
011	0	0	100	1 1 0
011	0	1	010	1 1 0
...

It now remains to synthesize these 6 functions

LOST - 000
E/G - 001
A - 010
B - 011
C - 100

CS 150 - Spring, 2004 - Moore and Mealy Machines - 26

Synthesis of Next State and Output Functions


state	inputs	next state	outputs
X,Y,Z	L,R	X',Y',Z'	F TR TL
000	0 0	000	1 0 0
000	- 1	001	1 0 0
000	1 -	001	1 0 0
001	0 0	011	0 0 1
001	- 1	010	0 0 1
001	1 -	010	0 0 1
010	0 0	011	1 0 1
010	0 1	010	1 0 1
010	1 -	001	1 0 1
011	- 0	100	1 1 0
011	- 1	010	1 1 0
100	- 0	100	1 1 0
100	- 1	010	1 1 0

e.g.
 $TR = X + YZ$
 $X' = X'R' + YZ'R' = R'TR$

CS 150 - Spring, 2004 - Moore and Mealy Machines - 27

Circuit Implementation

- Outputs are a function of the current state only - Moore machine

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 28

Verilog Sketch

```

module ant_brain (F, TR, TL, L, R)
  inputs L, R;
  outputs F, TR, TL;
  reg X, Y, Z;


  assign F = function(X, Y, Z, L, R);
  assign TR = function(X, Y, Z, L, R);
  assign TL = function(X, Y, Z, L, R);

  always @(posedge clk)
    begin
      X <= function (X, Y, Z, L, R);
      Y <= function (X, Y, Z, L, R);
      Z <= function (X, Y, Z, L, R);
    end
endmodule
    
```

CS 150 - Spring, 2004 - Moore and Mealy Machines - 29

Don't Cares in FSM Synthesis

 - What happens to the "unused" states (101, 110, 111)?
- Exploited as don't cares to minimize the logic
 - If states can't happen, then don't care what the functions do
 - if states do happen, we may be in trouble



Ant is in deep trouble if it gets in this state

CS 150 - Spring, 2004 - Moore and Mealy Machines - 30


State Minimization

- Fewer states may mean fewer state variables
- High-level synthesis may generate many redundant states
- Two states are equivalent if they are impossible to distinguish from the outputs of the FSM, i. e., for any input sequence the outputs are the same
- Two conditions for two states to be equivalent:
 - 1) Output must be the same in both states
 - 2) Must transition to equivalent states for all input combinations

CS 150 - Spring, 2004 - Moore and Mealy Machines - 31

Ant Brain Revisited


- Any equivalent states?

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 32

New Improved Brain


- Merge equivalent B and C states
- Behavior is exactly the same as the 5-state brain
- We now need only 2 state variables rather than 3

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 33

New Brain Implementation

state	inputs	next state	outputs
X,Y	L,R	X',Y'	F TR,TL
00	00	00	1 0 0
00	-1	01	1 0 0
00	1-	01	1 0 0
01	00	11	0 0 1
01	-1	01	0 0 1
01	1-	01	0 0 1
10	00	11	1 0 1
10	01	10	1 0 1
10	1-	01	1 0 1
11	-0	11	1 1 0
11	-1	10	1 1 0

 

CS 150 - Spring, 2004 - Moore and Mealy Machines - 34

Sequential Logic Implementation Summary

- Models for representing sequential circuits
 - 1) Abstraction of sequential elements
 - 1) Finite state machines and their state diagrams
 - 1) Inputs/outputs
 - 1) Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
 - 1) Deriving state diagram
 - 1) Deriving state transition table
 - 1) Determining next state and output functions
 - 1) Implementing combinational logic

CS 150 - Spring, 2004 - Moore and Mealy Machines - 35