

Testing of Logic Circuits

- Fault Models
- Test Generation and Coverage
- Fault Detection
- Design for Test


CS 150 - Spring 2004 - Lec. #14 Testing - 1

Fault Model

- Stuck-At Model
 - Assume selected wires (gate input or output) are "stuck at" logic value 0 or 1
 - Models certain kinds of fabrication flaws that short circuit wires to ground or power
 - ┆ Wire w stuck-at-0: w/0
 - ┆ Wire w stuck-at-1: w/1
 - Often assume there is only one fault at a time—even though in real circuits multiple simultaneous faults are possible
 - Obviously a very simplistic model!

CS 150 - Spring 2004 - Lec. #14 Testing - 2


Fault Model

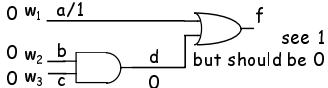- Simple example:
 

- Generate a testcase to determine if a is stuck at 1
 - ┆ Try 000
 - ┆ If a stuck at 1, expect to see $f = 0$, but see 1 instead

CS 150 - Spring 2004 - Lec. #14 Testing - 3

Fault Model

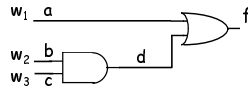- Simple example
 

Test w1 w2 w3	Fault Detected									
	a/0	a/1	b/0	b/1	c/0	c/1	d/0	d/1	f/0	f/1
000		X								X
001		X		X				X		X
010		X				X		X		X
011			X		X		X		X	X
100	X								X	X
101	X								X	X
110	X								X	X
111									X	X

Test Set

CS 150 - Spring 2004 - Lec. #14 Testing - 4

Problems with Fault Model

- In general, n-input circuits require much less than 2^n test inputs to cover all possible stuck-at-faults in the circuit
- However, this number is usually still too large in real circuits for practical purposes
- Finding minimum test cover is an NP-hard problem too

CS 150 - Spring 2004 - Lec. #14 Testing - 5


Path Sensitization

- Wire-at-time testing too laborious
- Better to focus on wiring paths, enabling multi-wire testing at the same time
- "Activate" a path so that changes in signal propagating along the path affects the output

CS 150 - Spring 2004 - Lec. #14 Testing - 6

Path Sensitization

Simple Example:

 

To activate the path, set inputs so that w_1 can influence f

E.g. $w_2 = 1, w_3 = 0, w_4 = 1$

AND gates: one input at 1 passes the other input
NOR gates: one input at 0 inverts the other input

To test: w_1 set to 1 should generate $f = 0$ if path ok
faults $a/0, b/0, c/1$ cause $f = 1$
 w_1 set to 0 should generate $f = 1$ if path ok
faults $a/1, b/1, c/0$ cause $f = 0$

One test can capture several faults at once!

CS 150 - Spring 2004 - Lec. #14 Testing - 7

Path Sensitization

Good news: one test checks for several faults



- Number of paths much smaller than number of wires
- Still an impractically large number of paths for large-scale circuits

Path idea can be used to "propagate" a fault to the output to observe the fault

- Set inputs and intermediate values so as to pass an internal wire to the output while setting inputs to drive that internal wire to a known value
- If propagated value isn't as expected, then we have found a fault on the isolated wire



CS 150 - Spring 2004 - Lec. #14 Testing - 8

Fault Propagation

  


CS 150 - Spring 2004 - Lec. #14 Testing - 9

Fault Propagation

  

CS 150 - Spring 2004 - Lec. #14 Testing - 10

Tree Structured Circuits

 

To test inputs stuck-at-0 at given AND gate


- Set inputs at other gates to generate AND output of zero
- Force inputs at selected gate to generate a one
- If f is 1 then circuit ok, else fault

To test inputs stuck-at-1 at given AND gate

- Drive input to test to 0, rest of inputs driven to 1
- Other gates driven with inputs that force gates to 0
- If f is 0 then fault, else OK

CS 150 - Spring 2004 - Lec. #14 Testing - 11

Tree Structured Circuits

 


	Product Term								Test							
	w_1	\bar{w}_1	w_2	\bar{w}_2	w_3	\bar{w}_3	w_4	\bar{w}_4	w_1	\bar{w}_1	w_2	\bar{w}_2	w_3	\bar{w}_3	w_4	\bar{w}_4
1	1	1	1	1	0	1	0	0	0	0	0	0	0	0	0	0
2	0	1	0	1	1	1	1	0	1	1	0	1	1	1	0	0
3	0	0	0	1	0	1	1	1	1	1	1	1	1	1	1	1
4	0	1	1	1	1	0	1	1	0	0	1	1	0	1	1	0
5	1	0	1	1	0	0	0	1	1	0	0	1	1	0	0	1
6	1	1	0	0	1	1	0	0	0	0	1	0	0	0	0	0
7	1	0	0	1	0	1	0	1	1	1	1	0	1	1	1	1
8	0	0	0	0	0	1	1	0	1	1	0	1	1	0	1	1

CS 150 - Spring 2004 - Lec. #14 Testing - 12

Random Testing

- So far: deterministic testing
- Alternative: random testing
 - ▮ Generate random input patterns to distinguish between the correct function and the faulty function

 


CS 150 - Spring 2004 - Lec. #14 Testing - 13

Sequential Testing

- Due to embedded state inside flip-flops, it is difficult to employ the same methods as with combinational logic
- Alternative approach: design for test
 - ▮ Scan Path technique: FF inputs pass through multiplexer stages to allow them to be used in normal mode as well as a special test shift register mode

CS 150 - Spring 2004 - Lec. #14 Testing - 14

Scan Path Technique

 


- Configure FFs into shift register mode
- Scan in pattern of 0s and 1s
- Non-state inputs can also be on the scan path
- Run system for one clock cycle in normal mode—next state captured in scan path
- Return to shift register mode and shift out the captured state and outputs

CS 150 - Spring 2004 - Lec. #14 Testing - 15

Scan Path Example


- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs

 

CS 150 - Spring 2004 - Lec. #14 Testing - 16

Scan Path Example


- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs

 

CS 150 - Spring 2004 - Lec. #14 Testing - 17

Scan Path Example

- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs

 

CS 150 - Spring 2004 - Lec. #14 Testing - 18

Scan Path Example

- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs
 - ▮ Normal w=0

CS 150 - Spring 2004 - Lec. #14 Testing - 19

Scan Path Example

- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs
 - ▮ Normal w=0
 - ▮ Output z=0, Y1=0, Y2=0

CS 150 - Spring 2004 - Lec. #14 Testing - 20

Scan Path Example

- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs
 - ▮ Normal w=0
 - ▮ Output z=0, Y1=0, Y2=0
 - ▮ Observe z directly

CS 150 - Spring 2004 - Lec. #14 Testing - 21

Scan Path Example

- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs
 - ▮ Normal w=0
 - ▮ Output z=0, Y1=0, Y2=0
 - ▮ Observe z directly
 - ▮ Scan out Y1, Y2

CS 150 - Spring 2004 - Lec. #14 Testing - 22

Scan Path Example

- w,y1,y2 test vector 001
 - ▮ Scan 01 into y1, y2 FFs
 - ▮ Normal w=0
 - ▮ Output z=0, Y1=0, Y2=0
 - ▮ Observe z directly
 - ▮ Scan out Y1, Y2


CS 150 - Spring 2004 - Lec. #14 Testing - 23

Built-in Self-Test (BIST)

- Test Vector Generator
 - ▮ Pseudorandom tests with a feedback shift register
 - ▮ Seed generates a sequence of test patterns
 - ▮ Outputs combined using the same technique
 - ▮ Generates a unique signature that can be checked to determine if the circuit is correct


CS 150 - Spring 2004 - Lec. #14 Testing - 24

Linear Feedback Shift Register

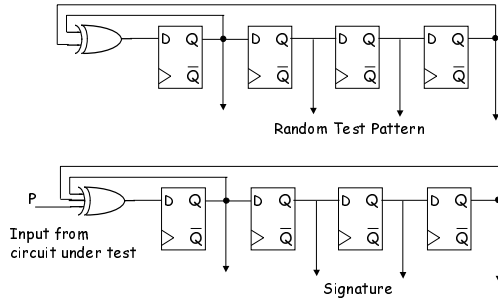

CS 150 - Spring 2004 - Lec. #14 Testing - 25

Linear Feedback Shift Register

 


- Starting with the pattern 1000, generates 15 different patterns in sequence and then repeats

CS 150 - Spring 2004 - Lec. #14 Testing - 26


Linear Feedback Shift Register

- Multi-input Compressor

 

CS 150 - Spring 2004 - Lec. #14 Testing - 27


Complete Self-Test System

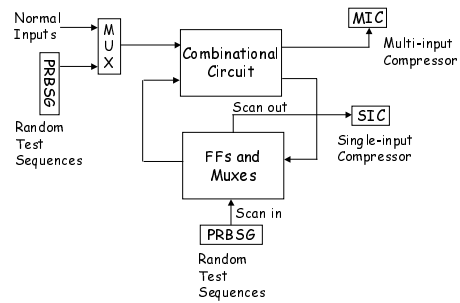

CS 150 - Spring 2004 - Lec. #14 Testing - 28

Built-in Logic Block Observer (Bilbo)

 
- Test generation and compression in a single circuit!
 - $M_1, M_2 = 11$: Regular mode
 - $M_1, M_2 = 00$: Shift register mode
 - $M_1, M_2 = 10$: Signature generation mode
 - $M_1, M_2 = 01$: Reset mode



Normal/Scan

CS 150 - Spring 2004 - Lec. #14 Testing - 29

Bilbo Architecture

 

- Scan initial pattern in Bilbo1, reset FFs in Bilbo2
- Use Bilbo1 as PRBS generator for given number of clock cycles and use Bilbo2 to produce signature
- Scan out Bilbo2 and compare signature; Scan in initial test pattern for CN2; Reset the FFs in Bilbo1
- Use Bilbo2 as PRBS generator for a given number of clock cycles and use Bilbo1 to produce signature
- Scan out Bilbo1 and compare signature;

CS 150 - Spring 2004 - Lec. #14 Testing - 30

Summary

- **Fault models**
 - Approach for determining how to develop a test pattern sequence
 - Weakness is the single fault assumption
- **Scan Path**
 - Technique for applying test inputs deep within the system, usually for asserting state
 - Technique for getting internal state to edges of circuit for observation
- **Built-in Test**
 - Founded on the approach of random testing
 - Generate pseudo random sequences; compute signature; determine if signature generated is same as signature of a correctly working circuitry