


State Machine Signaling

- **Timing Behavior**
 - Glitches/hazards and how to avoid them
- **FSM Partitioning**
 - What to do when the state machine doesn't fit!
- **State Machine Signaling**
 - State Machine Retiming
 - Introducing Idle States (synchronous model)
 - Four Cycle Signaling (asynchronous model)
- **Dealing with Asynchronous Inputs**
 - Metastability and synchronization

CS 150 - Spring 2004 - Lec #16 - Signaling - 1

Momentary Changes in Outputs


- Can be useful—pulse shaping circuits
- Can be a problem—incorrect circuit operation (glitches/hazards)
- **Example: pulse shaping circuit**
 - $A' \cdot A = 0$
 - delays matter in function

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 2

Oscillatory Behavior

- **Another pulse shaping circuit**

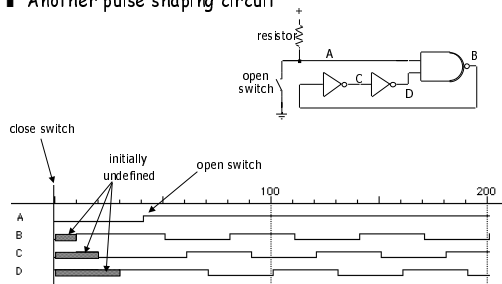

CS 150 - Spring 2004 - Lec #16 - Signaling - 3

Hazards/Glitches

- **Hazards/glitches: unwanted switching at the outputs**
 - Occur when different paths through circuit have different propagation delays
 - As in pulse shaping circuits we just analyzed
 - Dangerous if logic causes an action while output is unstable
 - May need to guarantee absence of glitches
- **Usual solutions**
 - 1) Wait until signals are stable (by using a clock): preferable (easiest to design when there is a clock - *synchronous design*)
 - 2) Design hazard-free circuits: sometimes necessary (clock not used - *asynchronous design*)

CS 150 - Spring 2004 - Lec #16 - Signaling - 4


Types of Hazards

- **Static 1-hazard**
 - Input change causes output to go from 1 to 0 to 1
- **Static 0-hazard**
 - Input change causes output to go from 0 to 1 to 0
- **Dynamic hazards**
 - Input change causes a double change from 0 to 1 to 0 to 1 OR from 1 to 0 to 1 to 0

CS 150 - Spring 2004 - Lec #16 - Signaling - 5

Static Hazards

- Due to a literal and its complement momentarily taking on the same value
 - Thru different paths with different delays and reconverging
- May cause an output that should have stayed at the same value to momentarily take on the wrong value
- **Example:**

 


CS 150 - Spring 2004 - Lec #16 - Signaling - 6

Dynamic Hazards

- Due to the same versions of a literal taking on opposite values
 - Thru different paths with different delays and reconverging
- May cause an output that was to change value to change 3 times instead of once


Example:

 


CS 150 - Spring 2004 - Lec #16 - Signaling - 7

Eliminating Static Hazards

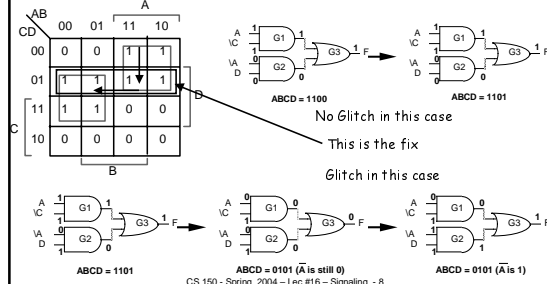- Following 2-level logic function has a hazard, e.g., when inputs change from $ABCD = 0101$ to 1101



Eliminating Dynamic Hazards

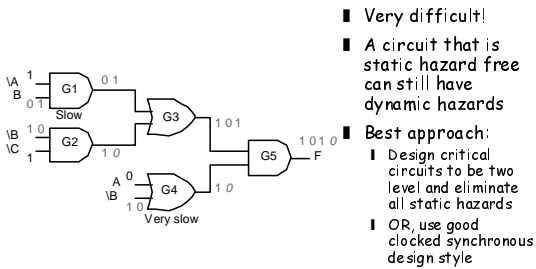


CS 150 - Spring 2004 - Lec #16 - Signaling - 9


FSM Partitioning

Why Partition?

 - What if programmable logic is limited in number of inputs and outputs that can be used in a particular device?
- For PALs/PLAs, the number of product terms are limited, thus limiting the complexity of the next state and output functions



Partitioning the State Machine

 


- Suppose that FSM is partitioned so that states at the right are in one partition and states at the left are in the other
- How do you support intersignaling between the state machine partitions?
- It is usually a good idea to partition the machine so there are as few cross links as possible (min cut set in graph theoretic terms)


CS 150 - Spring 2004 - Lec #16 - Signaling - 11

Partitioning the State Machine

 - Solution: introduce idle states S_A and S_B
 - Machine at left enters S_A allowing machine at right to exit S_B
 - When machine at right returns to S_B , machine at left exits S_A




Rules for Introducing Idle States

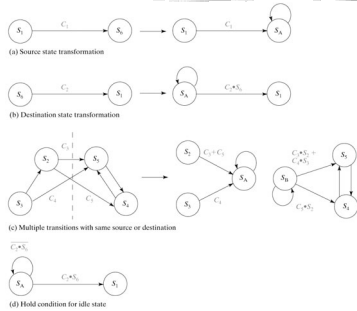

CS 150 - Spring 2004 - Lec #16 - Signaling - 13


Example: Partitioning the Up/Down Counter

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 14


Example Partitioning: Traffic Light Controller

- Main Controller vs. Counter/Timer
 - ST triggers transfer of control
 - TS or TL triggers return of control

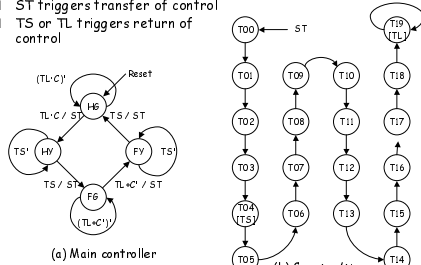

CS 150 - Spring 2004 - Lec #16 - Signaling - 15

Partitioned FSM Block Diagram

 


- Interface between the two partitions are the signals ST , TS , TL
- NOTE: Main Controller and Timer use the same clock and are operating in a synchronous mode

CS 150 - Spring 2004 - Lec #16 - Signaling - 16

State Machine Retiming


- Moore vs. (Async) Mealy Machine
 - Vending Machine Example

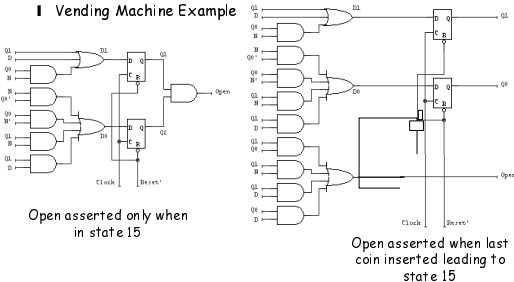

CS 150 - Spring 2004 - Lec #16 - Signaling - 17

State Machine Retiming


- Retiming the Moore Machine: Faster generation of outputs
- Synchronizing the Mealy Machine: Add a FF, delaying the output
- These two implementations have identical timing behavior

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 18

State Machine Retiming


- Timing behavior is the same, but are the implementations really identical?

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 19

Generalized Inter-FSM Signaling


- Interlocked Synchronized Signaling

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 20

Asynchronous Signaling


- Also known as "speed-independent" signaling
- Requester/client/master vs. Provider/Server/Slave

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 21

Asynchronous Signaling

 - First consider the common clock case (synchronous)




- Master asserts Request
- Slave recognizes request, processes request, indicates completion by asserting Acknowledgement
- Master accepts results, removes Request
- Slave sees Request removed, removes Acknowledgement

CS 150 - Spring 2004 - Lec #16 - Signaling - 22

Asynchronous Signaling

 - What if Slave can't respond in single cycle? Solution: Wait signaling




- Slave inhibits master by asserting wait
- When slave unasserts wait, master knows request has been processed, and can latch results

CS 150 - Spring 2004 - Lec #16 - Signaling - 23

True Asynchronous Signaling

- Now remove the assumption of a single common clock
- How do we make sure that receiver has seen the sender's signal? Solution: Interlocked signaling
- Four cycle signaling: assert Req, process request, assert ack, latch result, remove Req, remove Ack and start again
- Sometimes called "Return to Zero" signaling

 


CS 150 - Spring 2004 - Lec #16 - Signaling - 24

True Asynchronous Signaling

Alternative scheme: Two-Cycle Signaling

- ┆ Non-return-to-zero signaling
- ┆ Transaction start by Req lo-to-hi, finishes Ack lo-to-lo
- ┆ Next transaction starts by Req hi-to-lo, finishes Ack hi-to-lo
- ┆ Requires EXTRA state to keep track of the current sense of the transitions—faster than 4 cycle case, but usually involves more hardware

 


CS 150 - Spring 2004 - Lec #16 - Signaling - 25

True Asynchronous Timing

Self-Timed Circuits

- ┆ Uses Req/Ack signaling as described
- ┆ Components can be constructed with NO internal clocks
- ┆ Determines on its own when the request has been processed
- ┆ Concept of the delay line simply slows down the pass through of the Req to the Ack—usually matched to the worst case delay path
- ┆ Becoming MORE important for large scale VLSI chips where global clock distribution is a challenge

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 26

Metastability and Asynchronous inputs

Clocked synchronous circuits

- ┆ Inputs, state, and outputs sampled or changed in relation to a common reference signal (called the clock)
- ┆ E.g., master/slave, edge-triggered

Asynchronous circuits

- ┆ Inputs, state, and outputs sampled or changed independently of a common reference signal (glitches/hazards a major concern)
- ┆ E.g., R-S latch

Asynchronous inputs to synchronous circuits


- ┆ Inputs can change at any time, will not meet setup/hold times
- ┆ Dangerous, synchronous inputs are greatly preferred
- ┆ Cannot be avoided (e.g., reset signal, memory wait, user input)

CS 150 - Spring 2004 - Lec #16 - Signaling - 27


Synchronization Failure

Occurs when FF input changes close to clock edge

 - ┆ FF may enter a metastable state - neither a logic 0 nor 1 -
- ┆ May stay in this state an indefinite amount of time
- ┆ Is not likely in practice but has some probability



 small, but non-zero probability that the FF output will get stuck in an in-between state




oscilloscope traces demonstrating synchronizer failure and eventual decay to steady state

CS 150 - Spring 2004 - Lec #16 - Signaling - 28

Dealing with Synchronization Failure

Probability of failure can never be reduced to 0, but it can be reduced

- (1) slow down the system clock: this gives the synchronizer more time to decay into a steady state; synchronizer failure becomes a big problem for very high speed systems
- (2) use fastest possible logic technology in the synchronizer: this makes for a very sharp "peak" upon which to balance
- (3) cascade two synchronizers: this effectively synchronizes twice (both would have to fail)


 


CS 150 - Spring 2004 - Lec #16 - Signaling - 29

Handling Asynchronous Inputs

Never allow asynchronous inputs to fan-out to more than one flip-flop

- ┆ Synchronize as soon as possible and then treat as synchronous signal

  


CS 150 - Spring 2004 - Lec #16 - Signaling - 30

Handling Asynchronous Inputs (cont'd)

■ What can go wrong?

- Input changes too close to clock edge (violating setup time constraint)

 

CS 150 - Spring 2004 - Lec #16 - Signaling - 31

Signaling Summary

- Glitches/Hazards
 - Introduce redundant logic terms to avoid them OR use synchronous design!
- FSM Partitioning
 - Replacing monolithic State Machine with simpler communicating state machine
 - Technique of introducing idle states
- State Machine Retiming
 - Rearranging the logic/FFs in a state machine to speed up its output signaling behavior
- Machine-to-machine Signaling
 - Synchronous vs. asynchronous
 - Four vs. Two Cycle Signaling
- Asynchronous inputs and their dangers
 - Synchronizer failure: what it is and how to minimize its impact

CS 150 - Spring 2004 - Lec #16 - Signaling - 32