

Arithmetic Circuits

(Part I)

Randy H. Katz
University of California, Berkeley

Spring 2004

Motivation

Arithmetic circuits are excellent examples of comb. logic design

- *Time vs. Space Trade-offs*

Doing things fast requires more logic and thus more space

Example: carry lookahead logic

- *Arithmetic Logic Units*

Critical component of processor datapath

Inner-most "loop" of most computer instructions

Overview

- *Binary Number Representation*
Sign & Magnitude, Ones Complement, Twos Complement
- *Binary Addition*
Full Adder Revisited
- *ALU Design*
- *BCD Circuits*
- *Combinational Multiplier Circuit*
- *Design Case Study: 8 Bit Multiplier*
- *Sequential Multiplier Circuit*

Number Systems

Representation of Negative Numbers

Representation of positive numbers same in most systems

Major differences are in how negative numbers are represented

Three major schemes:


- sign and magnitude
- ones complement
- twos complement

Assumptions:

- we'll assume a 4 bit machine word
- 16 different values can be represented
- roughly half are positive, half are negative

Number Systems

Sign and Magnitude Representation

 

High order bit is sign: 0 = positive (or zero), 1 = negative

Three low order bits is the magnitude: 0 (000) thru 7 (111)

Number range for n bits = $\pm 2^{n-1} - 1$

Representations for 0

Number Systems

Sign and Magnitude

Cumbersome addition/subtraction

Must compare magnitudes to determine sign of result

Ones Complement

N is positive number, then \bar{N} is its negative 1's complement

$$\bar{N} = (2^n - 1) - N$$

Example: 1's complement of 7

$$2^4 = 10000$$

$$-1 = \underline{00001}$$

$$1111$$

$$-7 = \underline{0111}$$

Short cut method:

$$1000 - 7 = -7 \text{ in 1's comp.}$$

simply compute bit wise complement

0111 \rightarrow 1000

Contemporary Logic Design
Arithmetic Circuits

Number Systems Ones Complement

Subtraction implemented by addition & 1's complement

Still two representations of 0! This causes some problems

Some complexities in addition

© R.H. Katz Transparency No. 17-7

Contemporary Logic Design
Arithmetic Circuits

Number Representations Twos Complement

like 1's comp except shifted one position clockwise

Only one representation for 0

One more negative number than positive number

© R.H. Katz Transparency No. 17-8

Contemporary Logic Design
Arithmetic Circuits

Number Systems Twos Complement Numbers

$N^* = 2^n - N$

$2^4 = 10000$

Example: Twos complement of 7 sub 7 = 0111
1001 = repr. of -7

Example: Twos complement of -7 $2^4 = 10000$
sub -7 = 1001
0111 = repr. of 7

Shortcut method:
Twos complement = bitwise complement + 1
0111 → 1000 + 1 → 1001 (representation of -7)
1001 → 0110 + 1 → 0111 (representation of 7)

© R.H. Katz Transparency No. 17-9

Contemporary Logic Design
Arithmetic Circuits

Number Representations Addition and Subtraction of Numbers

Sign and Magnitude

result sign bit is the same as the operands' sign

4	0100		-4	1100
	<u>+ 3</u>	0011	+ (-3)	1011
	7	0111	-7	1111

when signs differ, operation is subtract, sign of result depends on sign of number with the larger magnitude

4	0100		-4	1100
	<u>- 3</u>	1011	+ 3	0011
	1	0001	-1	1001

© R.H. Katz Transparency No. 17-10

Contemporary Logic Design
Arithmetic Circuits

Number Systems Addition and Subtraction of Numbers

Ones Complement Calculations

4	0100		-4	1011
	<u>+ 3</u>	0011	+ (-3)	1100
	7	0111	-7	10111
		End around carry	↳	1
				1000

4	0100		-4	1011
	<u>- 3</u>	1100	+ 3	0011
	1	10000	-1	1110
		End around carry	↳	1
				0001

© R.H. Katz Transparency No. 17-11

Contemporary Logic Design
Arithmetic Circuits

Number Systems Addition and Subtraction of Binary Numbers

Ones Complement Calculations

Why does end-around carry work?

Its equivalent to subtracting 2^n and adding 1

$M - N = M + \bar{N} = M + (2^n - 1 - N) = (M - N) + 2^n - 1$ ($M > N$)

$-M + (-N) = \bar{M} + \bar{N} = (2^n - M - 1) + (2^n - N - 1)$ $M + N < 2^{n-1}$
 $= 2^n + [2^n - 1 - (M + N)] - 1$

after end around carry:
 $= 2^n - 1 - (M + N)$

this is the correct form for representing $-(M + N)$ in 1's compl

© R.H. Katz Transparency No. 17-12

Contemporary Logic Design
Arithmetic Circuits

Number Systems

Addition and Subtraction of Binary Numbers

Twos Complement Calculations

4	0100	-4	1100
+ 3	0011	+ (-3)	1101
7	0111	-7	1001

If carry-in to sign = carry-out then ignore carry

if carry-in differs from carry-out then overflow

4	0100	-4	1100
- 3	1101	+ 3	0011
1	10001	-1	1111

Simpler addition scheme makes twos complement the most common choice for integer number systems with in digital systems

© R.H. Katz Transparency No. 17-13

Contemporary Logic Design
Arithmetic Circuits

Number Systems

Addition and Subtraction of Binary Numbers

Twos Complement Calculations

Why can the carry-out be ignored?

$-M + N$ when $N > M$:

$$M^* + N = (2^n - M) + N = 2^n + (N - M)$$

Ignoring carry-out is just like subtracting 2^n

$-M + -N$ where $N + M < 2^{n-1}$

$$-M + (-N) = M^* + N^* = (2^n - M) + (2^n - N) = 2^n - (M + N) + 2^n$$

After ignoring the carry, this is just the right twos compl representation for $-(M + N)$

© R.H. Katz Transparency No. 17-14

Contemporary Logic Design
Arithmetic Circuits

Number Systems

Overflow Conditions

Add two positive numbers to get a negative number
or two negative numbers to get a positive number

5 + 3 = -8!
-7 - 2 = +7!

© R.H. Katz Transparency No. 17-15

Contemporary Logic Design
Arithmetic Circuits

Number Systems

Overflow Conditions

5	0101	-7	1000
+ 3	0011	-2	1100
-8	1000	7	0111

Overflow

5	0000	-3	1111
+ 2	0010	-5	1011
7	0111	-8	1000

No overflow

Overflow when carry in to sign does not equal carry out

© R.H. Katz Transparency No. 17-16

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Half Adder

With twos complement numbers, addition is sufficient

A_i	B_i	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

A_i	B_i
0	0
0	1
1	0
1	1

Sum = $\bar{A}_i B_i + A_i \bar{B}_i$
Carry = $A_i B_i$
= $A_i \oplus B_i$

Half-adder Schematic

© R.H. Katz Transparency No. 17-17

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Full Adder

Cascaded Multi-bit Adder

usually interested in adding more than two bits
this motivates the need for the full adder

© R.H. Katz Transparency No. 17-18

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Full Adder

A	B	CI	S	CO
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

CI	AB	00	01	11	10
0	0	0	1	0	1
1	0	1	0	1	0

AB	00	01	11	10
00	0	0	1	0
01	0	1	1	1
11	1	1	1	1
10	1	0	1	0

$S = CI \text{ xor } A \text{ xor } B$
 $CO = B CI + A CI + A B = CI(A + B) + A B$

© R.H. Katz Transparency No. 17-19

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Full Adder/Half Adder

Standard Approach: 6 Gates

Alternative Implementation: 5 Gates

$A B + CI(A \text{ xor } B) = A B + B CI + A CI$

© R.H. Katz Transparency No. 17-20

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Adder/Subtractor

$A - B = A + (-B) = A + \bar{B} + 1$

© R.H. Katz Transparency No. 17-21

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Lookahead Circuits

Critical delay: the propagation of carry from low to high order stages

final sum and carry

© R.H. Katz Transparency No. 17-22

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Lookahead Circuits

Critical delay: the propagation of carry from low to high order stages

$1111 + 0001$
 worst case addition

T0: Inputs to the adder are valid
 T2: Stage 0 carry out (C1) 2 delays to compute sum
 T4: Stage 1 carry out (C2) but last carry not ready until 6 delays later
 T6: Stage 2 carry out (C3)
 T8: Stage 3 carry out (C4)

© R.H. Katz Transparency No. 17-23

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Lookahead Logic

Carry Generate $Gi = Ai Bi$ must generate carry when $A = B = 1$
 Carry Propagate $Pi = Ai \text{ xor } Bi$ carry in will equal carry out here

Sum and Carry can be reexpressed in terms of generate/propagate:

$$Si = Ai \text{ xor } Bi \text{ xor } Ci = Pi \text{ xor } Ci$$

$$Ci+1 = Ai Bi + Ai Ci + Bi Ci$$

$$= Ai Bi + Ci(Ai + Bi)$$

$$= Ai Bi + Ci(Ai \text{ xor } Bi)$$

$$= Gi + Ci Pi$$

© R.H. Katz Transparency No. 17-24

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Lookahead Logic

Reexpress the carry logic as follows:

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

Each of the carry equations can be implemented in a two-level logic network

Variables are the adder inputs and carry in to stage 0!

© R.H. Katz Transparency No. 17-25

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Lookahead Implementation

adder with Propagate and Generate Outputs

Increasingly complex logic

© R.H. Katz Transparency No. 17-26

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Lookahead Logic

Cascaded Carry Lookahead

Carry lookahead logic generates individual carries

sums computed much faster

© R.H. Katz Transparency No. 17-27

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Lookahead Logic

Cascaded Carry Lookahead

4 bit adders with internal carry lookahead

second level carry lookahead unit, extends lookahead to 16 bits

© R.H. Katz Transparency No. 17-28

Contemporary Logic Design
Arithmetic Circuits

Networks for Binary Addition

Carry Select Adder

Redundant hardware to make carry calculation go faster

compute the high order sums in parallel

one addition assumes carry in = 0

the other assumes carry in = 1

© R.H. Katz Transparency No. 17-29

Contemporary Logic Design
Arithmetic Circuits

Arithmetic Logic Unit Design

Sample ALU

M	S1	S0	Function	Comment
M = 0, Logical Bitwise Operations	0	0	$F_i = A_i$	Input A_i transferred to output
	0	1	$F_i = \text{not } A_i$	Complement of A_i transferred to output
	1	0	$F_i = A_i \text{ xor } B_i$	Compute XOR of A_i, B_i
	1	1	$F_i = A_i \text{ xnor } B_i$	Compute XNOR of A_i, B_i
M = 1, C0 = 0, Arithmetic Operations	0	0	$F = A$	Input A passed to output
	0	1	$F = \text{not } A$	Complement of A passed to output
	1	0	$F = A \text{ plus } B$	Sum of A and B
	1	1	$F = (\text{not } A) \text{ plus } B$	Sum of B and complement of A
M = 1, C0 = 1, Arithmetic Operations	0	0	$F = A \text{ plus } 1$	Increment A
	0	1	$F = (\text{not } A) \text{ plus } 1$	Two's complement of A
	1	0	$F = A \text{ plus } B \text{ plus } 1$	Increment sum of A and B
	1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A

Logical and Arithmetic Operations

Not all operations appear useful, but "fall out" of internal logic

© R.H. Katz Transparency No. 17-30

Arithmetic Logic Unit Design

Sample ALU

Traditional Design Approach

Truth Table & Espresso

23 product terms!

Equivalent to 25 gates

```

.i 6
.o 2
-11b m s1 s0 ci ai bi
-ob fi co
.p 23
111101 10
110111 10
1-0100 10
1-1110 10
10010- 10
10111- 10
-10001 10
010-01 10
-11011 10
011-11 10
--1000 10
0-1-00 10
--0010 10
0-0-10 10
-0100- 10
001-0- 10
-0001- 10
000-1- 10
-1-1-01 10
--1-01 01
--0-11 01
--110- 01
--011- 01
.e

```

M	S1	S0	Ci	Ai	Bi	Fi	Ci+1
0	0	0	X	0	X	0	X
0	1	X	0	X	1	X	X
1	0	X	0	X	0	X	X
1	1	X	0	X	1	X	X
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0
0	0	0	1	0	0	0	0
0	0	0	1	1	0	0	0
0	1	0	0	0	1	0	0
0	1	0	0	1	1	0	0
0	1	1	0	0	0	1	0
0	1	1	0	1	0	1	0
0	1	1	1	0	0	1	0
0	1	1	1	1	0	1	0
1	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0
1	0	0	1	0	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	1	0	0
1	0	1	0	1	1	0	0
1	0	1	1	0	0	1	0
1	0	1	1	1	0	1	0
1	1	0	0	0	1	1	0
1	1	0	0	1	1	1	0
1	1	0	1	0	1	1	0
1	1	0	1	1	1	1	0
1	1	1	0	0	1	1	0
1	1	1	0	1	1	1	0
1	1	1	1	0	1	1	0
1	1	1	1	1	1	1	0

© R.H. Katz Transparency No. 17-31

Arithmetic Logic Unit Design

Sample ALU

Multi level Implementation

```

.model alu.espresso
.inputs m s1 s0 ci ai bi
.outputs fi co
.names m ci co [30] [33] [35] fi
-1-11- 1
--01-1 1
--00-0 1
.names m ci [30] [33] co
-1-1 1
-111- 1
.names s0 ai [30]
01 1
10 1
.names m s1 bi [33]
-0- 1
-0- 1
.end

```

12 Gates

© R.H. Katz Transparency No. 17-32

Arithmetic Logic Unit Design

Sample ALU

Clever Multi-level Logic Implementation

8 Gates (but 3 are XOR)

S1 = 0 blocks Bi
Happens when operations involve Ai only

Same is true for Ci when M = 0

Addition happens when M = 1
Bi, Ci to Xor gates X2, X3

S0 = 0, X1 passes A
S0 = 1, X1 passes A

Arithmetic Mode:
Or gate inputs are Ai Ci and Bi (Ai xor Ci)

Logic Mode:
Cascaded XORs form output from Ai and Bi

© R.H. Katz Transparency No. 17-33

Arithmetic Logic Unit Design

74181 TTL ALU

S3	S2	S1	S0	M = 1		M = 0, Arithmetic Functions	
				Logic Function	Cn = 0	Cn = 1	
0	0	0	0	F = not A	F = A minus 1	F = A	
0	0	0	1	F = A nand B	F = A B minus 1	F = A B	
0	0	1	0	F = (not A) + B	F = A (not B) minus 1	F = A (not B)	
0	0	1	1	F = 1	F = minus 1	F = zero	
0	1	0	0	F = A nor B	F = A plus (A + not B)	F = A plus (A + not B) plus 1	
0	1	0	1	F = not B	F = A B plus (A + not B)	F = A B plus (A + not B) plus 1	
0	1	1	0	F = A xor B	F = A minus B minus 1	F = (A + not B) plus 1	
0	1	1	1	F = A + not B	F = A + not B	F = A minus B	
1	0	0	0	F = (not A) B	F = A plus (A + B)	F = (A + not B) plus 1	
1	0	0	1	F = A xor B	F = A plus B	F = A plus (A + B) plus 1	
1	0	1	0	F = B	F = A (not B) plus (A + B)	F = A (not B) plus (A + B) plus 1	
1	0	1	1	F = A + B	F = (A + B)	F = (A + B) plus 1	
1	1	0	0	F = 0	F = A	F = A plus A plus 1	
1	1	0	1	F = A (not B)	F = A B plus A	F = AB plus A plus 1	
1	1	1	0	F = A B	F = A (not B) plus A	F = A (not B) plus A plus 1	
1	1	1	1	F = A	F = A	F = A plus 1	

© R.H. Katz Transparency No. 17-34

Arithmetic Logic Unit Design

74181 TTL ALU

Note that the sense of the carry in and out are OPPOSITE from the input bits

Fortunately, carry lookahead generator maintains the correct sense of the signals

© R.H. Katz Transparency No. 17-35

Arithmetic Logic Unit Design

16-bit ALU with Carry Lookahead

© R.H. Katz Transparency No. 17-36

Lecture Review

We have covered:

- *Binary Number Representation*
positive numbers the same
difference is in how negative numbers are represented
twos complement easiest to handle:
one representation for zero, slightly
complicated complementation, simple addition
- *Binary Networks for Additions*
basic HA, FA
carry lookahead logic
- *ALU Design*
specification and implementation