

What we HOPE you learned in CS 150 ...

- Language of logic design
 - ┆ Logic optimization, state, timing, CAD tools
- Concept of state in digital systems
 - ┆ Analogous to variables and program counters in software systems
- Hardware system building
 - ┆ Datapath + control = digital systems
- Hardware system design *methodology*
 - ┆ Hardware description languages: Verilog
 - ┆ Tools to simulate design behavior: *output* = function (*inputs*)
 - ┆ Logic compilers synthesize hardware blocks of our designs
 - ┆ Mapping onto programmable hardware (code generation)
- Contrast with software design
 - ┆ Both map specifications to physical devices
 - ┆ Both must be flawless...the price we pay for using discrete math

CS 150 - Spring 2004 - Lecture #21: Recap - 1

Current state of digital design

- Changes in industrial practice
 - ┆ Larger designs
 - ┆ Shorter time to market
 - ┆ Cheaper products
- Scale
 - ┆ Pervasive use of computer-aided design tools over hand methods
 - ┆ Multiple levels of design representation
- Time
 - ┆ Emphasis on abstract design representations
 - ┆ Programmable rather than fixed function components
 - ┆ Automatic synthesis techniques
 - ┆ Importance of sound design methodologies
- Cost
 - ┆ Higher levels of integration
 - ┆ Use of simulation to debug designs

CS 150 - Spring 2004 - Lecture #21: Recap - 2

CS 150: concepts/skills/abilities

- Basics of logic design (concepts)
- Sound design methodologies (concepts)
- Modern specification methods (concepts)
- Familiarity with full set of CAD tools (skills)
- Appreciation for differences and similarities (abilities) in hardware and software design

New ability: to accomplish the logic design task with the aid of computer-aided design tools and map a problem description into an implementation with programmable logic devices after validation via simulation and understanding of the advantages/disadvantages as compared to a software implementation

CS 150 - Spring 2004 - Lecture #21: Recap - 3

Representation of digital designs

- Physical devices (transistors, relays)
- *Switches*
- *Truth tables*
- *Boolean algebra*
- *Gates*
- **Waveforms** ← *Simulation & ChipScope*
- **Finite state behavior** ← *Verilog*
- **Register-transfer behavior** ← *Structural & Behavioral Descriptions*
- Concurrent abstract specifications

CS 150 - Spring 2004 - Lecture #21: Recap - 4

Digital System Design

- Door combination lock:
 - ┆ punch in 3 values in sequence and the door opens; if there is an error the lock must be reset; once the door opens the lock must be reset
 - ┆ inputs: sequence of input values, reset
 - ┆ outputs: door open/close
 - ┆ memory: must remember combination or always have it available as an input

CS 150 - Spring 2004 - Lecture #21: Recap - 5

Implementation in software

```
integer combination_lock ( ) {
    integer v1, v2, v3;
    integer error = 0;
    static integer c[3] = 3, 4, 2;

    while (!new_value ());
    v1 = read_value ( );
    if (v1 != c[1]) then error = 1;

    while (!new_value ());
    v2 = read_value ( );
    if (v2 != c[2]) then error = 1;

    while (!new_value ());
    v3 = read_value ( );
    if (v2 != c[3]) then error = 1;

    if (error == 1) then return(0); else return (1);
}
```

CS 150 - Spring 2004 - Lecture #21: Recap - 6


Implementation as a sequential digital system

Encoding:

- how many bits per input value?
- how many values in sequence?
- how do we know a new input value is entered?
- how do we represent the states of the system?

Behavior:

- clock wire tells us when it's ok to look at inputs (i.e., they have settled after change)
- sequential: sequence of values must be entered
- sequential: remember if an error occurred
- finite-state specification

 


CS 150 - Spring 2004 - Lecture #21: Recap - 7

Sequential example (cont'd): abstract control

Finite-state diagram

- States: 5 states
 - represent point in execution of machine
 - each state has outputs
- Transitions: 6 from state to state, 5 self transitions, 1 global
 - changes of state occur when clock says it's ok
 - based on value of inputs
- Inputs: reset, new, results of comparisons
- Output: open/closed

 


CS 150 - Spring 2004 - Lecture #21: Recap - 8

Sequential example (cont'd): data-path vs. control

Internal structure

- data-path
 - storage for combination
 - comparators
- control
 - finite-state machine controller
 - control for data-path
 - state changes controlled by clock

 


CS 150 - Spring 2004 - Lecture #21: Recap - 9

Sequential example (cont'd): finite-state machine

Finite-state machine

- refine state diagram to include internal structure

 


CS 150 - Spring 2004 - Lecture #21: Recap - 10

Sequential example (cont'd): finite-state machine

Finite-state machine

 - generate state table (much like a truth-table)



reset	new	equal	state	next state	mux	open/closed
1	-	-	-	S1	C1	closed
0	0	-	S1	S1	C1	closed
0	1	0	S1	ERR	-	closed
0	1	1	S1	S2	C2	closed
0	0	-	S2	S2	C2	closed
0	1	0	S2	ERR	-	closed
0	1	1	S2	S3	C3	closed
0	0	-	S3	S3	C3	closed
0	1	0	S3	ERR	-	closed
0	1	1	S3	OPEN	-	open
0	-	-	OPEN	OPEN	-	open
0	-	-	ERR	ERR	-	closed

CS 150 - Spring 2004 - Lecture #21: Recap - 11

Sequential example (cont'd): encoding

Encode state table

- state can be: S1, S2, S3, OPEN, or ERR
 - needs at least 3 bits to encode: 000, 001, 010, 011, 100
 - and as many as 5: 00001, 00010, 00100, 01000, 10000
 - choose 4 bits: 0001, 0010, 0100, 1000, 10000
- output mux can be: C1, C2, or C3
 - needs 2 to 3 bits to encode
 - choose 3 bits: 001, 010, 100
- output open/closed can be: open or closed
 - needs 1 or 2 bits to encode
 - choose 1 bits: 1, 0

CS 150 - Spring 2004 - Lecture #21: Recap - 12

Sequential example (cont'd): encoding

Encode state table

- state can be: S1, S2, S3, OPEN, or ERR
 - choose 4 bits: 0001, 0010, 0100, 1000, 0000
- output mux can be: C1, C2, or C3
 - choose 3 bits: 001, 010, 100
- output open/closed can be: open or closed
 - choose 1 bits: 1, 0

reset	new	equal	state	next state	mux	open/closed
1	-	-	-	0001	001	0
0	0	-	0001	0001	001	0
0	1	0	0001	0000	-	0
0	1	1	0001	0010	010	0
0	0	-	0010	0010	010	0
0	1	0	0010	0000	-	0
0	1	1	0010	0100	100	0
0	0	-	0100	0100	100	0
0	1	0	0100	0000	-	0
0	1	1	0100	1000	-	1
0	-	-	1000	1000	-	1
0	-	-	0000	0000	-	0

good choice of encoding!


mux is identical to last 3 bits of state

open/closed is identical to first bit of state

CS 150 - Spring 2004 - Lecture #21: Recap - 13


Sequential example (cont'd): controller implementation

Implementation of the controller

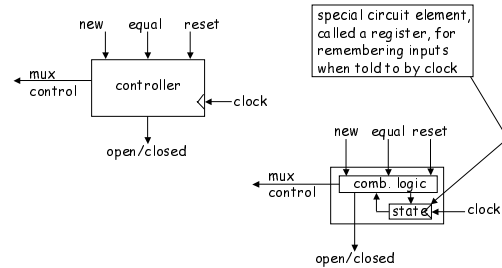


CS 150 - Spring 2004 - Lecture #21: Recap - 14

Design hierarchy

 

CS 150 - Spring 2004 - Lecture #21: Recap - 15

Design methodology

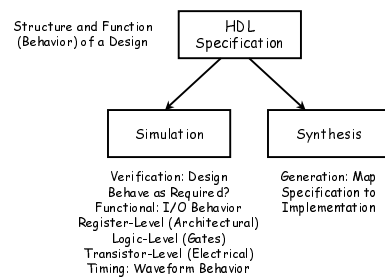

CS 150 - Spring 2004 - Lecture #21: Recap - 16

Combinational Logic Implementation

- K-map method to map truth tables into minimized gate level descriptions**
- Alternative implementation approaches:**
 - Two-level logic, multi-level logic, logic implementation with multiplexers
 - Programmable logic in the form of PALs, PLAs, and ROMs
 - Field programmable logic in the form of devices like Xilinx
- Combinational logic building blocks**
 - Arithmetic and logic units, including adders/subtractors and other arithmetic functions (e.g., combinational multipliers)

CS 150 - Spring 2004 - Lecture #21: Recap - 17

Sequential Logic Implementation

- Models for representing sequential circuits**
 - Abstraction of sequential elements
 - Finite state machines and their state diagrams
 - Inputs/outputs
 - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure**
 - Deriving state diagram
 - Deriving state transition table
 - Determining next state and output functions
 - Implementing combinational logic
- Sequential logic building blocks**
 - Registers, Register files (with multiple read and write ports), Shifters, Counters, RAMs
 - Arbitrators

CS 150 - Spring 2004 - Lecture #21: Recap - 18

State Machine Implementation

- **Partitioned State Machines**
 - Ways to organize single complex monolithic state machine into simpler, interacting state machines based on functional partitioning
 - Time state approach offers one conceptual method
 - Much more relevant is what you likely did in your course project
- **Issues of synchronization across independently clocked subsystems**
 - Synchronization of signals
 - Four cycle handshake

CS150 - Spring 2004 - Lecture #21: Recap - 19

Final Exam

- **Exam Group 2**
- **May 14, 12:30-3:30 PM**
- **Room 10 Evans**

CS150 - Spring 2004 - Lecture #21: Recap - 20

Final Exam

- **(Long) Design Specification in English for an "interesting" digital subsystem**
 - Function described in terms of desired input/output behavior
 - You will need to be able to hand generate waveform diagrams to demonstrate that you understand the design specification!
- **You will have to partition the subsystem into control and datapath**
 - Design the control part as one or more interacting Finite State Machines
 - State Diagrams as well as Verilog for control!
 - Design the datapath blocks
 - Behavioral Verilog mostly, but gate level hand-drawn schematics for some selected parts
- **You will have to revise the design to improve its performance**

CS150 - Spring 2004 - Lecture #21: Recap - 21

Final Exam

- **The Exam is conceptual and DESIGN-skills oriented**
- **The Exam is not about obscure details of technologies like the Xilinx internal architecture or fast arithmetic, etc.**
- **The best way to study for The Exam is to review your course project and to reflect on the *process* you went through in designing and implementing it**
- **The Exam design problem won't be a network switch—it will be some kind of digital system with control and a datapath that can be specified in a couple of pages of English text!**
- **You will need to write a lot for this Exam! Bring multiple pencils, erasers, rulers, AND AT LEAST TWO BLUE BOOKS!! You won't need a computer or a calculator!**
- **Open course textbook and open course notes. They probably won't help you much ;-)**

CS150 - Spring 2004 - Lecture #21: Recap - 22