

CS150 Spring 2004

Problem Set #6 Solutions

Greg Gibeling

Note that this is a fully functional verilog description of the alarm clock in problem #1. We will post a student solution to problem #2 once the homework is graded. Please see the zip file for the actual verilog for this problem.

```
`timescale 1 ns/1 ns
`define half_cycle27 18.5

module Testbench;

    reg          Clock, Reset;
    reg          SetHour, SetMinute;
    reg          AlarmMode, AlarmOn;
    reg          Snooze;

    wire [4:0]   DisplayHour;
    wire [5:0]   DisplayMinute;
    wire         AlarmSounding;

    AlarmClock   CUT(    .Clock(      Clock),
                        .Reset(      Reset),
                        .SetHour(    SetHour),
                        .SetMinute(  SetMinute),
                        .AlarmMode(  AlarmMode),
                        .AlarmOn(    AlarmOn),
                        .Snooze(     Snooze),
                        .DisplayHour( DisplayHour),
                        .DisplayMinute(DisplayMinute),
                        .AlarmSounding(AlarmSounding));

    always #(`half_cycle27) Clock = ~Clock;

    initial begin
        Clock =          1'b0;
        Reset =          1'b1;
        SetHour =        1'b0;
        SetMinute =      1'b0;
        AlarmMode =      1'b0;
        AlarmOn =        1'b0;
        Snooze =         1'b0;

        #(`half_cycle27 * 2);
        Reset =          1'b0;
        SetHour =        1'b1;
        #(`half_cycle27 * 34);
        SetHour =        1'b0;
        SetMinute =      1'b1;
        #(`half_cycle27 * 208);
        SetMinute =      1'b0;
        #(`half_cycle27 * 2);
        AlarmMode =      1'b1;
        #(`half_cycle27 * 2);
        SetHour =        1'b1;
        #(`half_cycle27 * 38);
        SetHour =        1'b0;
        SetMinute =      1'b1;
        #(`half_cycle27 * 2);
        SetMinute =      1'b0;
        AlarmOn =        1'b1;
        #(`half_cycle27 * 84);
        Snooze =         1'b1;
        #(`half_cycle27 * 2);
    end
endmodule
```

```

        Snooze =                1'b0;
    end
endmodule

module AlarmClock(
    Clock,          // 27MHz Reference Clock
    Reset,          // Power-up reset

    SetHour,        // The set-hour button
    SetMinute,      // The set-minute button

    AlarmMode,     // 1 if the toggle is set to "alarm mode"
    AlarmOn,        // 1 if the alarm is activated

    Snooze,         // The snooze button

    DisplayHour,   // The hour to display
    DisplayMinute, // the minute to display
    AlarmSounding // 1 if the alarm is sounding
);

input      Clock, Reset;
input      SetHour, SetMinute;
input      AlarmMode, AlarmOn;
input      Snooze;

output [4:0] DisplayHour;
output [5:0] DisplayMinute;
output      AlarmSounding;

wire       Minute, Hour;
wire       NextClockMinute, NextClockHour;
wire       NextAlarmMinute, NextAlarmHour;
wire       SnoozeDone;

wire [4:0] ClockHour, AlarmHour;
wire [5:0] ClockMinute, AlarmMinute;

wire       AlarmStart;
reg        AlarmPending;

assign DisplayHour =      AlarmMode ? AlarmHour : ClockHour;
assign DisplayMinute =   AlarmMode ? AlarmMinute : ClockMinute;

assign NextClockMinute = Minute | (~AlarmMode & SetMinute);
assign NextClockHour =   (Hour & Minute & ~SetMinute) | (~AlarmMode & SetHour);
assign NextAlarmMinute = AlarmMode & SetMinute;
assign NextAlarmHour =   AlarmMode & SetHour;

assign AlarmStart =      AlarmOn & (AlarmHour == ClockHour) & (AlarmMinute ==
ClockMinute);
assign AlarmSounding =   (AlarmPending | AlarmStart) & SnoozeDone;

always @ (posedge Clock) begin
    if (Reset | (Minute & AlarmSounding)) AlarmPending <= 1'b0;
    else if (AlarmStart) AlarmPending <= 1'b1;
end

Divide2Minute D2M_Inst(
    .Clock(      Clock),
    .Reset(      Reset),
    .Minute(     Minute));

MinuteCount MC_Clock(
    .Clock(      Clock),
    .Reset(      Reset),
    .Enable(     NextClockMinute),
    .Minute(     ClockMinute),
    .Rollover(   Hour));

HourCount HC_Clock(
    .Clock(      Clock),
    .Reset(      Reset),
    .Enable(     NextClockHour),

```

```

        .Hour(      ClockHour),
        .Rollover(  ));

MinuteCount  MC_Alarm(  .Clock(      Clock),
                      .Reset(      Reset),
                      .Enable(     NextAlarmMinute),
                      .Minute(     AlarmMinute),
                      .Rollover(    ));

HourCount    HC_Alarm(  .Clock(      Clock),
                      .Reset(      Reset),
                      .Enable(     NextAlarmHour),
                      .Hour(       AlarmHour),
                      .Rollover(    ));

SnoozeDelay  SD_Inst(  .Clock(      Clock),
                      .Reset(      Reset),
                      .Set(        Snooze & AlarmSounding),
                      .Enable(     Minute),
                      .Done(       SnoozeDone));

endmodule

module Divide2Minute( Clock,      // Clock Signal
                     Reset,      // Power-up Reset
                     Minute      // Goes high for one cycle once per minute
                     );

input      Clock, Reset;
output    Minute;

reg  [30:0] Count;

// Note that we're assuming a 27MHz clock...
// assign      Minute =          (Count == 31'd1619999999);

// Use a more "reasonable" number to allow simulation to run...
assign Minute =          (Count == 31'd3);

always @ (posedge Clock) begin
    if (Reset | Minute) Count <=          31'd0;
    else Count <=          Count + 1;
end
endmodule

module MinuteCount(  Clock,      // Clock Signal
                   Reset,      // Power-up Reset
                   Enable,     // Count a minute
                   Minute,     // The current minute
                   Rollover    // Goes high when we're about to roll over
                   );

input      Clock, Reset, Enable;
output [5:0] Minute;
output    Rollover;

reg  [5:0] Minute;

assign Rollover =          (Minute == 6'd59);

always @ (posedge Clock) begin
    if (Reset) Minute <=          6'd0;
    else if (Enable) begin
        if (Rollover) Minute <=          6'd0;
        else Minute <=          Minute + 1;
    end
end
endmodule

```

```

module HourCount(      Clock,          // Clock Signal
                       Reset,          // Power-up Reset
                       Enable,         // Count an hour
                       Hour,           // The current hour
                       Rollover        // Goes high when we're about to roll over
                       );

    input      Clock, Reset, Enable;
    output [4:0] Hour;
    output      Rollover;

    reg      [4:0] Hour;

    assign Rollover =                (Hour == 5'd23);

    always @ (posedge Clock) begin
        if (Reset) Hour <=          5'd0;
        else if (Enable) begin
            if (Rollover) Hour <=   5'd0;
            else Hour <=            Hour + 1;
        end
    end
endmodule

```

```

module SnoozeDelay(   Clock,          // Clock Signal
                       Reset,          // Power-up Reset
                       Set,            // Start the snooze delay
                       Enable,         // Count a minute
                       Done            // Goes high when the delay has run out
                       );

    input      Clock, Reset, Set, Enable;
    output      Done;

    reg      [2:0] Count;

    assign Done =                (~|Count);

    always @ (posedge Clock) begin
        if (Reset) Count <=        3'h0;
        else if (Set) Count <=     3'h5;
        else if (Enable & ~Done) Count <= Count - 1;
    end
endmodule

```