


CS150 Spring 2004

Problem Set #7 Solutions

Greg Gibeling

S1: $A \leftarrow \text{REG}_x$
 S2: $B \leftarrow \text{REG}_y$
 S3: $\text{REG}_x \leftarrow B$
 S4: $\text{REG}_y \leftarrow A$

} RTL

 

Note: Control signals not listed are assumed to be inactive.

```

module ControlFSM(Clock, Reset, RD, WR, SEL, LDA, LDB, ADD, PASSA, PASSB);
  input      Clock, Reset;
  output     RD, WR;
  output     SEL;
  output     LDA, LDB;
  output     ADD, PASSA, PASSB;

  parameter  STATE_S0 =          3'h0,
             STATE_S1 =          3'h1,
             STATE_S2 =          3'b2,
             STATE_S3 =          3'h3,
             STATE_S4 =          3'h4,
             STATE_... =         ...;
  // There could be lots of states...

  reg  [2:0] CurrentState, NextState;
  reg  RD, WR;
  reg  SEL;
  reg  LDA, LDB;
  reg  ADD, PASSA, PASSB;

  always @ (posedge Clock) begin
    if (Reset) CurrentState <= STATE_S0;
    else CurrentState <= NextState;
  end

  always @ (CurrentState or ...) begin
    NextState = CurrentState;
    RD = 1'b0;
    WR = 1'b0;
    SEL = 1'bx;
    LDA = 1'b0;
    LDB = 1'b0;
    ADD = 1'bx;
    PASSA = 1'bx;
    PASSB = 1'bx;

    case (CurrentState)
      STATE_S0: begin
        // Somehow we get into S1, for this
  
```

```

        // problem we don't care how
        if (...) NextState = STATE_S1;
    end
    STATE_S1: begin
        RD =          1'b1;
        SEL =         1'b0;
        LDA =         1'b1;
        NextState =   STATE_S2;
    end
    STATE_S2: begin
        RD =          1'b1;
        SEL =         1'b1;
        LDB =         1'b1;
        NextState =   STATE_S3;
    end
    STATE_S3: begin
        WR =          1'b1;
        SEL =         1'b0;
        ADD =         1'b0;
        PASSA =       1'b0;
        PASSB =       1'b1;
        NextState =   STATE_S4;
    end
    STATE_S4: begin
        WR =          1'b1;
        SEL =         1'b1;
        ADD =         1'b0;
        PASSA =       1'b1;
        PASSB =       1'b0;
        // Normaly we would say where to go
        // next but for this problem we don't
        // really care or know
        NextState =   ...;
    end
    default: begin
        NextState =   3'hX;
        RD =          1'bx;
        WR =          1'bx;
        SEL =         1'bx;
        LDA =         1'bx;
        LDB =         1'bx;
        ADD =         1'bx;
        PASSA =       1'bx;
        PASSB =       1'bx;
    end
endcase
end
endmodule

```

