

University of California at Berkeley
College of Engineering
Department of Electrical Engineering and Computer Science

EECS150, Spring 2010


Midterm Review: Sequential Logic, Basic Combinational Logic, Verilog, Video

March 29, 2010

Brandon Myers


This sheet is meant to pack a lot on a little paper. Use a separate piece of paper for your answers.

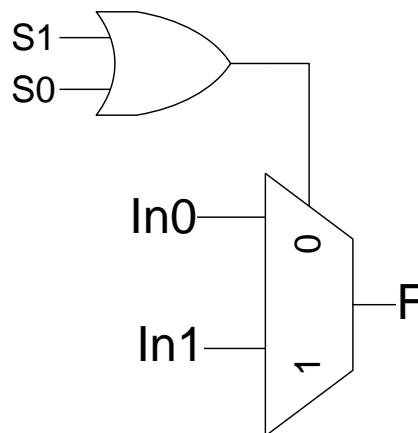1. Design a counter with one control input. When the input is high, the counter should sequence through three states: 11, 01, 10 and repeat. When the input is low the counter should sequence through the same states in the opposite order 11, 10, 01 and repeat.
 - (a) Implement the counter using D flip flops and whatever gates you like.
 - (b) Extra: Draw the state diagram and state transition table
2. Design a 4:16 decoder out of 2:4 decoders and 2-input gates.
3. Adapted from sp07-Mt1-Q3. Suppose we have the basic programmable logic block (instead of LUTs), shown below. All the inputs In_0, In_1, S_0, S_1 can be tied to input A, input B, 0, or 1.



Implement each of the following logic functions using the basic building block: A , A' , $A \text{ NAND } B$, $A \text{ NOR } B$, $A \text{ AND } B$, $A \text{ OR } B$, $A \text{ XOR } B$, $A \text{ XNOR } B$.

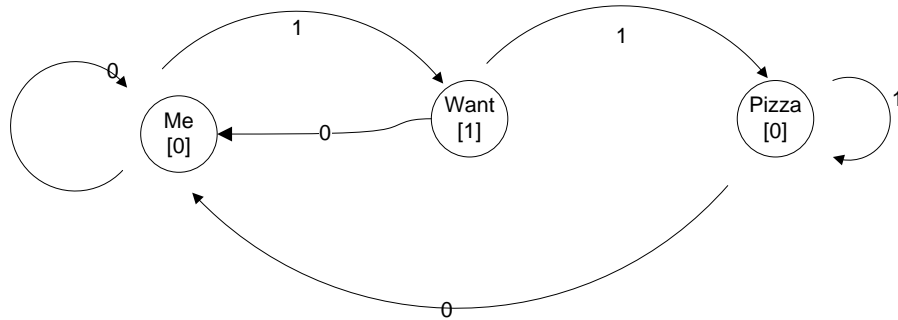4. Write a Verilog module for a level sensitive latch, with interface In , Out , and C ("clock"). It must have a parameter $Level$, which if 1 makes the latch sensitive to high and if 0 makes the latch sensitive to low.
5. Consider the FSM with the state-transition diagram below.



- (a) Describe the behavior of the FSM (when does it output 1?).
- (b) Write a Verilog module for the FSM.

6. Video. $W \times H$ F-fps display (i.e. W pixels/line, H lines, F frames per second). Horizontal blanking interval HB , vertical blanking interval VB , pixel clock frequency PF .

$$H * (W/PF + HB) + VB = 1/F$$

This equation comes from the fact that the total time to draw a frame ($1/F$) is equal to the time to draw every line (including HB at end of each line) plus VB .

7. The Bresenham Line Drawing Algorithm (without steepness/direction tests).

```

function line(x0, x1, y0, y1)
  int deltax := x1 - x0
  int deltay := y1 - y0
  int error := deltax / 2
  int y := y0
  for x from x0 to x1
    plot(x,y)
    error := error - deltay
    if error < 0 then
      y := y + 1
    error := error + deltax
  
```

Walk through the algorithm for input (1,1) to (7,4) (i.e. $(x_0, x_1, y_0, y_1) = (1, 7, 1, 4)$). Listing the pixel locations that will be drawn.