

Structural Verilog


UCB EECS150 Spring 2010
Lab Lecture #2

Agenda

- CAD Flow Extension
- Verilog
- Structural Verilog
- Administrative Info
- Lab #2: A Structural Accumulator
 - Circuit
 - Testing
 - Analysis of resource usage and timing
 - PreLab
- Questions?

UCB EECS150 Spring 2010, Lab Lecture #2 2


CAD Flow Extension (1)

 

UCB EECS150 Spring 2010, Lab Lecture #2 3

CAD Flow Extension (2)

- The Big Picture

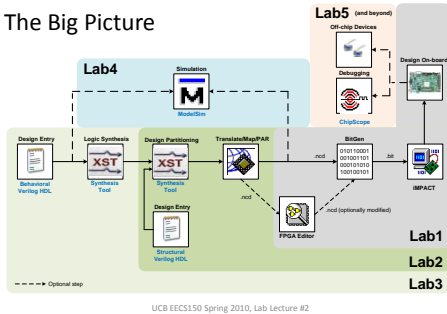


Verilog (1)

- What's an HDL?
 - Textual Description of a Circuit
 - Human and Machine Readable
 - Hierarchical
 - Meaningful Naming
- NOT A PROGRAM
 - Describe what the circuit IS
 - Not what it DOES


UCB EECS150 Spring 2010, Lab Lecture #2

Verilog + CAD

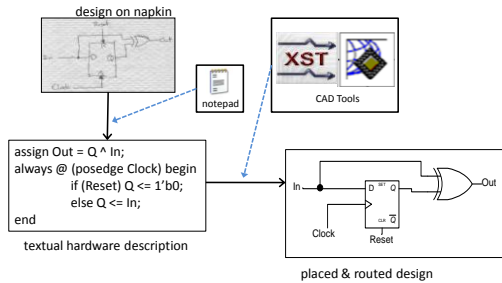

UCB EECS150 Spring 2010, Lab Lecture #2

Verilog + CAD

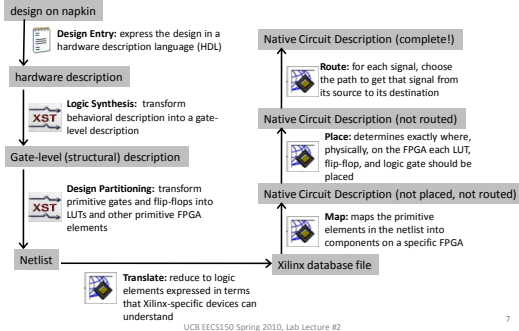





UCB EECS150 Spring 2010, Lab Lecture #2

7

Digital Design Productivity, Gates/Week

Source: DataQuest

  - Behavioral HDL  2K-10K
- RTL HDL  1K-2K
- Gates  100-200
- Transistors  10-20

UCB EECS150 Spring 2010, Lab Lecture #2

8

Structural Verilog (1)

- Verilog Subsets
 - Structural: primitive gates + modules
 - Gate level design
 - **You will ONLY use Structural Verilog in this lab**
 - Dataflow: compact boolean expressions
 - More compact expression of structural Verilog
 - Behavioral: abstract syntax
 - Timing nuances
 - You will see this starting next lab

UCB EECS150 Spring 2010, Lab Lecture #2

9

Structural Verilog (2)

- Structural 2:1 Mux example

```

module Mux21(A, B, S, Out):
  input wire A, B, S;
  output wire Out;

  wire notS, ATemp, BTemp;

  not invertS(notS, S);
  and and(ATemp, A, notS);
  andS(STemp, B, S);
  or result(Out, ATemp, BTemp);
endmodule
        
```

Key

- Module wrapper
- Input/Output wire declarations
- Wire declarations
- Gates

UCB EECS150 Spring 2010, Lab Lecture #2 10

Administrative Info (1)

- Homework submission
- Lab lecture conflicts
- Card key access
- Check-off procedure
- Questions?

UCB EECS150 Spring 2010, Lab Lecture #2 11


Lab #2 (1)

- Build a structural Accumulator
 - Work with a real design
 - Write parameterized Verilog
- Debugging
 - Synplicity RTL/Technology schematic
- Analysis
 - Resource consumption
 - Timing

UCB EECS150 Spring 2010, Lab Lecture #2 12

Lab #2 (2)

 - Structural Accumulator
 - ALU
 - 'FDRSE' Xilinx primitive flip-flop




UCB EECS150 Spring 2010, Lab Lecture #2

13

Lab #2 (3)

- ALU
 - We provide the Verilog for N-bit version
 - You must implement the 1-bit ALU model
 - **Must support our ALUOp**
 - Supports: +, -, &, |, ~, pass-through (7 operations)

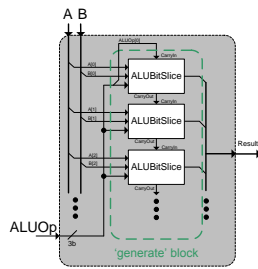


UCB EECS150 Spring 2010, Lab Lecture #2

14

Lab #2 (4)

 - FDRSE
 - Xilinx primitive
 - D-type flip-flop
 - Instantiated like a simple module
 - Specific Set/Reset characteristics
 - "Read all about it!" → virtex5_hdl.pdf
 - It's part of the PreLab!



UCB EECS150 Spring 2010, Lab Lecture #2

15


Lab #2 (5)

- Accumulator
 - We give you port specification
 - You will implement the rest of the circuit
- Use code examples
 - Mux21: Structural Verilog (gates, wires)
 - ALU: generate statements
- Abide by our interfaces!

UCB EECS150 Spring 2010, Lab Lecture #2 16

Lab #2 (6)

 - HW test harness
 - TA Accumulator vs. your Accumulator
 - Check all input combinations
 - Signal error



UCB EECS150 Spring 2010, Lab Lecture #2 17

Lab #2 (7)

- Circuit Analysis
 - Resource Usage
 - Accumulator(width) = how many LUTs / SLICES?
 - generate allows you to experiment
 - Timing
 - Locate nets → **“Technology Schematic”**
 - Calculate delay on the nets → **FPGA Editor**

UCB EECS150 Spring 2010, Lab Lecture #2 18

Lab #2 (8)

- PreLab
 - Read specified material
 - [Virtex-5 Libraries Guide for HDL Designs](#) (FDRSE section)
 - Design your ALUBitSlice and Accumulator
 - Write all of your Verilog
- Lab starts at debugging phase
 - Assumption:
you have written all of your Verilog ahead of time

UCB EECS150 Spring 2010, Lab Lecture #2

19

Acknowledgements & Contributors

Slides developed by Brandon Myers & John Wawrzynek (1/2010).

This work is based closely on slides by:

- Chris Fletcher (2008-2009)
- Greg Gibelg (2003-2005)

This work has been used by the following courses:

- UC Berkeley CS150 (Spring 2010): Components and Design Techniques for Digital Systems

UCB EECS150 Spring 2010, Lab Lecture #2

20
