

EECS150 - Digital Design
Lecture 20 - Combinational Logic
Circuits (Part 2)


April 1, 2010
John Wawrzynek

Outline

- Review of three representations for combinational logic:
 - truth tables,
 - graphical (logic gates), and
 - algebraic equations
- Relationship among the three
- Adder example
- Laws of Boolean Algebra
- Canonical Forms
- Boolean Simplification

Relationship Among Representations

 - * Theorem: Any Boolean function that can be expressed as a truth table can be written as an expression in Boolean Algebra using AND, OR, NOT.



How do we convert from one to the other?

Outline for remaining CL Topics

- K-map method of two-level logic simplification
- Multi-level Logic
- NAND/NOR networks
- EXOR revisited

Algorithmic Two-level Logic Simplification

Key tool: The Uniting Theorem:

$$xy' + xy = x(y' + y) = x(1) = x$$

ab	f
00	0
01	0
10	1
11	1

$$f = ab' + ab = a(b' + b) = a$$

b values change within the on-set rows

a values don't change

b is eliminated, a remains

ab	g
00	1
01	0
10	1
11	0

$$g = a'b' + ab' = (a' + a)b' = b'$$

b values stay the same

a values changes

b' remains, a is eliminated


Boolean Cubes

Visual technique for identifying when the Uniting Theorem can be applied


Alternative way to represent boolean functions.

Filled in nodes represent a 1 in the function.

 Moving between adjacent nodes represents changing only one input.



 
- Sub-cubes of on-nodes can be used for simplification.
 - On-set: filled in nodes, off-set: empty nodes




3-variable cube example

FA carry out:

a	b	c	cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

What about larger sub-cubes?

 




$$ab'c' + ab'c + abc' + abc$$

$$ac' + ac + ab = a + ab = a$$

- Both b & c change, a is asserted & remains constant.

Karnaugh Map Method

   - K-map is an alternative method of representing the TT and to help visual the adjacencies.



5 & 6 variable k-maps possible

Karnaugh Map Method

- Adjacent groups of 1's represent product terms

	a	0	1
b	0	0	1
	1	0	1

$f = a$

	a	0	1
b	0	1	1
	1	0	0

$g = b'$

	ab	00	01	11	10
c	0	0	0	1	0
	1	0	1	1	1

$cout = ab + bc + ac$

	ab	00	01	11	10
c	0	0	0	1	1
	1	0	0	1	1

$f = a$

K-map Simplification

1. Draw K-map of the appropriate number of variables (between 2 and 6)
2. Fill in map with function values from truth table.
3. Form groups of 1's.
 - ✓ Dimensions of groups must be even powers of two (1x1, 1x2, 1x4, ..., 2x2, 2x4, ...)
 - ✓ Form as large as possible groups and as few groups as possible.
 - ✓ Groups can overlap (this helps make larger groups)
 - ✓ Remember K-map is periodical in all dimensions (groups can cross over edges of map and continue on other side)
4. For each group write a product term.
 - the term includes the "constant" variables (use the uncomplemented variable for a constant 1 and complemented variable for constant 0)
5. Form Boolean expression as sum-of-products.

K-maps (cont.)

		ab			
		00	01	11	10
c	0	1	0	0	1
	1	0	0	1	1

$$f = b'c' + ac$$

		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$f = c + a'bd + b'd'$
(bigger groups are better)

Product-of-Sums Version

- Form groups of 0's instead of 1's.
- For each group write a sum term.
 - the term includes the "constant" variables (use the uncomplemented variable for a constant 0 and complemented variable for constant 1)
- Form Boolean expression as product-of-sums.


		ab			
		00	01	11	10
cd	00	1	0	0	1
	01	0	1	0	0
	11	1	1	1	1
	10	1	1	1	1

$$f = (b' + c + d)(a' + c + d')(b + c + d')$$

BCD incrementer example

Binary Coded Decimal

	a	b	c	d	w	x	y	z
0	0	0	0	0	0	0	0	1
1	0	0	0	1	0	0	1	0
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	1	0	0
4	0	1	0	0	0	1	0	1
5	0	1	0	1	0	1	1	0
6	0	1	1	0	0	1	1	1
7	0	1	1	1	1	0	0	0
8	1	0	0	0	1	0	0	1
9	1	0	0	1	0	0	0	0
	1	0	1	0	-	-	-	-
	1	0	1	1	-	-	-	-
	1	1	0	0	-	-	-	-
	1	1	0	1	-	-	-	-
	1	1	1	0	-	-	-	-
	1	1	1	1	-	-	-	-

 

BCD Incrementer Example

- Note one map for each output variable.
- Function includes "don't cares" (shown as "-" in the table).
 - These correspond to places in the function where we don't care about its value, because we don't expect some particular input patterns.
 - We are free to assign either 0 or 1 to each don't care in the function, as a means to increase group sizes.
- In general, you might choose to write product-of-sums or sum-of-products according to which one leads to a simpler expression.



BCD incrementer example

	W	X	
cd	ab	ab	
	00 01 11 10	00 01 11 10	
00	0 0 - 1	0 1 - 0	w =
01	0 0 - 0	0 1 - 0	
11	0 1 - -	1 0 - -	x =
10	0 0 - -	0 1 - -	
cd	ab	ab	
	00 01 11 10	00 01 11 10	
00	0 0 - 0	1 1 - 1	y =
01	1 1 - 0	0 0 - 0	
11	0 0 - -	0 0 - -	z =
10	1 1 - -	1 1 - -	

BCD incrementer example

	W	X	
cd	ab	ab	
	00 01 11 10	00 01 11 10	
00	0 0 - 1	0 1 - 0	w =
01	0 0 - 0	0 1 - 0	
11	0 1 - -	1 0 - -	x =
10	0 0 - -	0 1 - -	
cd	ab	ab	
	00 01 11 10	00 01 11 10	
00	0 0 - 0	1 1 - 1	y =
01	1 1 - 0	0 0 - 0	
11	0 0 - -	0 0 - -	z =
10	1 1 - -	1 1 - -	

Higher Dimensional K-maps

  

Multi-level Combinational Logic


- Example: reduced sum-of-products form
 $x = adf + aef + bdf + bef + cdf + cef + g$

- Implementation in 2-levels with gates:

cost: 1 7-input OR, 6 3-input AND

=> 50 transistors

 delay: 3-input OR gate delay + 7-input AND gate delay




- Factored form:

$$x = (a + b + c)(d + e)f + g$$

cost: 1 3-input OR, 2 2-input OR, 1 3-input AND

=> 20 transistors

 delay: 3-input OR + 3-input AND + 2-input OR




Footnote: NAND would be used in place of all ANDs and ORs.

Which is faster?

In general: Using multiple levels (more than 2) will reduce the cost. Sometimes also delay. Sometimes a tradeoff between cost and delay.


Multi-level Combinational Logic

 Another Example: $F = abc + abd + a'c'd' + b'c'd'$



let $x = ab$ $y = c+d$

$f = xy + x'y'$

 

Incorporates fanout.

No convenient hand methods exist for multi-level logic simplification:

- a) CAD Tools use sophisticated algorithms and heuristics
- b) Humans and tools often exploit some special structure (example adder)

Are these optimizations still relevant for LUT implementations?

NAND-NAND & NOR-NOR Networks





DeMorgan's Law Review:

$$(a + b)' = a' b'$$

$$(a b)' = a' + b'$$

$$a + b = (a' b')'$$

$$(a b) = (a' + b')'$$

    


push bubbles or introduce in pairs or remove pairs:

$$(x')' = x.$$


NAND-NAND & NOR-NOR Networks

- Mapping from AND/OR to NAND/NAND

 


NAND-NAND & NOR-NOR Networks

 - Mapping AND/OR to NOR/NOR
- Mapping OR/AND to NOR/NOR



 
- OR/AND to NAND/NAND (by symmetry with above)




Multi-level Networks

Convert to NANDs:

$$F = a(b + cd) + bc'$$

 

(note fanout)



 


EXOR Function

Parity, addition mod 2

$$x \oplus y = x'y + xy'$$

x	y	xor	xnor
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

   

Another approach:

