

EECS150 - Digital Design

Lecture 7 - Computer Aided Design

(CAD) - Part II (Logic Simulation)

Feb 8, 2011
John Wawrzynek

Procedural Assignments


The sequential semantics of the blocking assignment allows variables to be multiply assigned within a single always block. Unexpected behavior can result from mixing these assignments in a single block. Standard rules:

- i. Use blocking assignments to model combinational logic within an always block ("=").
- ii. Use non-blocking assignments to implement sequential logic ("<=").
- iii. Do not mix blocking and non-blocking assignments in the same always block.
- iv. Do not make assignments to the same variable from more than one always block.


Finite State Machine Review

State Transition Diagram

Implementation Circuit Diagram

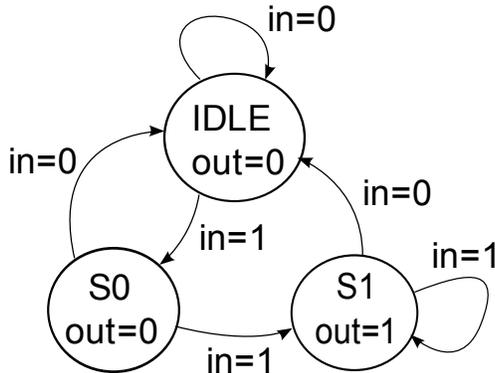

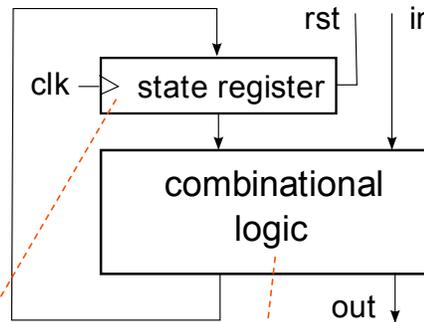Holds a symbol to keep track of which bubble the FSM is in.



CL functions to determine output value and next state based on input and current state.

$out = f(in, \text{current state})$

$next\ state = f(in, \text{current state})$

What does this one do?

Every Synchronous Digital System is a FSM.

Finite State Machines

```
module FSM1(clk, rst, in, out);
input clk, rst;
input in;
output out;
```

Must use reset to force to initial state.

reset not always shown in STD

```
// Defined state encoding:
parameter IDLE = 2'b00;
parameter S0 = 2'b01;
parameter S1 = 2'b10;
```

Constants local to this module.


```
reg out;
reg [1:0] state, next_state;
```

out not a register, but assigned in always block

Combinational logic signals for transition.

THE register to hold the "state" of the FSM.
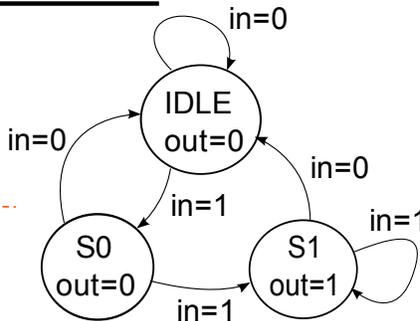
```
// always block for state register
always @(posedge clk)
if (rst) state <= IDLE;
else state <= next_state;
```



A separate always block should be used for combination logic part of FSM. Next state and output generation. (Always blocks in a design work in parallel.)

FSM CL block rewritten

```

always @*
begin
  next_state = IDLE;
  out = 1'b0;
  case (state)
    IDLE : if (in == 1'b1) next_state = S0;
    S0    : if (in == 1'b1) next_state = S1;
    S1    : begin
              out = 1'b1;
              if (in == 1'b1) next_state = S1;
            end
    default: ;
  endcase
end
endmodule


```

* for sensitivity list

Normal values: used unless specified below.

Within case only need to specify exceptions to the normal values.

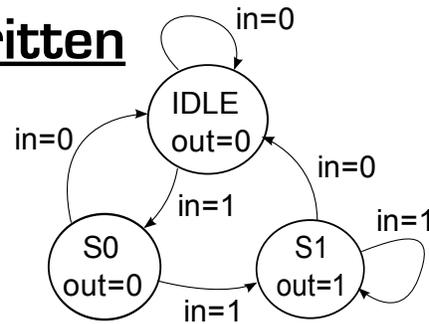Note: The use of "blocking assignments" allow signal values to be "rewritten", simplifying the specification.



Encoder Example

Nested IF-ELSE might lead to "priority logic"


Example: 4-to-2 encoder

```

always @(x)
begin : encode
  if (x == 4'b0001) y = 2'b00;
  else if (x == 4'b0010) y = 2'b01;
  else if (x == 4'b0100) y = 2'b10;
  else if (x == 4'b1000) y = 2'b11;
  else y = 2'bxx;
end

```

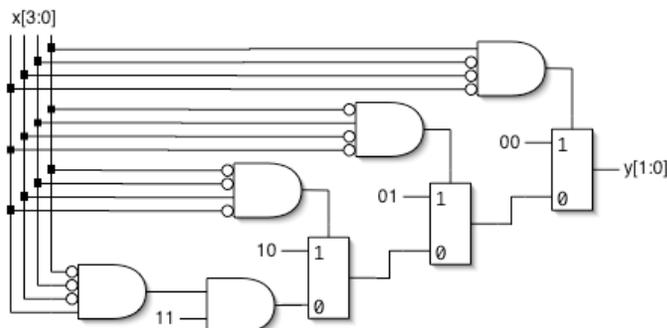
This style of cascaded logic may adversely affect the performance of the circuit.



Encoder Example (cont.)

To avoid "priority logic" use the case construct:

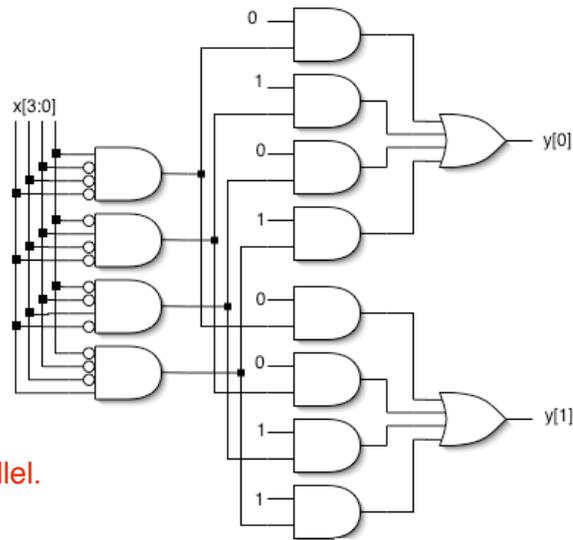
```
always @(x)
begin : encode
case (x)
4'b0001: y = 2'b00;
4'b0010: y = 2'b01;
4'b0100: y = 2'b10;
4'b1000: y = 2'b11;
default: y = 2'bxx;
endcase
end
```



All cases are matched in parallel.

Encoder Example (cont.)

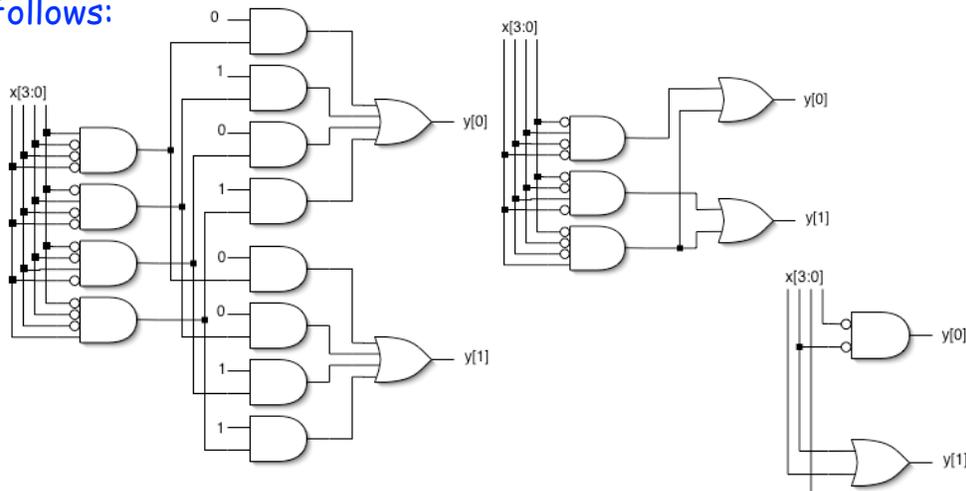This circuit would be simplified during synthesis to take advantage of constant values and other Boolean equalities as follows:




A similar simplification would be applied to the if-else version also.

Encoder Example (cont.)

If you can guarantee that only one 1 appears in the input, then simpler logic can be generated:
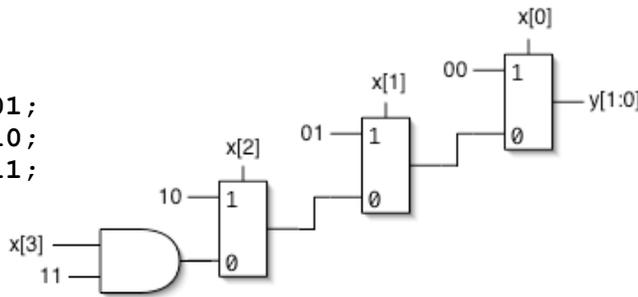
```
always @(x)
begin : encode
if (x[0]) y = 2'b00;
else if (x[1]) y = 2'b01;
else if (x[2]) y = 2'b10;
else if (x[3]) y = 2'b11;
else y = 2'bxx;
end
```



If the input applied has more than one 1, then this version functions as a "priority encoder". The least significant 1 gets priority (the more significant 1's are ignored). Again the circuit will be simplified when possible.

Verilog in EECS150

- Primarily use **behavior modeling**. With **instantiation** to build hierarchy and map to FPGA resources not supported by synthesis.
- Primary Style Guidelines:
 - Favor continuous assign and avoid always blocks unless:
 - no other alternative: ex: state elements, case
 - they help readability and clarity of code: ex: large nested if-else-if
 - Use named ports.
 - Separate CL logic specification from state elements.
 - Follow our rules for procedural assignments.
- Verilog is a big language. This is only an introduction.
 - Our text book is a good source. Read and use chapter 4.
 - When needed look at online IEEE Std 1364-2001 document.
 - Be careful of what you read on the web! Many bad examples out there.
 - We will be introducing more useful constructs throughout the semester. Stay tuned!

Final thoughts on Verilog Examples


Verilog may look like C, but it describes hardware! (Except in simulation test-benches - which actually behave like programs.)

Multiple physical elements with parallel activities and temporal relationships.

A large part of digital design is knowing how to write Verilog that gets you the desired circuit. First understand the circuit you want, then figure out how to code it in Verilog. If you do one of these activities without the other, you will struggle. These two activities will merge at some point for you.

Be suspicious of the synthesis tools! Check the output of the tools to make sure you get what you want.

EECS150 Design Methodology

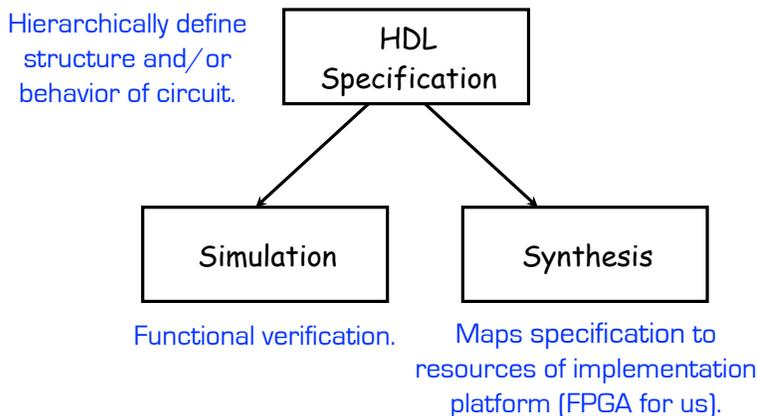

Let's look at the other branch.

Design Verification

- Industrial design teams spend a large percentage of the design time on design verification:
 - Removing functional bugs, messaging the design to meet performance, cost, and power constraints.
- Particularly important for IC design, less so for FPGAs.
- A variety of tools and strategies are employed.
 - **Simulation:** software that interprets the design description and mimics signal behavior and timing (and power consumption).
 - Simulation provides better controllability and observability over real hardware. Saves on wasted development time and money.
 - **Emulation:** hardware platform (usually FPGAs) are used to mimic behavior of another system. Fast simulation.
 - **Static Analysis:** tools examines circuit structure and reports on expected performance, power, or compares alternative design representations looking for differences.

Spring 2011

EECS150 - Lec7-CAD2


Page 13

Simulation

Verilog/VHDL simulators use 4 signals values:

0, 1, X (unknown), Z (undriven)

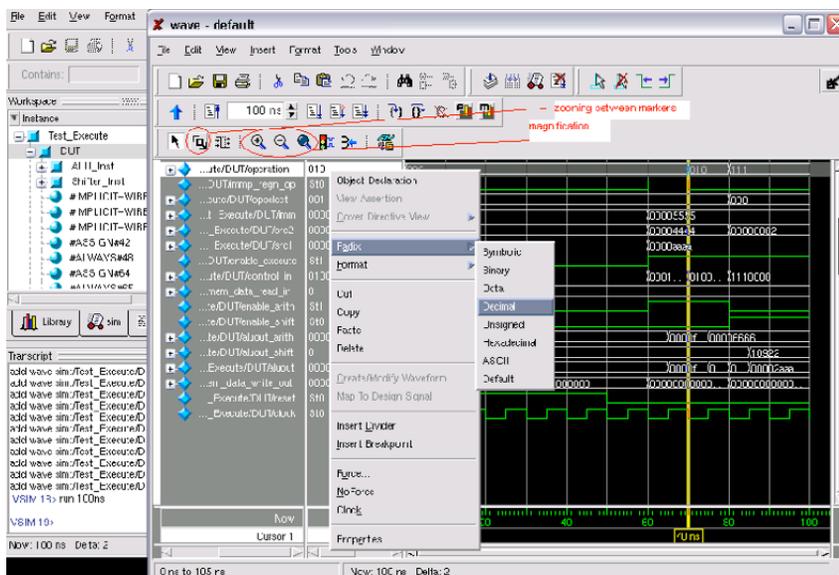Simulation engine algorithm typically "discrete event simulation"



ModelSim:
waveform
viewer, GUI.

Page 14

Discrete Event Simulation Engine


- A time-ordered list of events is maintained

Event: a value-change scheduled to occur at a given time

All events for a given time are kept together

- The scheduler removes events for a given time ...

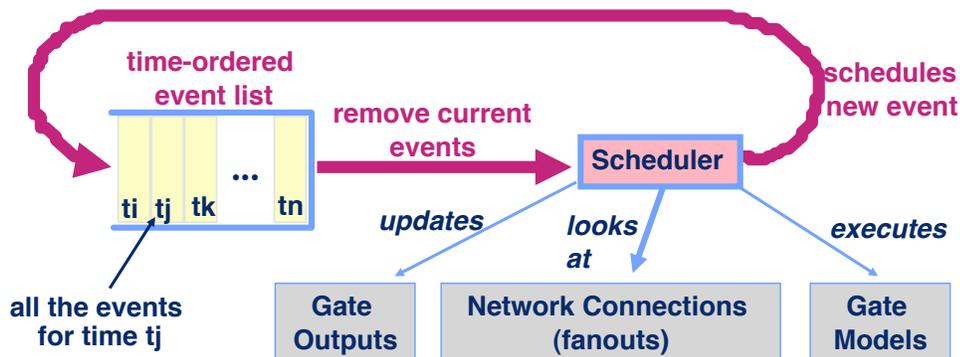... propagates values, executes models, and creates new events ...



Slide from Thomas. *The Verilog Hardware Description Language*,
By Thomas and Moorby, Kluwer Academic Publishers

Spring 2011

Page 15

Simulation Testing Strategies

- **Unit Testing:** Large systems are often too complex to test all at once, so an bottom-up hierarchical approach. Sub-modules are tested in isolation.
- **Combinational Logic blocks:** when practical, exhaustive testing. Otherwise a combination of random and directed tests.
- **Finite state machines:** test every possible transition and output.
- **Processors:** use software to expose bugs.
- In all cases, the simulated output values are checked against the expected values. Expected values are derived through a variety of means:
 - behavior model running along side the design under test
 - precomputed inputs and outputs (vectors)
 - co-simulation. Ex: C-language model runs along side ModelSim

Spring 2011

EECS150 - Lec7-CAD2

Page 16

Testbench

Top-level modules written specifically to test other modules.

```
module testmux; ----- Generally no ports.
  reg a, b, s;
  wire f;
  reg expected;

  mux2 myMux (.select(s), .in0(a), .in1(b), .out(f)); ----- Instantiation of DUT
  (device under test).

  initial ----- Initial block similar to "always" block
  begin ----- without a trigger. It triggers once
    s=0; a=0; b=1; expected=0; ----- automatically at the beginning of
    #10 a=1; b=0; expected=1; ----- simulation. (Also supported on FPGAs).
    #10 s=1; a=0; b=1; expected=1; ----- "#n" used to advance time in
  end ----- simulation. Delays some action by
  initial ----- a number of simulation time units.
  $monitor( ----- Note use of blocking
    "select=%b in0=%b in1=%b out=%b, expected out=%b time=%d", ----- assignments.
    s, a, b, f, expected, $time); ----- Note multiple initial blocks.
  endmodule // testmux ----- $monitor triggers whenever
  any of its inputs change.
  Sends output to console.

A variety of other "system functions exist for ----- Most simulators also include a
displaying output and controlling the simulation. ----- way to view waveforms of a
set of signals.
```

Spring 2011 EECS150 - Lec7-CAD2 Page 17

Mux4 Testbench

```
module testmux4;
  reg [5:0] count = 6'b000000; ----- Declaration and initialization all at once.
  reg a, b, c, d, expected; ----- Generally not available in synthesis.
  reg [1:0] S;
  wire f;
  mux4 myMux (.select(S), .in0(a), .in1(b), .in2(c), .in3(d), .out(f)); ----- DUT instantiation
  initial
  begin ----- Enumerate all possible input patterns.
    repeat(64) ----- Apply pattern to DUT
    begin
      {S, d, c, b, a} = count[5:0];
      case (S) ----- Behavioral model of mux4
        2'b00: expected = a;
        2'b01: expected = b;
        2'b10: expected = c;
        2'b11: expected = d;
      endcase // case(S)
      #8 $strobe( "select=%b in0=%b in1=%b in2=%b in3=%b out=%b, ----- $strobe displays data at a selected time. That
        expected=%b time=%d", S, a, b, c, d, f, expected, $time); ----- time is just before simulation time is
        #2 count = count + 1'b1; ----- advanced (after all other events).
      end ----- Delay to allow mux outputs to stabilize.
      $stop; ----- Here we assume mux delay < 8ns.
    end ----- Alternative to $strobe in this case,
  end ----- #8 if (f != expected) $display("Mismatch: ...");
endmodule
```

Spring 2011 EECS150 - Lec7-CAD2 Page 18


FSM Testbench Example

```

module testFSM;
  reg in;
  wire out;
  reg clk=0, rst;
  reg expect;
  FSM1 myFSM (.out(out), .in(in), .clk(clk), .rst(rst));
  always #5 clk = ~clk;
  initial
  begin
    rst=1;
    #10 in=0; rst=0; expect=0;
    #10 in=1; rst=0; expect=0;
    #10 in=0; rst=0; expect=0;
    #10 in=1; rst=0; expect=0;
    #10 in=1; rst=0; expect=1;
    #10 in=1; rst=0; expect=1;
    #10 in=0; rst=0; expect=0;
    #10 $stop;
  end
  always
  begin
    #4 $strobe($time, " in=%b, rst=%b, expect=%b out=%b", in, rst, expect, out);
    #6 ;
  end
endmodule

```

Test all arcs.

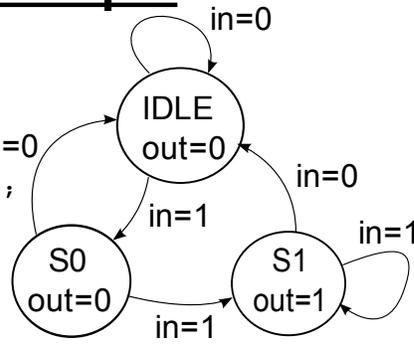

DUT instantiation

100MHz clk signal

start in IDLE

self-loop

transition to S0

transition to IDLE

transition to S0

transition to S1

self-loop

transition to IDLE

Note: Input changes are forced to occur on negative edge of clock.

Strobe output occurs 1ns before rising edge of clock.

Debug is easier if you have access to state value also. Either 1) bring out to ports, or 2) use waveform viewer.

19

Final Words (for now) on Simulation

Testing is not always fun, but you should view it as part of the design process. Untested potentially buggy designs are a dime-a-dozen. Verified designs have real value.

Devising a test strategy is an integral part of the the design process. It shows that you have your head around the design. It should not be an afterthought.