
 
 


EECS150 - Digital Design
Lecture 21 - Design Blocks

April 3, 2012
John Wawrzynek


Fixed Shifters / Rotators

 - "fixed" shifters
"hardwire" the shift amount into the circuit.
- Ex: verilog: $X \gg 2$
 - (right shift X by 2 places)
- Fixed shift/rotator is nothing but wires!
So what?



Variable Shifters / Rotators

 
- Example: $X \gg S$, where S is unknown when we synthesize the circuit.
- Uses: shift instruction in processors (ARM includes a shift on every instruction), floating-point arithmetic, division/multiplication by powers of 2, etc.
- One way to build this is a simple shift-register:
 - a) Load word,
 - b) shift enable for S cycles,
 - c) read word.




- Worst case delay $O(N)$, not good for processor design.
- Can we do it in $O(\log N)$ time and fit it in one cycle?

Log Shifter / Rotator

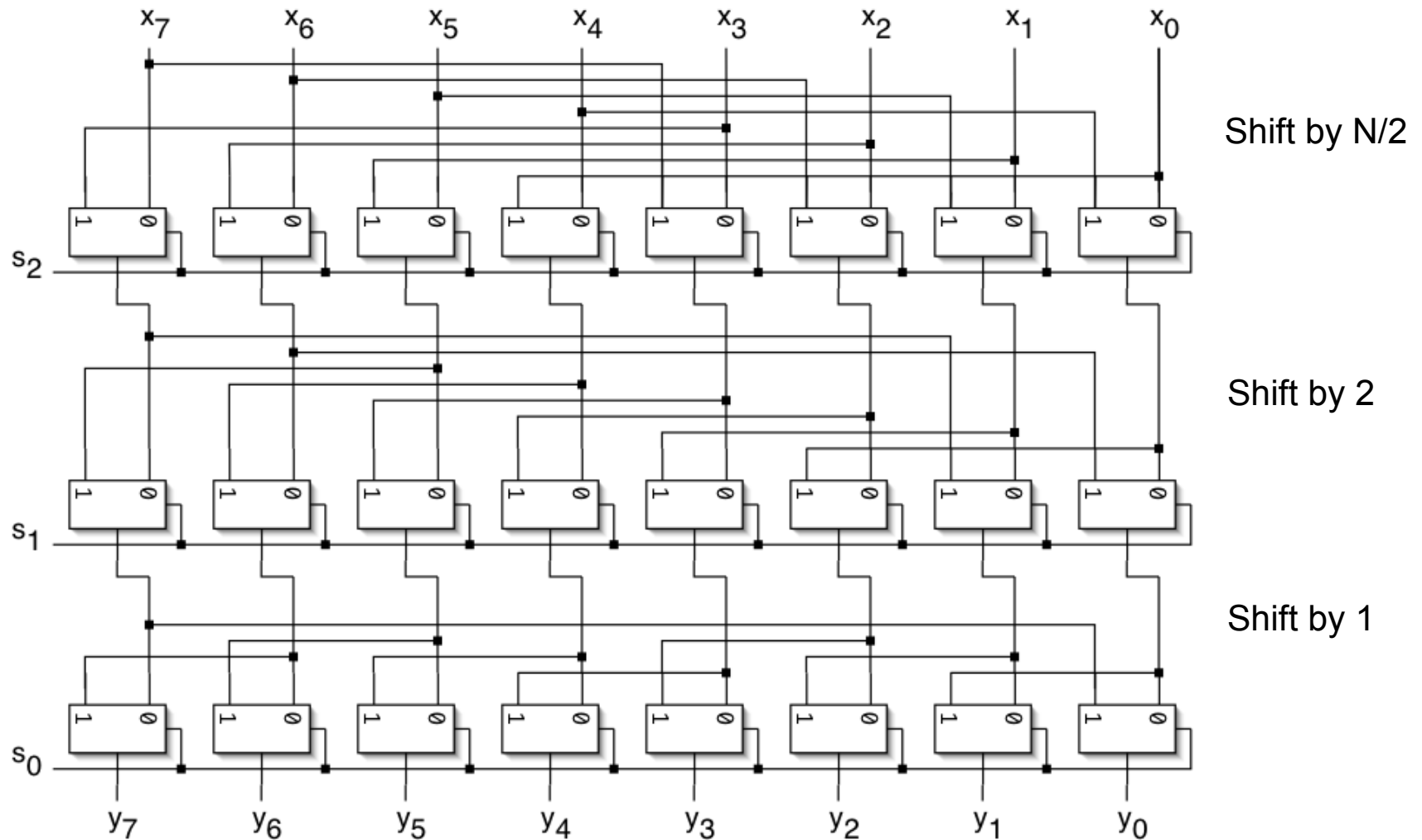- $\log(N)$ stages, each shifts (or not) by a power of 2 places,





LUT Mapping of Log shifter

 

Efficient with 2to1 multiplexors, for instance, 3LUTs.

Virtex6 has 6LUTs. Naturally makes 4to1 muxes:


Reorganize shifter to use 4to1 muxes.

  

Final stage uses F7 mux


“Improved” Shifter / Rotator

 - How about this approach? Could it lead to even less delay?



- What is the delay of these big muxes?
- Look a transistor-level implementation?


Barrel Shifter

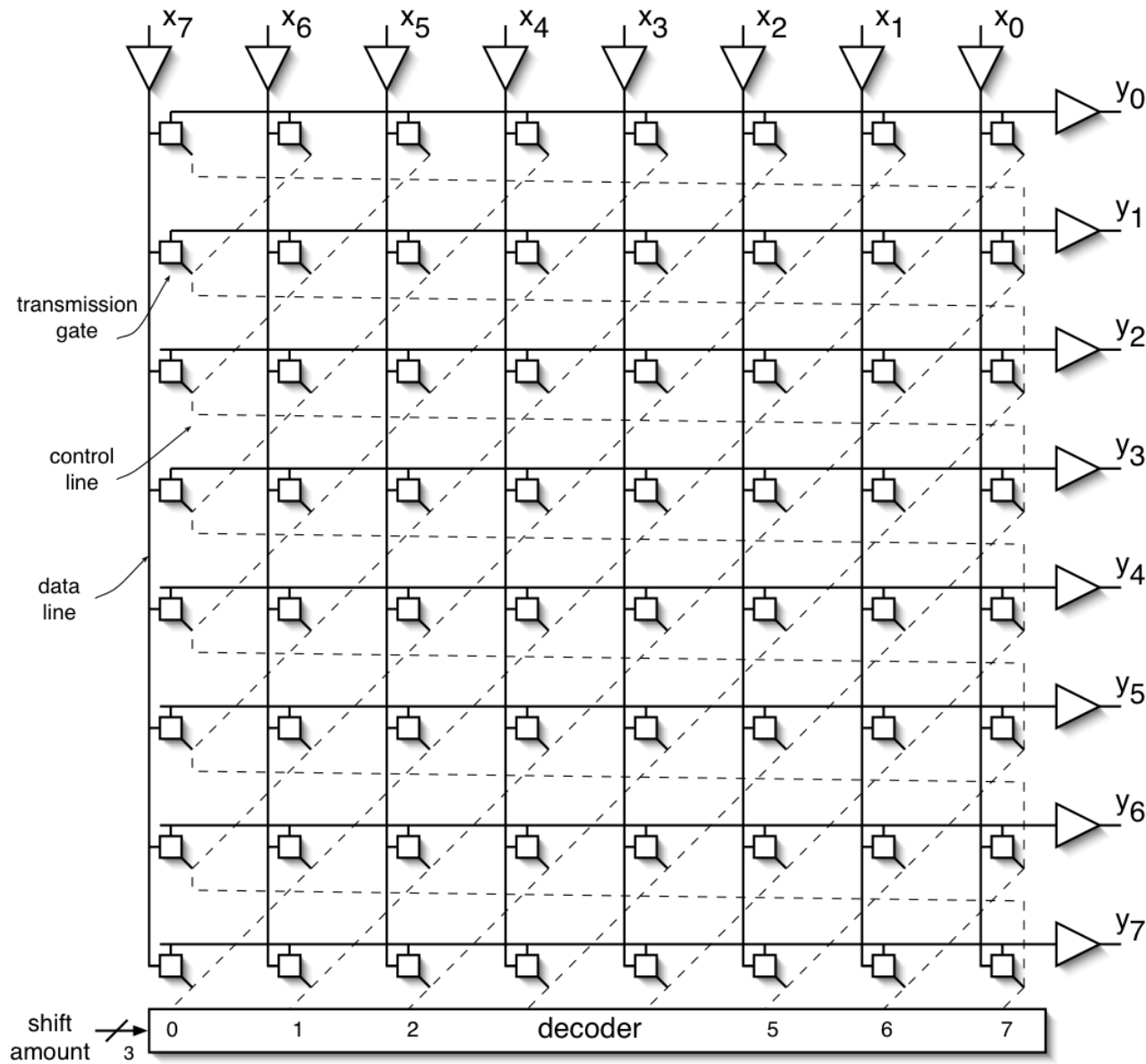

Cost/delay?

- (don't forget the decoder)


Connection Matrix

 

Generally useful structure:

- N^2 control points.
- What other interesting functions can it do?


Cross-bar Switch

 


- $N \log(N)$ control signals.
- Supports all interesting permutations
 - All one-to-one and one-to-many connections.
- Commonly used in communication hardware (switches, routers).

Linear Feedback Shift Registers (LFSRs)

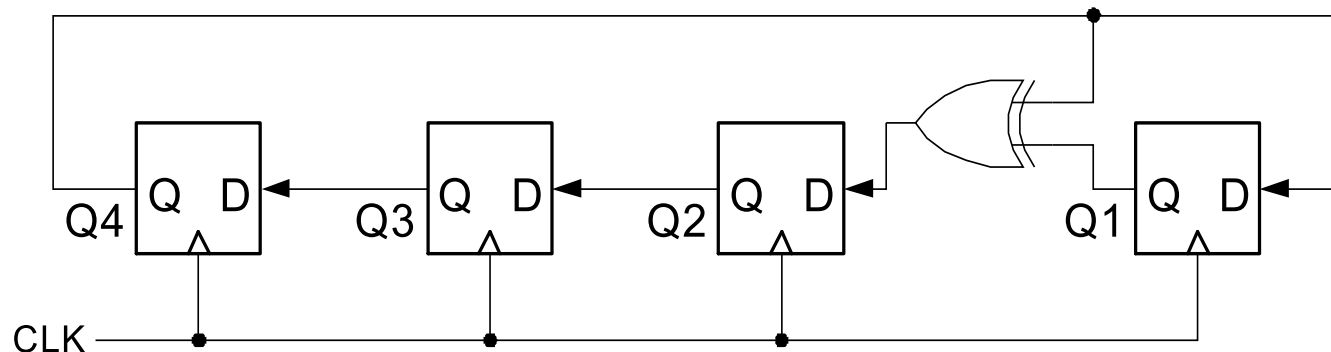
- These are n-bit counters exhibiting *pseudo-random* behavior.
- Built from simple shift-registers with a small number of xor gates.
- Used for:
 - random number generation
 - counters
 - error checking and correction
- Advantages:
 - very little hardware
 - high speed operation
- Example 4-bit LFSR:



4-bit LFSR

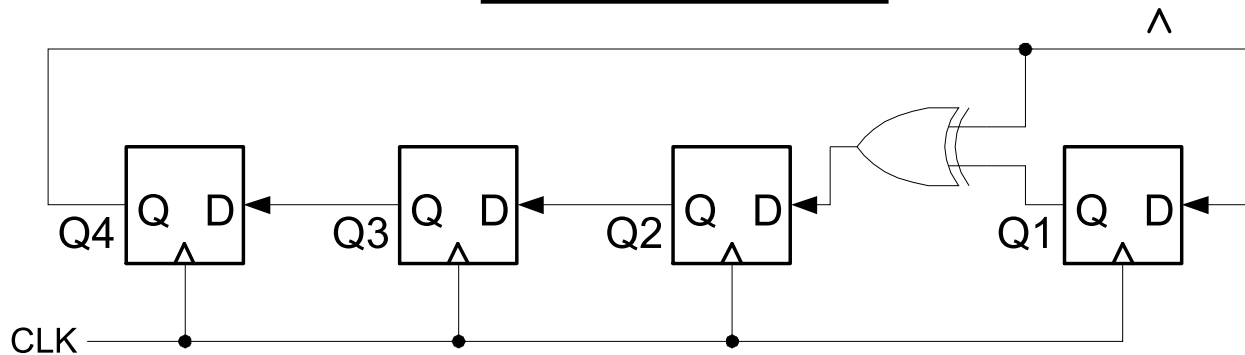

- Circuit counts through 2^4-1 different non-zero bit patterns.
- Leftmost bit decides whether the “10011” xor pattern is used to compute the next value or if the register just shifts left.
- Can build a similar circuit with any number of FFs, may need more xor gates.
- In general, with n flip-flops, 2^n-1 different non-zero bit patterns.
- (Intuitively, this is a counter that *wraps around* many times and in a strange way.)

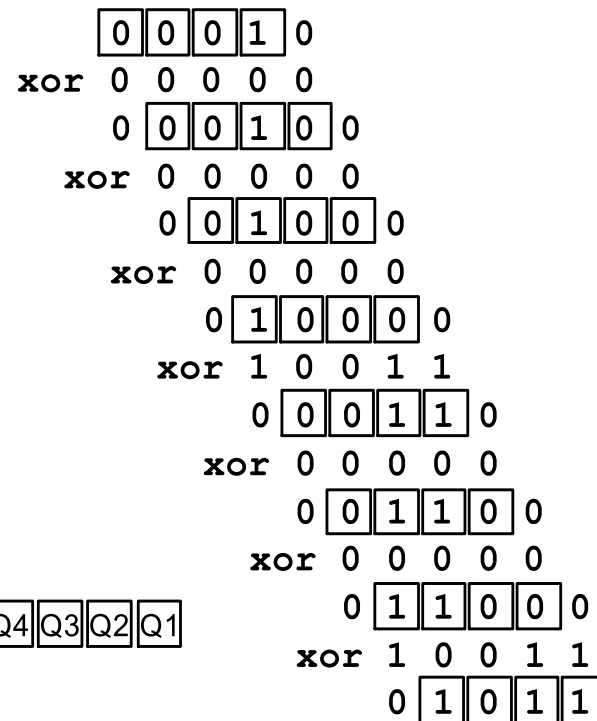

Q4 Q3 Q2 Q1

0001
 0010
 0100
 1000
 0011
 0110
 1100
 1011
 0101
 1010
 0111
 1110
 1111
 1101
 1001
 0001



Applications of LFSRs

- Performance:
 - In general, xors are only ever 2-input and never connect in series.
 - Therefore the minimum clock period for these circuits is:
$$T > T_{2\text{-input-xor}} + \text{clock overhead}$$
 - Very little latency, and independent of n!
- This can be used as a fast counter, if the particular sequence of count values is not important.
 - Example: micro-code micro-pc
- Can be used as a random number generator.
 - Sequence is a pseudo-random sequence:
 - numbers appear in a random sequence
 - repeats every $2^n - 1$ patterns
 - Random numbers useful in:
 - computer graphics
 - cryptography
 - automatic testing
- Used for error detection and correction
 - CRC (cyclic redundancy codes)
 - ethernet uses them

Galois Fields - the theory behind LFSRs

- LFSR circuits performs multiplication on a *field*.
- A field is defined as a *set* with the following:
 - two operations defined on it:
 - “addition” and “multiplication”
 - closed under these operations
 - associative and distributive laws hold
 - additive and multiplicative identity elements
 - additive inverse for every element
 - multiplicative inverse for every non-zero element
- Example fields:
 - set of rational numbers
 - set of real numbers
 - set of integers is *not* a field (why?)
- Finite fields are called *Galois* fields.
- Example:
 - Binary numbers 0,1 with XOR as “addition” and AND as “multiplication”.
 - Called GF(2).

Galois Fields - The theory behind LFSRs

- Consider *polynomials* whose coefficients come from GF(2).
- Each term of the form x^n is either present or absent.

- Examples: 0 , 1 , x , x^2 , and $x^7 + x^6 + 1$

$$= 1 \cdot x^7 + 1 \cdot x^6 + 0 \cdot x^5 + 0 \cdot x^4 + 0 \cdot x^3 + 0 \cdot x^2 + 0 \cdot x^1 + 1 \cdot x^0$$

- With addition and multiplication these form a field:
- “Add”: XOR each element individually with no carry:

$$\begin{array}{r} x^4 + x^3 + \quad + x + 1 \\ + x^4 + \quad + x^2 + x \\ \hline x^3 + x^2 \quad + 1 \end{array}$$

- “Multiply”: multiplying by x^n is like shifting to the left.

$$\begin{array}{r} x^2 + x + 1 \\ \times \quad x + 1 \\ \hline x^2 + x + 1 \\ x^3 + x^2 + x \\ \hline x^3 \quad + 1 \end{array}$$

Galois Fields - The theory behind LFSRs

- These polynomials form a *Galois (finite)* field if we take the results of this multiplication modulo a prime polynomial $p(x)$.
 - A prime polynomial is one that cannot be written as the product of two non-trivial polynomials $q(x)r(x)$
 - Perform modulo operation by subtracting a (polynomial) multiple of $p(x)$ from the result. If the multiple is 1, this corresponds to XOR-ing the result with $p(x)$.
- For any degree, there exists at least one prime polynomial.
- With it we can form $GF(2^n)$
- Additionally, ...
- Every Galois field has a primitive element, α , such that all non-zero elements of the field can be expressed as a power of α . By raising α to powers (modulo $p(x)$), all non-zero field elements can be formed.
- Certain choices of $p(x)$ make the simple polynomial x the primitive element. These polynomials are called *primitive*, and one exists for every degree.
- For example, $x^4 + x + 1$ is primitive. So $\alpha = x$ is a primitive element and successive powers of α will generate all non-zero elements of $GF(16)$. *Example on next slide.*

Galois Fields - The theory behind LFSRs

$$\alpha^0 = 1$$

$$\alpha^1 = x$$

$$\alpha^2 = x^2$$

$$\alpha^3 = x^3$$

$$\alpha^4 = x + 1$$

$$\alpha^5 = x^2 + x$$

$$\alpha^6 = x^3 + x^2$$

$$\alpha^7 = x^3 + x + 1$$

$$\alpha^8 = x^2 + 1$$

$$\alpha^9 = x^3 + x$$

$$\alpha^{10} = x^2 + x + 1$$

$$\alpha^{11} = x^3 + x^2 + x$$


$$\alpha^{12} = x^3 + x^2 + x + 1$$

$$\alpha^{13} = x^3 + x^2 + 1$$

$$\alpha^{14} = x^3 + 1$$

$$\alpha^{15} = 1$$

 - Note this pattern of coefficients matches the bits from our 4-bit LFSR example.



$$\begin{aligned} \alpha^4 &= x^4 \text{ mod } x^4 + x + 1 \\ &= x^4 \text{ xor } x^4 + x + 1 \\ &= x + 1 \end{aligned}$$

- In general finding primitive polynomials is difficult. Most people just look them up in a table, such as:

Primitive Polynomials

$$x^2 + x + 1$$

$$x^3 + x + 1$$

$$x^4 + x + 1$$

$$x^5 + x^2 + 1$$

$$x^6 + x + 1$$

$$x^7 + x^3 + 1$$

$$x^8 + x^4 + x^3 + x^2 + 1$$

$$x^9 + x^4 + 1$$

$$x^{10} + x^3 + 1$$

$$x^{11} + x^2 + 1$$

$$x^{12} + x^6 + x^4 + x + 1$$

$$x^{13} + x^4 + x^3 + x + 1$$

$$x^{14} + x^{10} + x^6 + x + 1$$

$$x^{15} + x + 1$$

$$x^{16} + x^{12} + x^3 + x + 1$$

$$x^{17} + x^3 + 1$$

$$x^{18} + x^7 + 1$$

$$x^{19} + x^5 + x^2 + x + 1$$

$$x^{20} + x^3 + 1$$

$$x^{21} + x^2 + 1$$

$$x^{22} + x + 1$$

$$x^{23} + x^5 + 1$$

$$x^{24} + x^7 + x^2 + x + 1$$

$$x^{25} + x^3 + 1$$

$$x^{26} + x^6 + x^2 + x + 1$$

$$x^{27} + x^5 + x^2 + x + 1$$

$$x^{28} + x^3 + 1$$

$$x^{29} + x + 1$$

$$x^{30} + x^6 + x^4 + x + 1$$

$$x^{31} + x^3 + 1$$

$$x^{32} + x^7 + x^6 + x^2 + 1$$

Galois Field

Multiplication by x

\Leftrightarrow

Hardware

shift left

Taking the result mod $p(x)$

\Leftrightarrow

XOR-ing with the coefficients of $p(x)$ when the most significant coefficient is 1.



Obtaining all $2^n - 1$ non-zero elements by evaluating x^k for $k = 1, \dots, 2^n - 1$

\Leftrightarrow

Shifting and XOR-ing $2^n - 1$ times.

Building an LFSR from a Primitive Polynomial

- For k -bit LFSR number the flip-flops with FF1 on the right.
- The feedback path comes from the Q output of the leftmost FF.
- Find the primitive polynomial of the form $x^k + \dots + 1$.
- The $x^0 = 1$ term corresponds to connecting the feedback directly to the D input of FF 1.
- Each term of the form x^n corresponds to connecting an xor between FF n and $n + 1$.
- 4-bit example, uses $x^4 + x + 1$
 - $x^4 \Leftrightarrow$ FF4's Q output
 - $x \Leftrightarrow$ xor between FF1 and FF2
 - $1 \Leftrightarrow$ FF1's D input
- To build an 8-bit LFSR, use the primitive polynomial $x^8 + x^4 + x^3 + x^2 + 1$ and connect xors between FF2 and FF3, FF3 and FF4, and FF4 and FF5.

  

Error Correction with LFSRs

- XOR Q4 with incoming bit sequence. Now values of shift-register don't follow a fixed pattern. Dependent on input sequence.
 - Look at the value of the register after 15 cycles: "1010"
 - Note the length of the input sequence is $2^4-1 = 15$ (same as the number of different nonzero patterns for the original LFSR)
 - Binary message occupies only 11 bits, the remaining 4 bits are "0000".
 - They would be replaced by the final result of our LFSR: "1010"
 - If we run the sequence back through the LFSR with the replaced bits, we would get "0000" for the final result.
 - 4 parity bits "neutralize" the sequence with respect to the LFSR.
- $$\begin{array}{r} 1\ 1\ 0\ 0\ 1\ 0\ 0\ 0\ 1\ 1\ 1\ 0\ 0\ 0\ 0 \Rightarrow 1\ 0\ 1\ 0 \\ 1\ 1\ 0\ 0\ 1\ 0\ 0\ 0\ 1\ 1\ 1\ 1\ 0\ 1\ 0 \Rightarrow 0\ 0\ 0\ 0 \end{array}$$
- If parity bits not all zero, an error occurred in transmission.
 - If number of parity bits = log total number of bits, then single bit errors can be corrected.
 - Using more parity bits allows more errors to be detected.
 - Ethernet uses 32 parity bits per frame (packet) with 16-bit LFSR.