

# **EECS150 - Digital Design**

## **Lecture 3 - Verilog Introduction**


Jan 29, 2013  
John Wawrzynek

## **Outline**

- Background and History of Hardware Description
- Brief Introduction to Verilog Basics
- Lots of examples
  - structural, data-flow, behavioral
- Verilog in EECS150
 
# Design Entry

- Schematic entry/editing used to be the standard method in industry and universities.
- Used in EECS150 until 2002
- ☺ Schematics are intuitive. They match our use of gate-level or block diagrams.
- ☺ Somewhat physical. They imply a physical implementation.
- ☹ Require a special tool (editor).
- ☹ Unless hierarchy is carefully designed, schematics can be confusing and difficult to follow on large designs.



- Hardware Description Languages (HDLs) are the new standard
  - except for PC board design, where schematics are still used.

# Hardware Description Languages

- **Basic Idea:**
  - Language constructs describe circuits with two basic forms:
  - **Structural descriptions:** connections of components. Nearly one-to-one correspondence to with schematic diagram.
  - **Behavioral descriptions:** use high-level constructs (similar to conventional programming) to describe the circuit function.
- Originally invented for simulation.
  - Now "logic synthesis" tools exist to automatically convert from HDL source to circuits.
  - High-level constructs greatly improves designer productivity.
  - However, this may lead you to falsely believe that hardware design can be reduced to writing programs!\*

## "Structural" example:

```
Decoder(output x0,x1,x2,x3;
        inputs a,b)
{
    wire abar, bbar;
    inv(bbar, b);
    inv(abar, a);
    and(x0, abar, bbar);
    and(x1, abar, b );
    and(x2, a, bbar);
    and(x3, a, b );
}
```

## "Behavioral" example:


```
Decoder(output x0,x1,x2,x3;
        inputs a,b)
{
    case [a b]
        00: [x0 x1 x2 x3] = 0x1;
        01: [x0 x1 x2 x3] = 0x2;
        10: [x0 x1 x2 x3] = 0x4;
        11: [x0 x1 x2 x3] = 0x8;
    endcase;
}
```

**Warning: this is a fake HDL!**

\*Describing hardware with a language is similar, however, to writing a parallel program.
 
# Sample Design Methodology

Hierarchically defines structure and/or function of circuit.



Verification: Does the design behave as required with regards to function, timing, and power consumption?

Maps specification to resources of implementation platform (FPGA or custom silicon).

**Note:** This is not the entire story. Other tools are useful for analyzing HDL specifications. More on this later.

## Verilog


- A brief history:
  - Originated at Automated Integrated Design Systems (renamed Gateway) in 1985. Acquired by Cadence in 1989.
  - Invented as simulation language. Synthesis was an afterthought. Many of the basic techniques for synthesis were developed at Berkeley in the 80's and applied commercially in the 90's.
  - Around the same time as the origin of Verilog, the US Department of Defense developed VHDL (A double acronym! VSIC (Very High-Speed Integrated Circuit) HDL). Because it was in the public domain it began to grow in popularity.
  - Afraid of losing market share, Cadence opened Verilog to the public in 1990.
  - An IEEE working group was established in 1993, and ratified IEEE Standard 1394 (Verilog) in 1995. We use IEEE Std 1364-2001.
  - Verilog is the language of choice of Silicon Valley companies, initially because of high-quality tool support and its similarity to C-language syntax.
  - VHDL is still popular within the government, in Europe and Japan, and some Universities.
  - Most major CAD frameworks now support both.
  - Latest Verilog version is "system Verilog".
  - Latest HDL: C++ based. OSCI (Open System C Initiative).

# Verilog Introduction

- A **module** definition describes a component in a circuit
- Two ways to describe module contents:
  - Structural Verilog
    - List of sub-components and how they are connected
    - Just like schematics, but using text
    - tedious to write, hard to decode
    - You get precise control over circuit details
    - May be necessary to map to special resources of the FPGA
  - Behavioral Verilog
    - Describe what a component does, not how it does it
    - Synthesized into a circuit that has this behavior
    - Result is only as good as the tools
- Build up a hierarchy of modules. Top-level module is your entire design (or the environment to test your design).
 
## Verilog Modules and Instantiation

- Modules define circuit components.
- Instantiation defines hierarchy of the design.



Note: A module is not a function in the C sense. There is no call and return mechanism. Think of it more like a hierarchical data structure.

# Structural Model - XOR example

```

module xor_gate ( out, a, b );
  input  a, b;
  output out;
  wire  aBar, bBar, t1, t2;

  not invA (aBar, a);
  not invB (bBar, b);
  and and1 (t1, a, bBar);
  and and2 (t2, b, aBar);
  or  or1 (out, t1, t2);

endmodule

```

**module name** (xor\_gate)

**port list** (out, a, b)

**port declarations** (input a, b; output out;)

**internal signal declarations** (wire aBar, bBar, t1, t2;)

**Built-in gates** (not, and, or)


**instances** (invA, invB, and1, and2, or1)

**Interconnections (note output is first)**


- **Notes:**

- The instantiated gates are not "executed". They are active always.
- xor gate already exists as a built-in (so really no need to define it).
- Undeclared variables assumed to be wires. Don't let this happen to you!

# Structural Example: 2-to1 mux

 

a) 2-input mux symbol

 

b) 2-input mux gate-level circuit diagram

```

/* 2-input multiplexor in gates */
module mux2 (in0, in1, select, out);
  input in0,in1,select;
  output out;
  wire s0,w0,w1;

  not (s0, select);
  and (w0, s0, in0),
      (w1, select, in1);
  or  (out, w0, w1);

endmodule // mux2


```

**C++ style comments** (/\* 2-input multiplexor in gates \*/) and **Instance names** (mux2)

**Multiple instances can share the same "master" name.**

**Built-ins gates can have > 2 inputs. Ex:** and (w0, a, b, c, d);
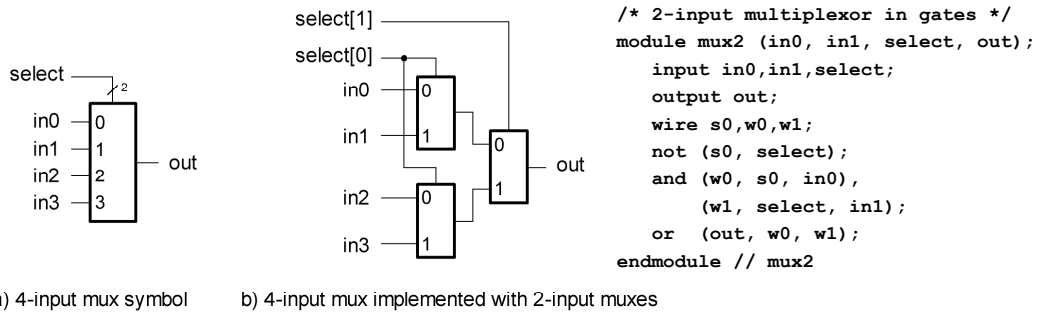
# Instantiation, Signal Array, Named ports



```

module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output out;
  wire w0,w1;
  mux2
    m0 (.select(select[0]), .in0(in0), .in1(in1), .out(w0)),
    m1 (.select(select[0]), .in0(in2), .in1(in3), .out(w1)),
    m3 (.select(select[1]), .in0(w0), .in1(w1), .out(out));
endmodule // mux4

```

Signal array. Declares select[1], select[0]

Named ports. Highly recommended.

## Simple Behavioral Model

```

module foo (out, in1, in2);
  input      in1, in2;
  output     out;

  assign out = in1 & in2;

endmodule

```

“continuous assignment”

Connects out to be the “and” of in1 and in2.

Shorthand for explicit instantiation of “and” gate (in this case).

The assignment continuously happens, therefore any change on the rhs is reflected in out immediately (except for the small delay associated with the implementation of the &).

Not like an assignment in C that takes place when the program counter gets to that place in the program.

# Example - Ripple Adder


```

module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

  assign r = a ^ b ^ ci;
  assign co = a&ci | a&b | b&cin;

endmodule

```

 


```

module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

  wire c1, c2, c3;
  FullAdder
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );
endmodule

```

 

# Continuous Assignment Examples

```

wire [3:0] X,Y,R;
wire [7:0] P;
wire r, a, cout, cin;

```

```

assign R = X | (Y & ~Z);
assign r = &X;
assign R = (a == 1'b0) ? X : Y;
assign P = 8'hff;
assign P = X * Y;
assign P[7:0] = {4{X[3]}, X[3:0]};
assign {cout, R} = X + Y + cin;
assign Y = A << 2;
assign Y = {A[1], A[0], 1'b0, 1'b0};

```

example reduction operator

use of bit-wise Boolean operators

conditional operator

example constants

arithmetic operators (use with care!)

(ex: sign-extension)

bit field concatenation

bit shift operator

equivalent bit shift

# Verilog Operators

Verilog Operator	Name	Functional Group			
()	bit-select or part-select		>	greater than	Relational
()	parenthesis		>=	greater than or equal to	Relational
!	logical negation	Logical	<	less than	Relational
~	negation	Bit-wise	<=	less than or equal to	Relational
&	reduction AND	Reduction	==	logical equality	Equality
	reduction OR	Reduction	!=	logical inequality	Equality
~&	reduction NAND	Reduction	===	case equality	Equality
~	reduction NOR	Reduction	!==	case inequality	Equality
^	reduction XOR	Reduction	&	bit-wise AND	Bit-wise
~^ or ^~	reduction XNOR	Reduction	^	bit-wise XOR	Bit-wise
			^~ or ~^	bit-wise XNOR	Bit-wise
+	unary (sign) plus	Arithmetic		bit-wise OR	Bit-wise
-	unary (sign) minus	Arithmetic	&&	logical AND	Logical
{}	concatenation	Concatenation		logical OR	Logical
{}	replication	Replication	?:	conditional	Conditional
*	multiply	Arithmetic			
/	divide	Arithmetic			
%	modulus	Arithmetic			
+	binary plus	Arithmetic			
-	binary minus	Arithmetic			
<<	shift left	Shift			
>>	shift right	Shift			

# Verilog Numbers

## Constants:

- 14** ordinary decimal number
- 14** 2's complement representation
- 12'b0000\_0100\_0110** binary number ("\_" is ignored)
- 12'h046** hexadecimal number with 12 bits

## Signal Values:

By default, Values are unsigned

e.g., **C[4:0] = A[3:0] + B[3:0];**

if A = 0110 (6) and B = 1010(-6)

C = 10000 not 00000

i.e., B is zero-padded, not sign-extended

**wire signed [31:0] x;**

Declares a signed (2's complement) signal array.



# Non-continuous Assignments

A bit strange from a hardware specification point of view.  
Shows off Verilog roots as a simulation language.

"always" block example:

```
module and_or_gate (out, in1, in2, in3);
  input  in1, in2, in3;
  output out;
  reg    out;
  always @(in1 or in2 or in3) begin
    out = (in1 & in2) | in3;
  end
endmodule
```

**reg** type declaration. Not really a register in this case. Just a Verilog rule.

**always** keyword

**@{in1 or in2 or in3}** "sensitivity" list, triggers the action in the body.

**begin** brackets multiple statements (not necessary in this example).

Isn't this just: `assign out = (in1 & in2) | in3;?`

Why bother?

# Always Blocks

Always blocks give us some constructs that are impossible or awkward in continuous assignments.

case statement example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0, in1, in2, in3;
  input [1:0] select;
  output out;
  reg out;

  always @ (in0 in1 in2 in3 select)
    case (select)
      2'b00: out=in0;
      2'b01: out=in1;
      2'b10: out=in2;
      2'b11: out=in3;
    endcase
endmodule // mux4
```

**case** keyword

The statement(s) corresponding to whichever constant matches "select" get applied.

Couldn't we just do this with nested "if"s?

Well yes and no!

# Always Blocks

## Nested if-else example:

```
module mux4 (in0, in1, in2, in3, select, out);
  input in0,in1,in2,in3;
  input [1:0] select;
  output out;
  reg out;


  always @ (in0 in1 in2 in3 select)
    if (select == 2'b00) out=in0;
    else if (select == 2'b01) out=in1;
    else if (select == 2'b10) out=in2;
    else out=in3;
endmodule // mux4
```

Nested if structure leads to "priority logic" structure, with different delays for different inputs (in3 to out delay > than in0 to out delay). Case version treats all inputs the same.
 
# Review - Ripple Adder Example


```
module FullAdder(a, b, ci, r, co);
  input a, b, ci;
  output r, co;

  assign r = a ^ b ^ ci;
  assign co = a&ci + a&b + b&cin;
endmodule
```



```
module Adder(A, B, R);
  input [3:0] A;
  input [3:0] B;
  output [4:0] R;

   wire c1, c2, c3;
  FullAdder
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );
endmodule
```



# Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a "generator" for different variations. Enables design/module reuse. Can simplify testing.

```
module Adder(A, B, R);
  parameter N = 4;
  input [N-1:0] A;
  input [N-1:0] B;
  output [N:0] R;
  wire [N:0] C;

  genvar i;
  generate
    for (i=0; i<N; i=i+1) begin:bit
      FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));
    end
  endgenerate

  assign C[0] = 1'b0;
  assign R[N] = C[N];
endmodule
```

**Declare a parameter with default value.**  
**Note: this is not a port. Acts like a "synthesis-time" constant.**  
**Replace all occurrences of "4" with "N".**  
**variable exists only in the specification - not in the final circuit.**  
**Keyword that denotes synthesis-time operations**  
**For-loop creates instances (with unique names)**

```
Adder adder4 ( ... );
Adder #(.N(64))
  adder64 ( ... );
```

**Overwrite parameter N at instantiation.**

Spring 2013

EECS150 - Lec03-Verilog

Page 21

# More on Generate Loop

Permits variable declarations, modules, user defined primitives, gate primitives, continuous assignments, initial blocks and always blocks to be instantiated multiple times using a for-loop.

```
// Gray-code to binary-code converter
module gray2bin1 (bin, gray);
  parameter SIZE = 8;
  output [SIZE-1:0] bin;
  input [SIZE-1:0] gray;

  genvar i;
  generate for (i=0; i<SIZE; i=i+1) begin:bit
    assign bin[i] = ^gray[SIZE-1:i];
  end endgenerate
endmodule
```

**variable exists only in the specification - not in the final circuit.**  
**Keywords that denotes synthesis-time operations**  
**For-loop creates instances of assignments**  
**Loop must have constant bounds**

**generate if-else-if** based on an expression that is deterministic at the time the design is synthesized.

**generate case** : selecting case expression must be deterministic at the time the design is synthesized.

Spring 2013

EECS150 - Lec03-Verilog

Page 22

# Verilog in EECS150

- We will primarily use **behavioral modeling** along with **instantiation** to 1) build hierarchy and, 2) map to FPGA resources not supported by synthesis.
- Favor continuous assign and avoid always blocks unless:
  - no other alternative: ex: state elements, case
  - helps readability and clarity of code: ex: large nested if else
- Use named ports.
- Verilog is a big language. This is only an introduction.
  - Our text book is a good source. Read and use chapter 4.
  - Be careful of what you read on the web. Many bad examples out there.
  - We will be introducing more useful constructs throughout the semester. Stay tuned!

## Final thoughts on Verilog Examples

Verilog looks like C, but it describes hardware

Multiple physical elements with parallel activities and temporal relationships.

A large part of digital design is knowing how to write Verilog that gets you the desired circuit. First understand the circuit you want then figure out how to code it in Verilog. If you do one of these activities without the other, you will struggle. These two activities will merge at some point for you.

Be suspicious of the synthesis tools! Check the output of the tools to make sure you get what you want.