

EECS150 - Digital Design


Lecture 6 - Logic Simulation

Feb 7, 2013
John Wawrzynek

Encoder Example

What is y if $x == 4'b1111$?

 
```
always @(x)
begin : encode
if (x == 4'b0001) y = 2'b00;
else if (x == 4'b0010) y = 2'b01;
else if (x == 4'b0100) y = 2'b10;
else if (x == 4'b1000) y = 2'b11;
else y = 2'bxx;
end
```



Encoder Example (cont.)

What is y if $x == 4'b1111$?

 
```
always @(x)
begin : encode
case (x)
4'b0001: y = 2'b00;
4'b0010: y = 2'b01;
4'b0100: y = 2'b10;
4'b1000: y = 2'b11;
default: y = 2'bxx;
endcase
end
```



Encoder Example (cont.)


If you can guarantee that only one 1 appears in the input, then simpler logic can be generated:
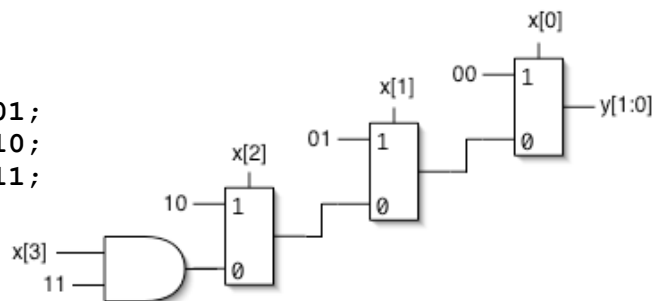
```
always @(x)
begin : encode
if (x[0]) y = 2'b00;
else if (x[1]) y = 2'b01;
else if (x[2]) y = 2'b10;
else if (x[3]) y = 2'b11;
else y = 2'bxx;
end
```



If the input applied has more than one 1, then this version functions as a "priority encoder". The least significant 1 gets priority (the more significant 1's are ignored). Again the circuit will be simplified when possible.

EECS150 Design Methodology

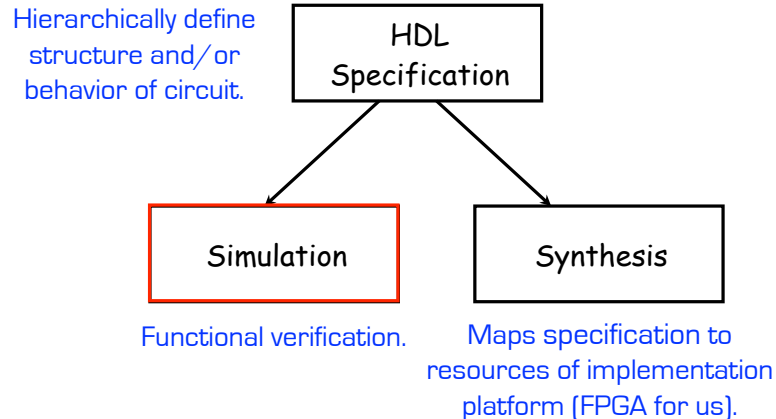

Let's look at the other branch.

Design Verification


- Industrial design teams spend a large percentage of the design time on design verification:
 - Removing functional bugs, messaging the design to meet performance, cost, and power constraints.
- Particularly important for IC design, less so for FPGAs.
- A variety of tools and strategies are employed.
 - **Simulation:** software that interprets the design description and mimics signal behavior and timing (and power consumption).
 - Simulation provides better controllability and observability over real hardware. Saves on wasted development time and money.
 - **Emulation:** hardware platform (usually FPGAs) are used to mimic behavior of another system. Fast simulation.
 - **Static Analysis:** tools examines circuit structure and reports on expected performance, power, or compares alternative design representations looking for differences.

Simulation

Verilog/VHDL simulators use 4 signals values:

0, 1, X (unknown), Z (undriven)

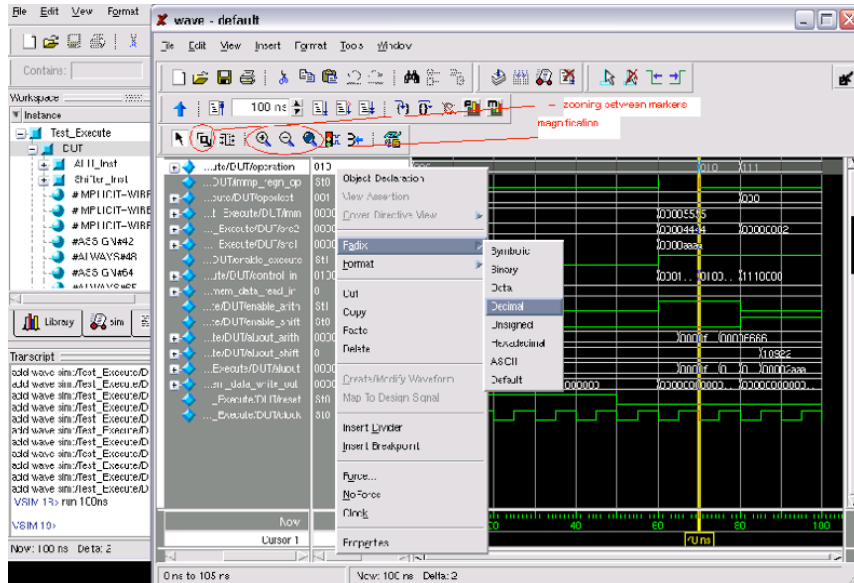
Simulation engine algorithm typically "discrete event simulation"



ModelSim:
waveform
viewer, GUI.

Discrete Event Simulation Engine

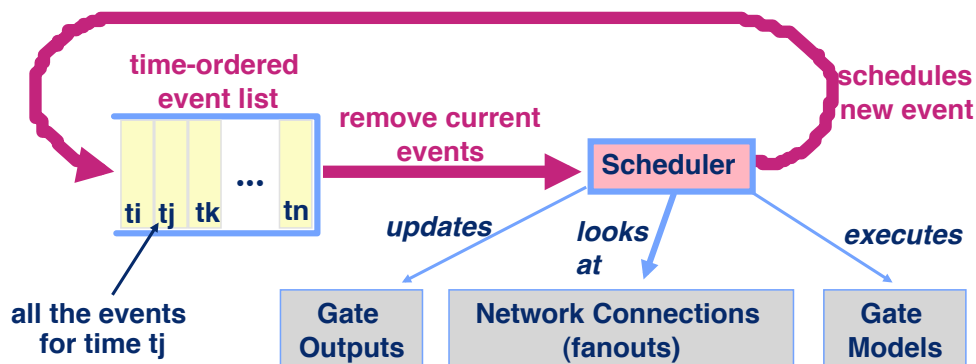- A time-ordered list of events is maintained
Event: a value-change scheduled to occur at a given time
 All events for a given time are kept together
- The scheduler removes events for a given time ...
 ... propagates values, executes models, and creates new events ...



Slide from Thomas. *The Verilog Hardware Description Language*,
By Thomas and Moorby, Kluwer Academic Publishers

Simulation Testing Strategies

- **Unit Testing:** Large systems are often too complex to test all at once, so an bottom-up hierarchical approach. Sub-modules are tested in isolation.
- **Combinational Logic blocks:** when practical, exhaustive testing. Otherwise a combination of random and directed tests.
- **Finite state machines:** test every possible transition and output.
- **Processors:** use software to expose bugs.
- In all cases, the simulated output values are checked against the expected values. Expected values are derived through a variety of means:
 - HDL behavior model running along side the design under test
 - precomputed inputs and outputs (vectors)
 - co-simulation. Ex: C-language model runs along side ModelSim

Testbench

Top-level modules written specifically to test other modules.

```
module testmux; ----- Generally no ports.
  reg a, b, s;
  wire f;
  reg expected;

  mux2 myMux (.select(s), .in0(a), .in1(b), .out(f));

  initial
  begin
    s=0; a=0; b=1; expected=0;
    #10 a=1; b=0; expected=1;
    #10 s=1; a=0; b=1; expected=1;
  end
  initial
  $monitor(
    "select=%b in0=%b in1=%b out=%b, expected out=%b time=%d",
    s, a, b, f, expected, $time);
endmodule // testmux
```

Usually never synthesized to circuits. Therefore free to use "simulation only" language constructs.

Instantiation of DUT (device under test).

Initial block similar to "always" block without a trigger. It triggers once automatically at the beginning of simulation. (Also supported on FPGAs).

"#n" used to advance time in simulation. Delays some action by a number of simulation time units.

Assignments used to set inputs.

Note multiple initial blocks.

\$monitor triggers whenever any of its inputs change. Sends output to console.

A variety of other "system functions exist for displaying output and controlling the simulation.

Most simulators also include a way to view waveforms of a set of signals.

Mux4 Testbench

```

module testmux4;
  reg [5:0] count = 6'b000000;
  reg a, b, c, d, expected;
  reg [1:0] S;
  wire f;
  mux4 myMux (.select(S), .in0(a), .in1(b), .in2(c), .in3(d), .out(f));
  initial
  begin
    repeat(64)
    begin
      {S, d, c, b, a} = count[5:0];
      case (S)
        2'b00: expected = a;
        2'b01: expected = b;
        2'b10: expected = c;
        2'b11: expected = d;
      endcase // case(S)
      #8 $strobe("select=%b in0=%b in1=%b in2=%b in3=%b out=%b,
                expected=%b time=%d", S, a, b, c, d, f, expected, $time);
      #2 count = count + 1'b1;
    end
  end
  $stop;
end
endmodule

```

Declaration and initialization all at once.
Generally not available in synthesis.

DUT instantiation

Enumerate all possible input patterns.

Apply pattern to DUT

Behavioral model of mux4

\$strobe displays data at a selected time. That time is just before simulation time is advanced (after all other events).

Wait a bit, then bump count.

Delay to allow mux outputs to stabilize. Here we assume mux delay < 2ns.

Alternative to \$strobe in this case,

#8 if (f != expected) \$display("Mismatch: ...);

FSM Testbench Example

```

module testFSM;
  reg in;
  wire out;
  reg clk=0, rst;
  reg expect;
  FSM1 myFSM (.out(out), .in(in), .clk(clk), .rst(rst));
  always #5 clk = ~clk;
  initial
  begin
    rst=1;
    #10 in=0; rst=0; expect=0;
    #10 in=1; rst=0; expect=0;
    #10 in=0; rst=0; expect=0;
    #10 in=1; rst=0; expect=0;
    #10 in=1; rst=0; expect=1;
    #10 in=1; rst=0; expect=1;
    #10 in=0; rst=0; expect=0;
    #10 $stop;
  end
  always
  begin
    #4 $strobe($time, " in=%b, rst=%b, expect=%b out=%b", in, rst, expect, out);
    #6 ;
  end
endmodule

```


Test all arcs.

DUT instantiation

100MHz clk signal

start in IDLE

 - self-loop
- transition to S0
- transition to IDLE
- transition to S0
- transition to S1
- self-loop
- transition to IDLE



Note: Input changes are forced to occur on negative edge of clock.

Strobe output occurs 1ns before rising edge of clock.

Debug is easier if you have access to state value also. Either 1) bring out to ports, or 2) use waveform viewer.

Final Words (for now) on Simulation

Testing is not always fun, but you should view it as part of the design process. Untested potentially buggy designs are a dime-a-dozen. Verified designs have real value.

Devising a test strategy is an integral part of the the design process. It shows that you have your head around the design. It should not be an afterthought.