



EECS150 - Digital Design

Lecture 25 - Latches & Flip-flops


April 23, 2012
John Wawrzynek

CMOS “Transparent” Latches

Positive level-sensitive latch:


 
 


Latch Implementation:

 


Designing with Latches


CMOS Flip-flops

   

 
- Setup time results from delay through *first* latch.



 - Clock to Q delay results from delay through *second* latch.




Cross-coupled NOR gates

 


remember,

| NOR | |
|-----|---|
| 00 | 1 |
| 01 | 0 |
| 10 | 0 |
| 11 | 0 |

 - If both $R=0$ & $S=0$, then cross-coupled NORs equivalent to a stable latch:




 
- If either R or S becomes $=1$ then state may change:



- What happens if R or S or both become $= 1$?

Asynchronous State Transition Diagram

Transitions triggered by input changes.

  

SR Latch:

| SR | Q |
|----|---------------|
| 00 | hold |
| 01 | 0 |
| 10 | 1 |
| 11 | indeterminate |

- S is "set" input
- R is "reset" input

QQ'=00 is often called a "forbidden state"

Nand-gate based SR latch

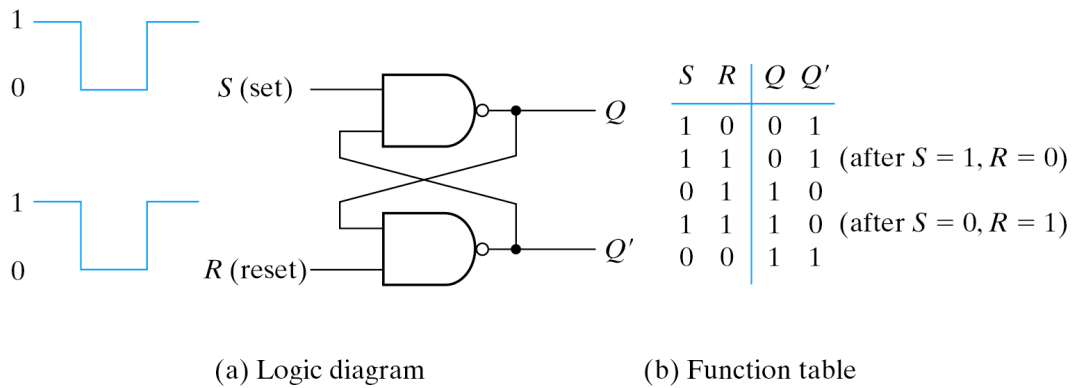


Fig. 5-4 SR Latch with NAND Gates

- Same behavior as cross-coupled NORs with inverted inputs.

Level-sensitive SR Latch


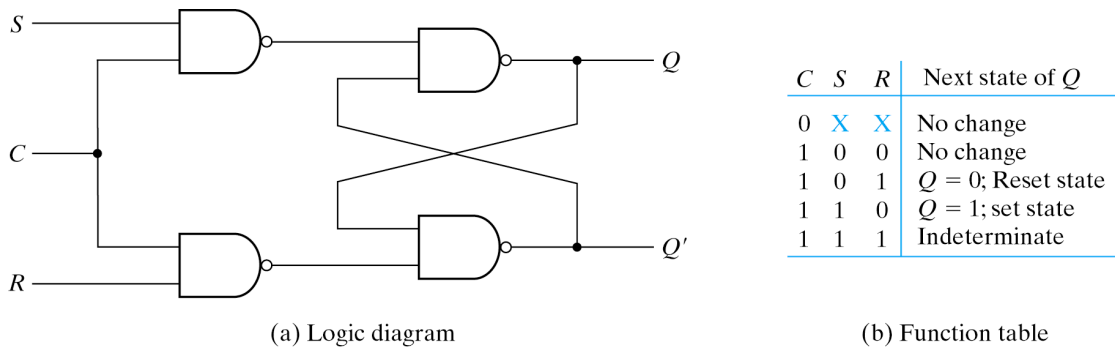


Fig. 5-5 SR Latch with Control Input

- The input "C" works as an "enable" signal, latch only changes output when C is high.
- Usually connected to **clock**.

D-latch

 

(a) Logic diagram


| C | D | Next state of Q |
|-----|-----|-----------------------|
| 0 | X | No change |
| 1 | 0 | $Q = 0$; Reset state |
| 1 | 1 | $Q = 1$; Set state |

(b) Function table

Fig. 5-6 D Latch

Compare to transistor version:

All state elements *could* be built using logic gates.

 

Spring 2013

Page 9

2 Alternative Flip-flops

 


Fig. 5-9 Master-Slave D Flip-Flop

 


Fig. 5-10 D-Type Positive-Edge-Triggered Flip-Flop


Spring 2013

EECS150 - Lec25-flipflops

Page 10

J-K FF

 - Add logic to eliminate “indeterminate” action of RS FF.
- New action is “toggle”
- J = “jam”
- K = “kill”



| J | K | Q(t) | Q(t+Δ) | |
|---|---|------|--------|--------|
| 0 | 0 | 0 | 0 | hold |
| 0 | 0 | 1 | 1 | |
| 0 | 1 | 0 | 0 | reset |
| 0 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 1 | set |
| 1 | 0 | 1 | 1 | |
| 1 | 1 | 0 | 1 | toggle |
| 1 | 1 | 1 | 0 | |

Storage Element Taxonomy


| | synchronous | | asynchronous |
|---------|-----------------|----------------|--------------|
| | level-sensitive | edge-triggered | |
| D-type | ★ | ✓ | n.a. |
| JK-type | ✓ | ✓ | n.a. |
| RS-type | ✓ | ✓ | ★ |
| | “latch” | “flip-flop” | “latch” |

★ “natural” form

✓ “possible” form

Design Example with RS FF

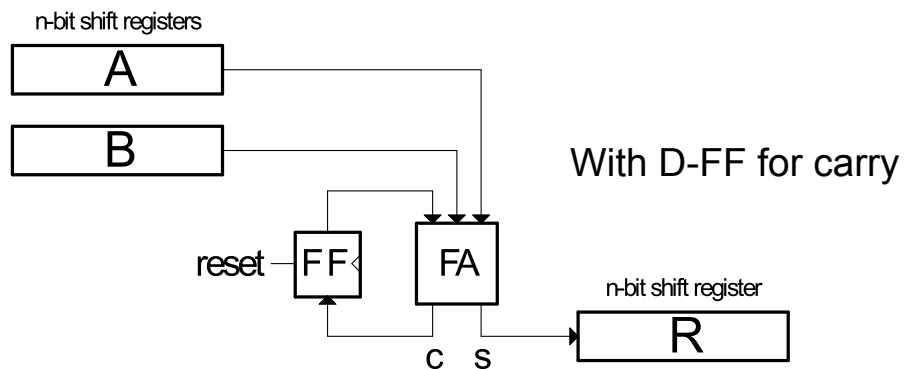- With D-type FF state elements, new state is computed based on inputs & present state bits - reloaded each cycle.
- With RS (or JK) FF state elements, inputs are used to determine conditions under which to set or reset state bits.
- Example: bit-serial adder (LSB first)



Bit-serial adder with RS FF

- RS FF stores the carry:

| a | b | c_i | c_{i+1} | s | |
|---|---|-------|-----------|---|----------------------|
| 0 | 0 | 0 | 0 | 0 | Carry kill a'b' |
| 0 | 0 | 1 | 0 | 1 | |
| 0 | 1 | 0 | 0 | 1 | |
| 0 | 1 | 1 | 1 | 0 | |
| 1 | 0 | 0 | 0 | 1 | |
| 1 | 0 | 1 | 1 | 0 | |
| 1 | 1 | 0 | 1 | 0 | Carry generate ab |
| 1 | 1 | 1 | 1 | 1 | |

