

**Lecture #14**  
**Introduction to Synchronous Digital Systems**



No CPS today

2005-10-19

There are two handouts today at the front and back of the room!

Lecturer PSOE, new dad Dan Garcia

[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)

Faster boot-up time! =>


Intel demonstrated a new technology called "Robson flash memory" which is used to slash the times it takes for apps to boot and laptops to start up. 0.4 vs 5.4 sec!



[www.pcworld.com/news/article/0,aid,123053,00.asp](http://www.pcworld.com/news/article/0,aid,123053,00.asp)



**What are "Machine Structures"?**

 

61C

Coordination of many *levels of abstraction*

We'll investigate lower abstraction layers!  
 (contract between HW & SW)



**Below the Program**

• High-level language program (in C)

```
swap int v[], int k){
    int temp;
    temp = v[k];
    v[k] = v[k+1];
    v[k+1] = temp;
}
```

C compiler

• Assembly language program (for MIPS)

```
swap: sll $2, $5, 2
      add $2, $4, $2
      lw $15, 0($2)
      lw $16, 4($2)
      sw $16, 0($2)
      sw $15, 4($2)
      jr $31
```

assembler

• Machine (object) code (for MIPS)

```
000000 000000 00101 000100000100000000
000000 001100 00010 0001000000100000 . . .
```



**Logic Design**

• Next 2 weeks: we'll study how a modern processor is built starting with basic logic elements as building blocks.

• Why study logic design?

- Understand what processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)
- Background for more detailed hardware courses (CS 150, CS 152)



**Logic Gates**

• Basic building blocks are logic *gates*.


- In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
- Can build gates with transistors and resistors

• Then found theoretical basis for design

- Can represent and reason about gates with truth tables and Boolean algebra
- Assume know truth tables and Boolean algebra from a math or circuits course.
- Section B.2 in the textbook has a review



**Physical Hardware**

 

Let's look closer...

PowerPC



## Transistors 101

### MOSFET

• Metal-Oxide-Semiconductor Field-Effect Transistor


• Come in two types:

- n-type NMOSFET
- p-type PMOSFET

• For n-type (p-type opposite)

• If current is NOT flowing in Gate, transistor turns "off" (cut-off) and Drain-Source NOT connected

 • If current IS flowing in Gate, transistor turns "on" (triode) and Drain-Source ARE connected




[www.wikipedia.org/wiki/Mosfet](http://www.wikipedia.org/wiki/Mosfet)

CS61C L14 Introduction to Synchronous Digital Systems (7)

Garcia, Fall 2005 © UCB


## Gate-level view vs. Block diagram

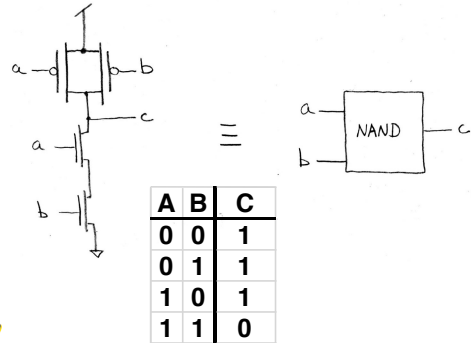

CS61C L14 Introduction to Synchronous Digital Systems (8)

Garcia, Fall 2005 © UCB


## Signals and Waveforms: Clocks

 

CS61C L14 Introduction to Synchronous Digital Systems (9)

Garcia, Fall 2005 © UCB


## Signals and Waveforms: Adders

 

CS61C L14 Introduction to Synchronous Digital Systems (10)

Garcia, Fall 2005 © UCB


## Signals and Waveforms: Grouping

 

CS61C L14 Introduction to Synchronous Digital Systems (11)

Garcia, Fall 2005 © UCB

## Signals and Waveforms: Circuit Delay

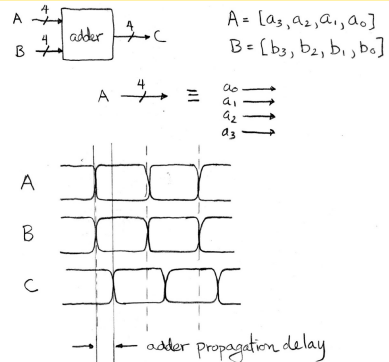

CS61C L14 Introduction to Synchronous Digital Systems (12)

Garcia, Fall 2005 © UCB

## Combinational Logic


- Complex logic blocks are built from basic AND, OR, NOT building blocks we'll see shortly.
- A **combinational** logic block is one in which the output is a function only of its current input.
- Combinational logic **cannot have memory** (e.g., a register is not a combinational unit).



CS61C L14 Introduction to Synchronous Digital Systems (13)

Garcia, Fall 2005 © UCB

## Circuits with STATE (e.g., register)

 

CS61C L14 Introduction to Synchronous Digital Systems (14)

Garcia, Fall 2005 © UCB

## And in semi conclusion...

- ISA is very important abstraction layer
  - Contract between HW and SW
- Basic building blocks are logic **gates**
- Clocks control pulse of our circuits
- Voltages are analog, quantized to 0/1
- Circuit delays are fact of life
- Two types
  - Stateless Combinational Logic (&,!,~)
  - State circuits (e.g., registers)




CS61C L14 Introduction to Synchronous Digital Systems (19)

Garcia, Fall 2005 © UCB
 
## Administrivia - Midterm 2005Sp

- Your TAs and readers stayed up until 4am to get your exams back to you!
- $\bar{x}$ : 47, Median: 48,  $\sigma$ : 14.4




CS61C L

wrcia, Fall 2005 © UCB
 
## Administrivia - Midterm 2005Fa

- Your TAs and readers stayed up until 4am to get your exams back to you!
- $\bar{x}$ : 45.4, Median: 49,  $\sigma$ : 13.7



CS61C L

wrcia, Fall 2005 © UCB

## Administrivia


- If you want an exam regrade, simply staple a note to the front of your exam and turn it in to your TA or Dan.
  - We'll collect them until the end of Monday's lecture and then regrade all.
  - Remember that your grade can go down.
- Project 1 is graded; you have one week to request a regrade there too...



CS61C L14 Introduction to Synchronous Digital Systems (19)

Garcia, Fall 2005 © UCB


### Accumulator Example

 

Want:  $S=0;$   
 for ( $i=0; i<n; i++$ )  
 $S = S + X_i$



### First try...Does this work?

 


Nope!

Reason #1... What is there to control the next iteration of the 'for' loop?


Reason #2... How do we say 'S=0'?




### Second try...How about this? Yep!

 

Rough timing...

 

 
### Register Details...What's in it anyway?



- n instances of a "Flip-Flop", called that because the output flips and flops betw. 0,1
- D is "data"
- Q is "output"
- Also called "d-q Flip-Flop", "d-type Flip-Flop"



 
### What's the timing of a Flip-flop? (1/2)



- Edge-triggered d-type flip-flop
  - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."



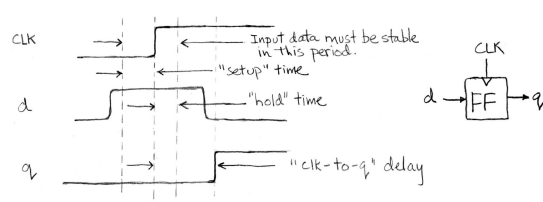
### What's the timing of a Flip-flop? (2/2)




- Edge-triggered d-type flip-flop
  - This one is "positive edge-triggered"
- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."


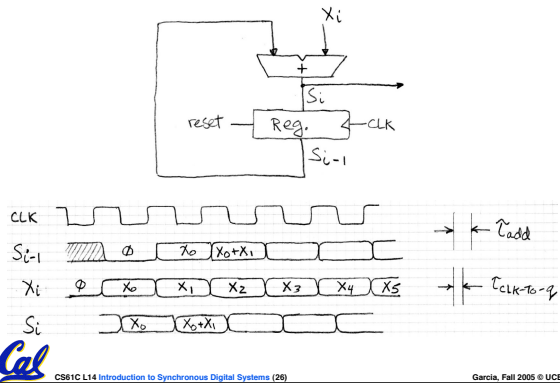
### Accumulator Revisited (proper timing 1/2)


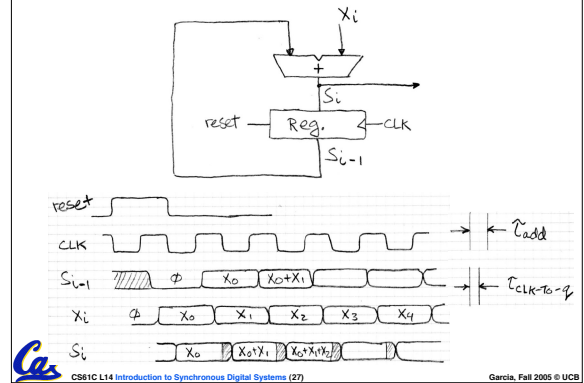
### Accumulator Revisited (proper timing 2/2)



### “And In conclusion...”

- We use **feedback** to maintain **state**
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
  - Setup and Hold times important

