

Lecture #14 Introduction to Synchronous Digital Systems



No
CPS
today

2005-10-19

There are two handouts
today at the front and
back of the room!

Lecturer PSOE, new dad Dan Garcia


www.cs.berkeley.edu/~ddgarcia

Faster boot-up time! ⇒

Intel demonstrated a new technology called “Robson flash memory” which is used to slash the times it takes for apps to boot and laptops to start up. 0.4 vs 5.4 sec!



What are “Machine Structures”?

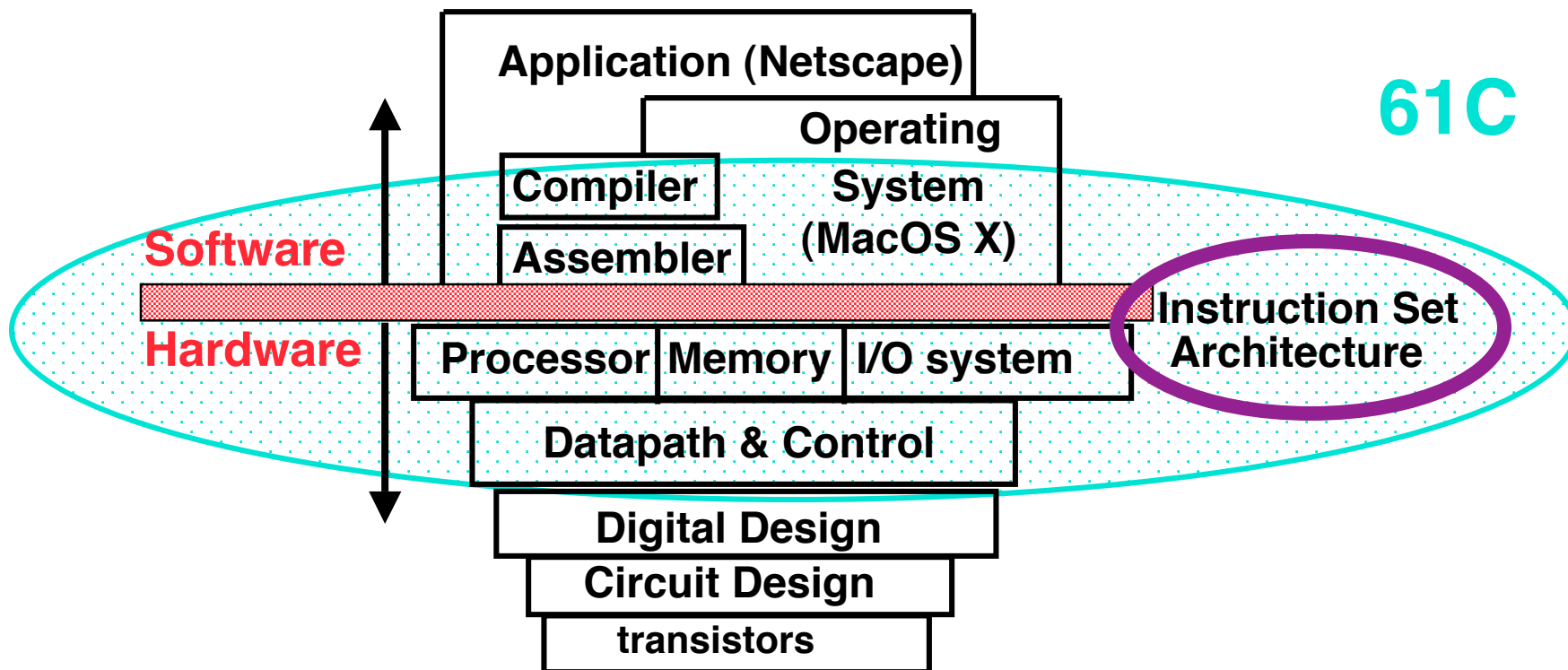

Coordination of many *levels of abstraction*


We'll investigate lower abstraction layers!
(contract between HW & SW)



Below the Program


- High-level language program (in C)
 
```
swap  int v[], int k){  
    int temp;  
    temp = v[k];  
    v[k] = v[k+1];  
    v[k+1] = temp;  
}
```




- Assembly language program (for MIPS)
 
```
swap:  sll    $2, $5, 2  
       add    $2, $4, $2  
       lw     $15, 0($2)  
       lw     $16, 4($2)  
       sw     $16, 0($2)  
       sw     $15, 4($2)  
       jr     $31
```



- Machine (object) code (for MIPS)
 
```
000000 00000 00101 0001000010000000  
000000 00100 00010 0001000000100000 . . .
```



Logic Design

- **Next 2 weeks: we'll study how a modern processor is built starting with basic logic elements as building blocks.**
- **Why study logic design?**
 - **Understand what processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)**
 - **Background for more detailed hardware courses (CS 150, CS 152)**




Logic Gates

- **Basic building blocks are logic *gates*.**
 - In the beginning, did ad hoc designs, and then saw patterns repeated, gave names
 - Can build gates with transistors and resistors
- **Then found theoretical basis for design**
 - Can represent and reason about gates with truth tables and Boolean algebra
 - Assume know truth tables and Boolean algebra from a math or circuits course.
 - Section B.2 in the textbook has a review



Physical Hardware

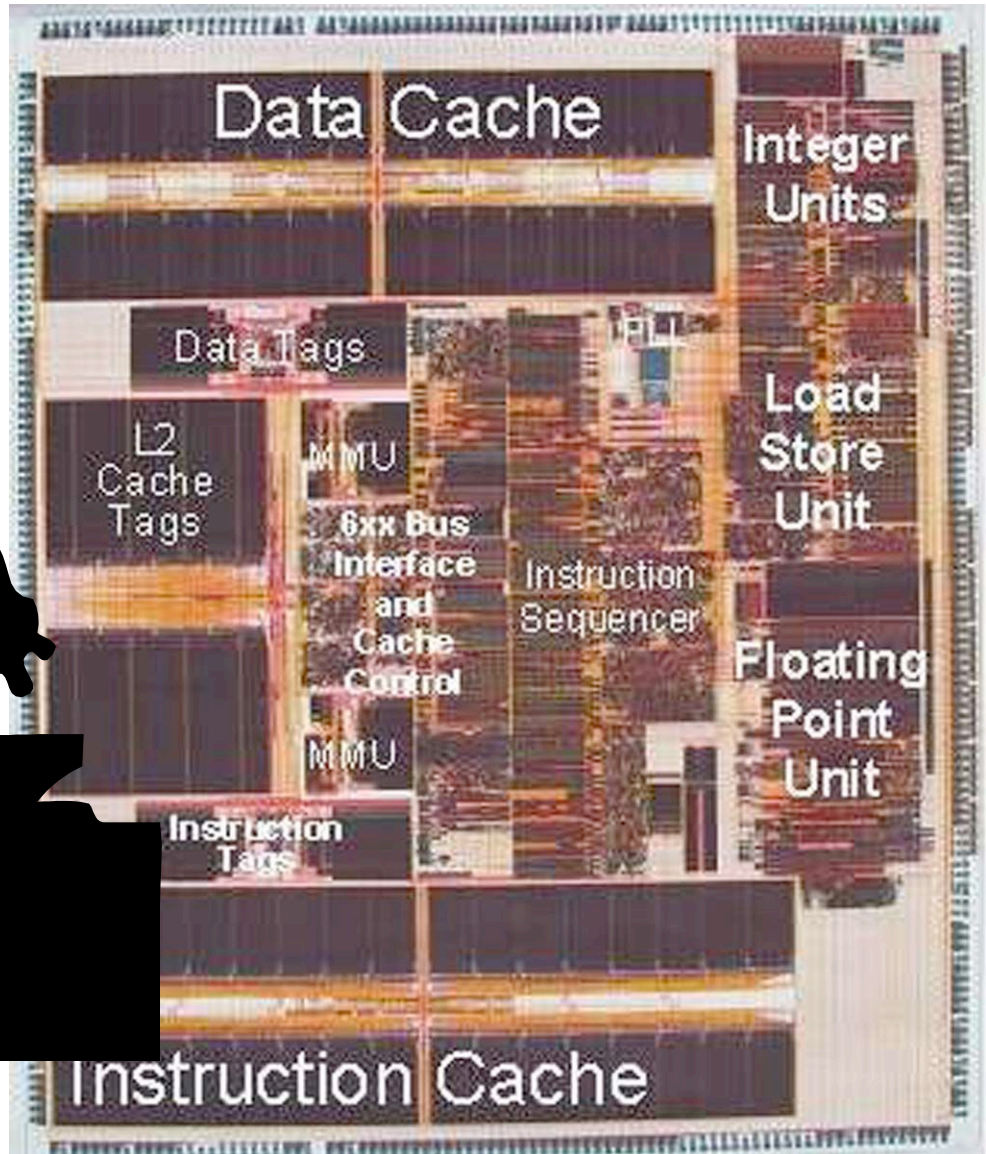

Let's look closer...




Transistors 101

- **MOSFET**

- **Metal-Oxide-Semiconductor Field-Effect Transistor**

- **Come in two types:**


- n-type NMOSFET
 - p-type PMOSFET

 

- **For n-type (p-type opposite)**

- **If current is NOT flowing in Gate, transistor turns “off” (cut-off) and Drain-Source NOT connected**

 - **If current IS flowing in Gate, transistor turns “on” (triode) and Drain-Source ARE connected**




Side view




www.wikipedia.org/wiki/Mosfet

Gate-level view vs. Block diagram

 


≡


 


A	B	C
0	0	1
0	1	1
1	0	1
1	1	0

Signals and Waveforms: Clocks

 


Signals and Waveforms: Adders

 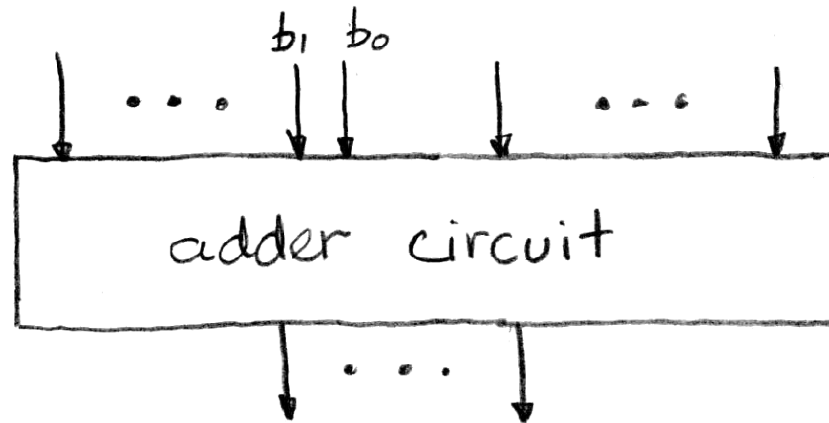

Signals and Waveforms: Grouping

x_3 x_2 x_1 x_0
↓ ↓ ↓ ↓


 


Signals and Waveforms: Circuit Delay



$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

  


Combinational Logic

- Complex logic blocks are built from basic AND, OR, NOT building blocks we'll see shortly.
- A *combinational* logic block is one in which the output is a function only of its current input.
- Combinational logic **cannot have memory** (e.g., a register is not a combinational unit).



Circuits with STATE (e.g., register)

 

Peer Instruction

- A. SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- B. SW **can depend** on particular HW implementation of ISA
- C. Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



And in semi conclusion...


- **ISA is very important abstraction layer**
 - **Contract between HW and SW**
- **Basic building blocks are logic *gates***
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types**
 - **Stateless Combinational Logic (&,!,~)**
 - **State circuits (e.g., registers)**



Administrivia - Midterm 2005Sp


- Your TAs and readers stayed up until 4am to get your exams back to you!
- \bar{x} : 47, Median: 48, σ : 14.4

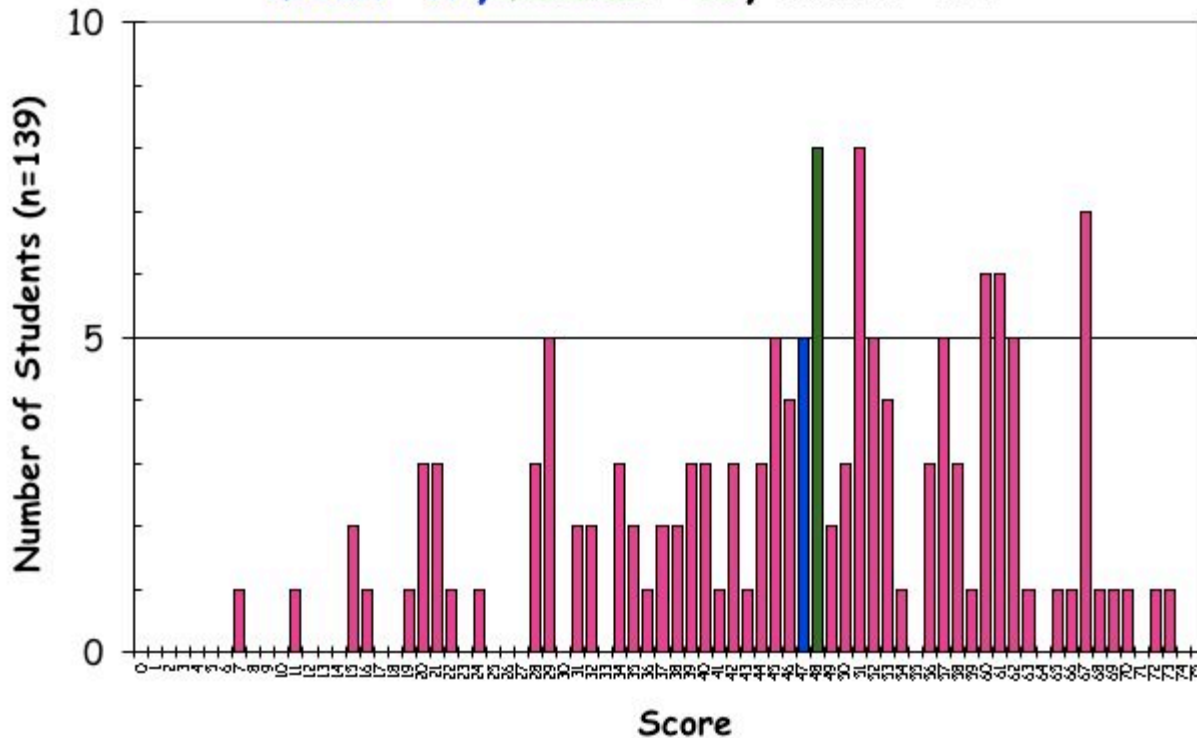UCB CS61C 2005Sp Midterm
mean=47, median=48, stdev=14



Administrivia - Midterm 2005Fa

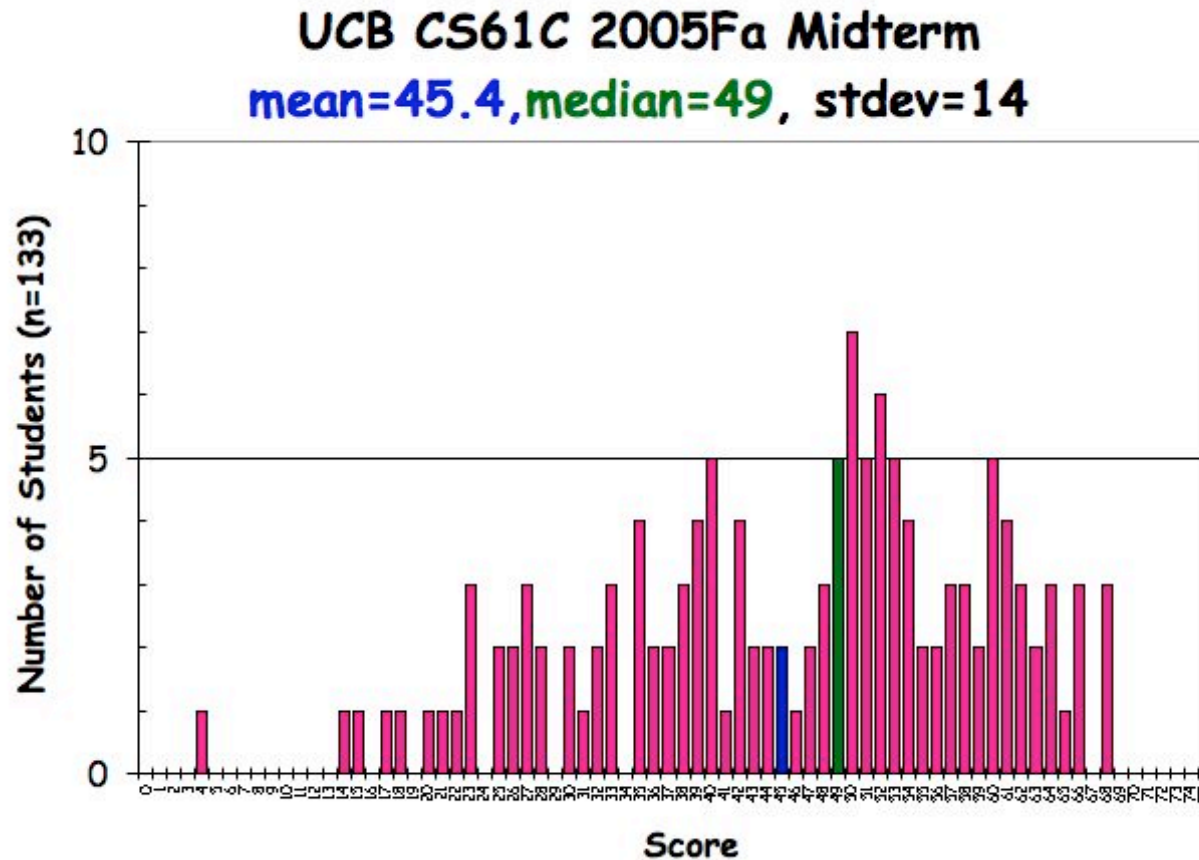- Your TAs and readers stayed up until 4am to get your exams back to you!
- \bar{x} : 45.4, Median: 49, σ : 13.7




Administrivia

- **If you want an exam regrade, simply staple a note to the front of your exam and turn it in to your TA or Dan.**
 - **We'll collect them until the end of Monday's lecture and then regrade all.**
 - **Remember that your grade can go down.**
- **Project 1 is graded; you have one week to request a regrade there too...**




Accumulator Example

 

Want: `S=0;`
 `for (i=0;i<n;i++)`
 `S = S + Xi`

First try...Does this work?

 


Nope!

Reason #1... What is there to control the next iteration of the 'for' loop?


Reason #2... How do we say: 's=0'?




Second try...How about this? Yep!

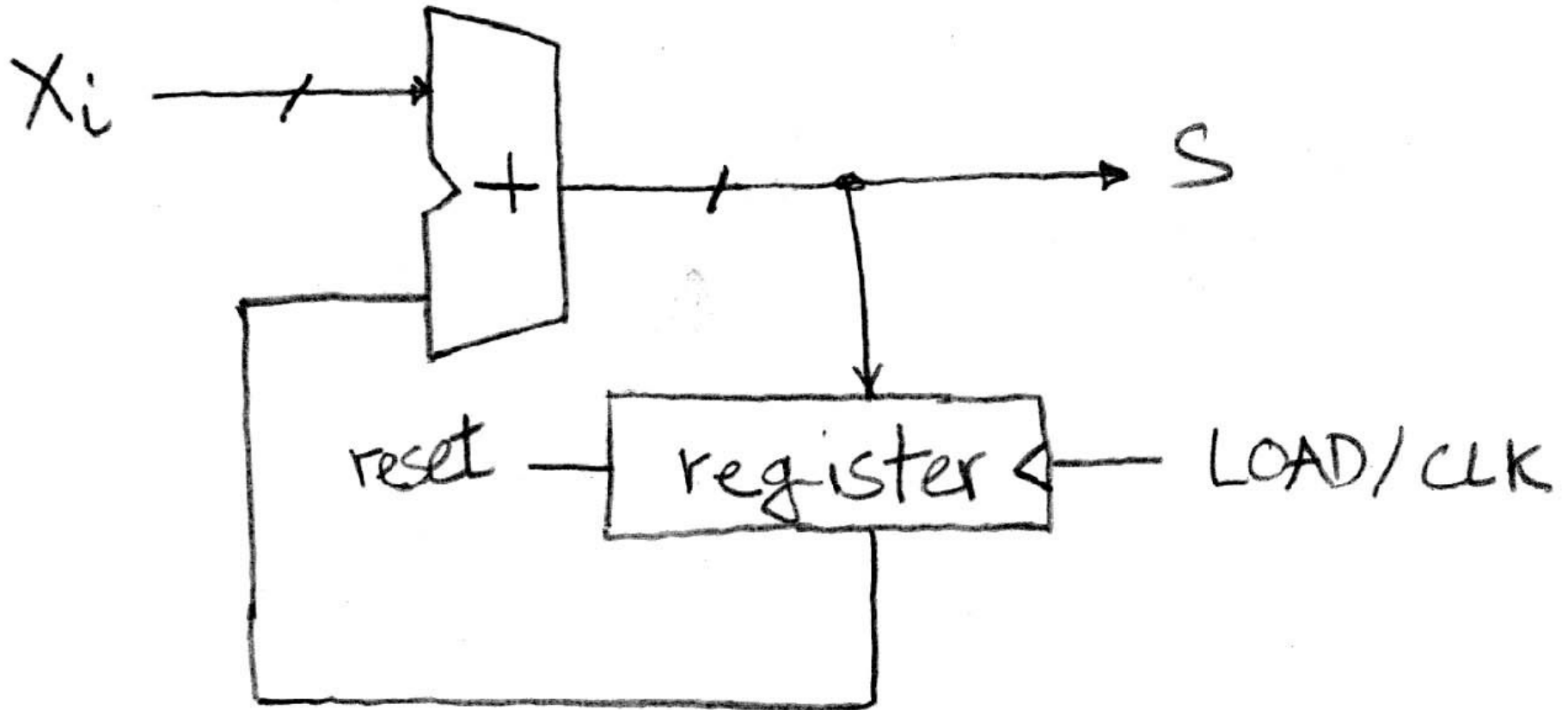

Rough timing...

 


Register Details...What's in it anyway?

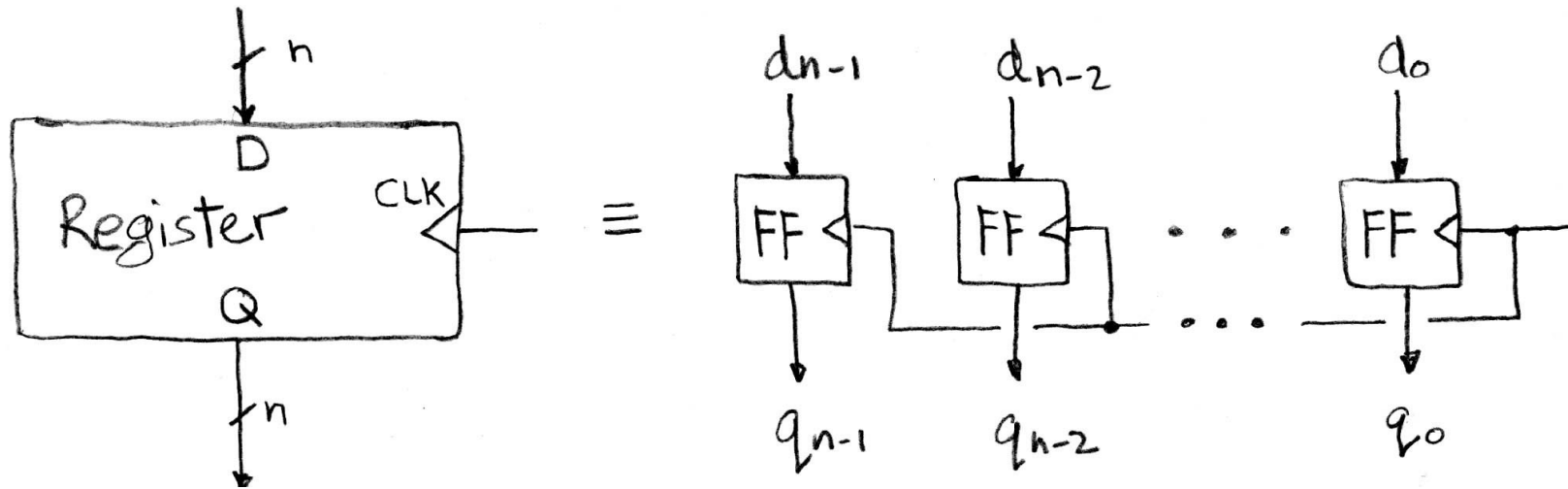


- n instances of a “Flip-Flop”, called that because the output flips and flops betw. 0,1
- D is “data”
- Q is “output”
- Also called “d-q Flip-Flop”, “d-type Flip-Flop”

What's the timing of a Flip-flop? (1/2)

 


- **Edge-triggered d-type flip-flop**

- This one is “positive edge-triggered”

 


- “On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored.”

What's the timing of a Flip-flop? (2/2)

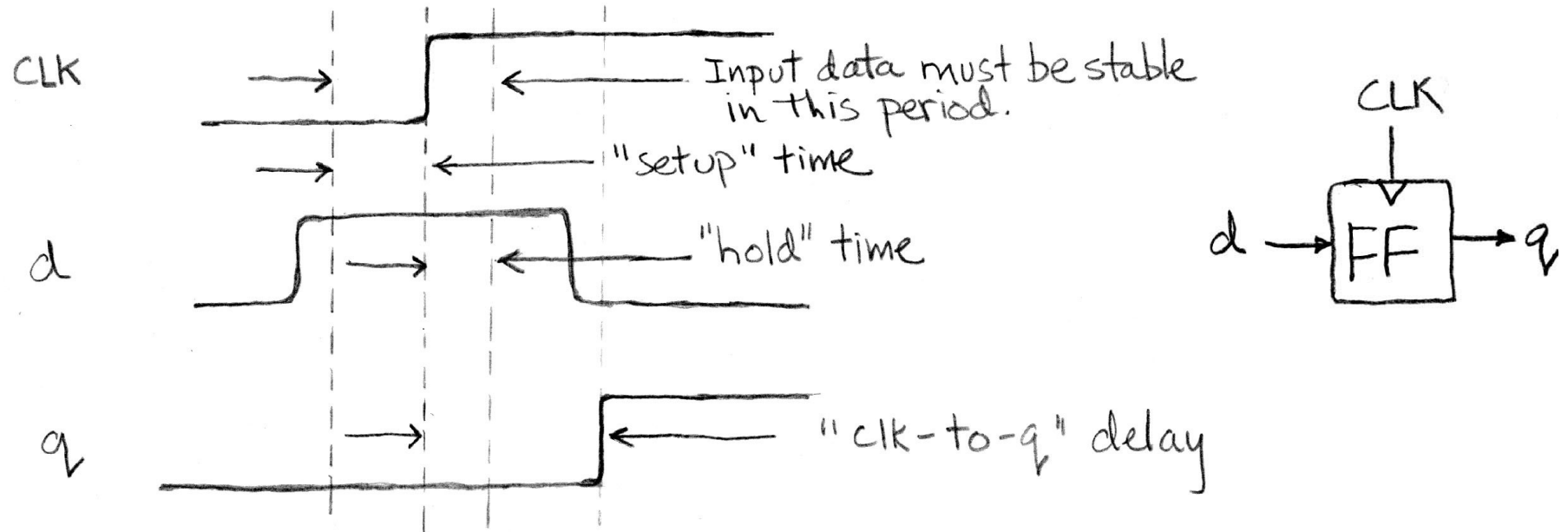



- **Edge-triggered d-type flip-flop**

- This one is "positive edge-triggered"


 


- "On the rising edge of the clock, the input d is sampled and transferred to the output. At all other times, the input d is ignored."

  Accumulator Revisited (proper timing 1/2)



  Accumulator Revisited (proper timing 2/2)



“And In conclusion...”

- We use **feedback** to maintain **state**
- Register files used to build memories
- D-FlipFlops used to build Register files
- Clocks tell us when D-FlipFlops change
 - Setup and Hold times important

