

**Lecture #16**  
 Representations of Combinatorial Logic Circuits



**CPS Today!** 2005-10-26 There are two handouts today at the front and back of the room!

Lecturer PSOE, new dad Dan Garcia

[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)

Car makes its own fuel ⇒


An Israeli company has invented a car that can produce its own Hydrogen using common metals like Magnesium and Aluminum. "Exhaust" is harmless metal oxide!



[www.isracast.com/tech\\_news/231005\\_tech.htm](http://www.isracast.com/tech_news/231005_tech.htm)  
CS61C L15 Representations of Combinatorial Logic Circuits (1) Garcia, Fall 2005 © UCB

 **Review**

- Pipeline big-delay CL for faster clock
- Finite State Machines extremely useful
  - You'll see them again in 150, 152 & 164
- Use this table and techniques we learned to transform from 1 to another




CS61C L15 Representations of Combinatorial Logic Circuits (2) Garcia, Fall 2005 © UCB

**Today**

- Data Multiplexors
- Arithmetic and Logic Unit
- Adder/Subtractor
- Programmable Logic Arrays

CS61C L15 Representations of Combinatorial Logic Circuits (3) Garcia, Fall 2005 © UCB

 **Data Multiplexor (here 2-to-1, n-bit-wide)**




**Truth table**

S	C
0	A
1	B

CS61C L15 Representations of Combinatorial Logic Circuits (4) Garcia, Fall 2005 © UCB

**N instances of 1-bit-wide mux**


How many rows in TT?

 

$$\begin{aligned}
 c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\
 &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\
 &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\
 &= \bar{s}(a(1)) + s((1)b) \\
 &= \bar{s}a + sb
 \end{aligned}$$

CS61C L15 Representations of Combinatorial Logic Circuits (5) Garcia, Fall 2005 © UCB


**How do we build a 1-bit-wide mux?**

 

CS61C L15 Representations of Combinatorial Logic Circuits (6) Garcia, Fall 2005 © UCB

### 4-to-1 Multiplexor?

How many rows in TT?

 

$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$




CS61C L15 Representations of Combinatorial Logic Circuits (7)

Garcia, Fall 2005 © UCB

### Is there any other way to do it?

Hint: NCAA tourney!

 

Ans: Hierarchically!




CS61C L15 Representations of Combinatorial Logic Circuits (8)

Garcia, Fall 2005 © UCB

### Do you really understand NORs?

- If one input is 1, what is a NOR?
- If one input is 0, what is a NOR?

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

 


CS61C L15 Representations of Combinatorial Logic Circuits (9)

Garcia, Fall 2005 © UCB

### Do you really understand NANDs?

- If one input is 1, what is a NAND?
- If one input is 0, what is a NAND?

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

 

CS61C L15 Representations of Combinatorial Logic Circuits (10)

Garcia, Fall 2005 © UCB

### What does it mean to “clobber” midterm?

- You **STILL** have to take the final even if you aced the midterm!
- The final will contain midterm-material Qs and new, post-midterm Qs
- They will be graded separately
- If you do “better” on the midterm-material, we will **clobber your midterm with the “new” score!** If you do worse, midterm unchanged.
- What does “better” mean?
  - Better w.r.t. Standard Deviations around mean
- What does “new” mean?
  - Score based on remapping St. Dev. score on final midterm-material to midterm score St. Dev.



CS61C L15 Representations of Combinatorial Logic Circuits (11)

Garcia, Fall 2005 © UCB

### “Clobber the midterm” example

- Midterm
  - Mean: 45
  - Standard Deviation: 14
  - You got a 31, one  $\sigma$  below. I.e., mean -  $\sigma$
- Final Midterm-Material Questions
  - Mean: 40
  - Standard Deviation: 20
  - You got a 60, one  $\sigma$  above
  - Your new midterm score is now mean +  $\sigma$
  - **= 45 + 14 = 59 (~ double your old score!)**



CS61C L15 Representations of Combinatorial Logic Circuits (12)

Garcia, Fall 2005 © UCB

## Administrivia

- Any administrivia?




CS61C L15 Representations of Combinatorial Logic Circuits (13)

Garcia, Fall 2005 © UCB
 
## Arithmetic and Logic Unit

- Most processors contain a special logic block called “Arithmetic and Logic Unit” (ALU)
- We’ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when  $S=00$ ,  $R=A+B$   
 when  $S=01$ ,  $R=A-B$   
 when  $S=10$ ,  $R=A \text{ AND } B$   
 when  $S=11$ ,  $R=A \text{ OR } B$



CS61C L15 Representations of Combinatorial Logic Circuits (14)

Garcia, Fall 2005 © UCB

## Our simple ALU

 

CS61C L15 Representations of Combinatorial Logic Circuits (15)

Garcia, Fall 2005 © UCB

## Adder/Subtractor Design -- how?

- Truth-table, then determine canonical form, then minimize and implement as we’ve seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer



CS61C L15 Representations of Combinatorial Logic Circuits (16)

Garcia, Fall 2005 © UCB

## Adder/Subtractor – One-bit adder LSB...

	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
	$s_3$	$s_2$	$s_1$	$s_0$

	$a_0$	$b_0$	$s_0$	$c_1$
	0	0	0	0
	0	1	1	0
	1	0	1	0
	1	1	0	1

$s_0 =$   
 $c_1 =$



CS61C L15 Representations of Combinatorial Logic Circuits (17)

Garcia, Fall 2005 © UCB

## Adder/Subtractor – One-bit adder (1/2)...

	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
	$s_3$	$s_2$	$s_1$	$s_0$

$a_i$	$b_i$	$c_i$	$s_i$	$c_{i+1}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$s_i =$   
 $c_{i+1} =$



CS61C L15 Representations of Combinatorial Logic Circuits (18)

Garcia, Fall 2005 © UCB
 
### Adder/Subtractor – One-bit adder (2/2)...




$$s_i = \text{XOR}(a_i, b_i, c_i)$$

$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$



### N 1-bit adders ⇒ 1 N-bit adder

 


What about overflow?  
Overflow =  $c_n$ ?


 
### What about overflow?

• Consider a 2-bit signed # & overflow:

- 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



• Highest adder

- $C_1 = \text{Carry-in} = C_{in}$ ,  $C_2 = \text{Carry-out} = C_{out}$
- No  $C_{out}$  or  $C_{in} \Rightarrow$  NO overflow!

What op?


- $C_{in}$ , and  $C_{out} \Rightarrow$  NO overflow!
- $C_{in}$ , but no  $C_{out} \Rightarrow$  A,B both > 0, overflow!
- $C_{out}$ , but no  $C_{in} \Rightarrow$  A,B both < 0, overflow!



### What about overflow?

• Consider a 2-bit signed # & overflow:

- 10 = -2
- 11 = -1
- 00 = 0
- 01 = 1

 


• Overflows when...

- $C_{in}$ , but no  $C_{out} \Rightarrow$  A,B both > 0, overflow!
- $C_{out}$ , but no  $C_{in} \Rightarrow$  A,B both < 0, overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$



### Extremely Clever Subtractor


 


### Review: Finite State Machine (FSM)

• States represent possible output values.

• Transitions represent changes between states based on inputs.

  • Implement with CL and clocked register feedback.



## Finite State Machines extremely useful!

- They define
  - How **output signals** respond to input signals and previous state.
  - How we **change states** depending on input signals and previous state
- We could implement very detailed FSMs w/**Programmable Logic Arrays**



CS61C L15 Representations of Combinatorial Logic Circuits (25)

Garcia, Fall 2005 © UCB

## Taking advantage of sum-of-products

- Since sum-of-products is a convenient notation and way to think about design, offer hardware building blocks that match that notation
- One example is **Programmable Logic Arrays (PLAs)**
- Designed so that can select (program) ands, ors, complements **after** you get the chip
  - Late in design process, fix errors, figure out what to do later, ...




CS61C L15 Representations of Combinatorial Logic Circuits (26)

Garcia, Fall 2005 © UCB
 
## Programmable Logic Arrays

- Pre-fabricated building block of many AND/OR gates
- “Programmed” or “Personalized” by making or breaking connections among gates
- Programmable array block diagram for sum of products form



CS61C L15 Representations of Combinatorial Logic Circuits (27)

Garcia, Fall 2005 © UCB

## Enabling Concept

- Shared product terms among outputs

example:

$$\begin{aligned}
 F_0 &= A + B'C \\
 F_1 &= AC' + AB \\
 F_2 &= B'C + AB \\
 F_3 &= B'C + A
 \end{aligned}$$

input side: 3 inputs  
 1 = uncomplemented in term  
 0 = complemented in term  
 - = does not participate

### personality matrix

Product term	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

output side: 4 outputs  
 1 = term connected to output  
 0 = no connection to output

reuse of terms; 5 product terms




CS61C L15 Representations of Combinatorial Logic Circuits (28)

Garcia, Fall 2005 © UCB
 
## Before Programming

- All possible connections available before “programming”




CS61C L15 Representations of Combinatorial Logic Circuits (29)

Garcia, Fall 2005 © UCB
 
## After Programming

- Unwanted connections are “blown”
  - Fuse (normally connected, break unwanted ones)
  - Anti-fuse (normally disconnected, make wanted connections)




CS61C L15 Representations of Combinatorial Logic Circuits (30)

Garcia, Fall 2005 © UCB
 
### Alternate Representation

- Short-hand notation--don't have to draw all the wires
- X Signifies a connection is present and perpendicular signal is an input to gate



CS61C L15 Representations of Combinatorial Logic Circuits (31)

Garcia, Fall 2005 © UCB

### “And In conclusion...”

- Use muxes to select among input
  - S input bits selects  $2^S$  inputs
  - Each input can be n-bits wide, indep of S
- Implement muxes hierarchically
- ALU can be implemented using a mux
  - Coupled with basic block elements
- N-bit adder-subtractor done using N 1-bit adders with XOR gates on input
  - XOR serves as conditional inverter
- Programmable Logic Arrays are often used to implement our CL



CS61C L15 Representations of Combinatorial Logic Circuits (32)

Garcia, Fall 2005 © UCB

### Peer Instruction

- SW can peek at HW (past ISA abstraction boundary) for optimizations
- SW can depend on particular HW implementation of ISA
- Timing diagrams serve as a critical debugging tool in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TTF
8:	TTT



CS61C L15 Representations of Combinatorial Logic Circuits (33)

Garcia, Fall 2005 © UCB

### Peer Instruction

- HW feedback akin to SW recursion
- We can implement a D-Q flipflop as simple CL (And, Or, Not gates)
- You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TTF
8:	TTT



CS61C L15 Representations of Combinatorial Logic Circuits (34)

Garcia, Fall 2005 © UCB

### Peer Instruction

- $(a+b) \cdot (\bar{a}+b) = b$
- N-input gates can be thought of cascaded 2-input gates. I.e.,  $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$  where  $\Delta$  is one of AND, OR, XOR, NAND
- You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TTF
8:	TTT



CS61C L15 Representations of Combinatorial Logic Circuits (36)

Garcia, Fall 2005 © UCB

### Peer Instruction

- Truth table for mux with 4-bits of signals has  $2^4$  rows
- We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl
- If 1-bit adder delay is T, the N-bit adder delay would also be T

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TTF
8:	TTT



CS61C L15 Representations of Combinatorial Logic Circuits (40)

Garcia, Fall 2005 © UCB