

Lecture #16

Representations of Combinatorial Logic Circuits



CPS
today!

2005-10-26

There are two handouts
today at the front and
back of the room!

Lecturer PSOE, new dad Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Car makes its own fuel ⇒

**An Israeli company has
invented a car that can produce its
own Hydrogen using common metals
like Magnesium and Aluminum.**




“Exhaust” is harmless metal oxide!

www.isracast.com/tech_news/231005_tech.htm

Review

 - **Pipeline big-delay CL for faster clock**
- **Finite State Machines extremely useful**
 - You'll see them again in 150, 152 & 164
- **Use this table and techniques we learned to transform from 1 to another**




Today

- **Data Multiplexors**
- **Arithmetic and Logic Unit**
- **Adder/Subtractor**
- **Programmable Logic Arrays**



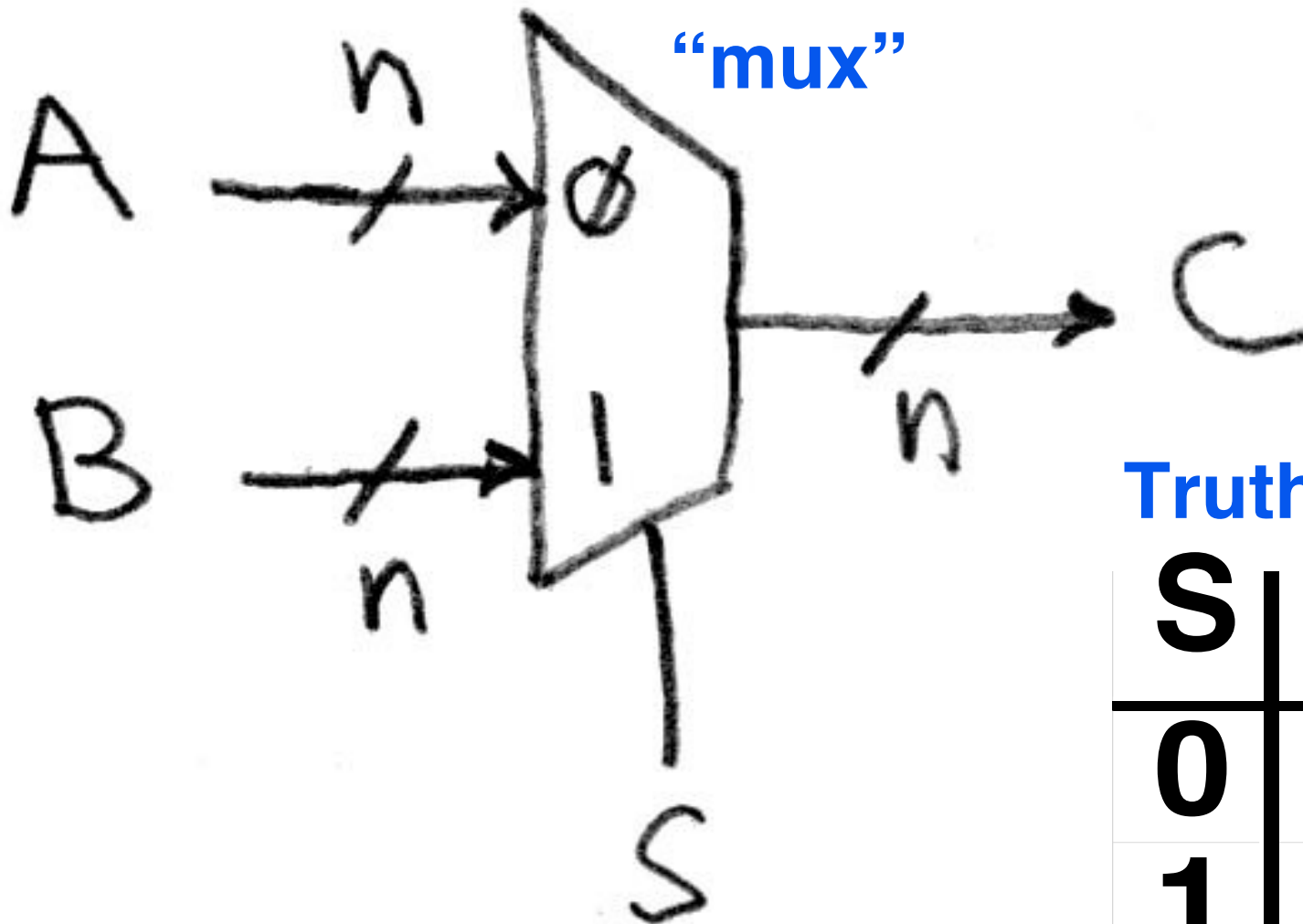Data Multiplexor (here 2-to-1, n-bit-wide)




Truth table

S	C
0	A
1	B

N instances of 1-bit-wide mux

How many rows in TT?

 


$$\begin{aligned}c &= \bar{s}a\bar{b} + \bar{s}ab + s\bar{a}b + sab \\ &= \bar{s}(a\bar{b} + ab) + s(\bar{a}b + ab) \\ &= \bar{s}(a(\bar{b} + b)) + s((\bar{a} + a)b) \\ &= \bar{s}(a(1) + s((1)b) \\ &= \bar{s}a + sb\end{aligned}$$




How do we build a 1-bit-wide mux?

$$\bar{s}a + sb$$

 

4-to-1 Multiplexor?


How many rows in TT?

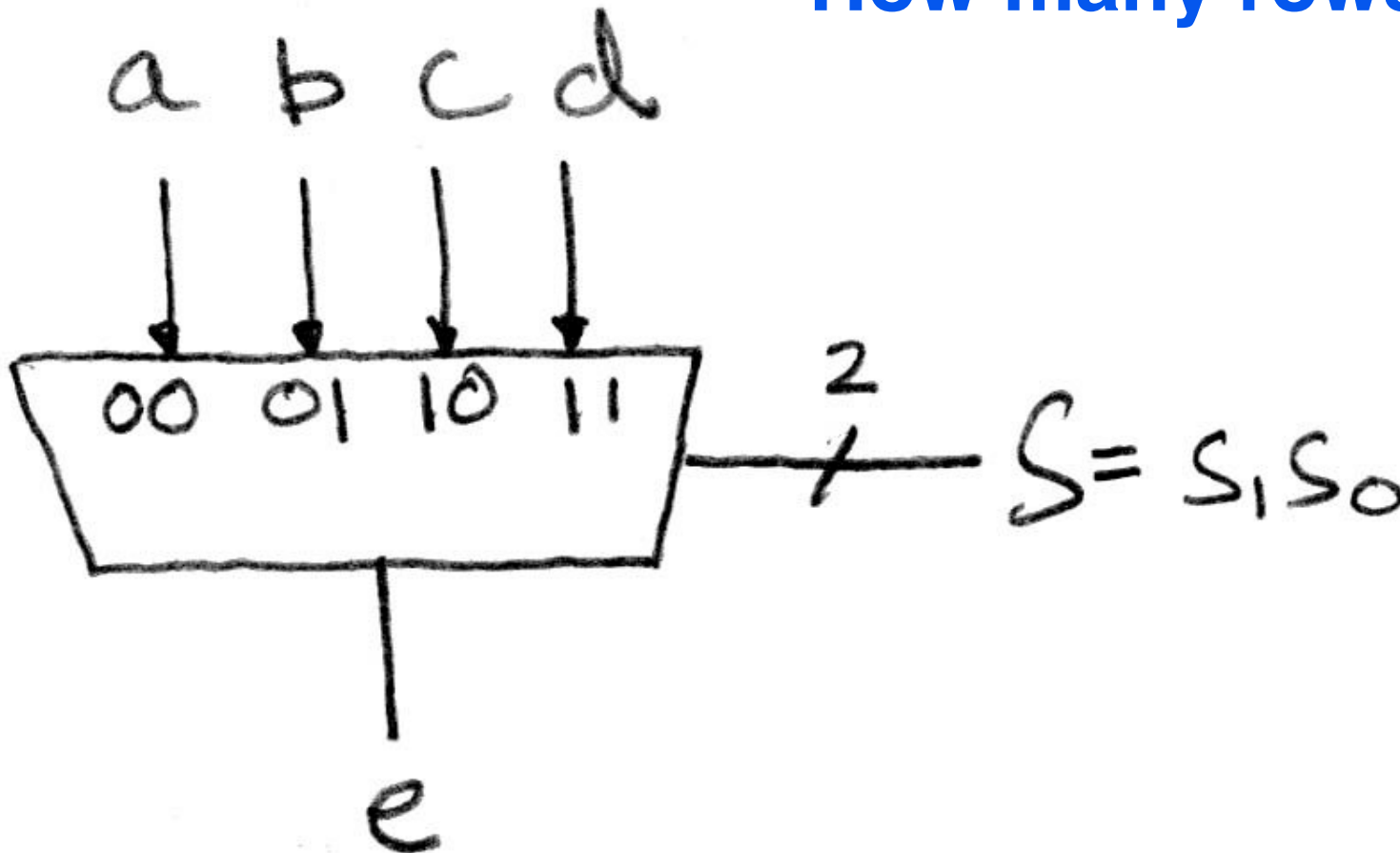

$$e = \overline{s_1}\overline{s_0}a + \overline{s_1}s_0b + s_1\overline{s_0}c + s_1s_0d$$

Is there any other way to do it?

Hint: NCAA tourney!

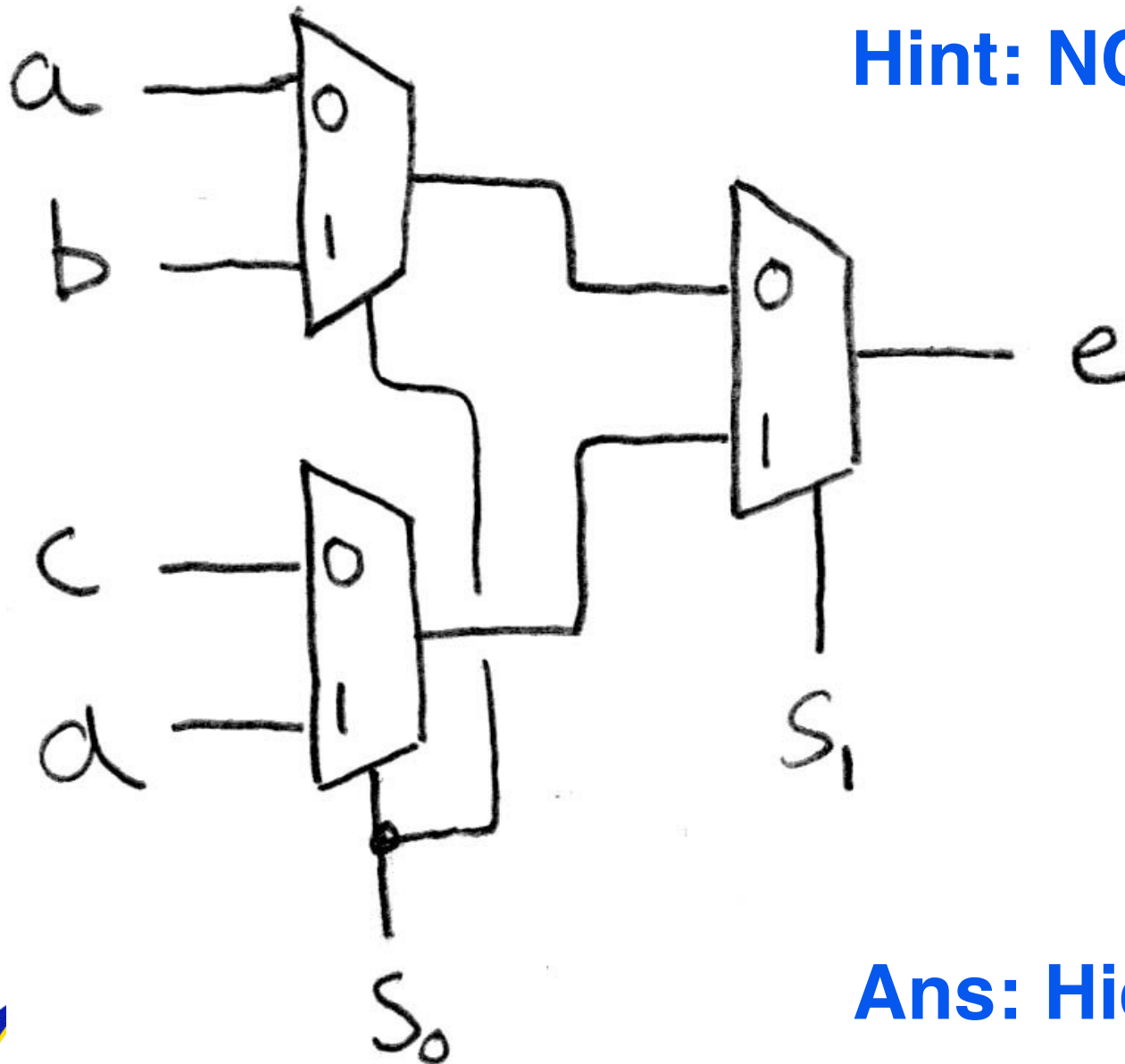


Ans: Hierarchically!



Do you really understand NORs?

- If one input is 1, what is a NOR?
- If one input is 0, what is a NOR?

A	B	NOR
0	0	1
0	1	0
1	0	0
1	1	0

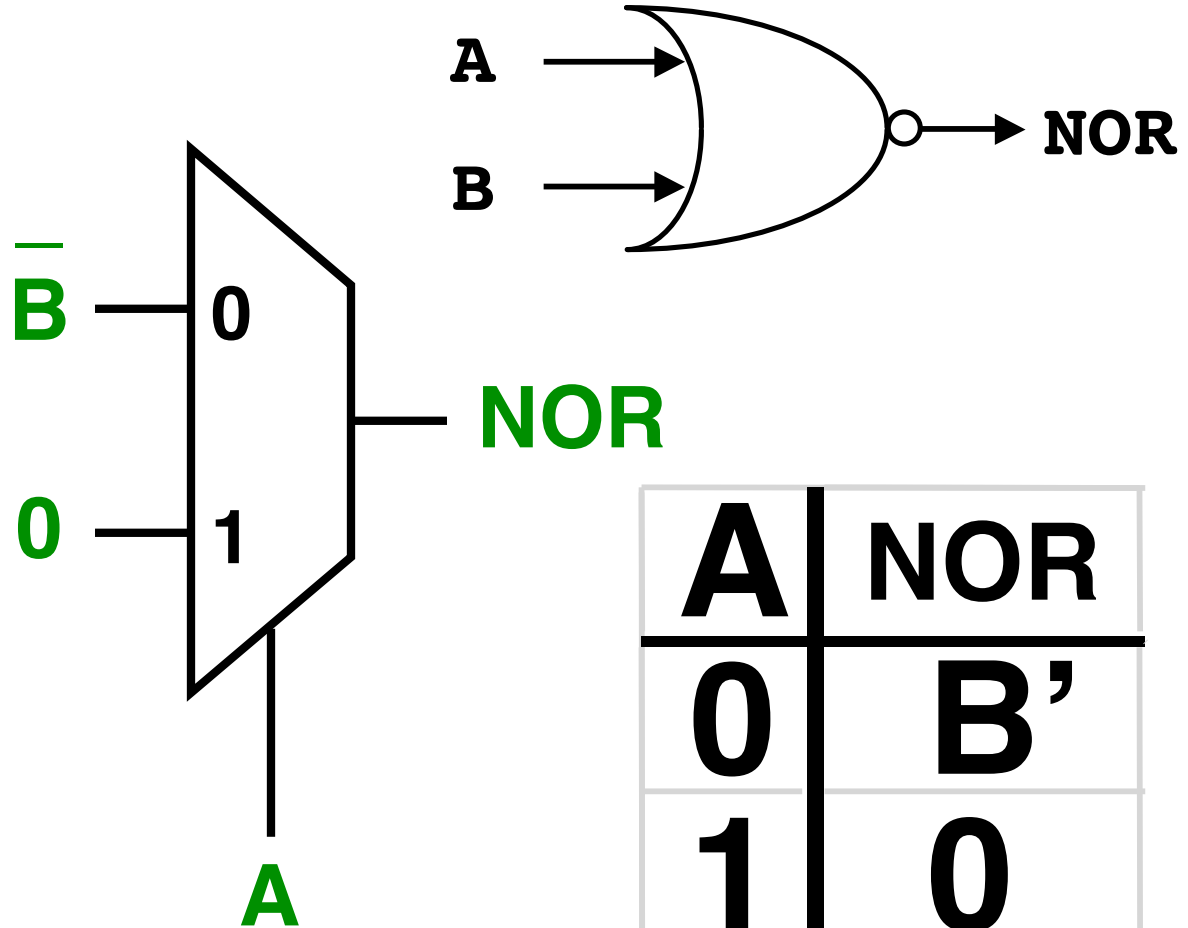


A	NOR
0	B'
1	0

Do you really understand NANDs?

- If one input is 1, what is a NAND?
- If one input is 0, what is a NAND?

A	B	NAND
0	0	1
0	1	1
1	0	1
1	1	0

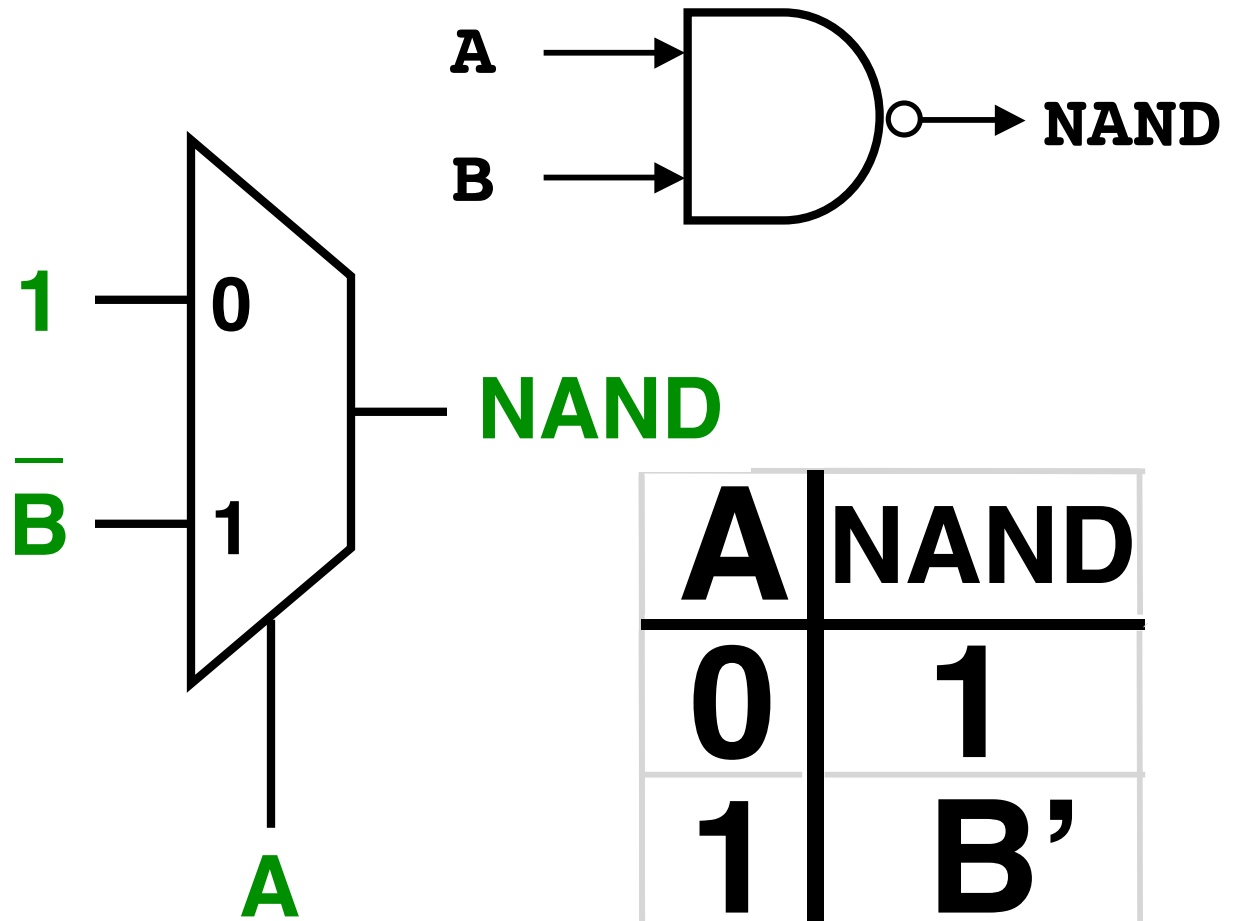

A	NAND
0	1
1	B'

What does it mean to “clobber” midterm?

- You **STILL** have to take the final even if you aced the midterm!
- The final will contain midterm-material Qs and new, post-midterm Qs
- They will be graded separately
- If you do “**better**” on the midterm-material, we will **clobber your midterm with the “new” score!** **If you do worse, midterm unchanged.**
- What does “**better**” mean?
 - Better w.r.t. Standard Deviations around mean
- What does “**new**” mean?
 - Score based on remapping St. Dev. score on final midterm-material to midterm score St. Dev.



“Clobber the midterm” example

- **Midterm**

- Mean: 45
- Standard Deviation: 14
- **You got a 31, one σ below. I.e., mean - σ**



- **Final Midterm-Material Questions**

- Mean: 40
- Standard Deviation: 20
- **You got a 60, one σ above**
- **Your new midterm score is now mean + σ
= 45 + 14 = 59 (~ double your old score)!**




Administrivia

- **Any administrivia?**



Arithmetic and Logic Unit

 
- Most processors contain a special logic block called “Arithmetic and Logic Unit” (ALU)
- We’ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR



when $S=00$, $R=A+B$
when $S=01$, $R=A-B$
when $S=10$, $R=A \text{ AND } B$
when $S=11$, $R=A \text{ OR } B$



Our simple ALU

 

Adder/Subtractor Design -- how?

- **Truth-table, then determine canonical form, then minimize and implement as we've seen before**
- **Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer**



Adder/Subtractor – One-bit adder LSB...

$$\begin{array}{rcccc} & a_3 & a_2 & a_1 & a_0 \\ + & b_3 & b_2 & b_1 & b_0 \\ \hline s_3 & s_2 & s_1 & s_0 \end{array}$$

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



Adder/Subtractor – One-bit adder (1/2)...

+	a_3	a_2	a_1	a_0
	b_3	b_2	b_1	b_0
	s_3	s_2	s_1	s_0



a_i	b_i	c_i	s_i	c_{i+1}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$s_i =$$

$$c_{i+1} =$$




  Adder/Subtractor – One-bit adder (2/2)...



$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

N 1-bit adders \Rightarrow 1 N-bit adder

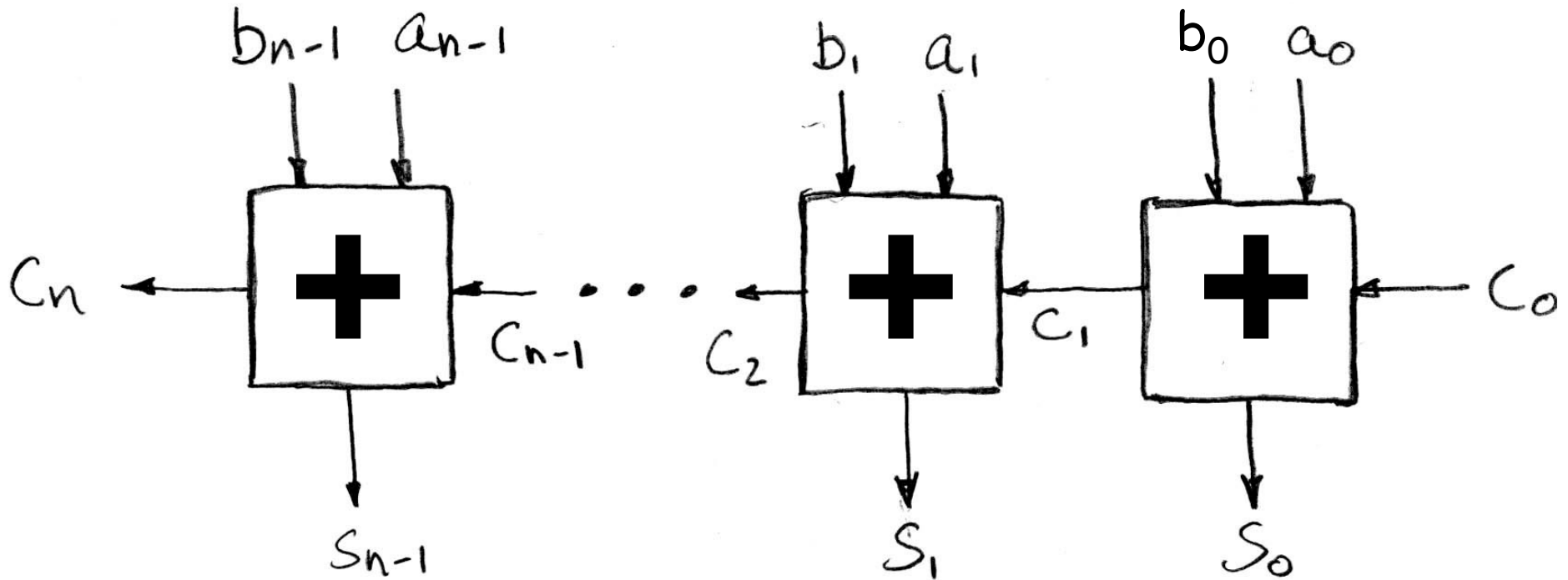


**What about overflow?
Overflow = c_n ?**

What about overflow?

- Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



- Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!

What op?

- C_{in} , and $C_{out} \Rightarrow$ NO overflow!

• C_{in} , but no $C_{out} \Rightarrow A, B \text{ both } > 0$, overflow!


• C_{out} , but no $C_{in} \Rightarrow A, B \text{ both } < 0$, overflow!



What about overflow?

- Consider a 2-bit signed # & overflow:

10 = -2
11 = -1
00 = 0
01 = 1

 


- Overflows when...

- C_{in} , but no $C_{out} \Rightarrow A, B$ both > 0 , overflow!
- C_{out} , but no $C_{in} \Rightarrow A, B$ both < 0 , overflow!



$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$

Extremely Clever Subtractor

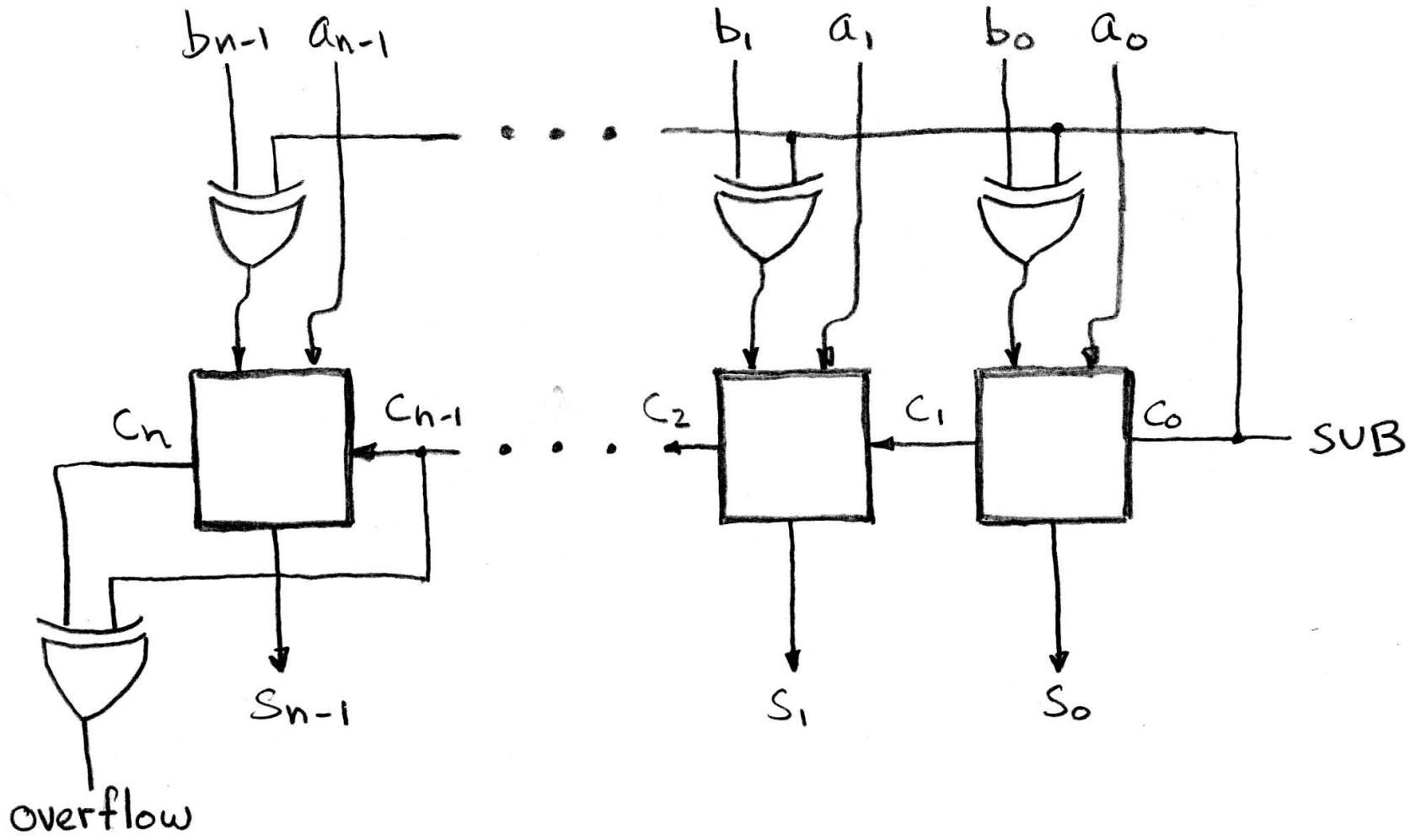

Review: Finite State Machine (FSM)

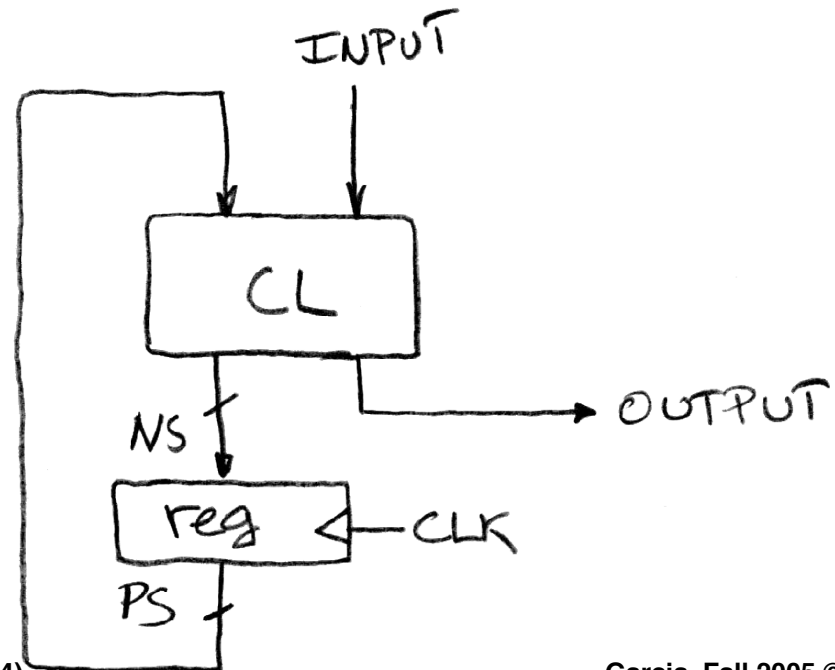 - **States** represent possible output values.
- **Transitions** represent changes between states based on inputs.
- **Implement** with CL and clocked register feedback.



Finite State Machines extremely useful!

- They define
 - How **output signals** respond to input signals and previous state.
 - How we **change states** depending on input signals and previous state
- We could implement very detailed FSMs w/**Programmable Logic Arrays**




Taking advantage of sum-of-products

- Since sum-of-products is a convenient notation and way to think about design, offer hardware building blocks that match that notation
- One example is **Programmable Logic Arrays (PLAs)**
- Designed so that can select (program) ands, ors, complements after you get the chip
 - Late in design process, fix errors, figure out what to do later, ...



Programmable Logic Arrays

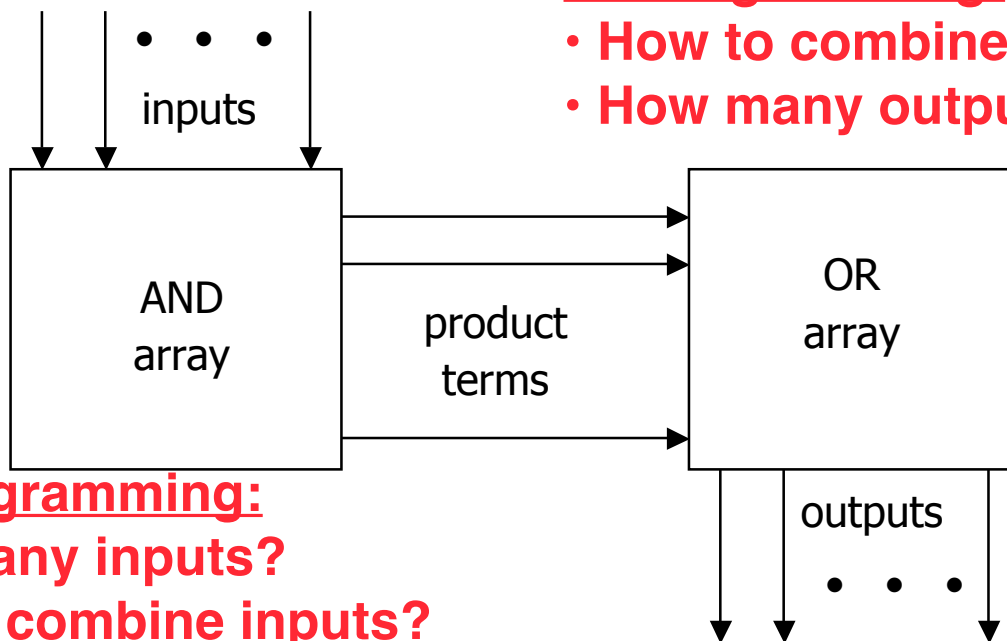- Pre-fabricated building block of many AND/OR gates
 - “Programmed” or “Personalized” by making or breaking connections among gates
 - Programmable array block diagram for sum of products form



Or Programming:

- How to combine product terms?
- How many outputs?

And Programming:

- How many inputs?
- How to combine inputs?
- How many product terms?



Enabling Concept

- Shared product terms among outputs

example:

$$\begin{aligned}
 F0 &= A + B' C' \\
 F1 &= A C' + A B \\
 F2 &= B' C' + A B \\
 F3 &= B' C + A
 \end{aligned}$$

input side: 3 inputs

1 = uncomplemented in term
 0 = complemented in term
 - = does not participate

personality matrix

Product term	inputs			outputs			
	A	B	C	F0	F1	F2	F3
AB	1	1	-	0	1	1	0
B'C	-	0	1	0	0	0	1
AC'	1	-	0	0	1	0	0
B'C'	-	0	0	1	0	1	0
A	1	-	-	1	0	0	1

output side: 4 outputs


1 = term connected to output
 0 = no connection to output

reuse of terms;
 5 product terms




Before Programming

 - All possible connections available before “programming”



After Programming

 - Unwanted connections are "blown"
 - Fuse (normally connected, break unwanted ones)
 - Anti-fuse (normally disconnected, make wanted connections)





Alternate Representation

- Short-hand notation--don't have to draw all the wires
- X Signifies a connection is present and perpendicular signal is an input to gate

notation for implementing

$$F0 = A B + A' B'$$

$$F1 = C D' + C' D$$

  

“And In conclusion...”

- **Use muxes to select among input**
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- **Implement muxes hierarchically**
- **ALU can be implemented using a mux**
 - Coupled with basic block elements
- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - XOR serves as conditional inverter
- **Programmable Logic Arrays** are often used to implement our CL



Peer Instruction

- A. SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- B. SW **can depend** on particular HW implementation of ISA
- C. Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Peer Instruction

- A. HW feedback akin to SW recursion**
- B. We can implement a D-Q flipflop as simple CL (And, Or, Not gates)**
- C. You can build a FSM to signal when an equal number of 0s and 1s has appeared in the input.**

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT

Peer Instruction

- A. $(a+b) \cdot (\bar{a}+b) = b$
- B. N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta bc \Delta d \Delta e) = a \Delta (bc \Delta (d \Delta e))$
where Δ is one of AND, OR, XOR, NAND
- C. You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Peer Instruction

- A. Truth table for mux with 4-bits of signals has 2^4 rows
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T

	ABC
1 :	FFF
2 :	FFT
3 :	FTF
4 :	FTT
5 :	TFF
6 :	TFT
7 :	TF F
8 :	TTT