



Lecture #17 Single Cycle CPU Datapath



CPS
today!

2005-10-31

There is one handout
today at the front and
back of the room!

Lecturer PSOE, new dad Dan Garcia

www.cs.berkeley.edu/~ddgarcia

Halloween plans? ⇒ Try the Castro, SF!

Today 2005-10-31,
from 7pm-mid
(\$5 donation)

go at least
once...



CS61C L17 Single Cycle CPU Datapath (1)




halloweeninthecastro.com

Happy Halloween, everyone!

Garcia, Fall 2005 © UCB

 Wed's talk : Jim Larus, μ soft (Cal Ph.D.)



“An Overview of the Singularity Project”

- 306 Soda Hall, Wed 2005-11-02 @ 4-5pm
- Dr. Larus is the author of **SPIM!**
- <ftp://ftp.research.microsoft.com/pub/tr/TR-2005-135.pdf>

“**Singularity** is a research project in Microsoft

Research that started with the question: what would a software platform look like if it was designed from scratch with the primary goal of dependability?

Singularity is working to answer this question by building on advances in programming languages and tools to develop a new system architecture and operating system (named **Singularity**), with the aim of producing a more robust and dependable software platform. **Singularity** demonstrates the practicality of new technologies and architectural decisions, which should lead to the construction of more robust and dependable systems.”




Review


- **Use muxes to select among input**
 - S input bits selects 2^S inputs
 - Each input can be n-bits wide, indep of S
- **Implement muxes hierarchically**
- **ALU can be implemented using a mux**
 - Coupled with basic block elements
- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - XOR serves as conditional inverter
- **Programmable Logic Arrays** are often used to implement our CL



Anatomy: 5 components of any Computer

 

This week
and next

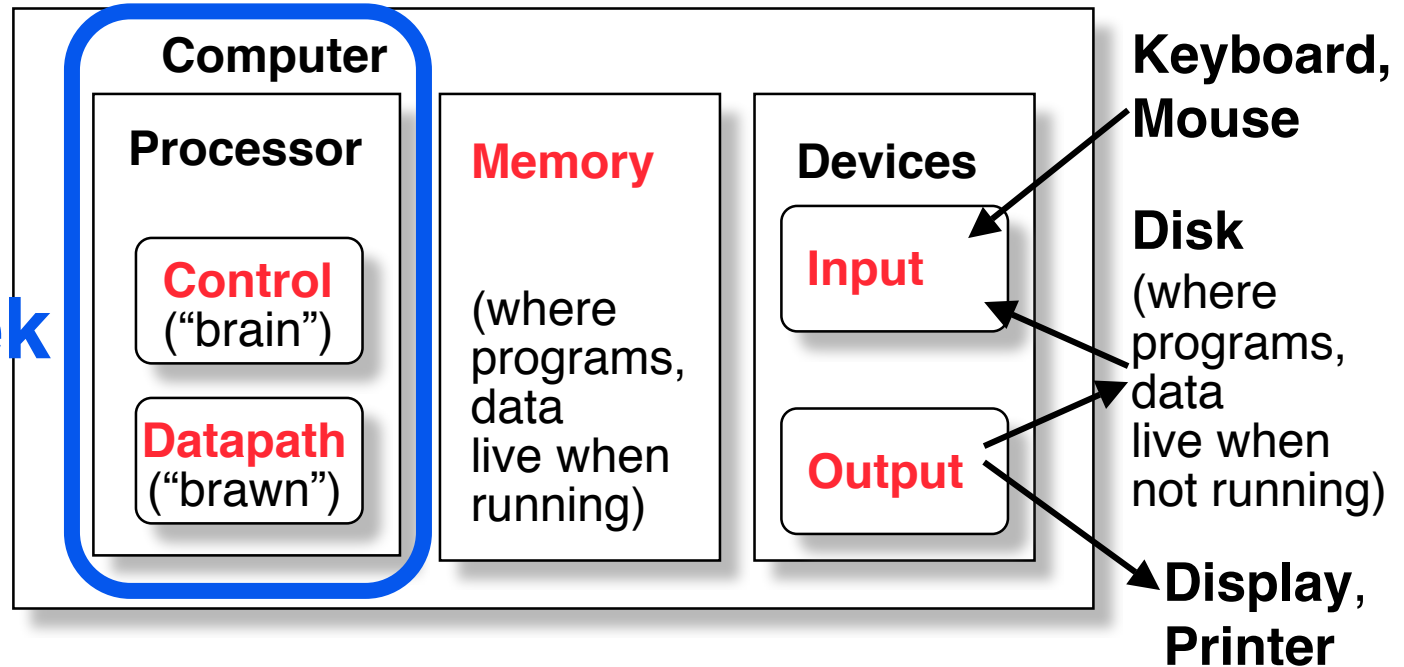

Outline of Today's Lecture

- **Design a processor: step-by-step**
- **Requirements of the Instruction Set**
- **Hardware components that match the instruction set requirements**



How to Design a Processor: step-by-step


- **1. Analyze instruction set architecture (ISA)**
⇒ datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- **2. Select set of datapath components and establish clocking methodology**
- **3. Assemble datapath meeting requirements**
- **4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.**
- **5. Assemble the control logic**




Review: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:

- R-type

 

- I-type

 

- J-type




- The different fields are:

- op**: operation (“opcode”) of the instruction
- rs, rt, rd**: the source and destination register specifiers
- shamt**: shift amount
- funct**: selects the variant of the operation in the “op” field
- address / immediate**: address offset or immediate value
- target address**: target address of jump instruction




Step 1a: The MIPS-lite Subset for today


• ADDU and SUBU

 


• OR Immediate:

 

• LOAD and STORE Word

 

• BRANCH:

 

Register Transfer Language

- RTL gives the meaning of the instructions

$\{op, rs, rt, rd, shamt, funct\} = \text{MEM}[PC]$

$\{op, rs, rt, \text{Imm16}\} = \text{MEM}[PC]$

- All start by fetching the instruction

inst Register Transfers

ADDU $R[rd] = R[rs] + R[rt];$ **PC = PC + 4**

SUBU $R[rd] = R[rs] - R[rt];$ **PC = PC + 4**

ORI $R[rt] = R[rs] \mid \text{zero_ext}(\text{Imm16});$ **PC = PC + 4**

LOAD $R[rt] = \text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})];$ **PC = PC + 4**

STORE $\text{MEM}[R[rs] + \text{sign_ext}(\text{Imm16})] = R[rt];$ **PC = PC + 4**

BEQ if ($R[rs] == R[rt]$) then

PC = PC + 4 + (sign_ext(Imm16) || 00)

else PC = PC + 4



Step 1: Requirements of the Instruction Set

- **Memory (MEM)**
 - instructions & data
- **Registers (R: 32 x 32)**
 - read RS
 - read RT
 - Write RT or RD
- **PC**
- **Extender (sign extend)**
- **Add and Sub register or extended immediate**
- **Add 4 or extended immediate to PC**




Step 2: Components of the Datapath

- **Combinational Elements**
- **Storage Elements**
 - **Clocking methodology**





Combinational Logic Elements (Building Blocks)

• Adder

 

• MUX

  

ALU Needs for MIPS-lite + Rest of MIPS

- Addition, subtraction, logical OR, ==:

ADDU $R[rd] = R[rs] + R[rt]; \dots$

SUBU $R[rd] = R[rs] - R[rt]; \dots$

ORI $R[rt] = R[rs] | \text{zero_ext}(\text{Imm16}) \dots$

BEQ $\text{if} (R[rs] == R[rt]) \dots$

- Test to see if output == 0 for any ALU operation gives == test. How?
- P&H also adds AND,
Set Less Than (1 if $A < B$, 0 otherwise)
- ALU follows chap 5



Administrivia

- **Project 2 graded**
 - You have a week (2005-11-07) to regrade
- **My wed OH this week moved to Fri @ 2p**
- **Final Exam location TBA (exam grp 14)**
 - **Sat**, 2005-12-17, 12:30–3:30pm
 - **ALL** students are required to complete **ALL** of the exam (even if you aced the midterm)
 - **Same format as the midterm**
 - 3 Hours
 - Closed book, **except for 2 study sheets + green**
 - Leave your backpacks, books at home



Storage Element: Idealized Memory

- **Memory (idealized)**


- One input bus: Data In
- One output bus: Data Out

- **Memory word is selected by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus


- **Clock input (CLK)**

 - The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
 - Address valid \Rightarrow Data Out valid after “access time.”



Storage Element: Register (Building Block)

 - **Similar to D Flip Flop except**
 - N-bit input and output
 - Write Enable input
- **Write Enable:**
 - negated (or deasserted) (0):
Data Out will not change
 - asserted (1):
Data Out will become Data In




Storage Element: Register File

- Register File consists of 32 registers:

- Two 32-bit output busses:

busA and busB

- One 32-bit input bus: busW

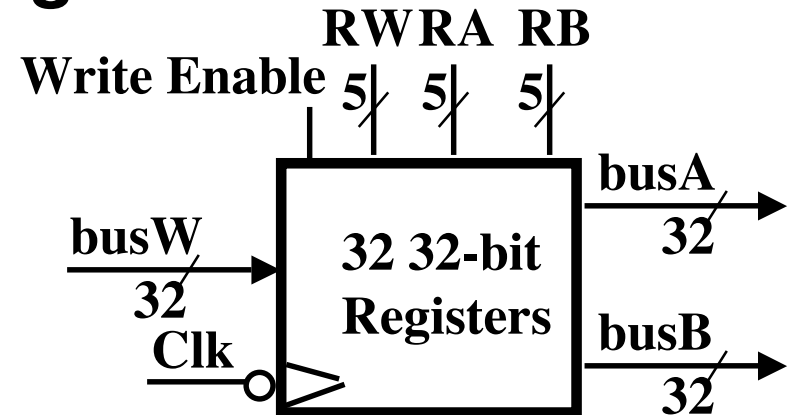

- Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- Clock input (CLK)

- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:

- RA or RB valid => busA or busB valid after “access time.”




Step 3: Assemble DataPath meeting requirements

- Register Transfer Requirements
⇒ Datapath Assembly
- Instruction Fetch
- Read Operands and Execute Operation



3a: Overview of the Instruction Fetch Unit

 
- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} = \text{PC} + 4$
 - Branch and Jump: $\text{PC} = \text{“something else”}$




3b: Add & Subtract

• $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: `addU rd,rs,rt`

 • Ra, Rb, and Rw come from instruction's **Rs**, **Rt**, and **Rd** fields




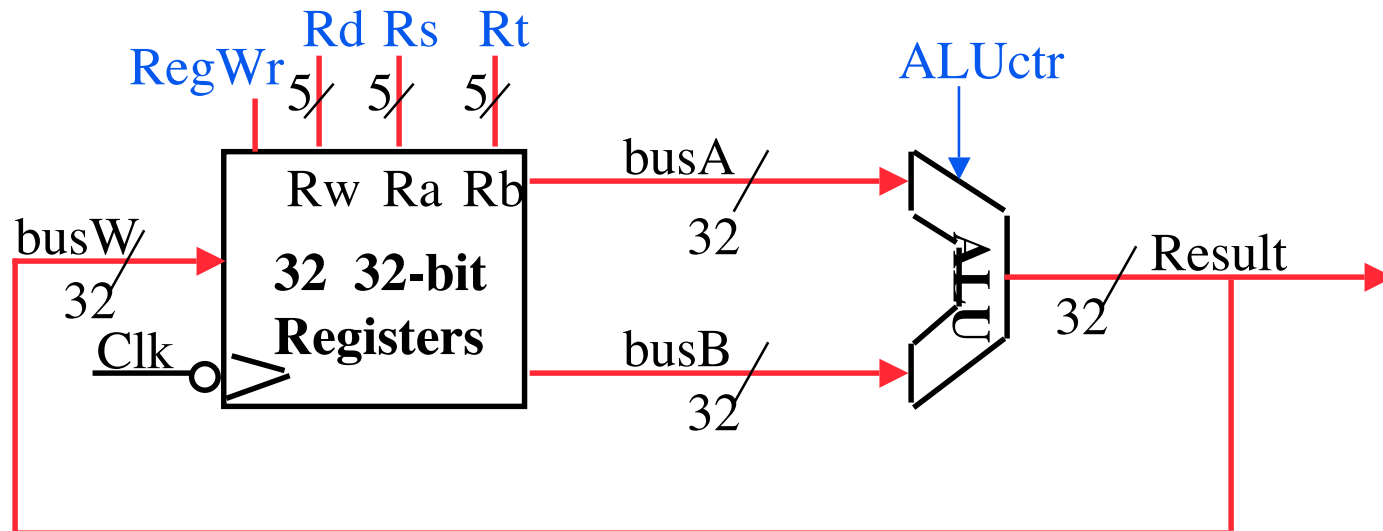• **ALUctr** and **RegWr**: control logic after decoding the instruction



• Already defined register file, ALU



Clocking Methodology

 

- **Storage elements clocked by same edge**
- **Being physical devices, flip-flops (FF) and combinational logic have some delays**
 - **Gates: delay from input change to output change**
 - **Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF, and we have the usual clock-to-Q delay**
- **“Critical path” (longest path through logic) determines length of clock period**



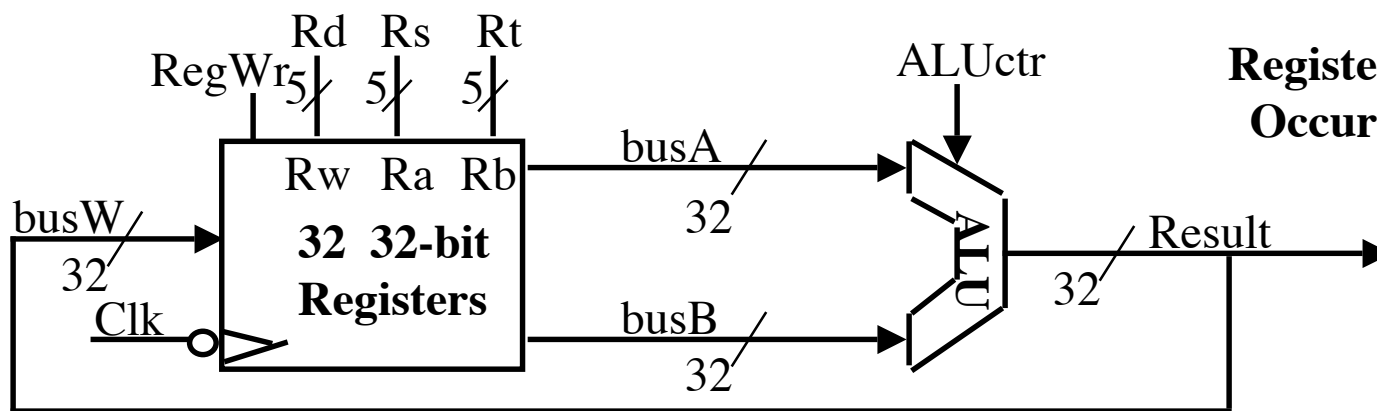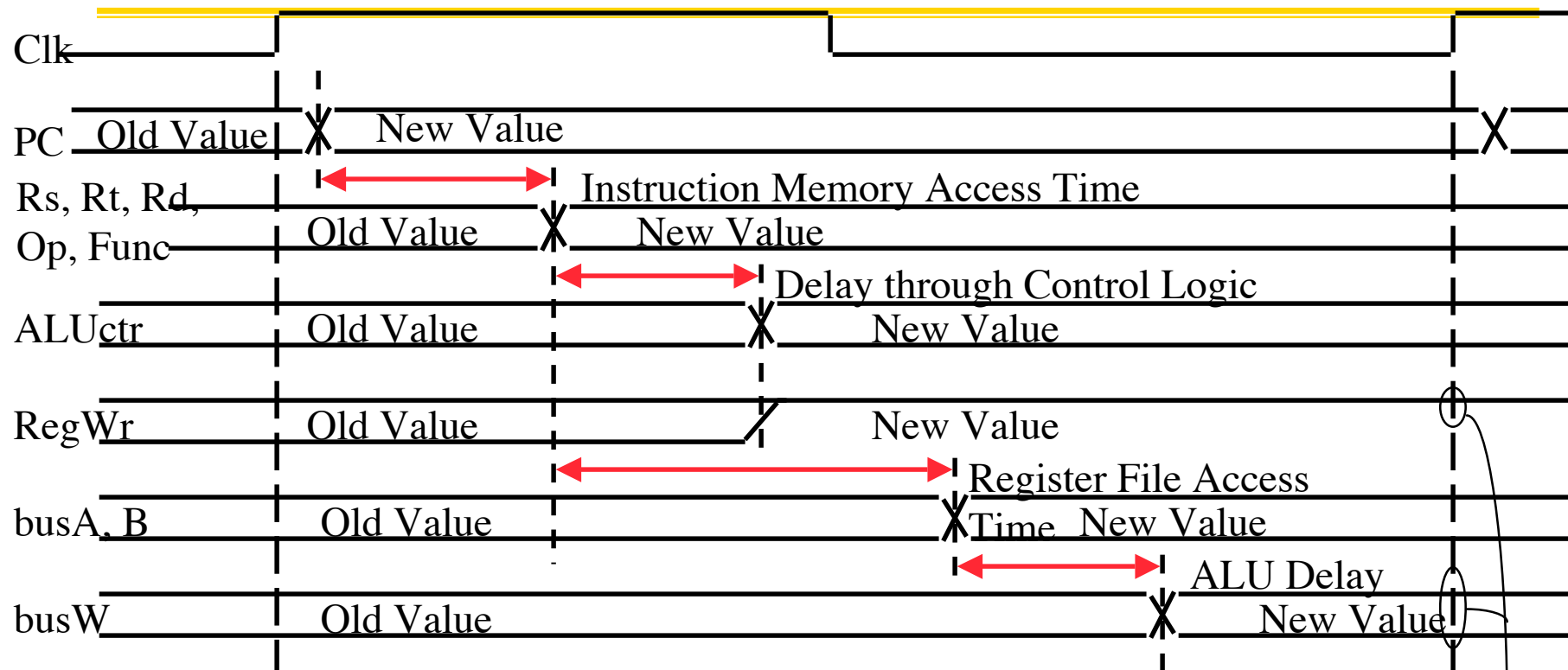Register-Register Timing: One complete cycle




Register Write Occurs Here




3c: Logical Operations with Immediate

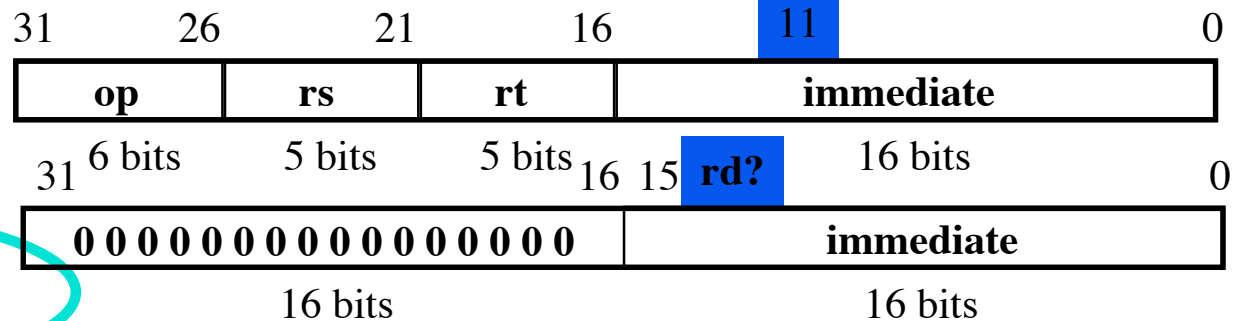- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$





What about Rt register read??

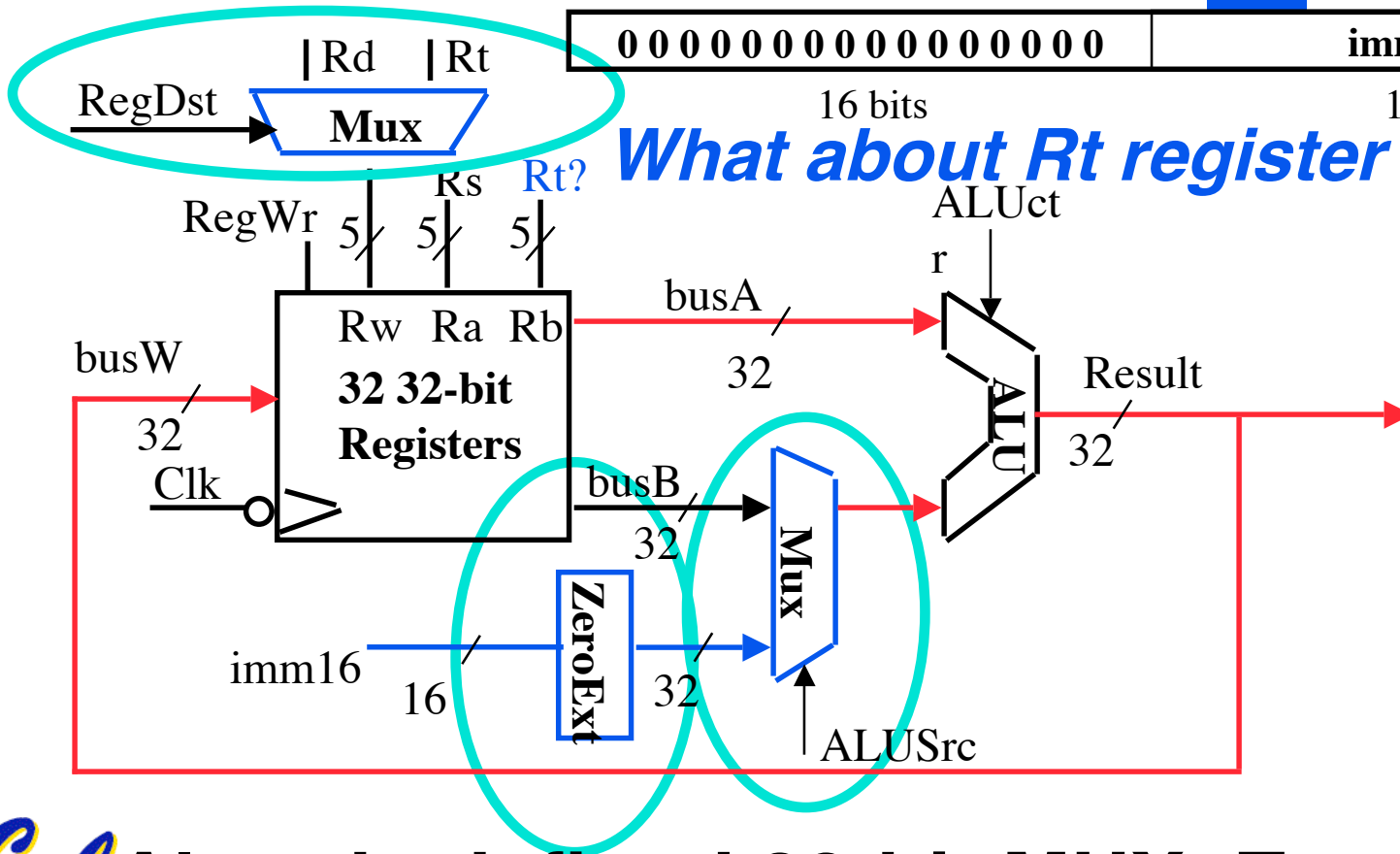

• Already defined 32-bit MUX; Zero Ext?


3d: Load Operations

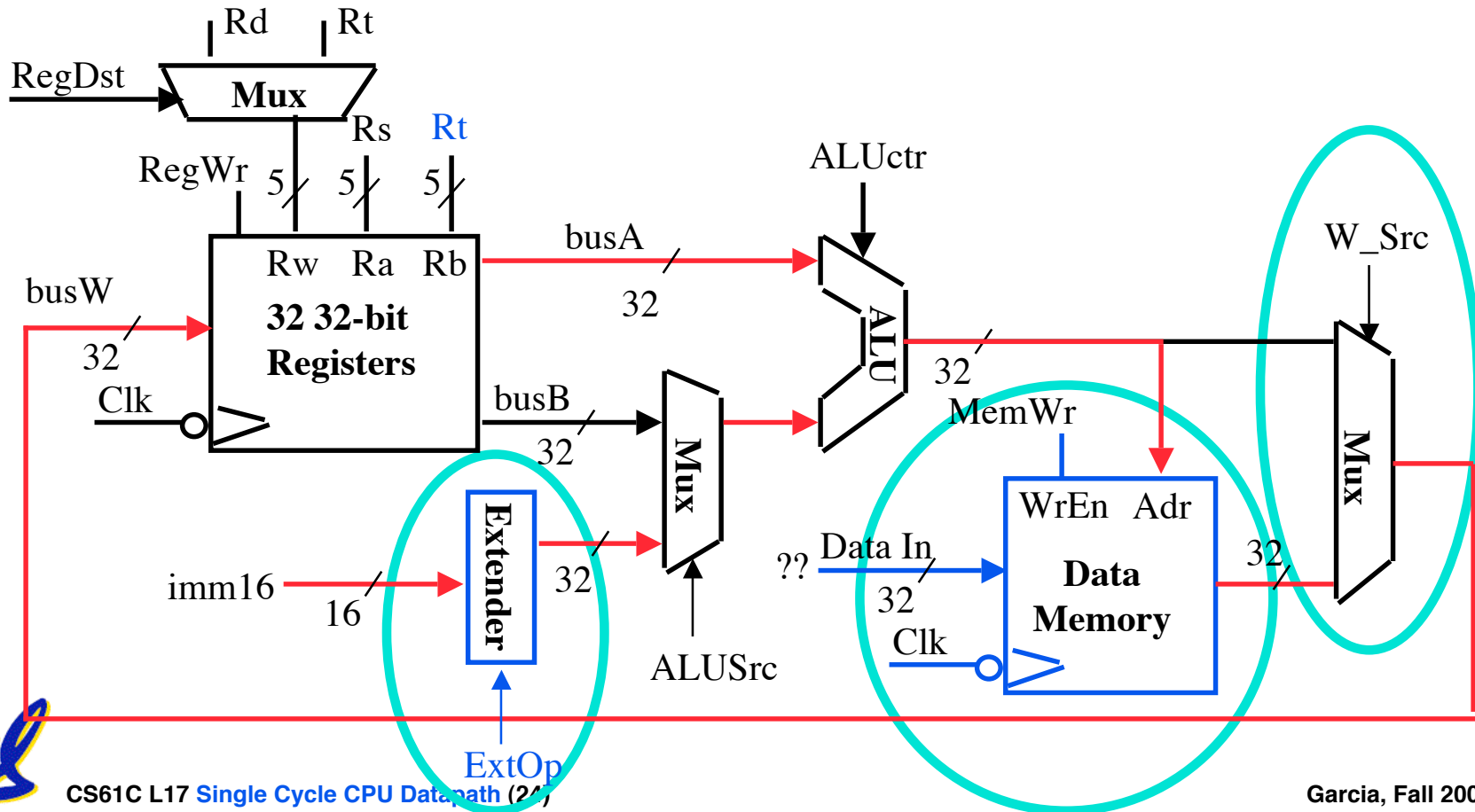 - $R[rt] = Mem[R[rs] + SignExt[imm16]]$
Example: `lw rt, rs, imm16`




3e: Store Operations

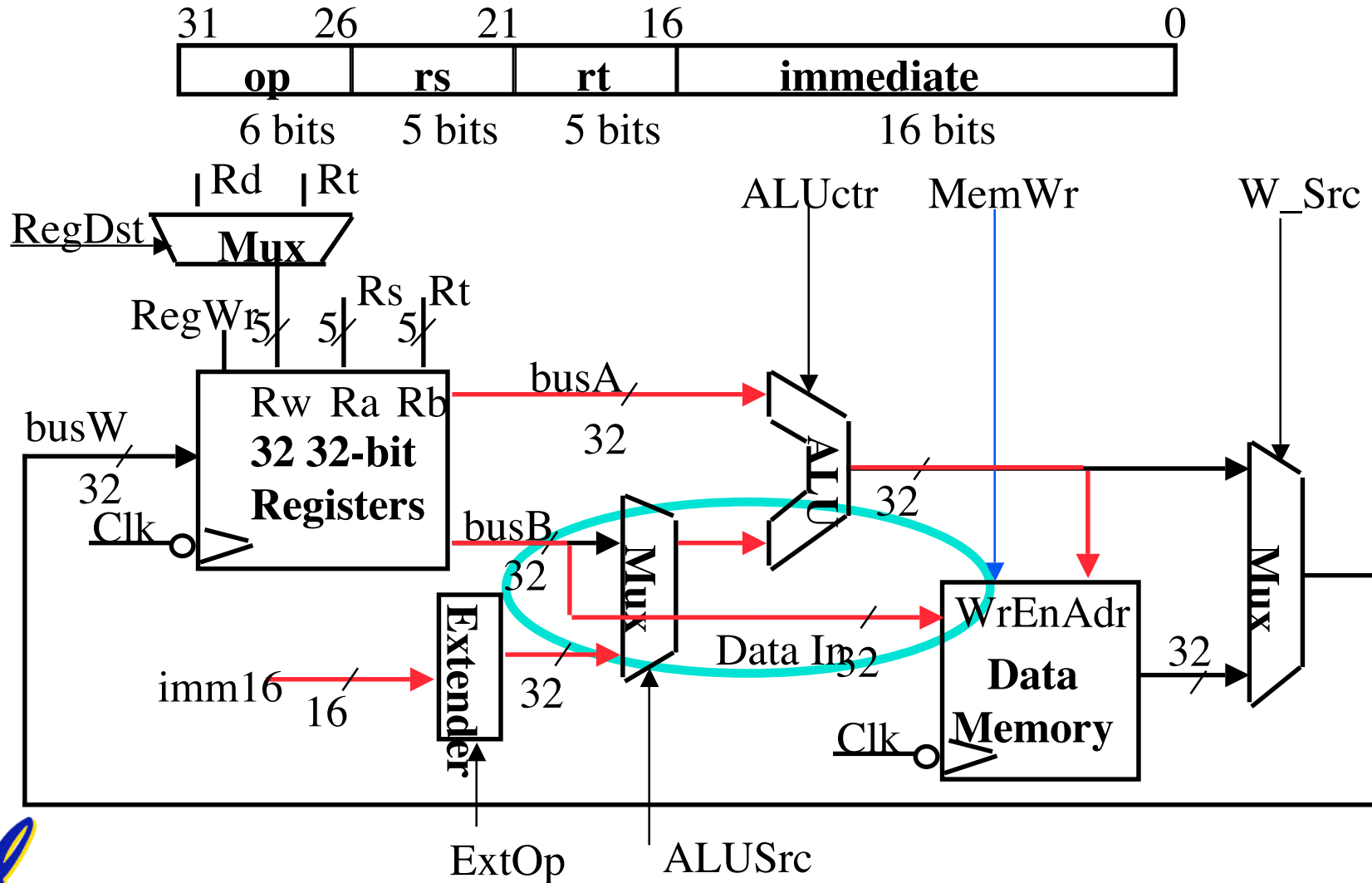- $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]] = R[\text{rt}]$
 Ex.: `sw rt, rs, imm16`



3f: The Branch Instruction


 


- **beq rs, rt, imm16**
 - **mem[PC] Fetch the instruction from memory**
 - **Equal = R[rs] == R[rt] Calculate branch condition**
 - **if (Equal) Calculate the next instruction's address**
 - **PC = PC + 4 + (SignExt(imm16) x 4)**
 - else**
 - **PC = PC + 4**




Datapath for Branch Operations

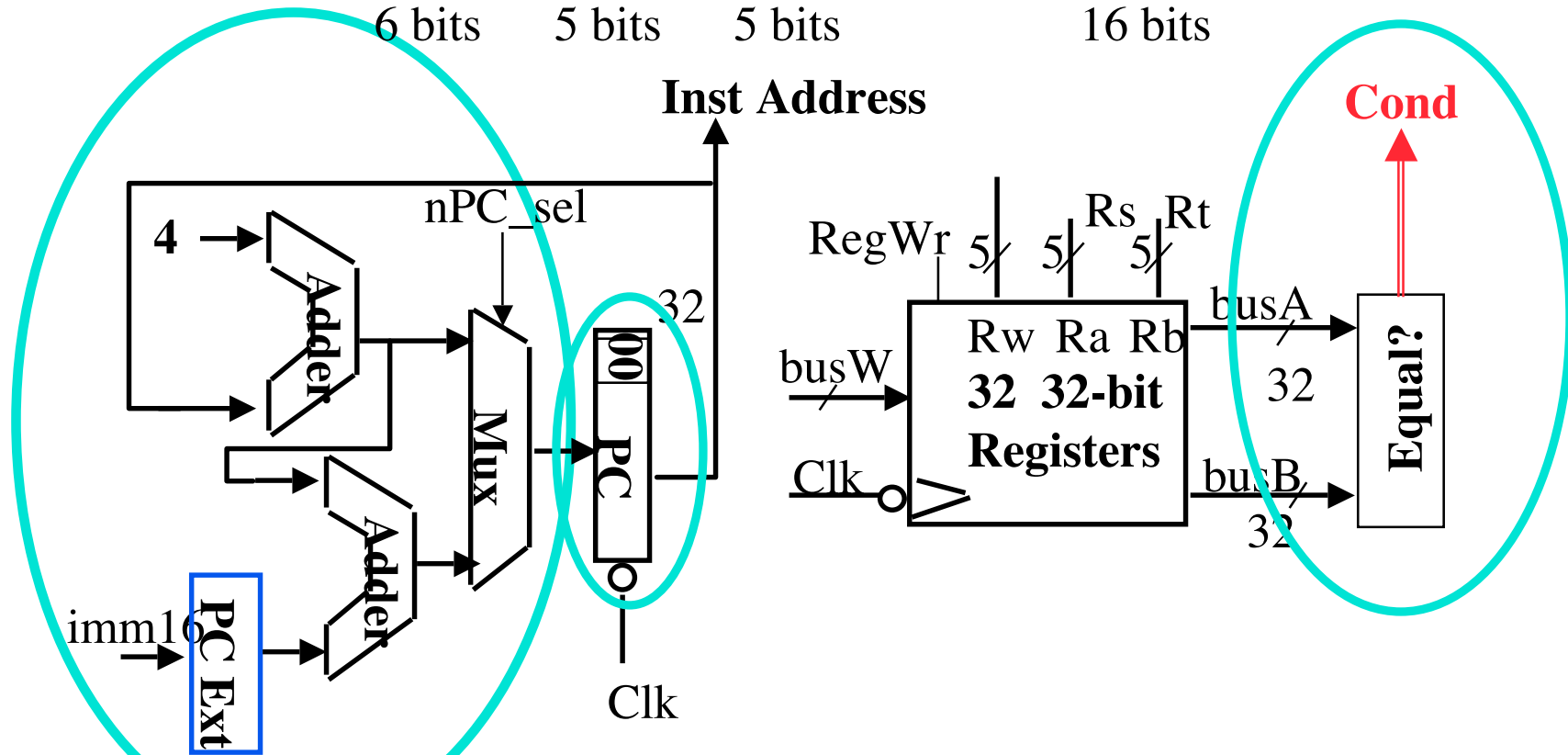 - **beq** rs, rt, imm16
Datapath generates condition (equal)




• **Already MUX, adder, sign extend, zero**

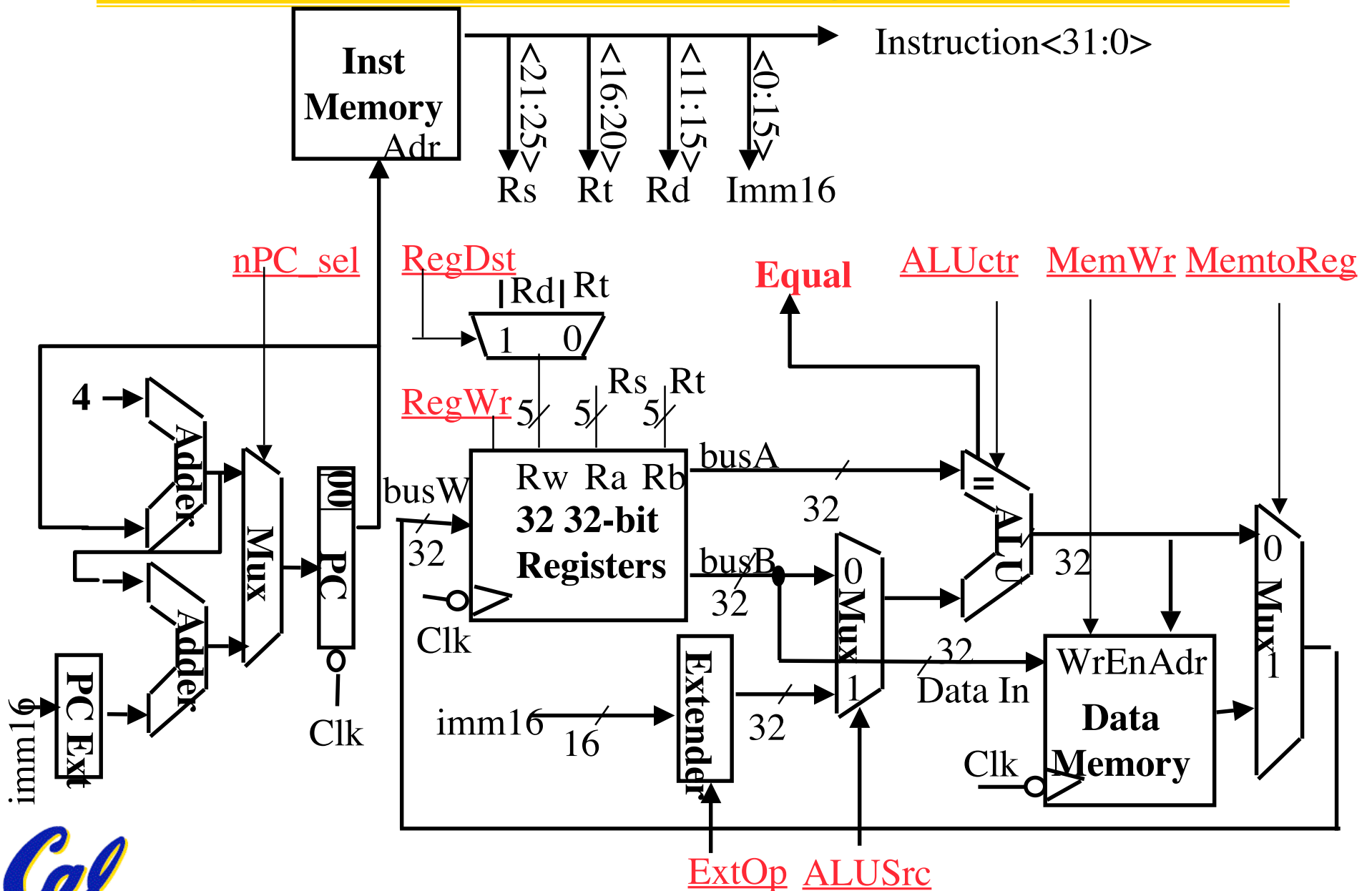Putting it All Together: A Single Cycle Datapath



An Abstract View of the Implementation

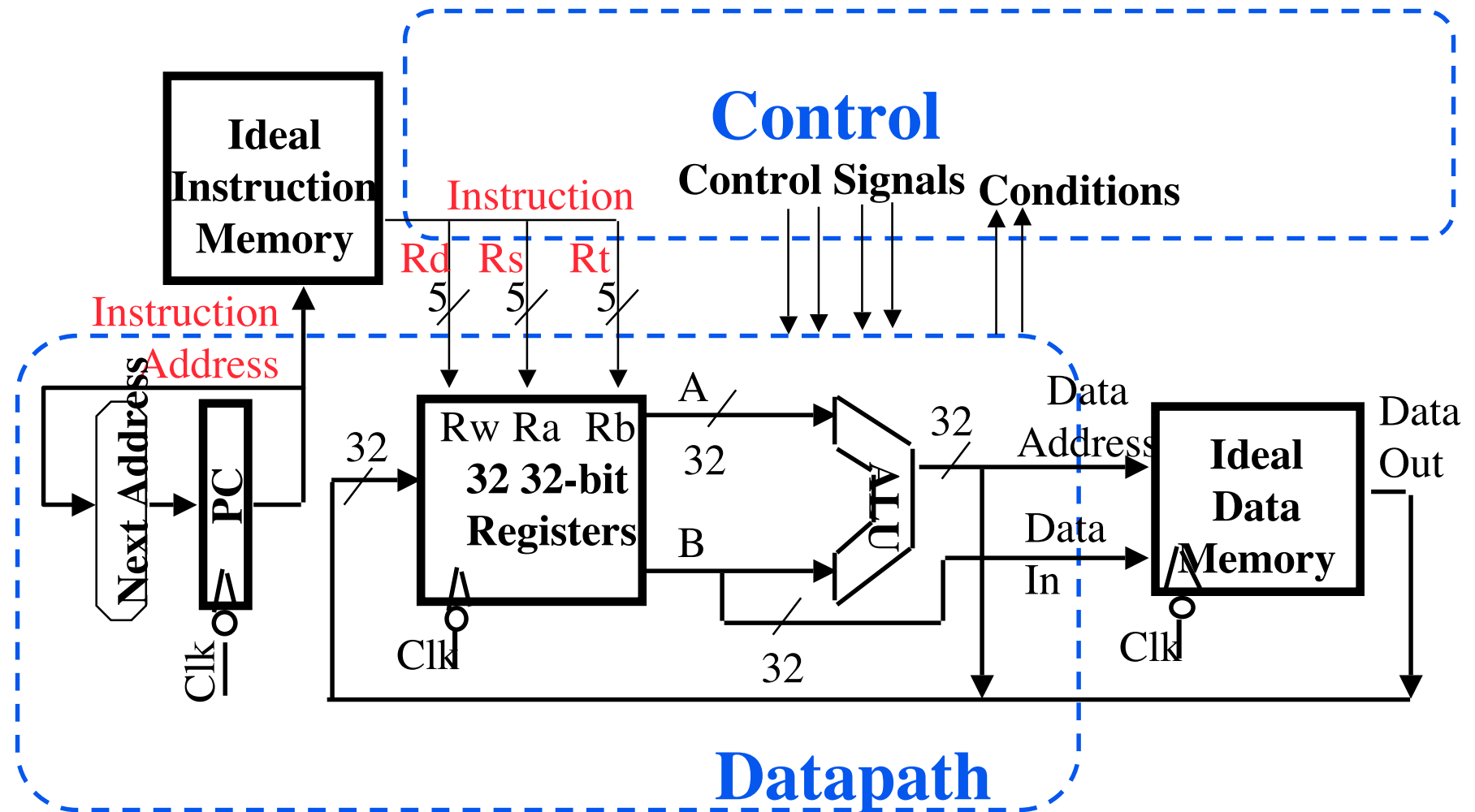

Peer Instruction

- A. If the destination reg is the same as the source reg, we **could compute the incorrect value!**
- B. We're going to be able to read 2 registers and write a 3rd in **1 cycle**
- C. Datapath is hard, **Control is easy**

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT

Peer Instruction

- A. Our **ALU** is a synchronous device
- B. We should use the main **ALU** to compute $PC=PC+4$
- C. The **ALU** is inactive for memory reads or writes.

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Peer Instruction

- A. SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- B. SW **can depend** on particular HW implementation of ISA
- C. Timing diagrams serve as a **critical debugging tool** in the EE toolkit

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Peer Instruction

- A. $(a+b) \cdot (\bar{a}+b) = b$
- B. N-input gates can be thought of cascaded 2-input gates. I.e.,
 $(a \Delta b \Delta c \Delta d) = a \Delta (b \Delta (c \Delta d))$
where Δ is one of AND, OR, XOR, NAND
- C. You can use NOR(s) with clever wiring to simulate AND, OR, & NOT

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT



Peer Instruction

- A. Truth table for mux with 4-bits of signals has 2^4 rows
- B. We could cascade N 1-bit shifters to make 1 N-bit shifter for sll, srl
- C. If 1-bit adder delay is T, the N-bit adder delay would also be T

	ABC
1:	FFF
2:	FFT
3:	FTF
4:	FTT
5:	TFF
6:	TFT
7:	TF
8:	TTT

Summary: Single cycle datapath

- **5 steps to design a processor**
 - 1. Analyze instruction set \Rightarrow datapath requirements
 - 2. Select set of datapath components & establish clock methodology
 - 3. Assemble datapath meeting the requirements
 - 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
 - 5. Assemble the control logic
- **Control is the hard part**
- **Next time!**

