

inst.eecs.berkeley.edu/~cs61c  
**CS61C : Machine Structures**

## Lecture 20

# Introduction to Synchronous Digital Systems



**2010-03-08**

Hello to Alejandro Torrijos  
listening from España!

**Lecturer SOE Dan Garcia**

**[www.cs.berkeley.edu/~ddgarcia](http://www.cs.berkeley.edu/~ddgarcia)**

**What to call 1,000 yottas? ⇒  
UC Davis physics student Austin  
Sendek has earned his 15 min of  
fame by suggesting that the next SI unit be (you  
guessed it) ... “hella”. He wanted to pay homage  
to Northern California (UCB, UCD, Stanford, LBNL).**




[www.huffingtonpost.com/2010/03/02/hella-number-scientists-n\\_n\\_482260.html](http://www.huffingtonpost.com/2010/03/02/hella-number-scientists-n_n_482260.html)

CS61C L20 Synchronous Digital Systems (1)


Garcia, Spring 2010 © UCB

# Review

---

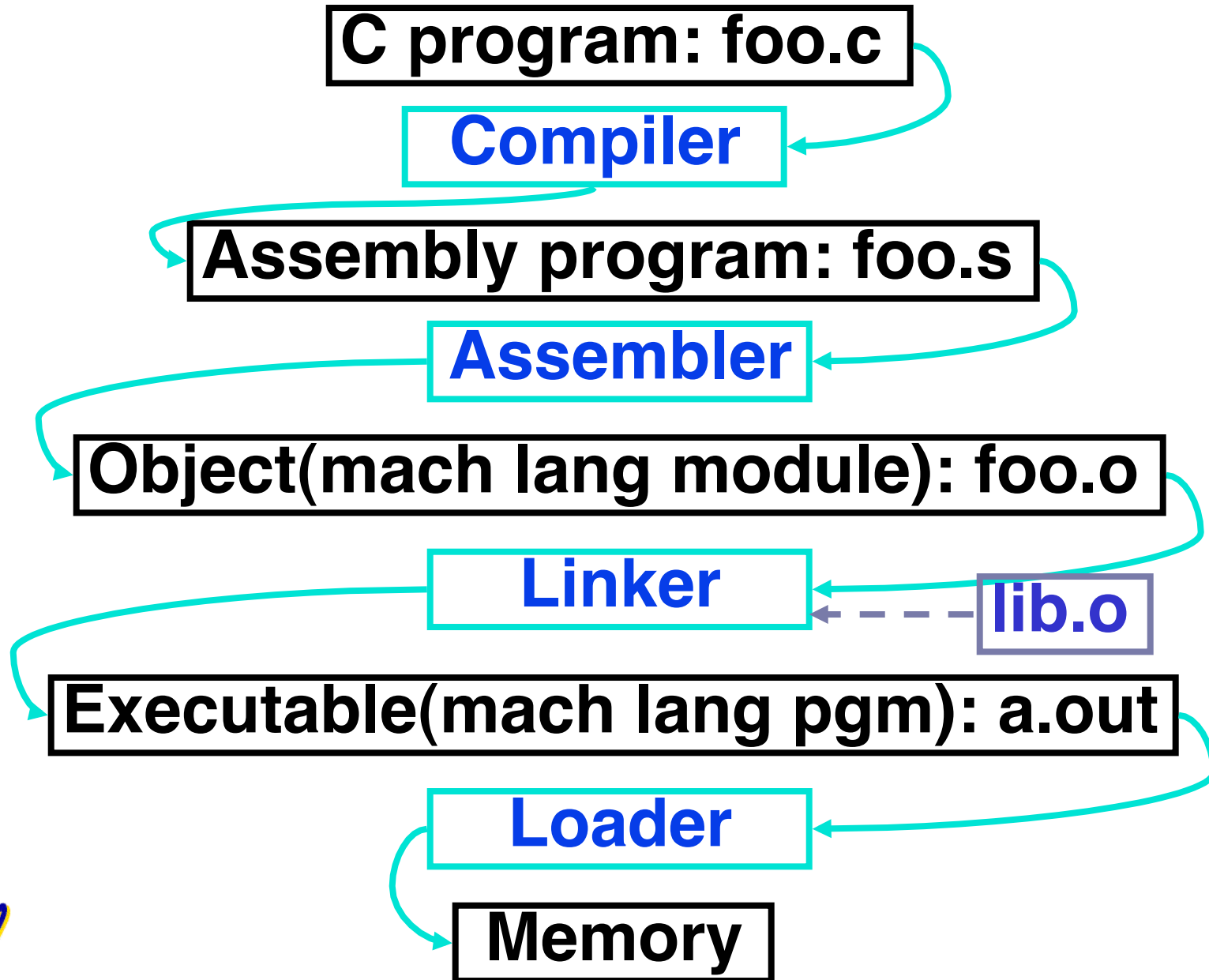

# What are “Machine Structures”?

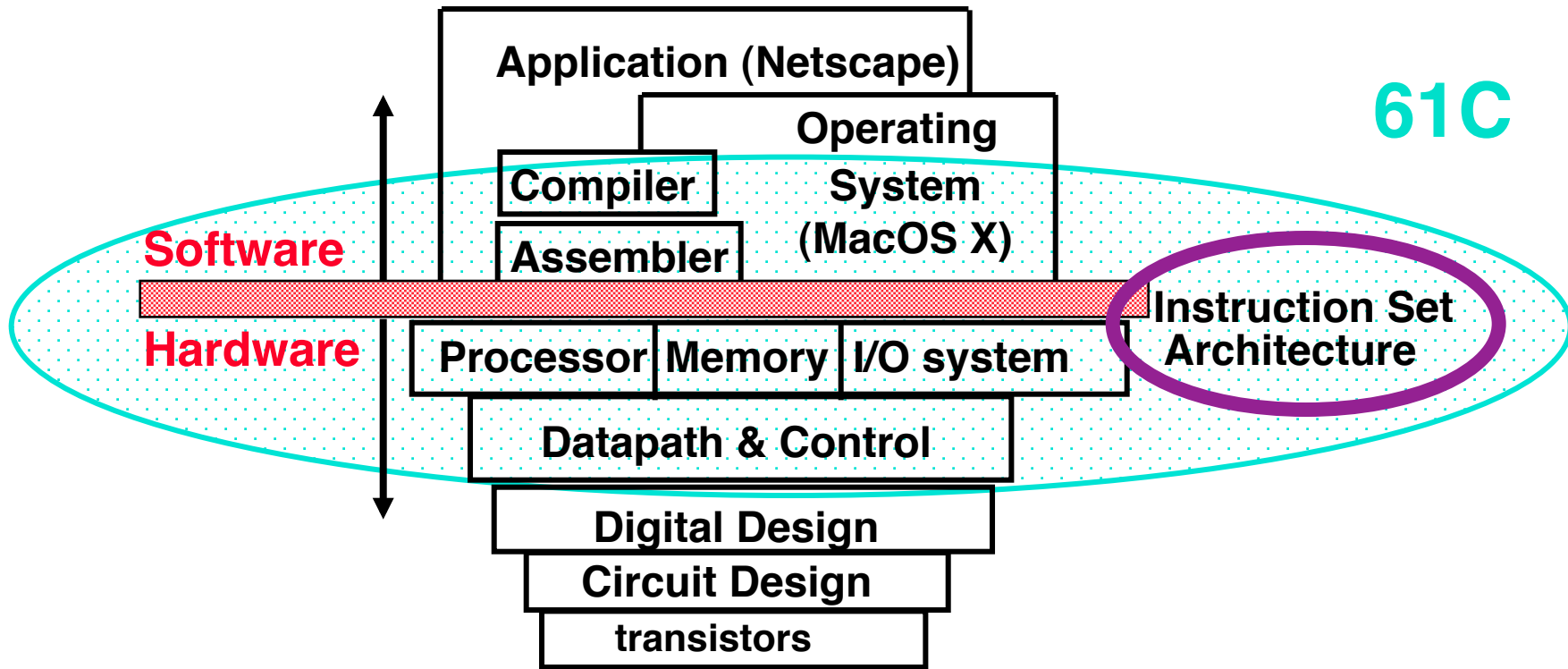

Coordination of many *levels of abstraction*


ISA is an important abstraction level:  
contract between HW & SW


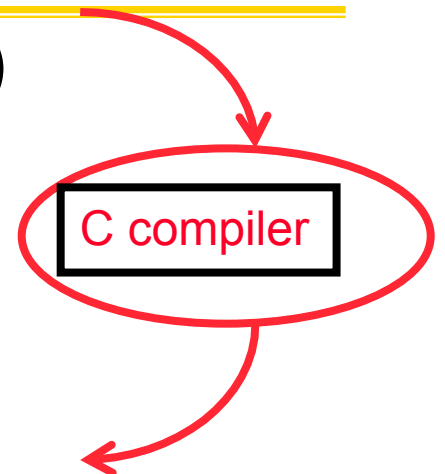
# Below the Program


- High-level language program (in C)

```
swap int v[], int k){  
    int temp;  
    temp = v[k];  
    v[k] = v[k+1];  
    v[k+1] = temp;  
}
```



- Assembly language program (for MIPS)
 
```
swap: sll    $2, $5, 2  
      add    $2, $4, $2  
      lw     $15, 0($2)  
      lw     $16, 4($2)  
      sw     $16, 0($2)  
      sw     $15, 4($2)  
      jr     $31
```



- Machine (object) code (for MIPS)

```
000000 00000 00101 000100000100000000  
000000 00100 00010 00010000000100000 . . .
```



# Synchronous Digital Systems

---

*The hardware of a processor, such as the MIPS, is an example of a Synchronous Digital System*

## Synchronous:

- Means all operations are coordinated by a central **clock**.
  - It keeps the “heartbeat” of the system!

## Digital:

- Mean all values are represented by discrete values
- Electrical signals are treated as 1's and 0's and grouped together to form words.



# Logic Design

---


- **Next 4 weeks: we'll study how a modern processor is built; starting with basic elements as building blocks.**
- **Why study hardware design?**
  - **Understand capabilities and limitations of hardware in general and processors in particular.**
  - **What processors can do fast and what they can't do fast (avoid slow things if you want your code to run fast!)**
  - **Background for more detailed hardware courses (CS 150, CS 152)**
  - **There is just so much you can do with processors. At some point you may need to design your own custom hardware.**



# PowerPC Die Photograph




Let's look closer...

 
 
# Transistors 101


- **MOSFET**

- Metal-Oxide-Semiconductor Field-Effect Transistor
- Come in two types:
  - n-type NMOSFET
  - p-type PMOSFET



- For **n-type** (**p-type** opposite)

 - If voltage not enough between G & S, transistor turns “off” (cut-off) and Drain-Source NOT connected
- If the G & S voltage is high enough, transistor turns “on” (saturation) and Drain-Source ARE connected




Side view




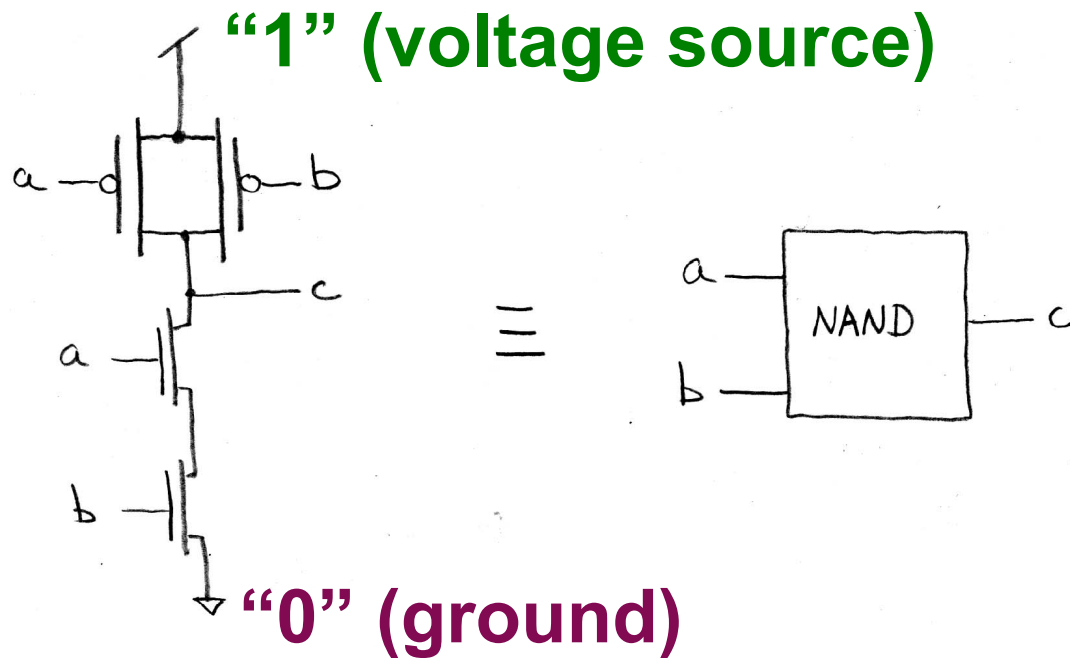
# Transistor Circuit Rep. vs. Block diagram


- Chips is composed of nothing but transistors and wires.
- Small groups of transistors form useful building blocks.



a	b	c
0	0	1
0	1	1
1	0	1
1	1	0

- Block are organized in a hierarchy to build higher-level blocks: ex: adders.



# Signals and Waveforms: Clocks

 


## • Signals

- When **digital** is only treated as 1 or 0
- Is transmitted over wires continuously
- Transmission is effectively instant
  - Implies that any wire only contains 1 value at a time


# Signals and Waveforms

  

# Signals and Waveforms: Grouping


 


# Signals and Waveforms: Circuit Delay

 

$$A = [a_3, a_2, a_1, a_0]$$

$$B = [b_3, b_2, b_1, b_0]$$

  

→ ← adder propagation delay



# Type of Circuits


---

- **Synchronous Digital Systems are made up of two basic types of circuits:**
- **Combinational Logic (CL) circuits**
  - Our previous adder circuit is an example.
  - **Output is a function of the inputs only.**
  - Similar to a pure function in mathematics,  $y = f(x)$ . (No way to store information from one invocation to the next. No side effects)
- **State Elements: circuits that store information.**



# Circuits with STATE (e.g., register)

---

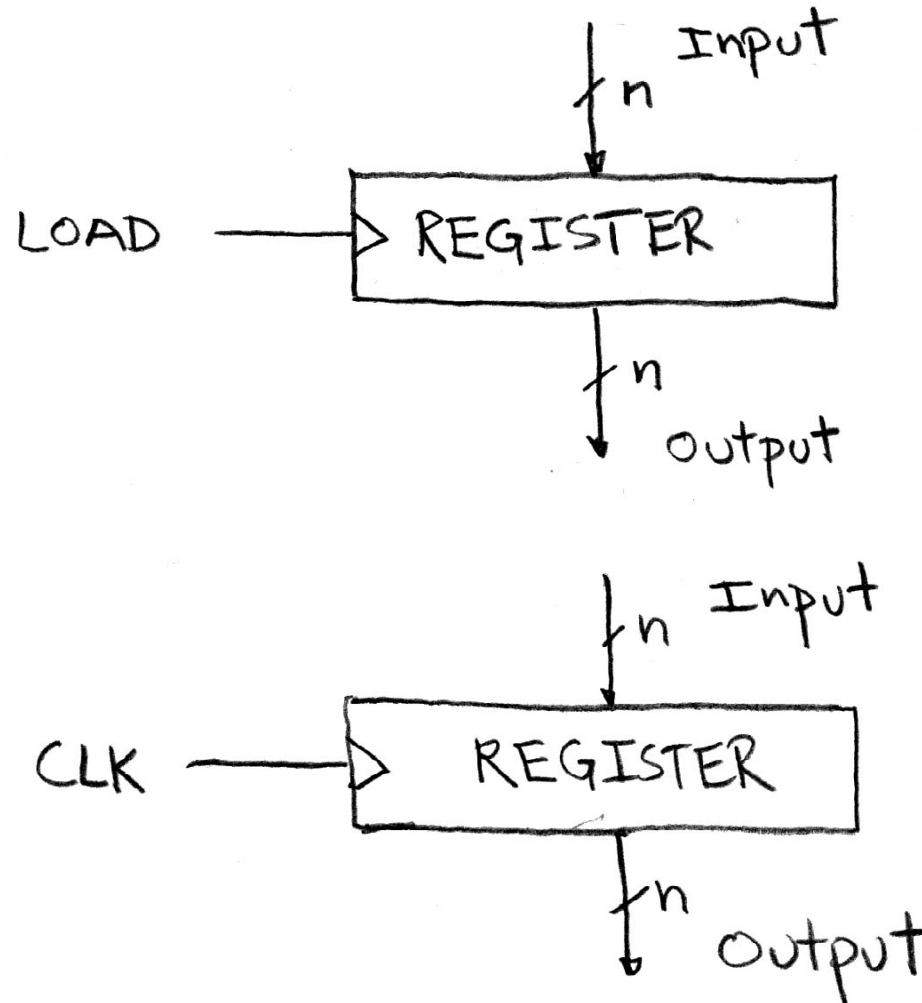

# Peer Instruction

---

- 1) SW **can peek** at HW (past ISA abstraction boundary) for optimizations
- 2) SW **can depend** on particular HW implementation of ISA

	12
a)	<b>FF</b>
b)	<b>FT</b>
c)	<b>TF</b>
d)	<b>TT</b>





## And in conclusion...

---

- **ISA is very important abstraction layer**
  - **Contract between HW and SW**
- **Clocks control pulse of our circuits**
- **Voltages are analog, quantized to 0/1**
- **Circuit delays are fact of life**
- **Two types of circuits:**
  - **Stateless Combinational Logic (&,!,~)**
  - **State circuits (e.g., registers)**



# Sample Debugging Waveform

