

CS 61C:  
Great Ideas in Computer Architecture  
*MIPS Datapath*


Instructors:

Nicholas Weaver & Vladimir Stojanovic

<http://inst.eecs.Berkeley.edu/~cs61c/sp16>
 
# Arithmetic and Logic Unit

- Most processors contain a special logic block called the “Arithmetic and Logic Unit” (ALU)
- We’ ll show you an easy one that does ADD, SUB, bitwise AND, bitwise OR




when  $S=00$ ,  $R=A+B$

when  $S=01$ ,  $R=A-B$

when  $S=10$ ,  $R=A \text{ AND } B$

when  $S=11$ ,  $R=A \text{ OR } B$

# Our simple ALU

 

# How to design Adder/Subtractor?

- Truth-table, then determine canonical form, then minimize and implement as we've seen before
- Look at breaking the problem down into smaller pieces that we can cascade or hierarchically layer

# Adder/Subtractor – One-bit adder LSB... (Half Adder)

	$a_3$	$a_2$	$a_1$	$a_0$
+	$b_3$	$b_2$	$b_1$	$b_0$
	$s_3$	$s_2$	$s_1$	$s_0$

$a_0$	$b_0$	$s_0$	$c_1$
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$


# Adder/Subtractor – One-bit full-adder (1/2)...

				$a_i$	$b_i$	$c_i$	$S_i$	$C_{i+1}$
				0	0	0	0	0
				0	0	1	1	0
				0	1	0	1	0
+	$a_3$	$a_2$	$a_1$	$a_0$	0	1	0	1
	$b_3$	$b_2$	$b_1$	$b_0$	0	1	1	0
	$s_3$	$s_2$	$s_1$	$s_0$	1	0	0	1
				1	0	0	1	0
				1	0	1	0	1
				1	1	0	0	1
				1	1	1	1	1

$$S_i =$$


$$C_{i+1} =$$

# Adder/Subtractor – One-bit adder (2/2)

 

$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$
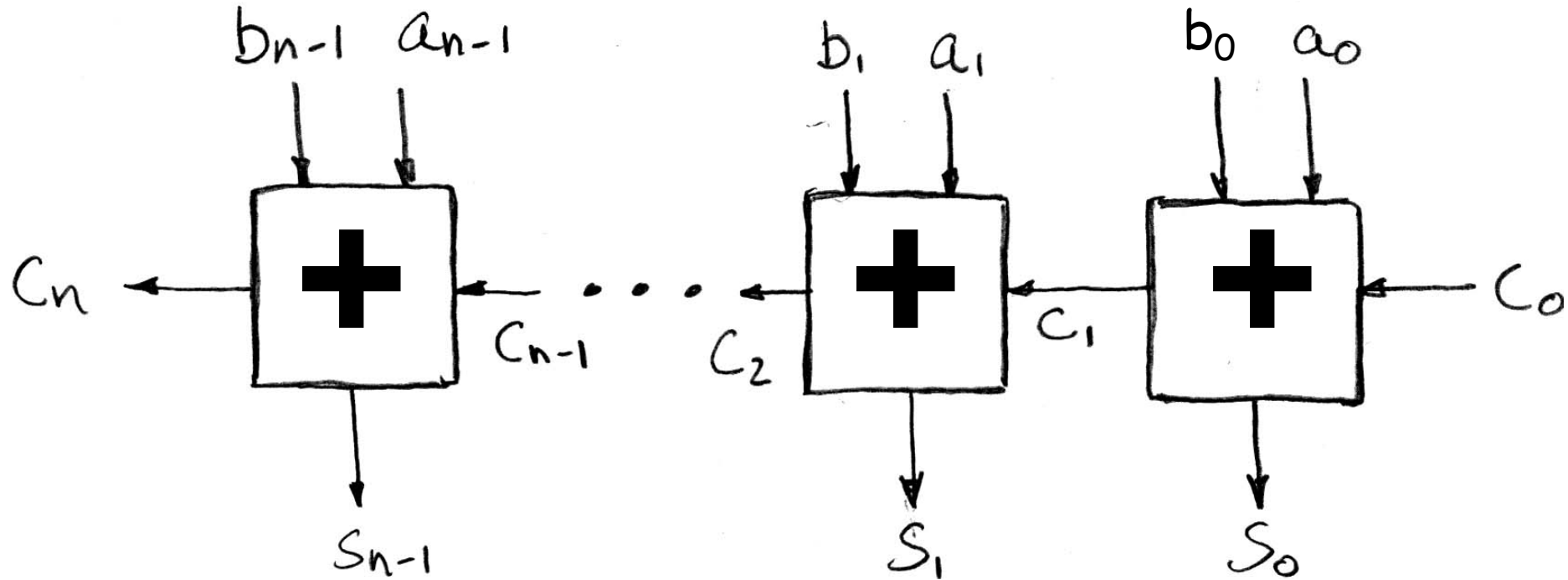
# N 1-bit adders $\Rightarrow$ 1 N-bit adder




**What about overflow?**

**Overflow =  $c_n$ ?**



# Extremely Clever Adder/Subtractor

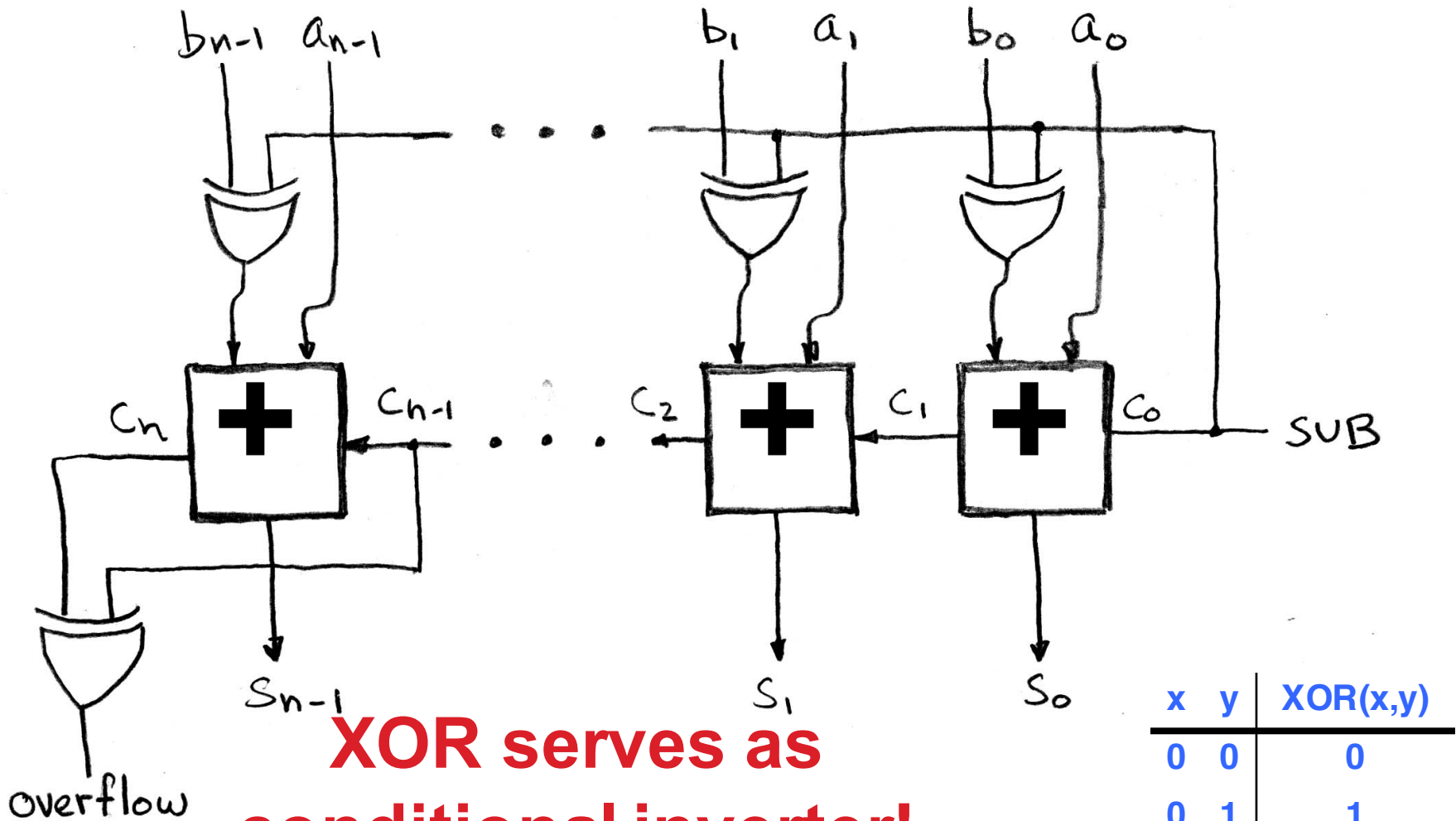

**XOR serves as  
conditional inverter!**

**Aka "Subtract is Invert and add 1"**

x	y	XOR(x,y)
0	0	0
0	1	1
1	0	1
1	1	0

# Clicker Question

Convert the truth table to a boolean expression  
(no need to simplify):

A:  $F = xy + x(\sim y)$

B:  $F = xy + (\sim x)y + (\sim x)(\sim y)$

C:  $F = (\sim x)y + x(\sim y)$

D:  $F = xy + (\sim x)y$


E:  $F = (x+y)(\sim x+\sim y)$

x	y	F(x,y)
0	0	0
0	1	1
1	0	0
1	1	1

# Administrivia

- Project 2-2 is out!

# Components of a Computer

 


# The CPU

- Processor (CPU): the active part of the computer that does all the work (data manipulation and decision-making)
- Datapath: portion of the processor that contains hardware necessary to perform operations required by the processor (the brawn)
- Control: portion of the processor (also in hardware) that tells the datapath what needs to be done (the brain)
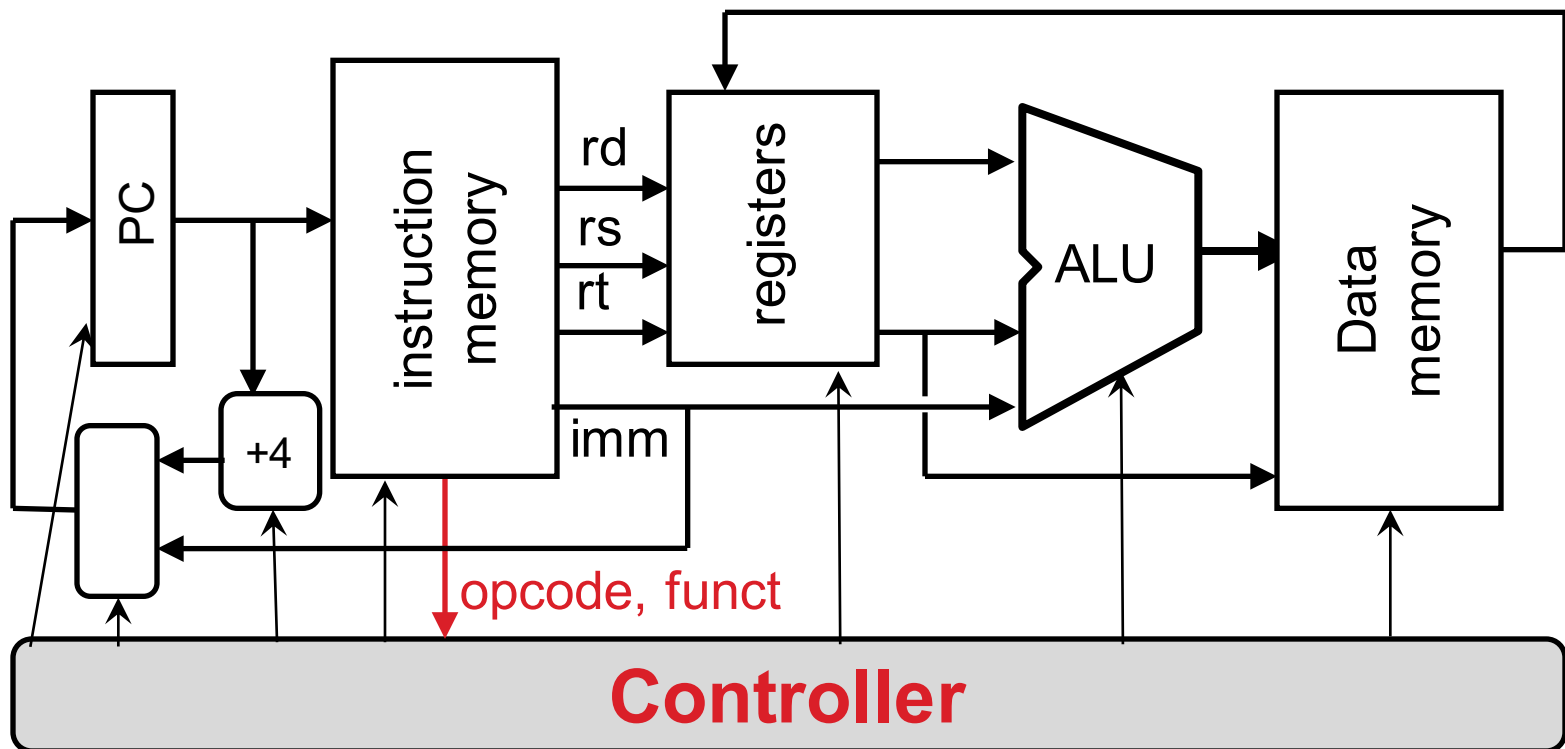
# Datapath and Control


- Datapath designed to support data transfers required by instructions
- Controller causes correct transfers to happen



# Five Stages of Instruction Execution

- Stage 1: Instruction Fetch
- Stage 2: Instruction Decode
- Stage 3: ALU (Arithmetic-Logic Unit)
- Stage 4: Memory Access
- Stage 5: Register Write

# Stages of Execution on Datapath

 



# Stages of Execution (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- Stage 1: Instruction Fetch
  - no matter what the instruction, the 32-bit instruction word must first be fetched from memory (the cache-memory hierarchy)
  - also, this is where we Increment PC (that is,  $PC = PC + 4$ , to point to the next instruction: byte addressing so + 4)

# Stages of Execution (2/5)

- Stage 2: Instruction Decode
  - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
  - first, read the opcode to determine instruction type and field lengths
  - second, read in data from all necessary registers
    - for add, read two registers
    - for addi, read one register
    - for jal, no reads necessary

# Stages of Execution (3/5)

- Stage 3: ALU (Arithmetic-Logic Unit)
  - the real work of most instructions is done here: arithmetic (+, -, \*, /), shifting, logic (&, |), comparisons (slt)
  - what about loads and stores?
    - lw \$t0, 40(\$t1)
    - the address we are accessing in memory = the value in \$t1 PLUS the value 40
    - so we do this addition in this stage


# Stages of Execution (4/5)

- Stage 4: Memory Access
  - actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
  - since these instructions have a unique step, we need this extra stage to account for them
  - as a result of the cache system, this stage is expected to be fast

# Stages of Execution (5/5)

- Stage 5: Register Write
  - most instructions write the result of some computation into a register
  - examples: arithmetic, logical, shifts, loads, slt
  - what about stores, branches, jumps?
    - don't write anything into a register at the end
    - these remain idle during this fifth stage or skip it all together


# Stages of Execution on Datapath

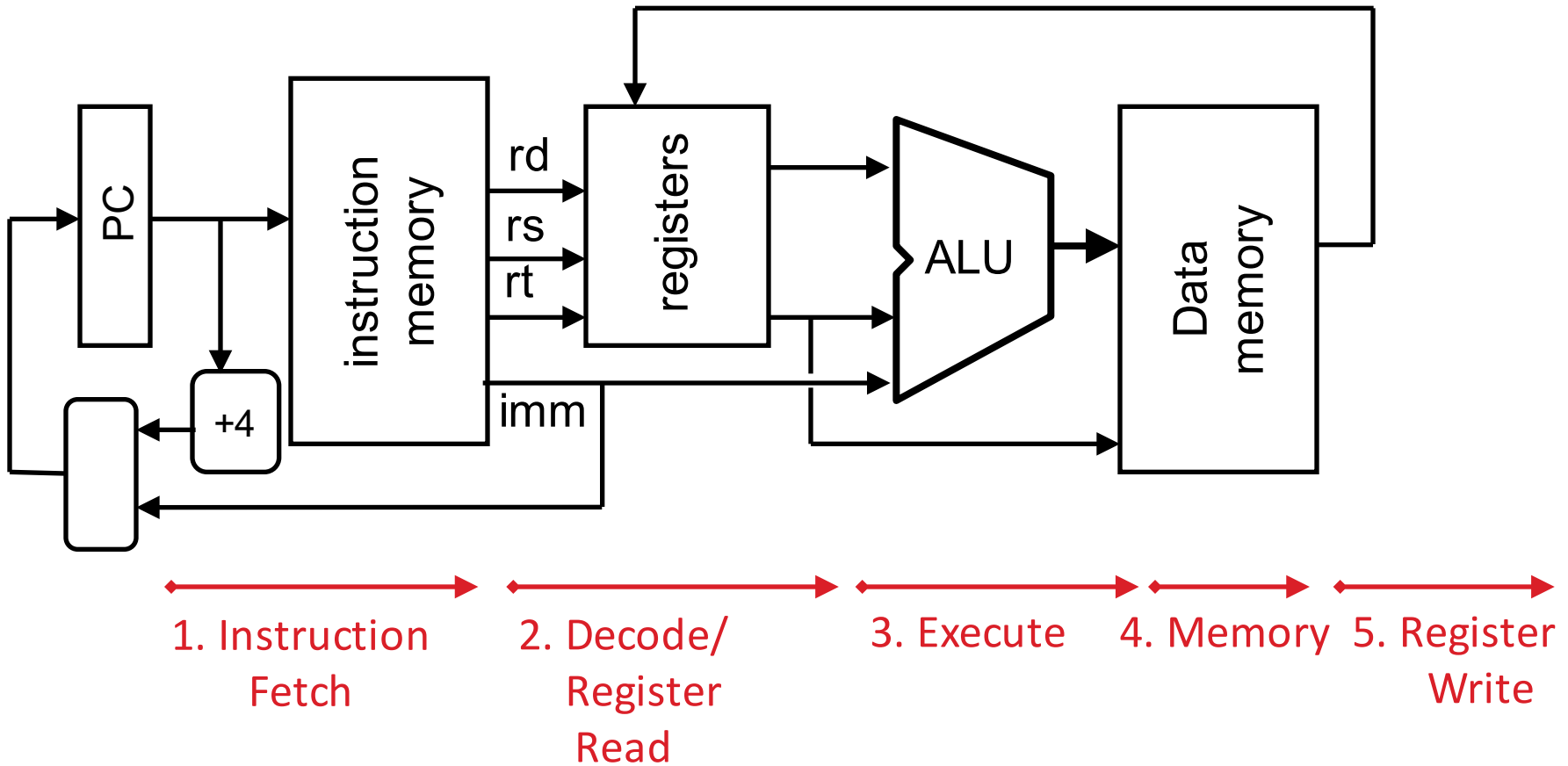

# Datapath Walkthroughs (1/3)

- add \$r3,\$r1,\$r2 # r3 = r1+r2
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an add, then read registers \$r1 and \$r2
  - Stage 3: add the two values retrieved in Stage 2
  - Stage 4: idle (nothing to write to memory)
  - Stage 5: write result of Stage 3 into register \$r3

# Example: add Instruction

 




# Datapath Walkthroughs (2/3)

- `slti $r3,$r1,17`  
# if (r1 <17 ) r3 = 1 else r3 = 0
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is an `slti`, then read register `$r1`
  - Stage 3: compare value retrieved in Stage 2 with the integer 17
  - Stage 4: idle
  - Stage 5: write the result of Stage 3 (1 if reg source was less than signed immediate, 0 otherwise) into register `$r3`


# Example: slti Instruction

 

# Datapath Walkthroughs (3/3)

- `sw $r3,16($r1) # Mem[r1+16]=r3`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a sw, then read registers \$r1 and \$r3
  - Stage 3: add 16 to value in register \$r1 (retrieved in Stage 2) to compute address
  - Stage 4: write value in register \$r3 (retrieved in Stage 2) into memory address computed in Stage 3
  - Stage 5: idle (nothing to write into a register)

# Example: sw Instruction

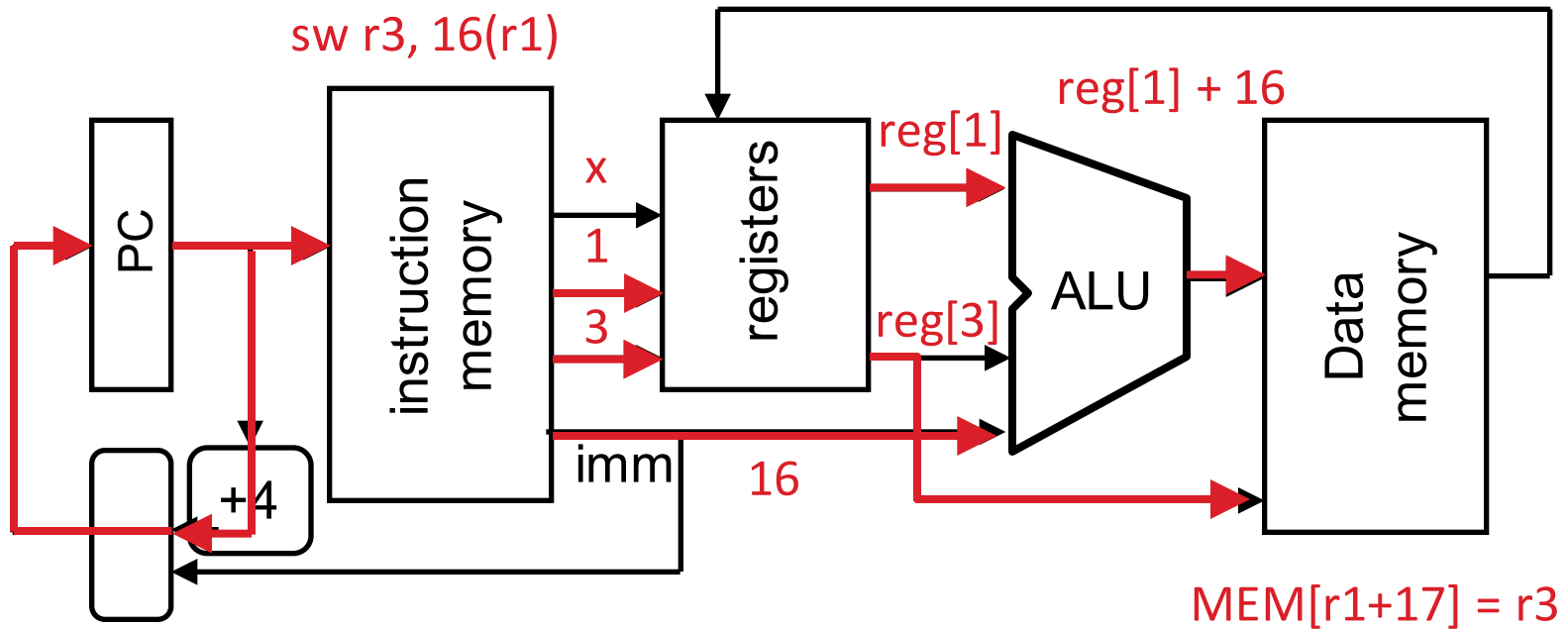


# Why Five Stages? (1/2)

- Could we have a different number of stages?
  - Yes, other ISAs have different natural number of stages
    - And these days, pipelining can be much more aggressive than the "natural" 5 stages MIPS uses
- Why does MIPS have five if instructions tend to idle for at least one stage?
  - Five stages are the union of all the operations needed by all the instructions.
  - One instruction uses all five stages: the load

# Why Five Stages? (2/2)

- `lw $r3,16($r1) # r3=Mem[r1+16]`
  - Stage 1: fetch this instruction, increment PC
  - Stage 2: decode to determine it is a `lw`, then read register `$r1`
  - Stage 3: add 16 to value in register `$r1` (retrieved in Stage 2)
  - Stage 4: read value from memory address computed in Stage 3
  - Stage 5: write value read in Stage 4 into register `$r3`

# Example: lw Instruction

 

# Clickers/Peer Instruction

- Which type of MIPS instruction is active in the fewest stages?

A: LW

B: BEQ

C: J

D: JAL

E: ADDU



# Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic
 
# The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:




- The different fields are:
  - **op**: operation (“opcode”) of the instruction
  - **rs, rt, rd**: the source and destination register specifiers
  - **shamt**: shift amount
  - **funct**: selects the variant of the operation in the “op” field
  - **address / immediate**: address offset or immediate value
  - **target address**: target address of jump instruction

# The MIPS-lite Subset

- ADDU and SUBU


- `addu rd,rs,rt`

- `subu rd,rs,rt`

 

- OR Immediate:

- `ori rt,rs,imm16`

 


- LOAD and

- STORE Word


- `lw rt,rs,imm16`

- `sw rt,rs,imm16`

 

- BRANCH:

- `beq rs,rt,imm16`

 

# Register Transfer Level (RTL)

- Colloquially called “Register Transfer Language”
- RTL gives the meaning of the instructions
- All start by fetching the instruction itself

```
{op , rs , rt , rd , shamt , funct} ← MEM[ PC ]
```

```
{op , rs , rt , Imm16} ← MEM[ PC ]
```

## Inst    Register Transfers

```
ADDU    R[rd] ← R[rs] + R[rt]; PC ← PC + 4
```

```
SUBU    R[rd] ← R[rs] - R[rt]; PC ← PC + 4
```

```
ORI     R[rt] ← R[rs] | zero_ext(Imm16); PC ← PC + 4
```

```
LOAD    R[rt] ← MEM[ R[rs] + sign_ext(Imm16)]; PC ← PC + 4
```

```
STORE   MEM[ R[rs] + sign_ext(Imm16) ] ← R[rt]; PC ← PC + 4
```

```
BEQ     if ( R[rs] == R[rt] )  
          PC ← PC + 4 + {sign_ext(Imm16), 2'b00}  
          else PC ← PC + 4
```

# In Conclusion

- “Divide and Conquer” to build complex logic blocks from smaller simpler pieces (adder)
- Five stages of MIPS instruction execution
- Mapping instructions to datapath components
- Single long clock cycle per instruction