


CS 61C:  
Great Ideas in Computer Architecture  
Single-Cycle CPU  
*Datapath and Control II*

Instructors:

*Nicholas Weaver & Vladimir Stojanovic*



<http://inst.eecs.Berkeley.edu/~cs61c/sp16>

# Clocking Methodology

 



- Storage elements clocked by same edge
- Flip-flops (FFs) and combinational logic have some delays
  - Gates: delay from input change to output change
  - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period
 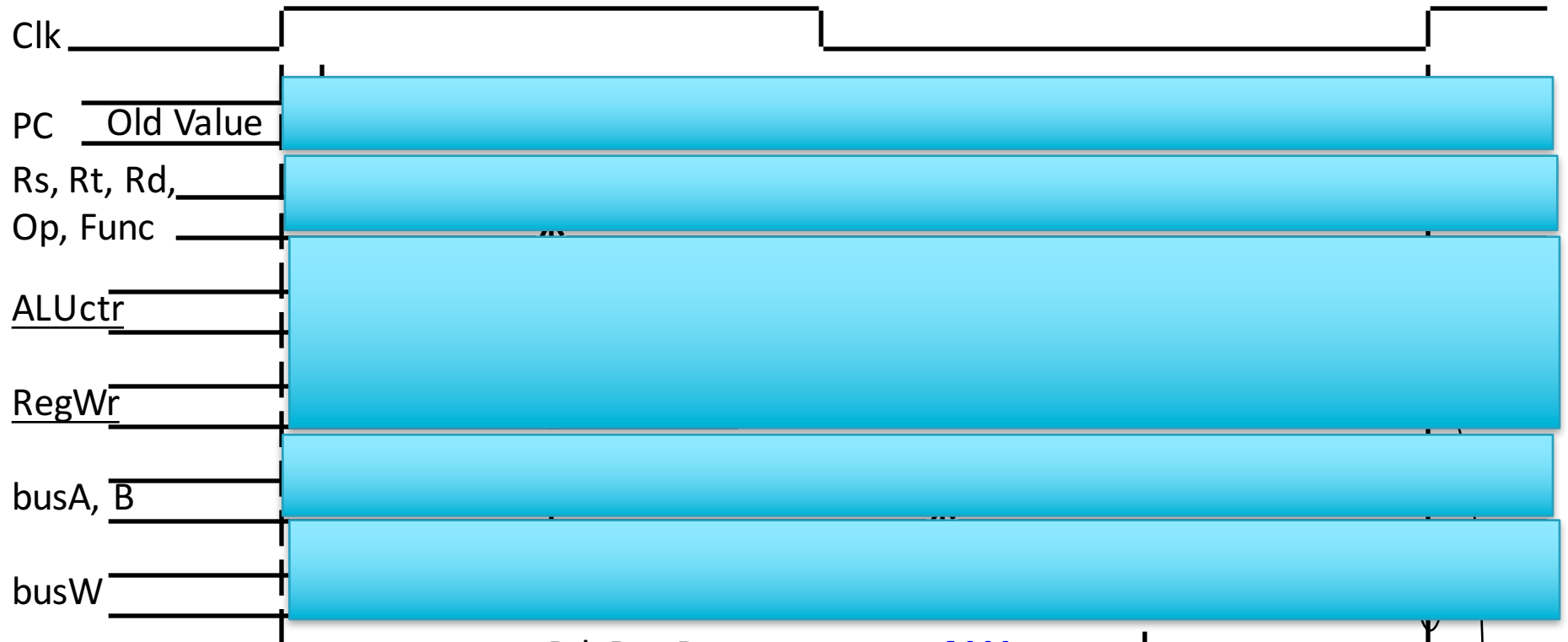
# Register-Register Timing: One Complete Cycle (Add/Sub)



Register Write  
Occurs Here

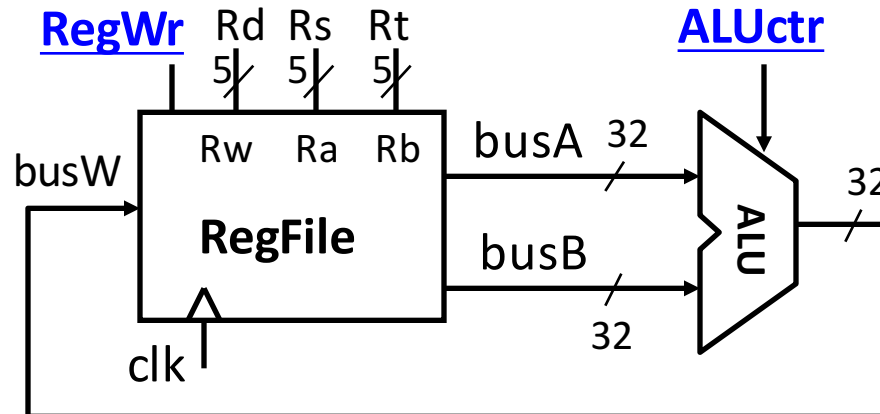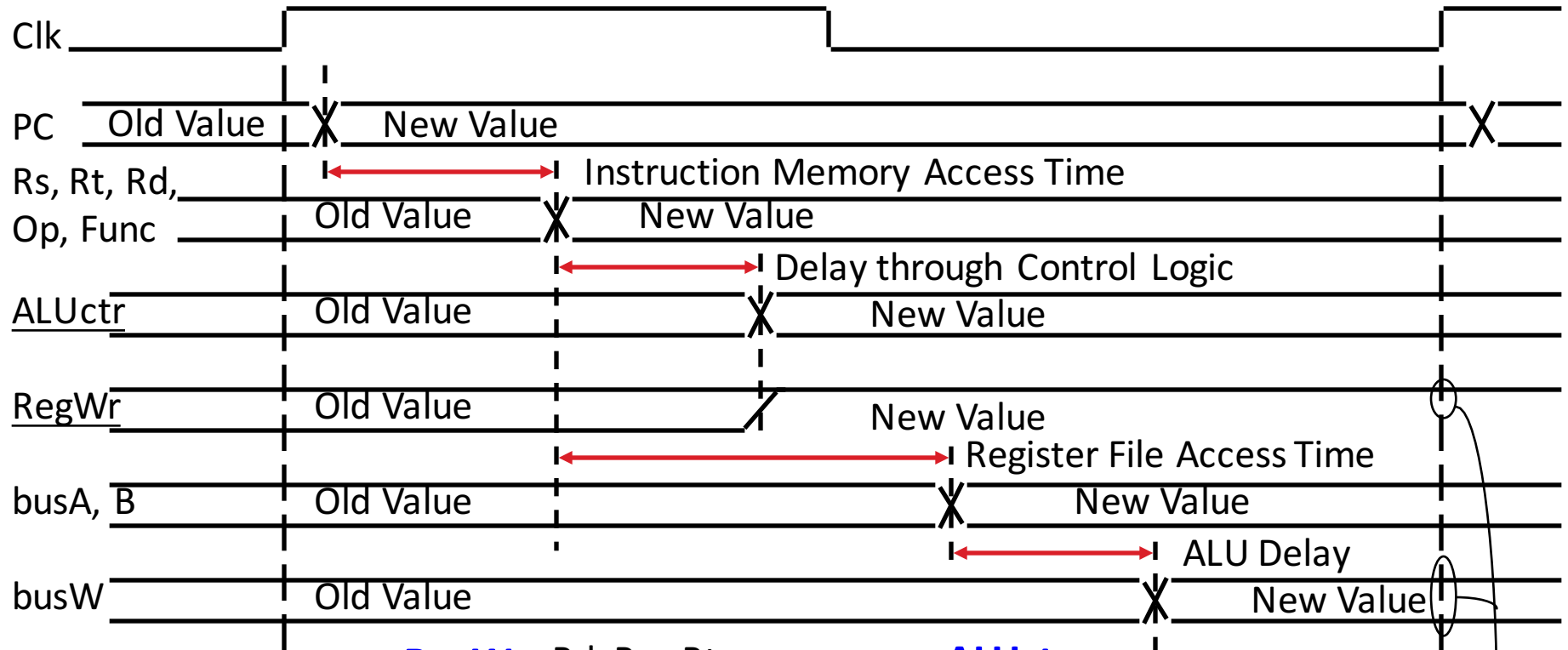
# Register-Register Timing: One Complete Cycle (Add/Sub)



Register Write Occurs Here

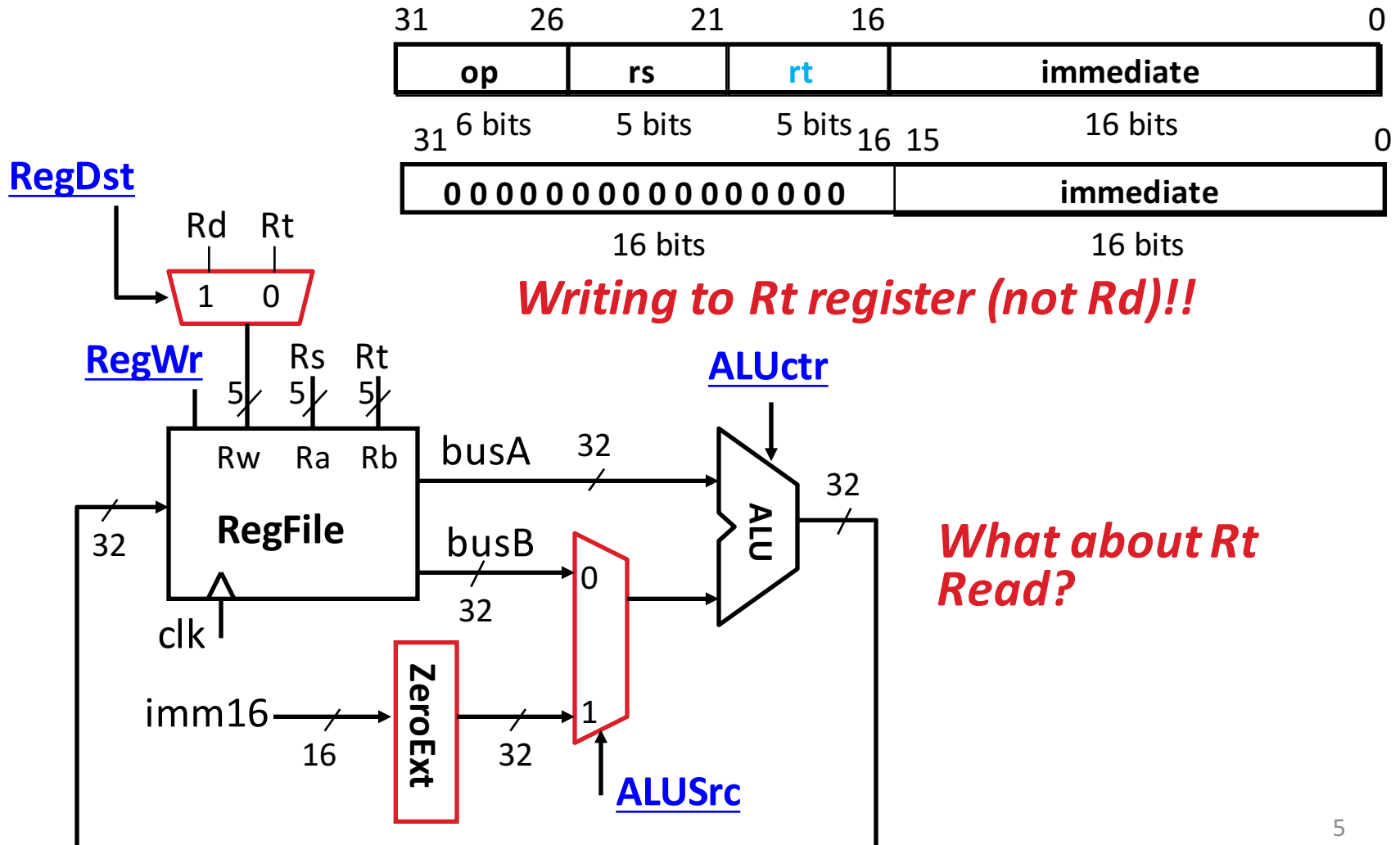
# 3c: Logical Op (or) with Immediate

- $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$


 
# 3d: Load Operations



- $R[rt] = Mem[R[rs] + SignExt[imm16]]$   
Example: `lw rt, rs, imm16`



# 3e: Store Operations

- $\text{Mem}[ R[\text{rs}] + \text{SignExt}[\text{imm16}] ] = R[\text{rt}]$



Ex.: `sw rt, rs, imm16`

  

# 3e: Store Operations


- $\text{Mem}[ R[\text{rs}] + \text{SignExt}[\text{imm16}] ] = R[\text{rt}]$

Ex.: `sw rt, rs, imm16`

  



# 3f: The Branch Instruction

 

`beq rs, rt, imm16`


- `mem[PC]` Fetch the instruction from memory
- Equal =  $(R[rs] == R[rt])$  Calculate branch condition
- if (Equal) Calculate the next instruction's address
  - $PC = PC + 4 + (\text{SignExt}(\text{imm16}) \times 4)$

else

- $PC = PC + 4$


# Datapath for Branch Operations

beq rs, rt, imm16

 


Datapath generates condition (Equal)


Inst Address

 
 
# Instruction Fetch Unit including Branch



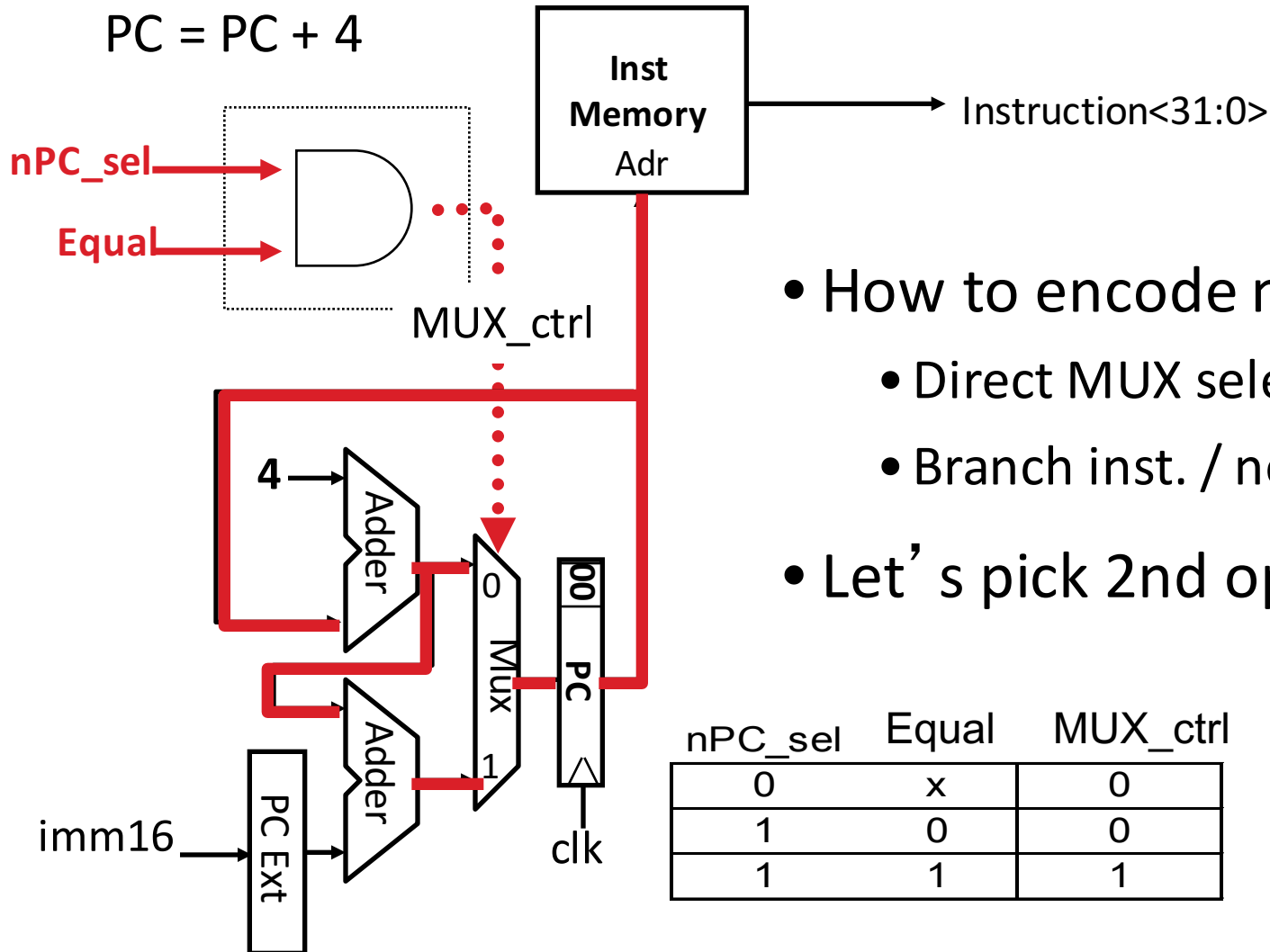- if (Equal == 1) then  $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$  ; else  $PC = PC + 4$




- How to encode nPC\_sel?
  - Direct MUX select?
  - Branch inst. / not branch inst.
- Let's pick 2nd option

nPC_sel	Equal	MUX_ctrl
0	x	0
1	0	0
1	1	1

Q: What logic gate?



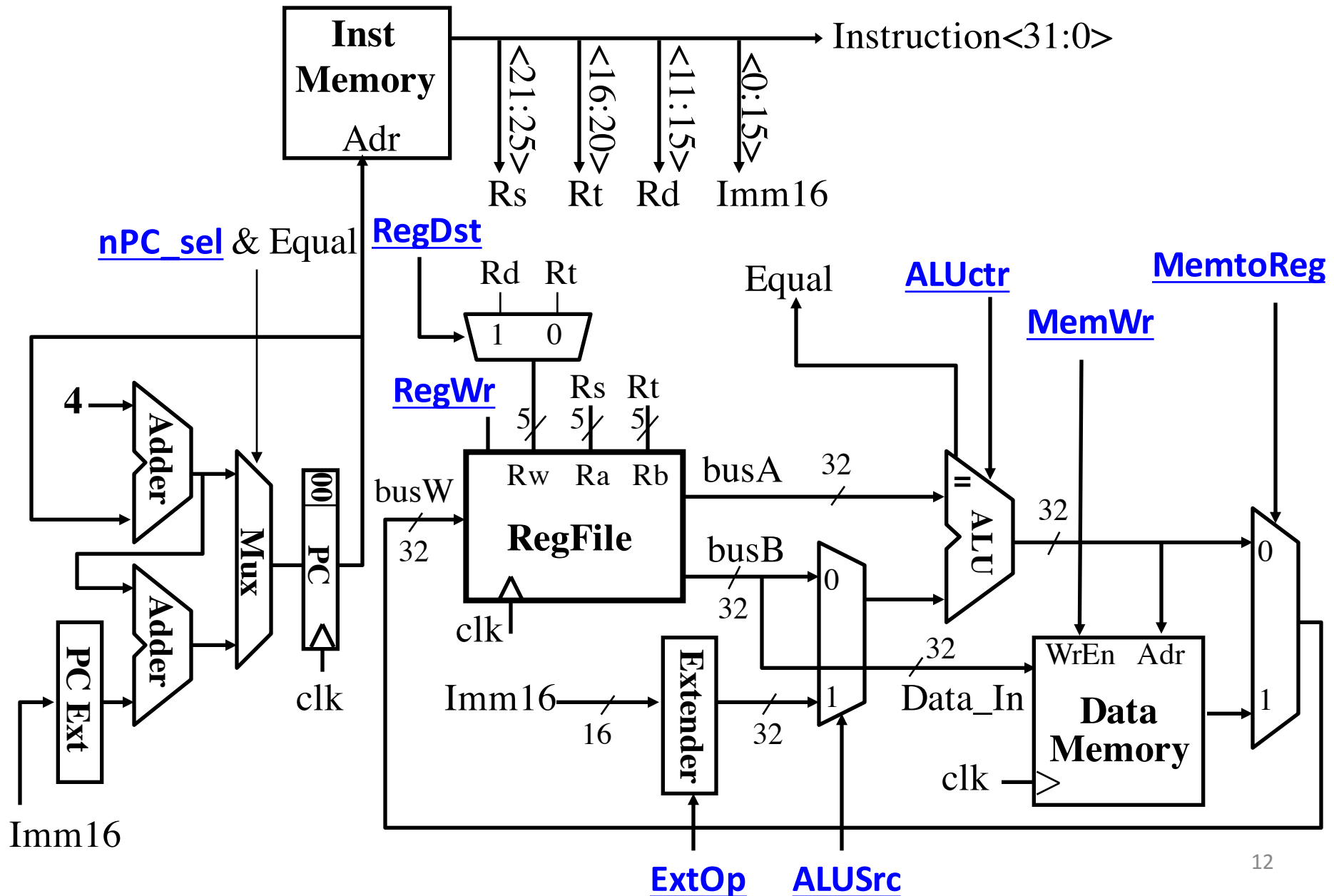
# Putting it All Together: A Single Cycle Datapath


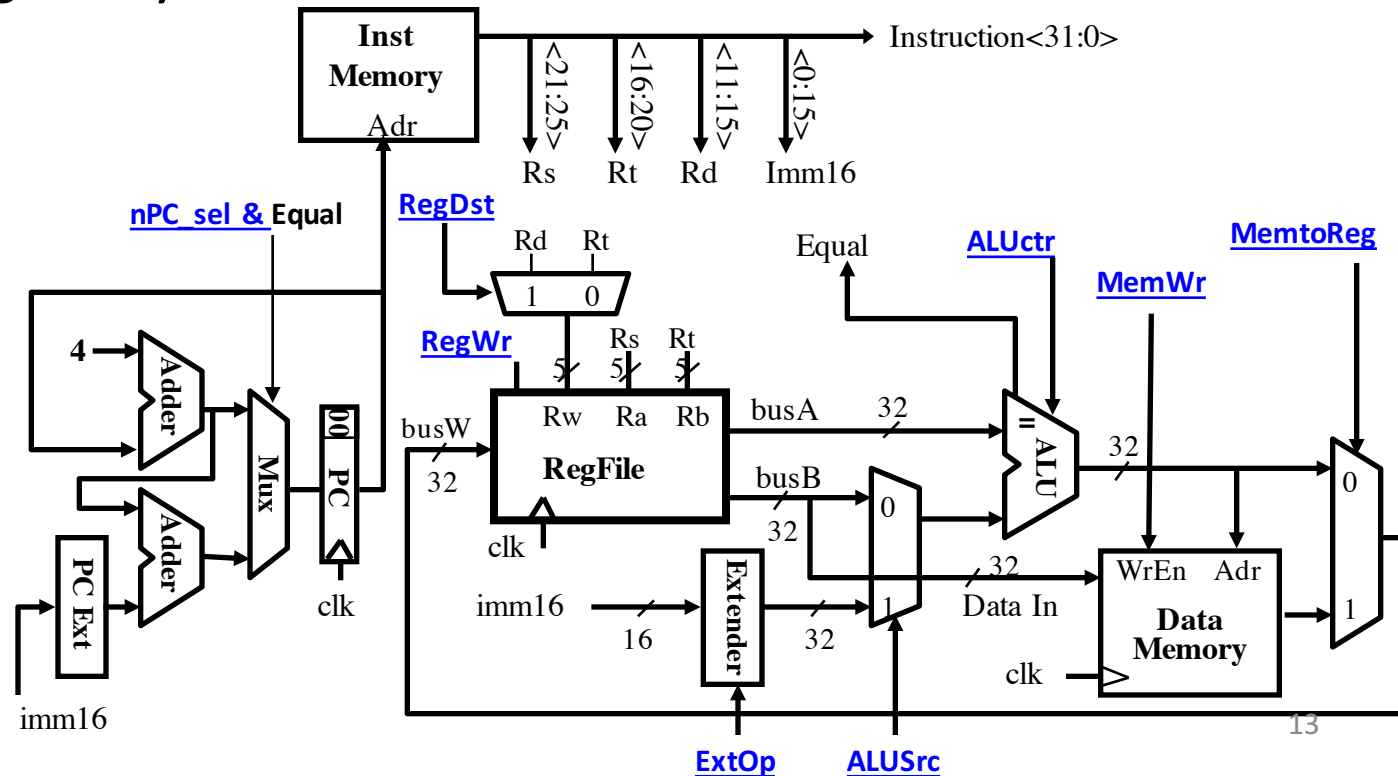
# Clickers/Peer Instruction

What new instruction would need no new datapath hardware?

- A: branch if reg==immediate
- B: add two registers and branch if result zero
- C: store with auto-increment of base address:
  - sw rt, rs, offset // rs incremented by offset after store
- D: shift left logical by two bits



# Administrivia

- Project 2-2 released, due 3/08 (a Tuesday!)
- Guerrilla Session:
  - Synchronous Digital Systems
  - Sat 3/05 1 - 3 PM @ 521 Cory

# Processor Design: 5 steps

Step 1: Analyze instruction set to determine datapath requirements

- Meaning of each instruction is given by register transfers
- Datapath must include storage element for ISA registers
- Datapath must support each register transfer

Step 2: Select set of datapath components & establish clock methodology


Step 3: Assemble datapath components that meet the requirements

Step 4: Analyze implementation of each instruction to determine setting of control points that realizes the register transfer

Step 5: Assemble the control logic

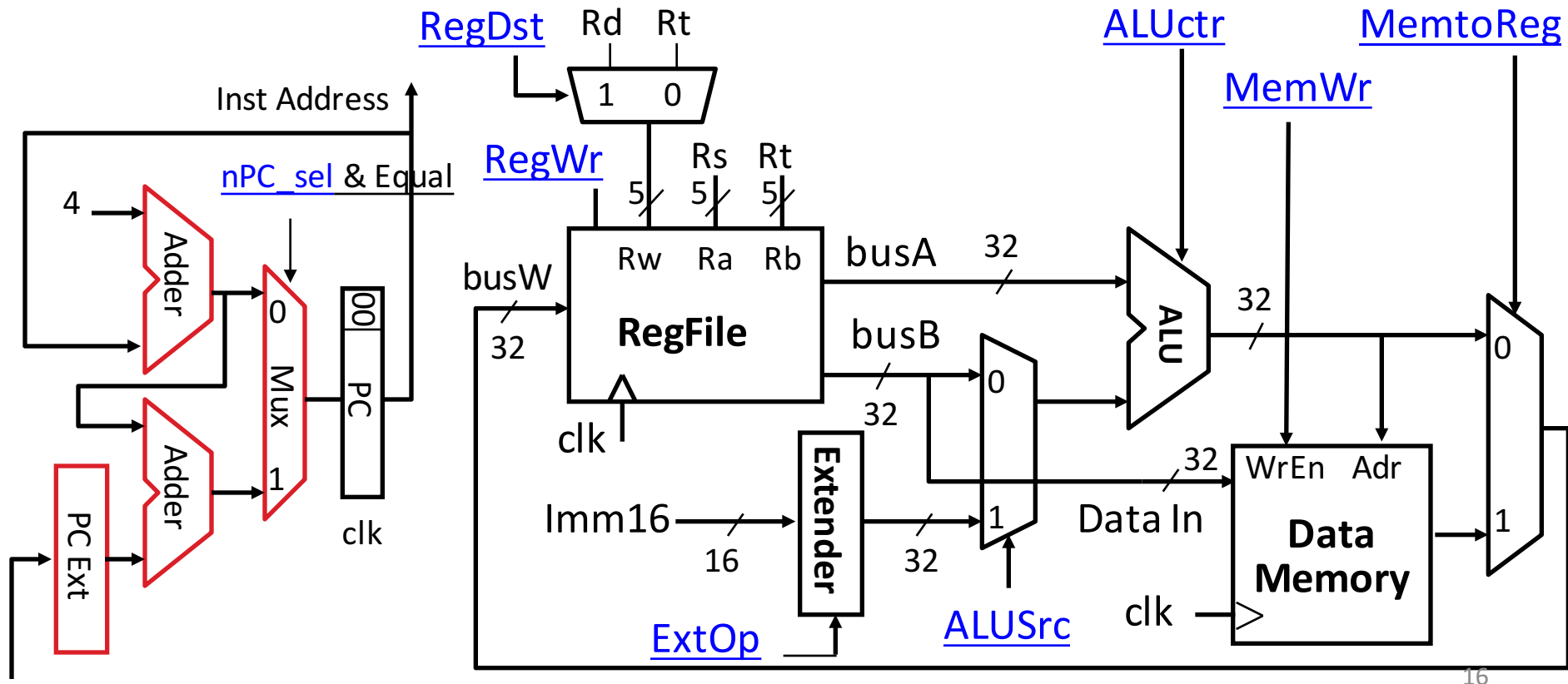
# Datapath Control Signals

- ExtOp: “zero”, “sign”
- ALUsrc: 0  $\Rightarrow$  regB; 1  $\Rightarrow$  immed
- ALUctr: “ADD”, “SUB”, “OR”
- MemWr: 1  $\Rightarrow$  write memory
- MemtoReg: 0  $\Rightarrow$  ALU; 1  $\Rightarrow$  Mem
- RegDst: 0  $\Rightarrow$  “rt”; 1  $\Rightarrow$  “rd”
- RegWr: 1  $\Rightarrow$  write register





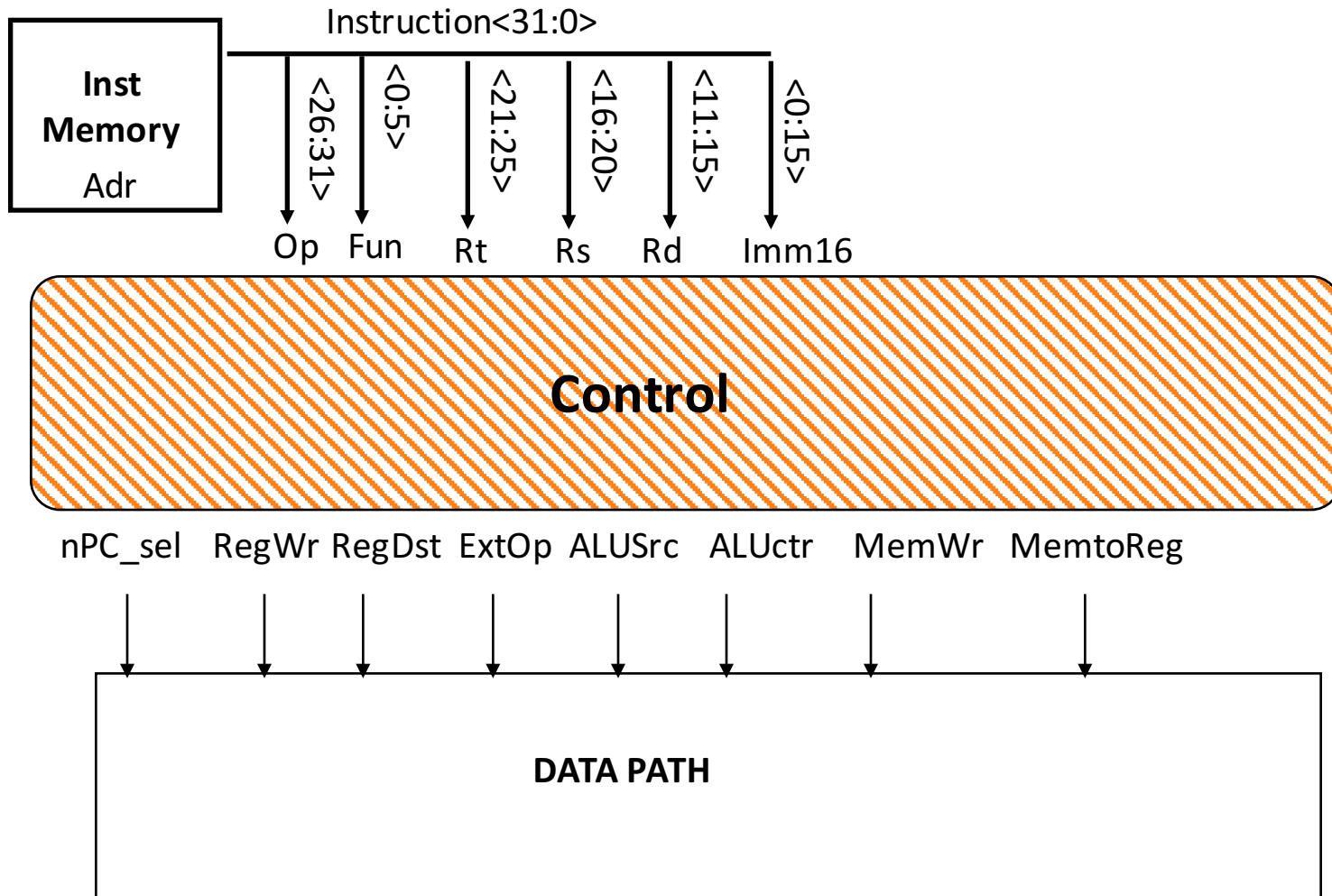
# Given Datapath: RTL $\rightarrow$ Control



# RTL: The Add Instruction

 


`add rd, rs, rt`

- $\text{MEM}[\text{PC}]$       Fetch the instruction from memory
- $\text{R}[\text{rd}] = \text{R}[\text{rs}] + \text{R}[\text{rt}]$       The actual operation
- $\text{PC} = \text{PC} + 4$       Calculate the next instruction's address


# Instruction Fetch Unit at the Beginning of Add

- Fetch the instruction from Instruction memory:  $\text{Instruction} = \text{MEM}[\text{PC}]$


– same for all instructions

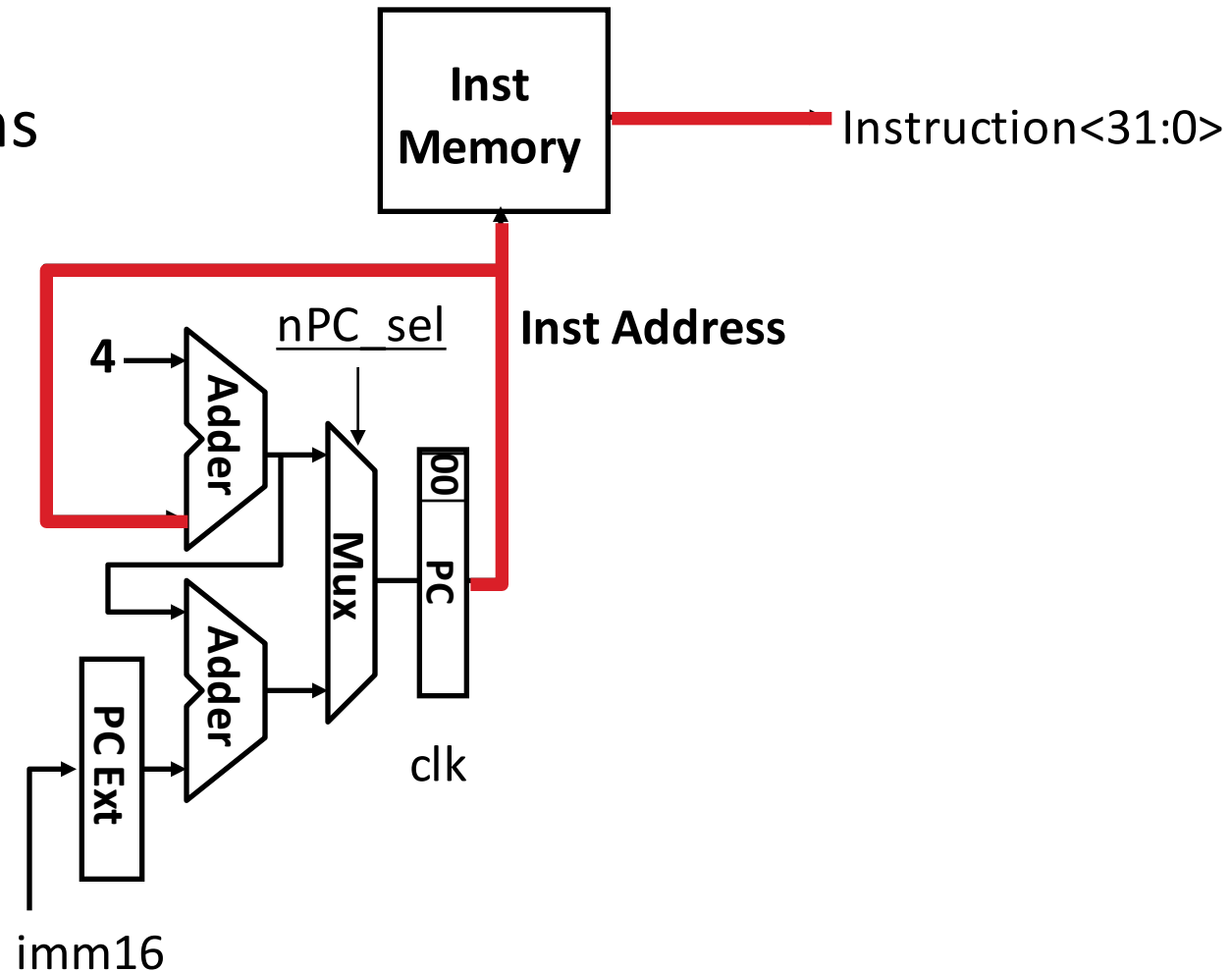

# Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

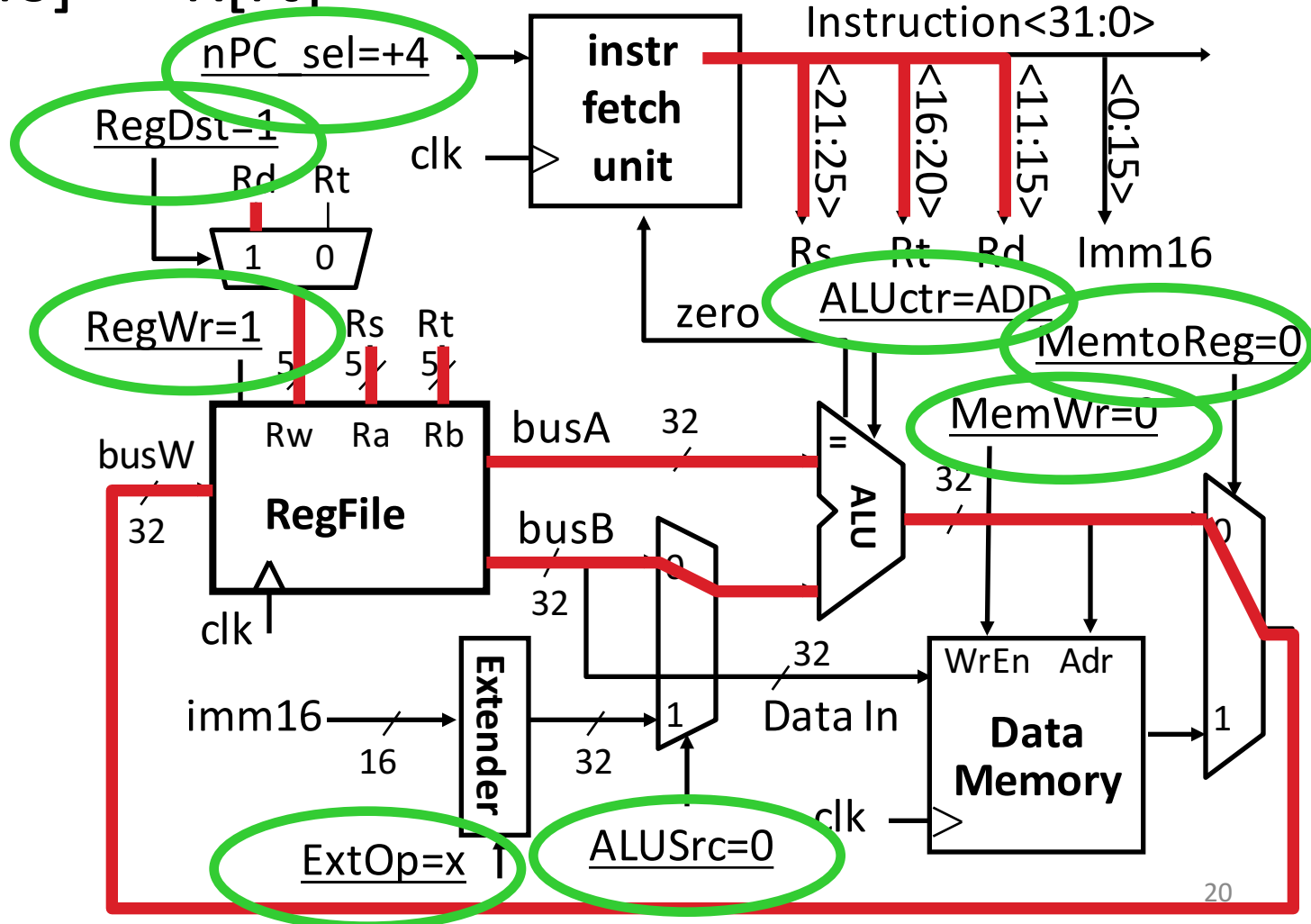
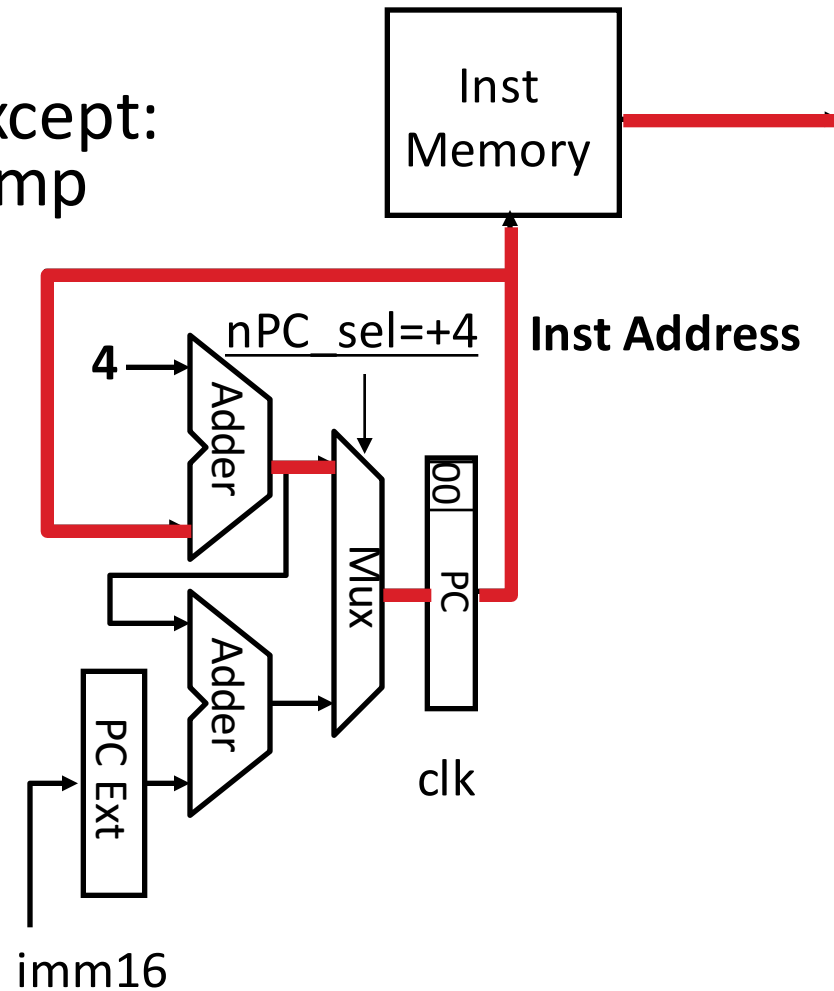
# Instruction Fetch Unit at End of Add


- $PC = PC + 4$ 
  - Same for all instructions except: Branch and Jump


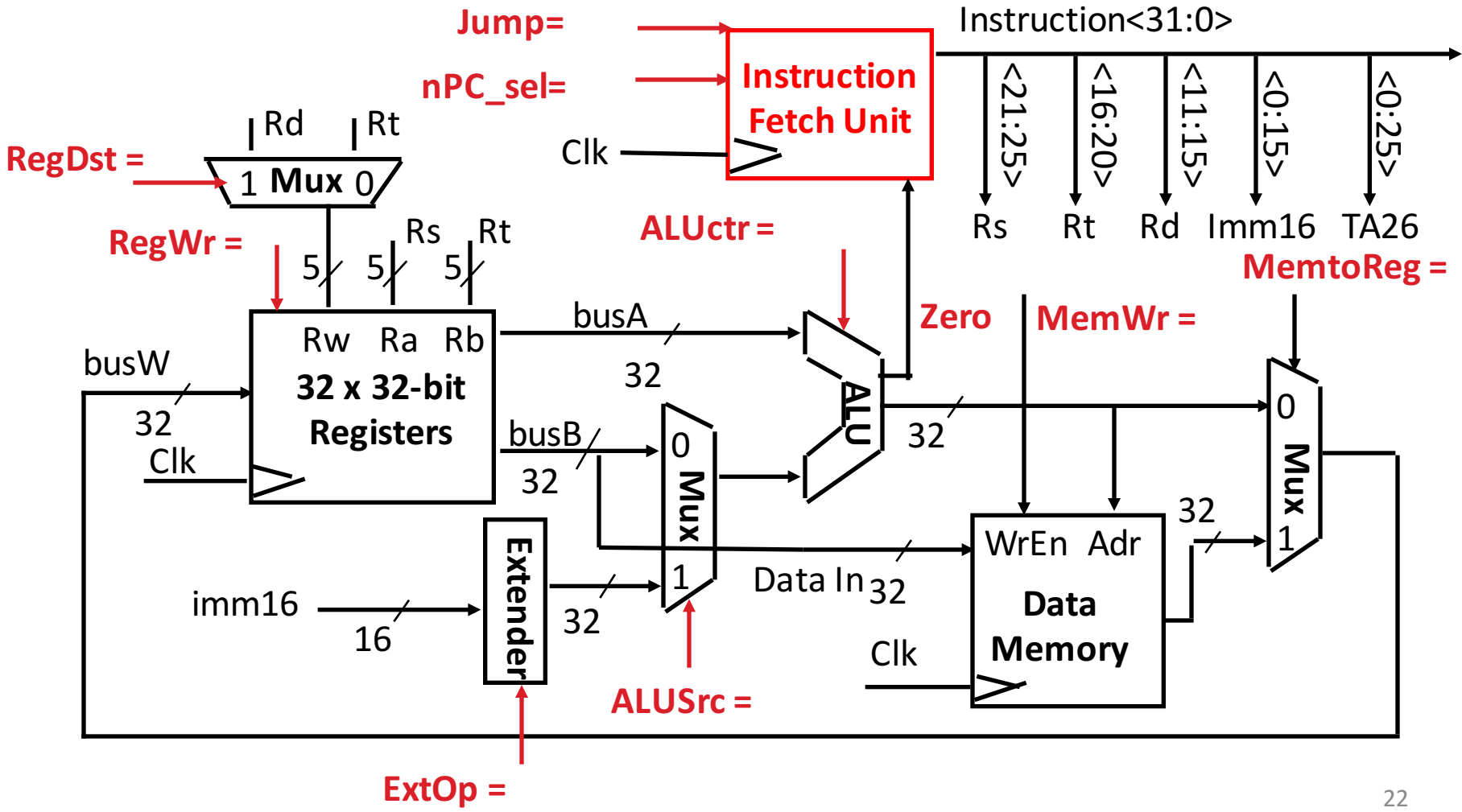
# Single Cycle Datapath during Jump




- New PC = { PC[31..28], target address, 00 }


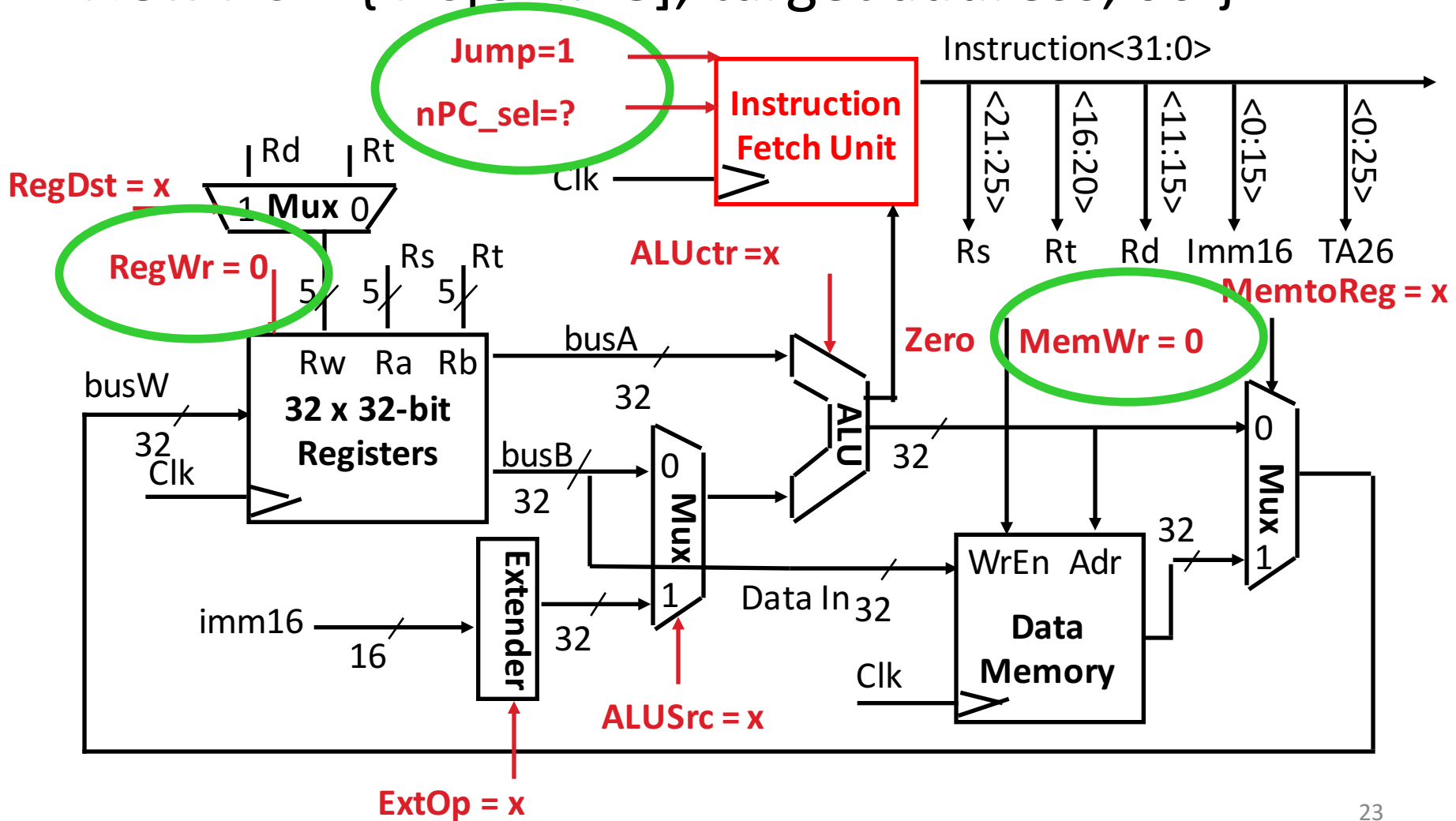
# Single Cycle Datapath during Jump




- New PC = { PC[31..28], target address, 00 }


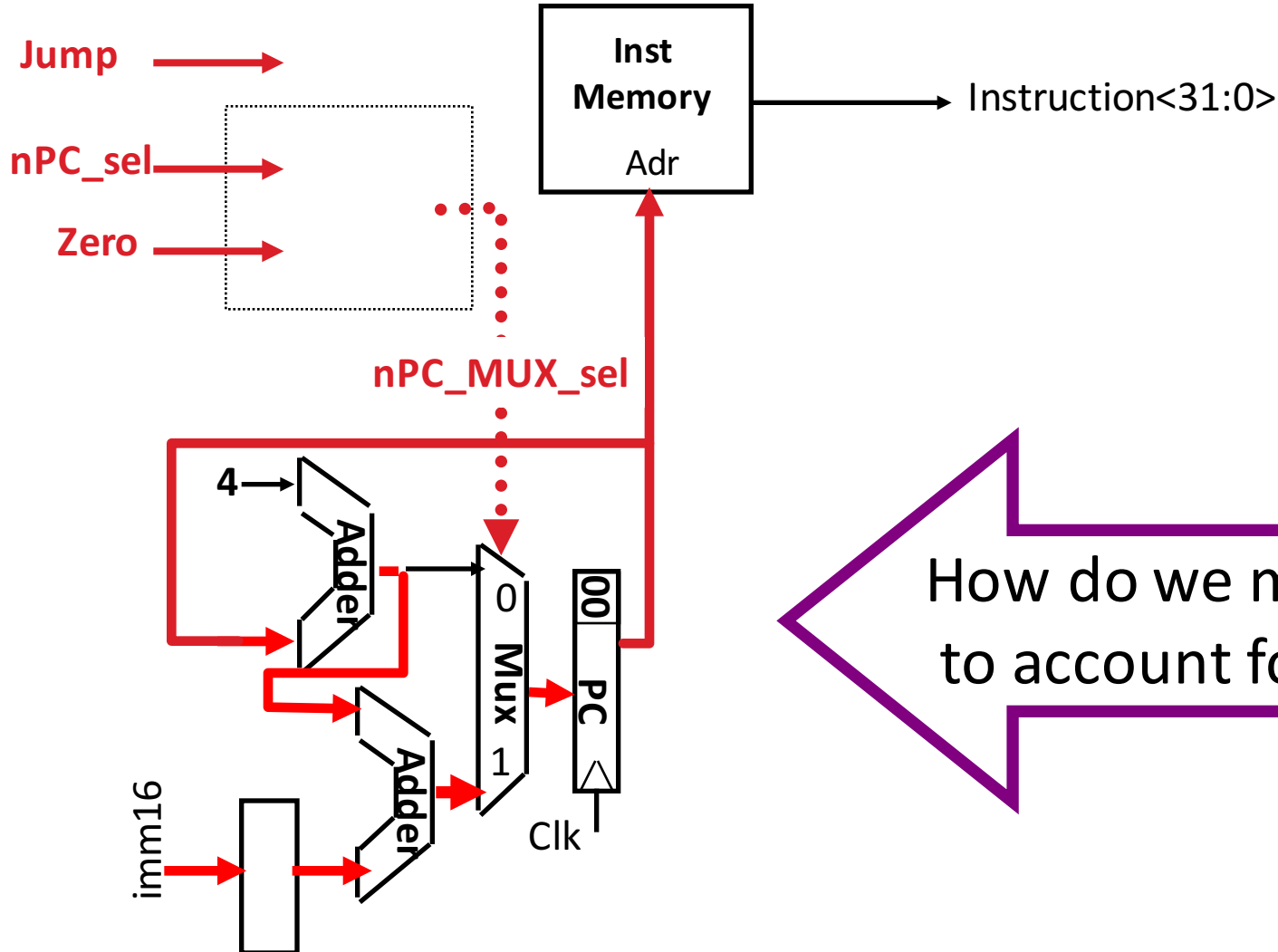
# Instruction Fetch Unit at the End of Jump



- New PC = { PC[31..28], target address, 00 }




How do we modify this to account for jumps?


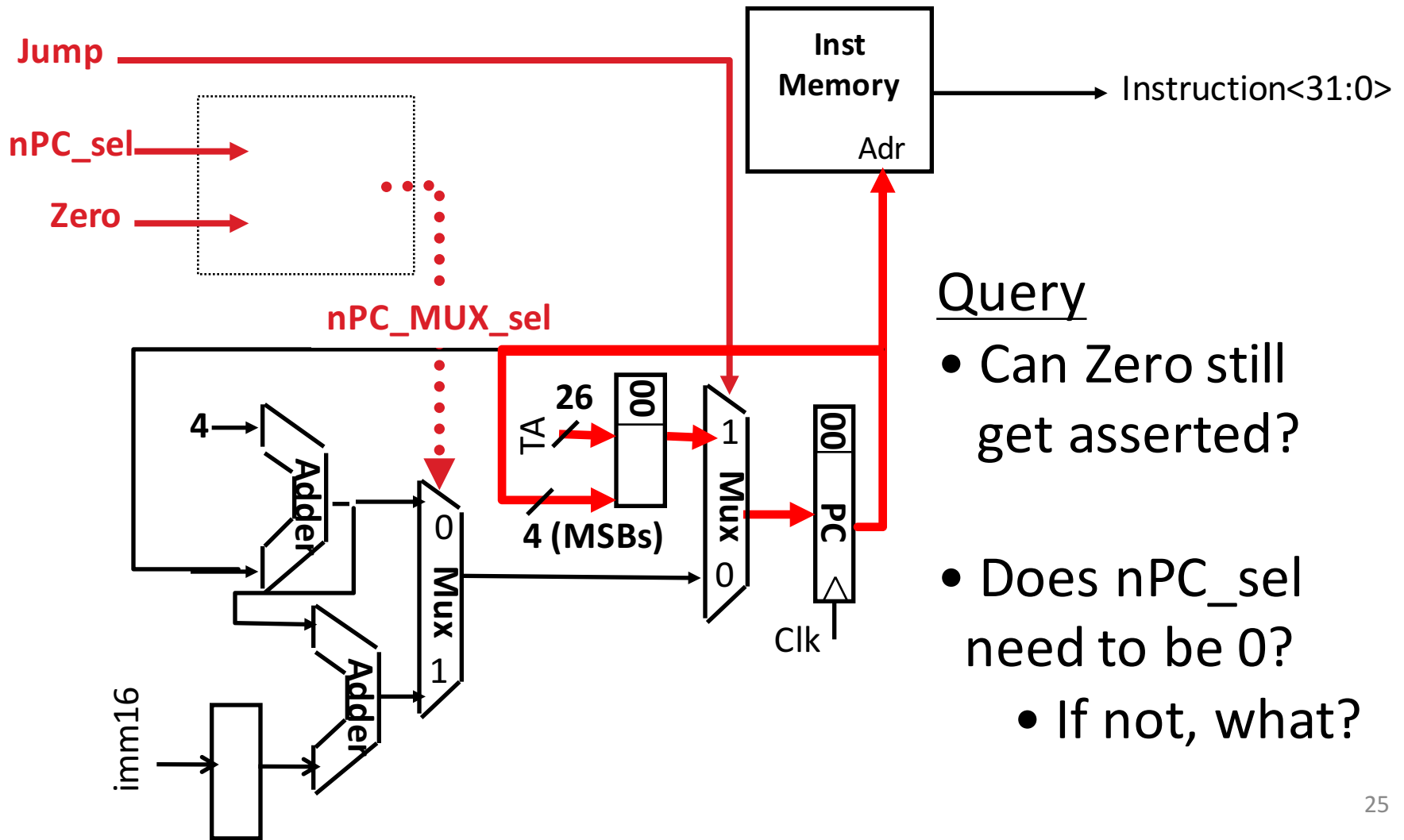
# Instruction Fetch Unit at the End of Jump



- New PC = { PC[31..28], target address, 00 }



## Query

- Can Zero still get asserted?
- Does nPC\_sel need to be 0?
  - If not, what?

# Clicker Question

Which of the following is TRUE?

- A. The clock can have a shorter period for instructions that don't use memory
- B. The ALU is used to set PC to PC+4 when necessary
- C. Worst-delay path in Instruction Fetch unit is Add+mux delay
- D. The CPU's control needs only *opcode* to determine the next PC value to select
- E. `npc_sel` affects the next PC address on a *jump*


# Summary of the Control Signals (1/2)

```
inst   Register Transfer
add     R[rd] ← R[rs] + R[rt]; PC ← PC + 4
        ALUSrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"
sub     R[rd] ← R[rs] - R[rt]; PC ← PC + 4
        ALUSrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"
ori     R[rt] ← R[rs] + zero_ext(Imm16); PC ← PC + 4
        ALUSrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"
lw      R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4
        ALUSrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,
        nPC_sel = "+4"
sw      MEM[ R[rs] + sign_ext(Imm16) ] ← R[rs]; PC ← PC + 4
        ALUSrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"
beq     if (R[rs] == R[rt]) then PC ← PC + sign_ext(Imm16) || 00
        else PC ← PC + 4
        nPC_sel = "br", ALUctr = "SUB"
```

# Summary of the Control Signals (2/2)

See Appendix A → **func**  
 See Appendix A → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	<b>add</b>	<b>sub</b>	<b>ori</b>	<b>lw</b>	<b>sw</b>	<b>beq</b>	<b>jump</b>
<b>RegDst</b>	1	1	0	0	x	x	x
<b>ALUSrc</b>	0	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	0	1	x	x	x
<b>RegWrite</b>	1	1	1	1	0	0	0
<b>MemWrite</b>	0	0	0	0	1	0	0
<b>nPCsel</b>	0	0	0	0	0	1	?
<b>Jump</b>	0	0	0	0	0	0	1
<b>ExtOp</b>	x	x	0	1	1	x	x
<b>ALUctr&lt;2:0&gt;</b>	Add	Subtract	Or	Add	Add	Subtract	x

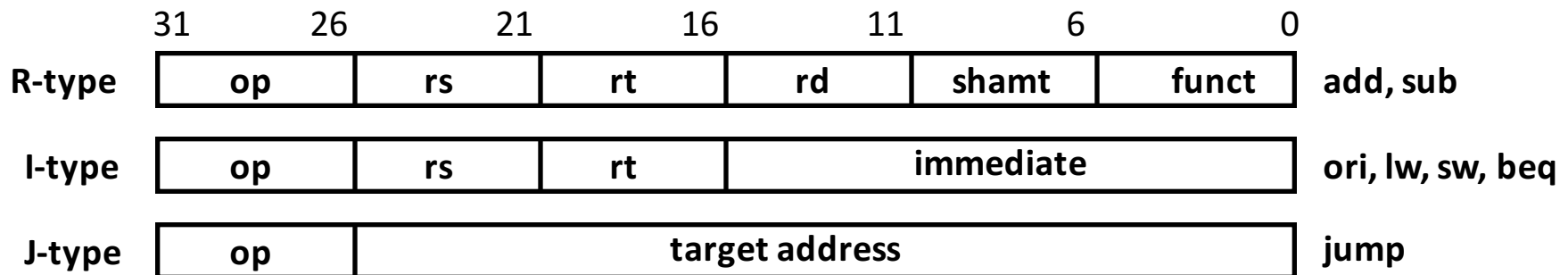

# Boolean Expressions for Controller

```
RegDst      = add + sub
ALUSrc      = ori + lw + sw
MemtoReg    = lw
RegWrite    = add + sub + ori + lw
MemWrite    = sw
nPCsel      = beq
Jump        = jump
ExtOp       = lw + sw
ALUctr[0]   = sub + beq      (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1]   = or
```

*Where:*


```
rtype = ~op5 • ~op4 • ~op3 • ~op2 • ~op1 • ~op0,
ori    = ~op5 • ~op4 • op3 • op2 • ~op1 • op0
lw     = op5 • ~op4 • ~op3 • ~op2 • op1 • op0
sw     = op5 • ~op4 • op3 • ~op2 • op1 • op0
beq    = ~op5 • ~op4 • ~op3 • op2 • ~op1 • ~op0
jump   = ~op5 • ~op4 • ~op3 • ~op2 • op1 • ~op0
```

```
add = rtype • func5 • ~func4 • ~func3 • ~func2 • ~func1 • ~func0
```


```
sub = rtype • func5 • ~func4 • ~func3 • ~func2 • func1 • ~func0
```

How do we  
implement this in  
gates?

# Controller Implementation

 


# P&H Figure 4.17

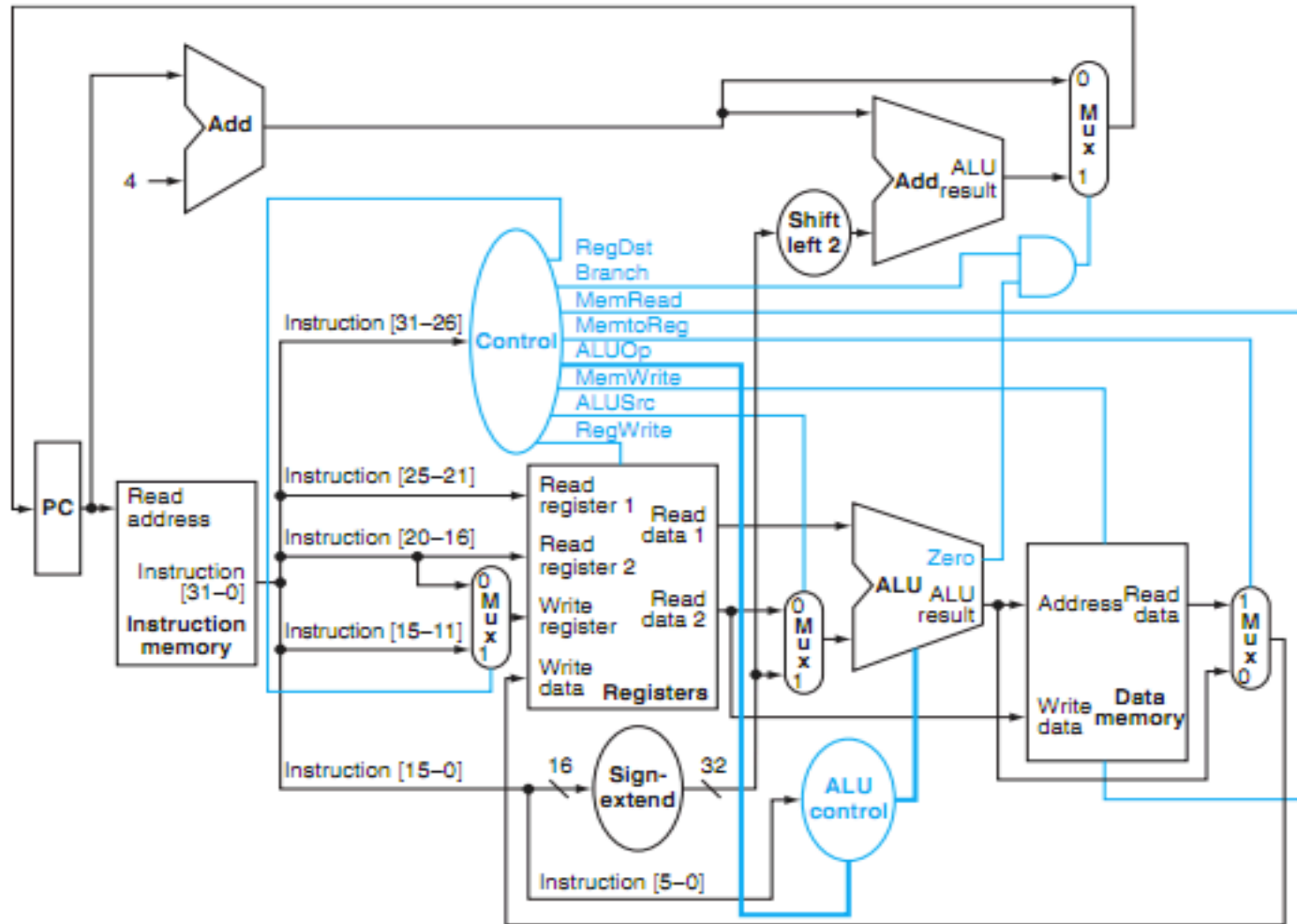

# Summary: Single-cycle Processor

- Five steps to design a processor:

 1. Analyze instruction set → datapath requirements
2. Select set of datapath components & establish clock methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic
  - Formulate Logic Equations
  - Design Circuits





# Single Cycle Performance

- Assume time for actions are
  - 100ps for register read or write; 200ps for other events
- Clock period is?

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

- Clock rate (cycles/second = Hz) =  $1/\text{Period (seconds/cycle)}$

# Single Cycle Performance

- Assume time for actions are
  - 100ps for register read or write; 200ps for other events
- Clock period is?

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

- What can we do to improve clock rate?
- Will this improve performance as well?
  - Want increased clock rate to mean faster programs

# Levels of Representation/Interpretation

High Level Language Program (e.g., C)

*Compiler*

Assembly Language Program (e.g., MIPS)

*Assembler*

Machine Language Program (MIPS)

*Machine Interpretation*

Hardware Architecture Description (e.g., block diagrams)

*Architecture Implementation*


Logic Circuit Description (Circuit Schematic Diagrams)

```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;
```


```
lw $t0, 0($2)
lw $t1, 4($2)
sw $t1, 0($2)
sw $t0, 4($2)
```

Anything can be represented as a *number*, i.e., data or instructions
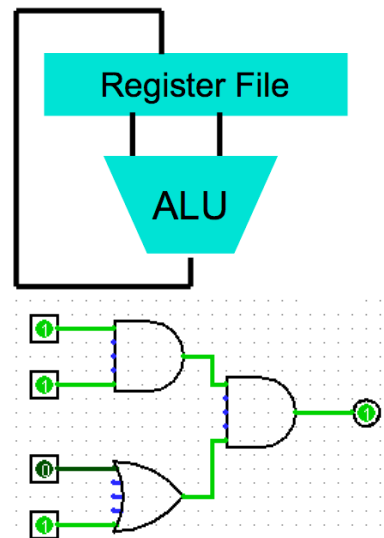
```
0000 1001 1100 0110 1010 1111 0101 1000
1010 1111 0101 1000 0000 1001 1100 0110
1100 0110 1010 1111 0101 1000 0000 1001
0101 1000 0000 1001 1100 0110 1010 1111
```



# No More Magic!

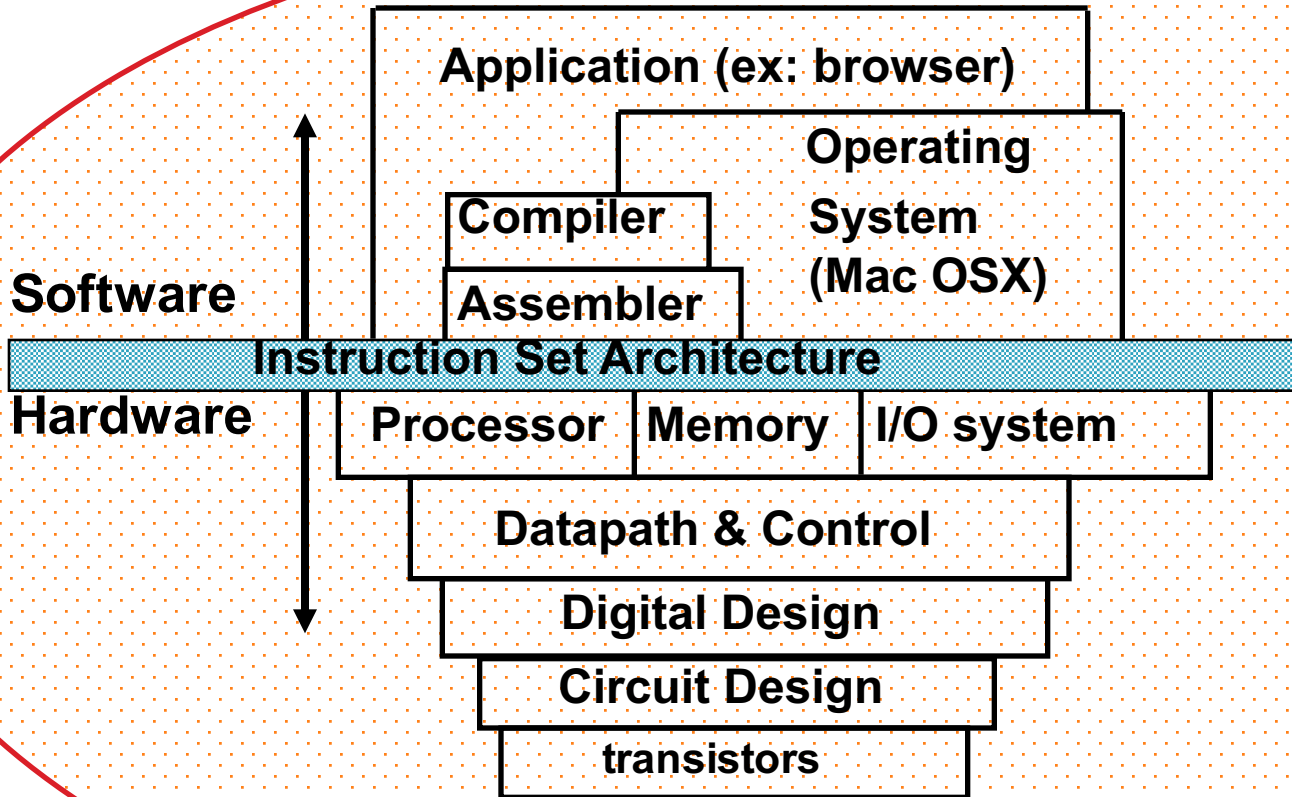

**CS61A**

**CS61B**

**CS61C ✓**

**CS61C ✓**

**CS61C ✓**

**CS61C ←**

**CS61C ✓**

**EE40**

**Phys 7B**