

CS 61C:
Great Ideas in Computer Architecture
Control and Pipelining


Instructors:

Vladimir Stojanovic and Nicholas Weaver

<http://inst.eecs.Berkeley.edu/~cs61c/sp16>

Datapath Control Signals

- ExtOp: “zero”, “sign”
- ALUsrc: 0 \Rightarrow regB; 1 \Rightarrow immed
- ALUctr: “ADD”, “SUB”, “OR”
- MemWr: 1 \Rightarrow write memory
- MemtoReg: 0 \Rightarrow ALU; 1 \Rightarrow Mem
- RegDst: 0 \Rightarrow “rt”; 1 \Rightarrow “rd”
- RegWr: 1 \Rightarrow write register

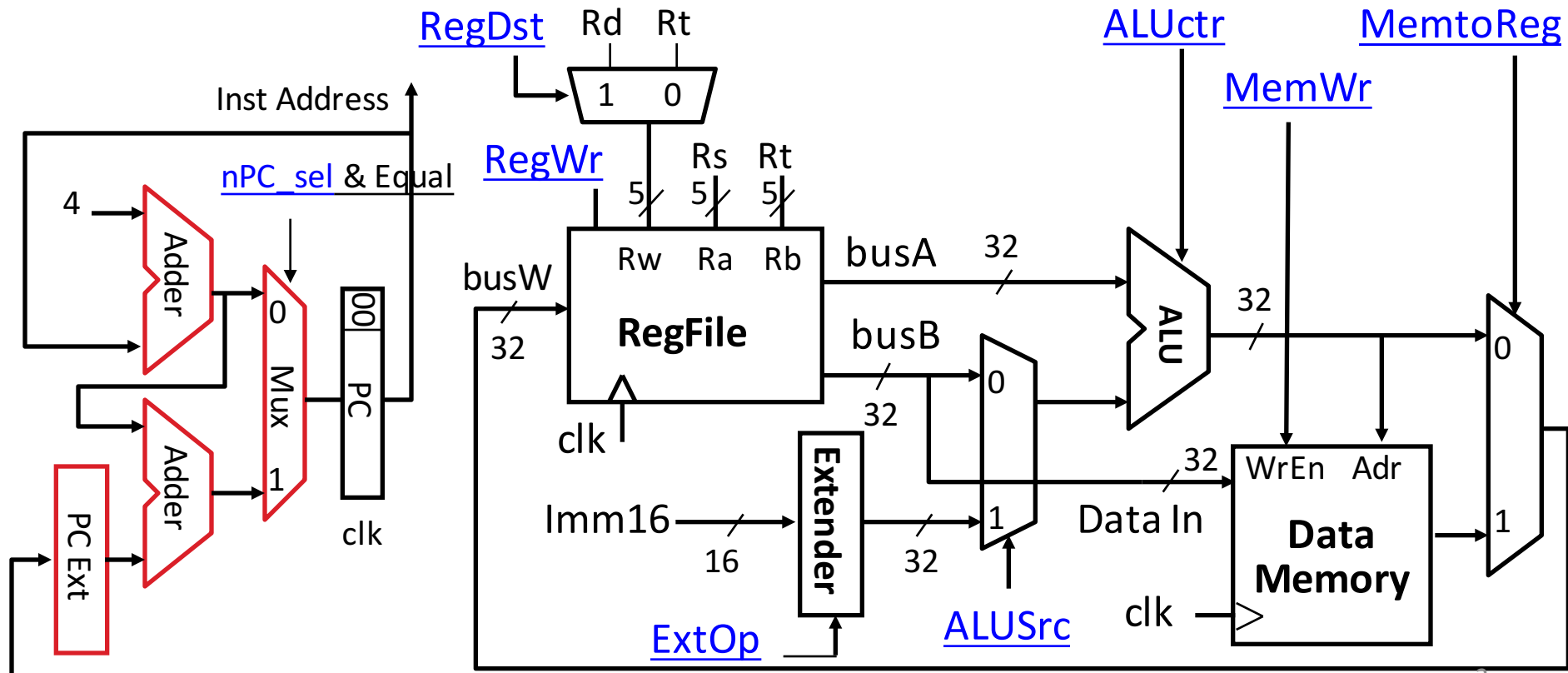

Imm16


Summary of the Control Signals (1/2)

```
inst   Register Transfer  
  
add     R[rd] ← R[rs] + R[rt]; PC ← PC + 4  
        ALUSrc=RegB, ALUctr="ADD", RegDst=rd, RegWr, nPC_sel="+4"  
  
sub     R[rd] ← R[rs] - R[rt]; PC ← PC + 4  
        ALUSrc=RegB, ALUctr="SUB", RegDst=rd, RegWr, nPC_sel="+4"  
  
ori     R[rt] ← R[rs] + zero_ext(Imm16); PC ← PC + 4  
        ALUSrc=Im, Extop="Z", ALUctr="OR", RegDst=rt, RegWr, nPC_sel="+4"  
  
lw      R[rt] ← MEM[ R[rs] + sign_ext(Imm16) ]; PC ← PC + 4  
        ALUSrc=Im, Extop="sn", ALUctr="ADD", MemtoReg, RegDst=rt, RegWr,  
        nPC_sel = "+4"  
  
sw      MEM[ R[rs] + sign_ext(Imm16) ] ← R[rs]; PC ← PC + 4  
        ALUSrc=Im, Extop="sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"  
  
beq     if (R[rs] == R[rt]) then PC ← PC + sign_ext(Imm16) || 00  
        else PC ← PC + 4  
  
        nPC_sel = "br", ALUctr = "SUB"
```

Summary of the Control Signals (2/2)

See Appendix A → **func**
 See Appendix A → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	add	sub	ori	lw	sw	beq	jump
RegDst	1	1	0	0	x	x	x
ALUSrc	0	0	1	1	1	0	x
MemtoReg	0	0	0	1	x	x	x
RegWrite	1	1	1	1	0	0	0
MemWrite	0	0	0	0	1	0	0
nPCsel	0	0	0	0	0	1	?
Jump	0	0	0	0	0	0	1
ExtOp	x	x	0	1	1	x	x
ALUctr<2:0>	Add	Subtract	Or	Add	Add	Subtract	x

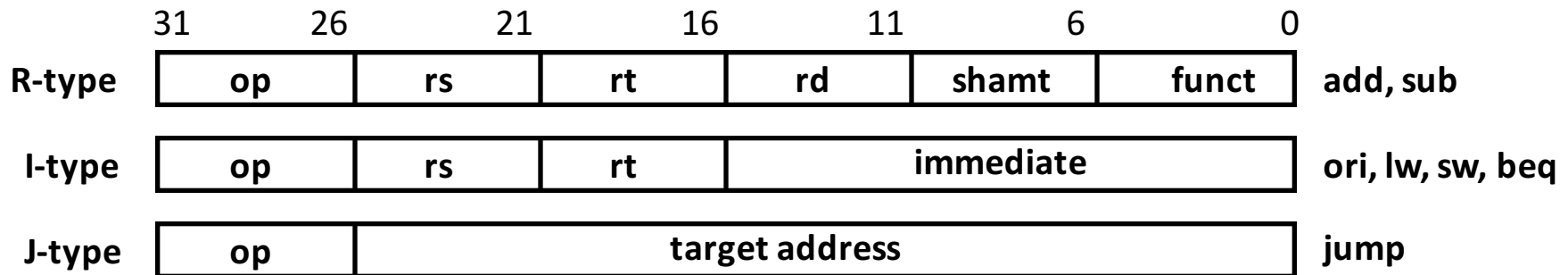

Boolean Expressions for Controller

```
RegDst      = add + sub
ALUSrc      = ori + lw + sw
MemtoReg    = lw
RegWrite     = add + sub + ori + lw
MemWrite    = sw
nPCsel      = beq
Jump        = jump
ExtOp       = lw + sw
ALUctr[0]   = sub + beq    (assume ALUctr is 00 ADD, 01 SUB, 10 OR)
ALUctr[1]   = or
```


Where:

```
rtype = ~op5 • ~op4 • ~op3 • ~op2 • ~op1 • ~op0,
ori    = ~op5 • ~op4 • op3 • op2 • ~op1 • op0
lw     = op5 • ~op4 • ~op3 • ~op2 • op1 • op0
sw     = op5 • ~op4 • op3 • ~op2 • op1 • op0
beq    = ~op5 • ~op4 • ~op3 • op2 • ~op1 • ~op0
jump   = ~op5 • ~op4 • ~op3 • ~op2 • op1 • ~op0
```


```
add = rtype • func5 • ~func4 • ~func3 • ~func2 • ~func1 • ~func0
sub = rtype • func5 • ~func4 • ~func3 • ~func2 • func1 • ~func0
```

How do we
implement this in
gates?

Controller Implementation

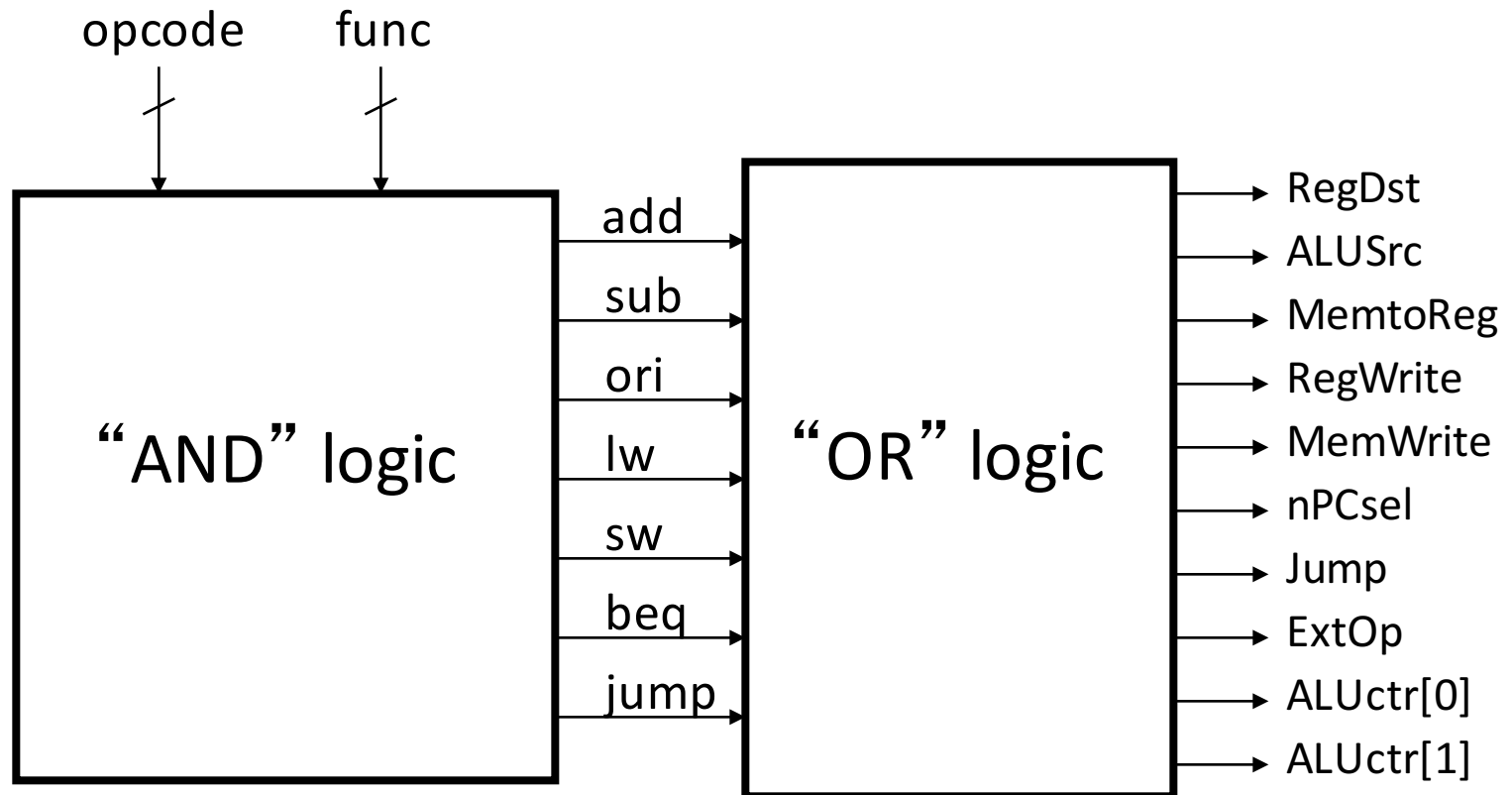

P&H Figure 4.17

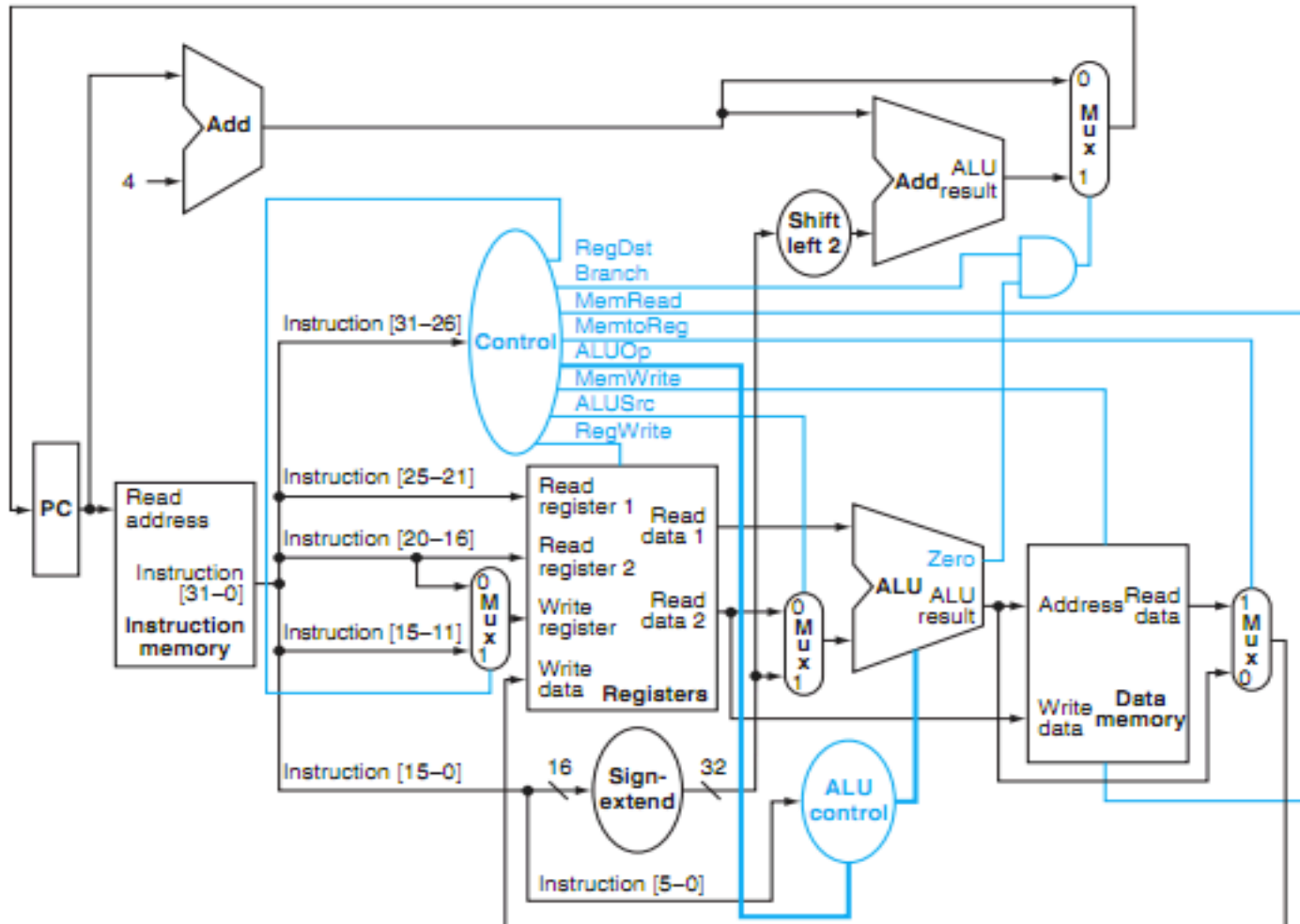

Summary: Single-cycle Processor

- Five steps to design a processor:

1. Analyze instruction set → datapath requirements


2. Select set of datapath components & establish clock methodology

3. Assemble datapath meeting the requirements

4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.

 5. Assemble the control logic

- Formulate Logic Equations
- Design Circuits



Single Cycle Performance

- Assume time for actions are
 - 100ps for register read or write; 200ps for other events
- Clock period is?

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

- Clock rate (cycles/second = Hz) = $1/\text{Period (seconds/cycle)}$

Single Cycle Performance

- Assume time for actions are
 - 100ps for register read or write; 200ps for other events
- Clock period is?

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

- What can we do to improve clock rate?
- Will this improve performance as well?
 - Want increased clock rate to mean faster programs

Levels of Representation/Interpretation

High Level Language Program (e.g., C)

Compiler

Assembly Language Program (e.g., MIPS)

Assembler

Machine Language Program (MIPS)

Machine Interpretation

Hardware Architecture Description (e.g., block diagrams)

Architecture Implementation



Logic Circuit Description (Circuit Schematic Diagrams)

```
temp = v[k];
v[k] = v[k+1];
v[k+1] = temp;
```


```
lw $t0, 0($2)
lw $t1, 4($2)
sw $t1, 0($2)
sw $t0, 4($2)
```

Anything can be represented as a *number*, i.e., data or instructions
  
```
0000 1001 1100 0110 1010 1111 0101 1000
1010 1111 0101 1000 0000 1001 1100 0110
1100 0110 1010 1111 0101 1000 0000 1001
0101 1000 0000 1001 1100 0110 1010 1111
```



No More Magic!

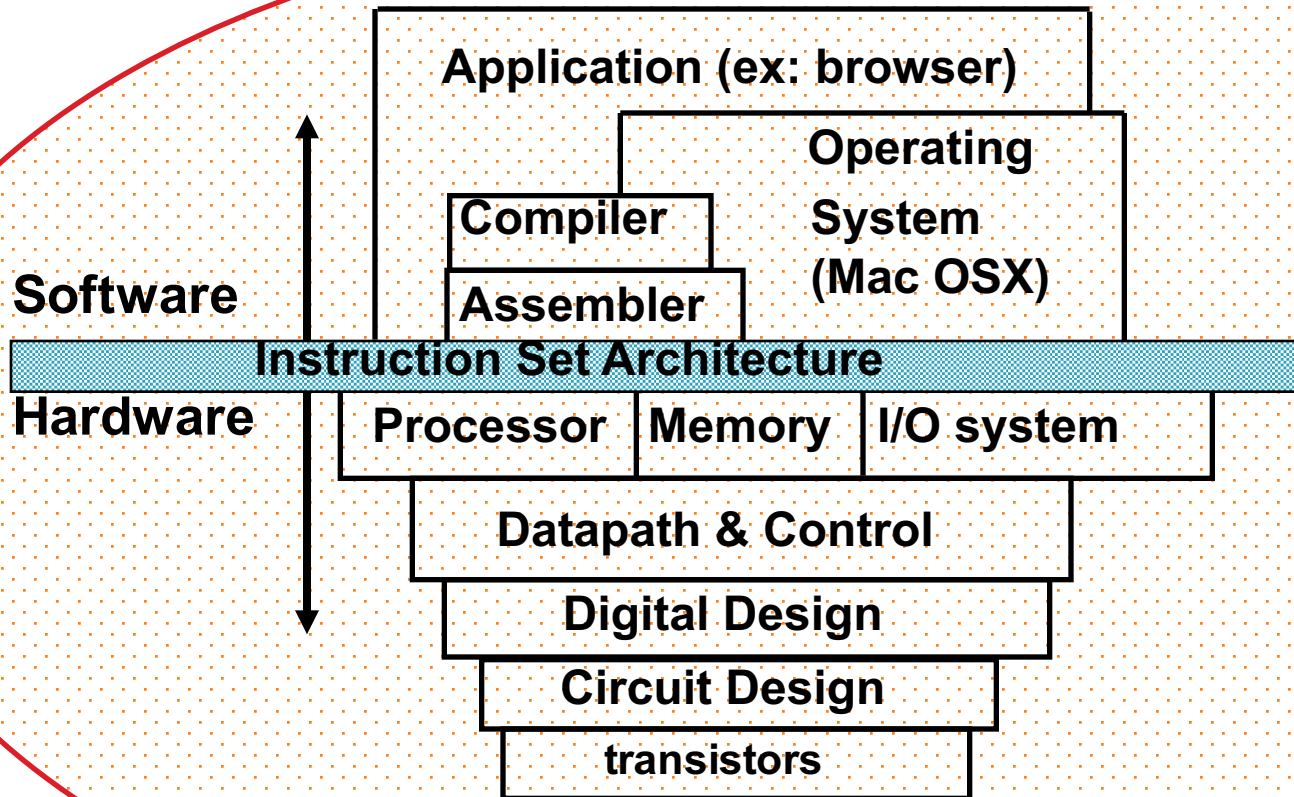

CS61A

CS61B

CS61C ✓

CS61C ✓

CS61C ✓

CS61C ←


CS61C ✓

EE40

Phys 7B

Administrivia




Review Grades for **Midterm 1**

 


- Project 2-2 due 3/8 @ 23:59:59 (Tue)
- Guerrilla Sessions: MIPS CPU
 - Wed 3/09 3 - 5 PM @ 241 Cory
 - Sat 3/12 1 - 3 PM @ 651 @ 611 Soda

Gotta Do Laundry

   - Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, fold, and put away
 - Washer takes 30 minutes
 - Dryer takes 30 minutes
 - “Folder” takes 30 minutes
 - “Stasher” takes 30 minutes to put clothes into drawers




Sequential Laundry

 


- Sequential laundry takes 8 hours for 4 loads

Pipelined Laundry

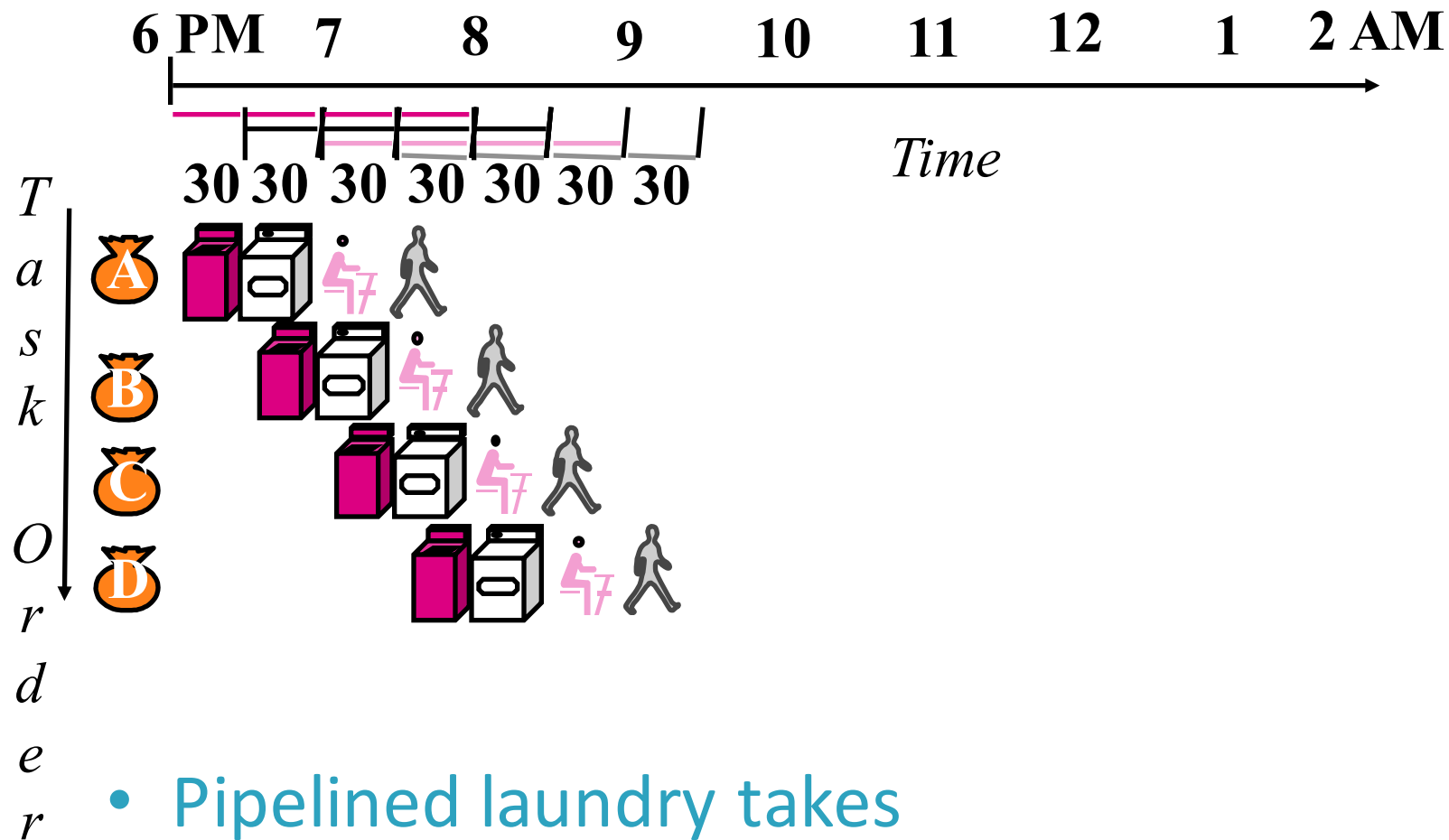


Pipelining Lessons (1/2)

 

- Pipelining doesn't help [latency](#) of single task, it helps [throughput](#) of entire workload
- [Multiple](#) tasks operating simultaneously using different resources
- Potential speedup = [Number pipe stages](#)
- Time to "[fill](#)" pipeline and time to "[drain](#)" it reduces speedup: 2.3x (8/3.5) v. 4x (8/2) in this example

Pipelining Lessons (2/2)

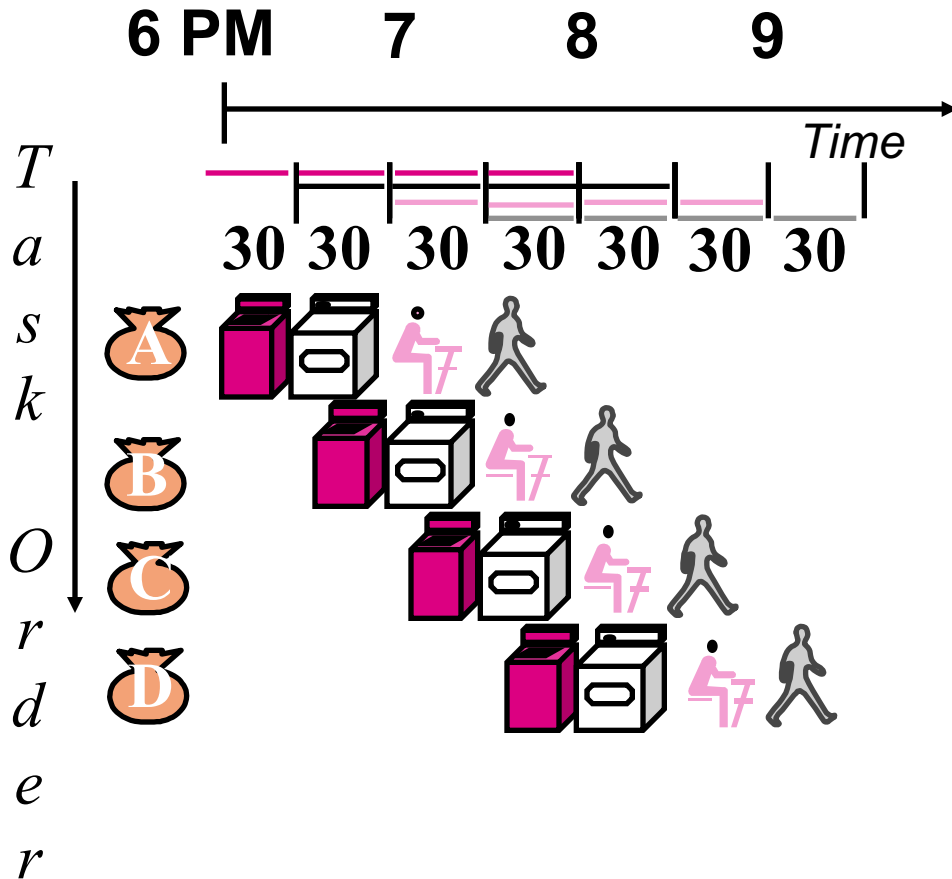


- Suppose new Washer takes 20 minutes, new Stasher takes 20 minutes. How much faster is pipeline?
- Pipeline rate limited by slowest pipeline stage
- Unbalanced lengths of pipe stages reduces speedup


Execution Steps in MIPS Datapath

- 1) IFtch: Instruction Fetch, Increment PC
- 2) Dcd: Instruction Decode, Read Registers
- 3) Exec:
 - Mem-ref: Calculate Address
 - Arith-log: Perform Operation
- 4) Mem:
 - Load: Read Data from Memory
 - Store: Write Data to Memory
- 5) WB: Write Data Back to Register

Single Cycle Datapath

 


Pipeline registers

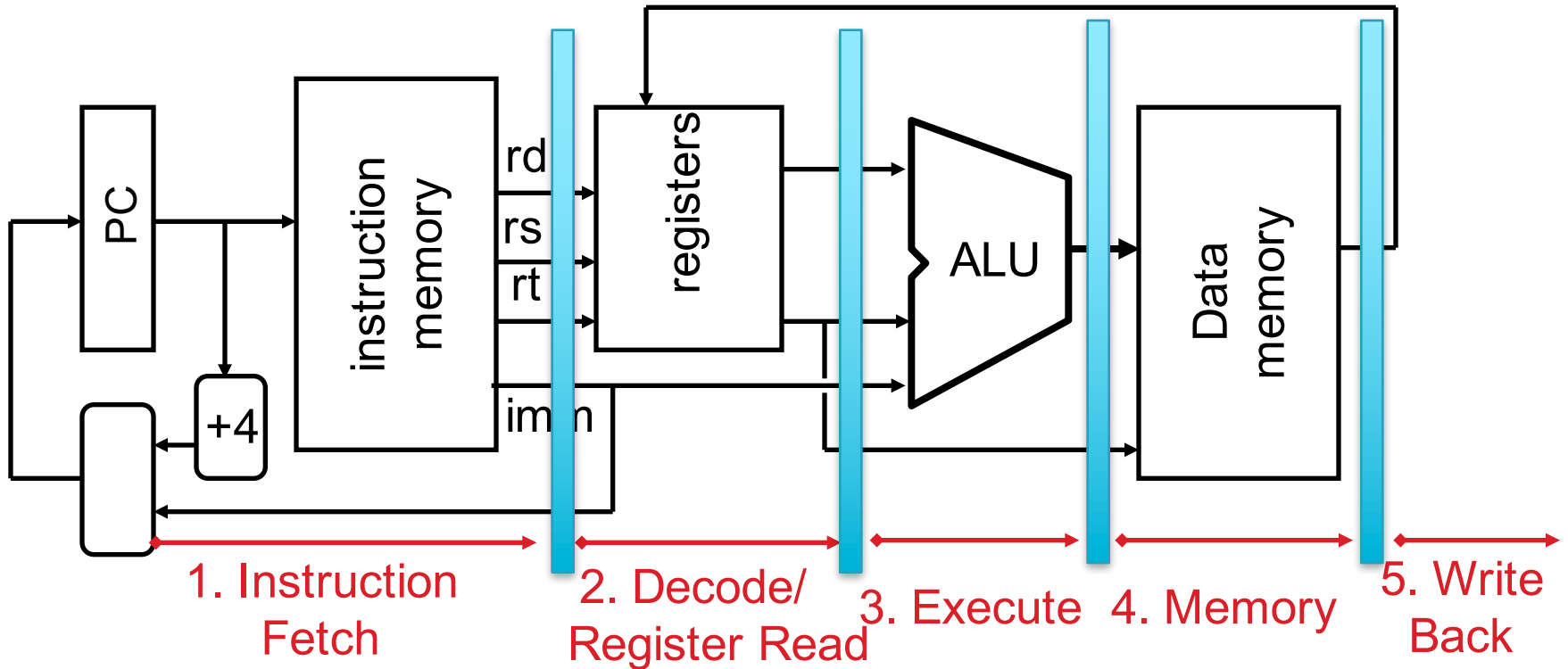


- Need registers between stages
 - To hold information produced in previous cycle


More Detailed Pipeline

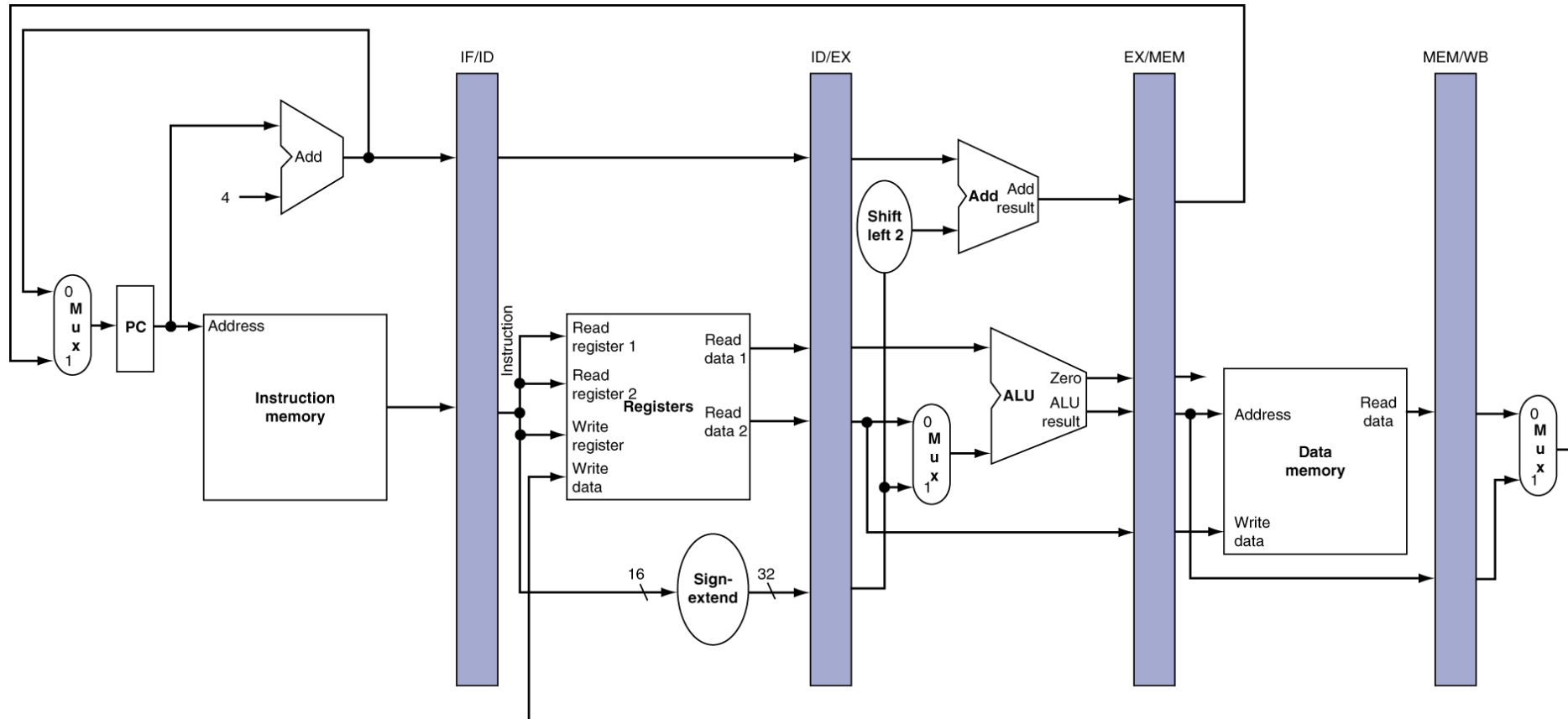



IF for Load, Store, ...

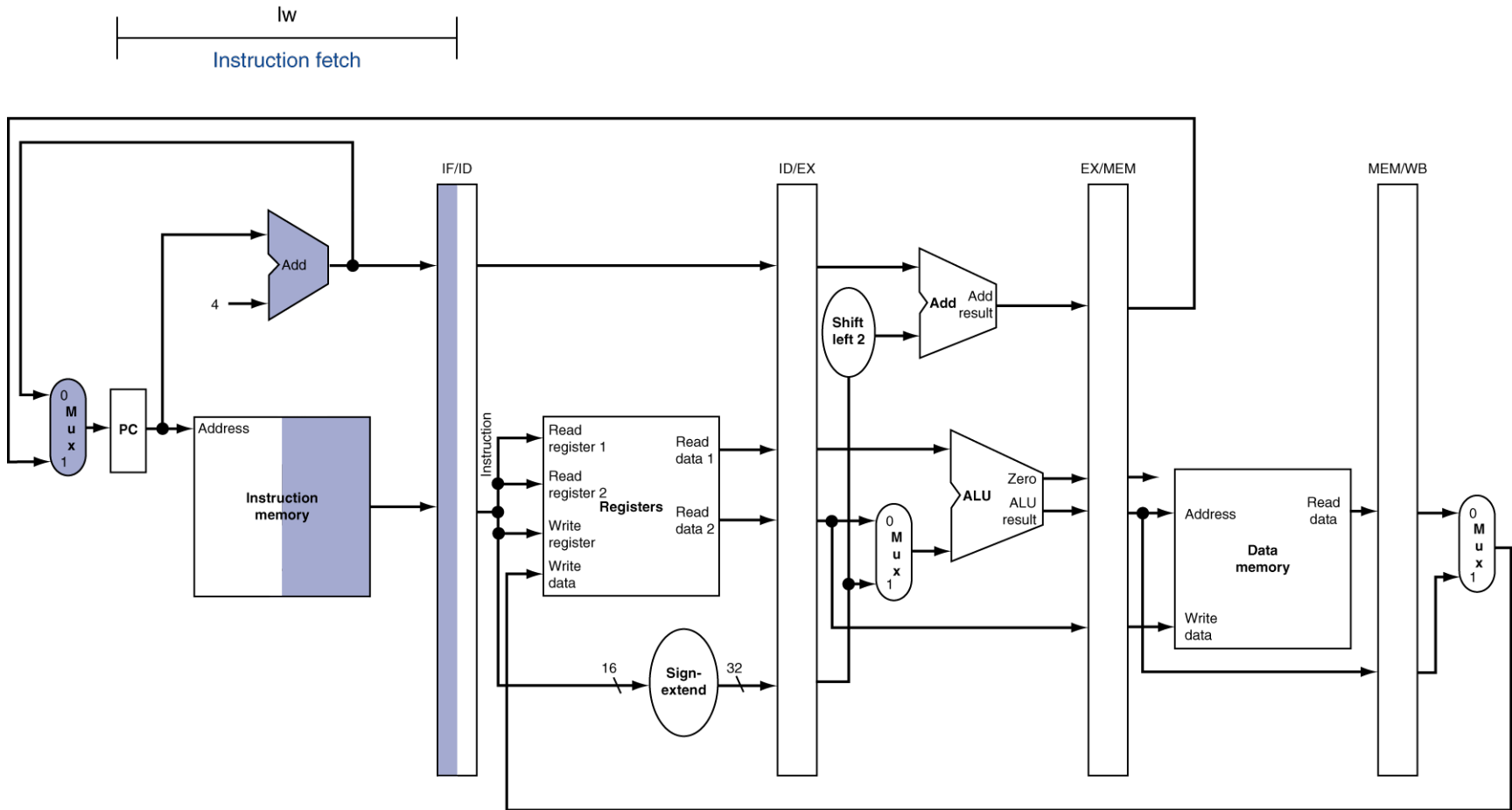


ID for Load, Store, ...

 


EX for Load

  


MEM for Load

 


WB for Load – Oops!

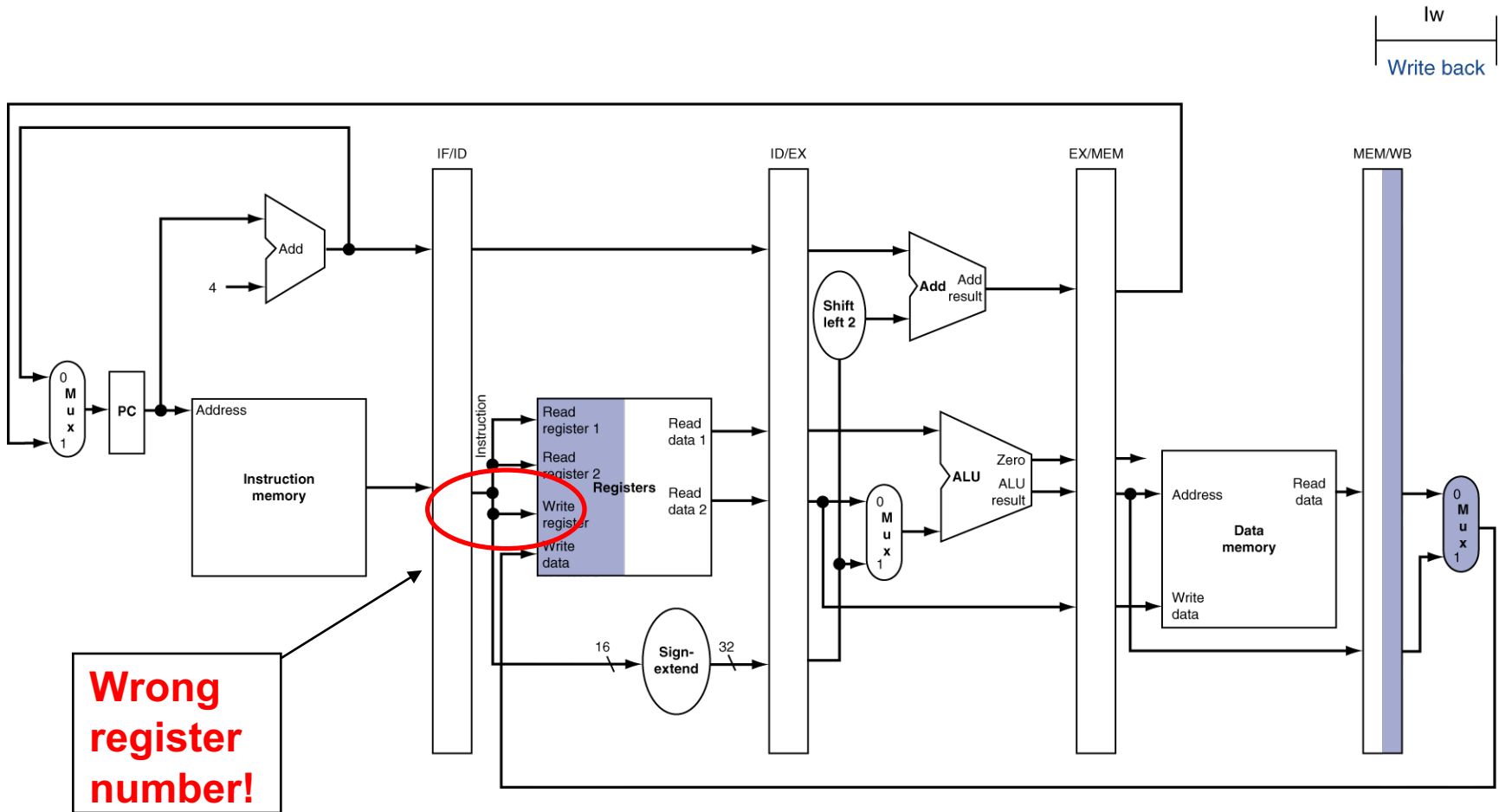

Corrected Datapath for Load

 


Pipelined Execution Representation

 


- Every instruction must take same number of steps, so some stages will idle
 - e.g. MEM stage for any arithmetic instruction

Graphical Pipeline Diagrams

 


 - Use datapath figure below to represent pipeline:



Graphical Pipeline Representation

 - RegFile: left half is write, right half is read



Pipelining Performance (1/3)

- Use T_c (“time between completion of instructions”) to measure speedup
 - $T_{c,\text{pipelined}} \geq \frac{T_{c,\text{single-cycle}}}{\text{Number of stages}}$
 - Equality only achieved if stages are *balanced* (i.e. take the same amount of time)
- If not balanced, speedup is reduced
- Speedup due to increased *throughput*
 - *Latency* for each instruction does not decrease



Pipelining Performance (2/3)

- Assume time for stages is
 - 100ps for register read or write
 - 200ps for other stages

Instr	Instr fetch	Register read	ALU op	Memory access	Register write	Total time
lw	200ps	100 ps	200ps	200ps	100 ps	800ps
sw	200ps	100 ps	200ps	200ps		700ps
R-format	200ps	100 ps	200ps		100 ps	600ps
beq	200ps	100 ps	200ps			500ps

- What is pipelined clock rate?
 - Compare pipelined datapath with single-cycle datapath

Pipelining Performance (3/3)

  

Clicker/Peer Instruction

Logic in some stages takes 200ps and in some 100ps. Clk-Q delay is 30ps and setup-time is 20ps. What is the maximum clock frequency at which a pipelined design can operate?

- A: 10GHz
- B: 5GHz
- C: 6.7GHz
- D: 4.35GHz
- E: 4GHz