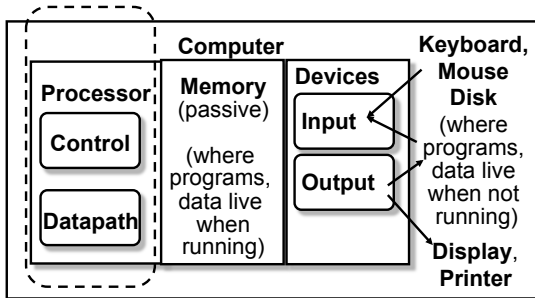


Five Components of a Computer



CS61CL L09 Single Cycle CPU Design (10)

Huddleston, Summer 2009 © UCB

The CPU

- **Processor (CPU):** the active part of the computer, which does all the work (data manipulation and decision-making)
- **Datapath:** portion of the processor which contains hardware necessary to perform operations required by the processor (the brawn)
- **Control:** portion of the processor (also in hardware) which tells the datapath what needs to be done (the brain)



CS61CL L09 Single Cycle CPU Design (11)

Huddleston, Summer 2009 © UCB

Stages of the Datapath : Overview

- **Problem:** a single, atomic block which “executes an instruction” (performs all necessary operations beginning with fetching the instruction) would be too bulky and inefficient
- **Solution:** break up the process of “executing an instruction” into stages, and then connect the stages to create the whole datapath
 - smaller stages are easier to design
 - easy to optimize (change) one stage without touching the others



CS61CL L09 Single Cycle CPU Design (12)

Huddleston, Summer 2009 © UCB

Stages of the Datapath (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- **Stage 1: Instruction Fetch**
 - no matter what the instruction, the 32-bit instruction must first be fetched from memory (the cache-memory hierarchy)
 - also, this is where we increment PC (that is, $PC = PC + 4$, to point to the next instruction: byte addressing so + 4)



CS61CL L09 Single Cycle CPU Design (13)

Huddleston, Summer 2009 © UCB

Stages of the Datapath (2/5)

- **Stage 2: Instruction Decode**
 - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
 - first, read the opcode to determine instruction type and field lengths
 - second, read in data from all necessary registers
 - for `add`, read two registers
 - for `addi`, read one register
 - for `jal`, no reads necessary



CS61CL L09 Single Cycle CPU Design (14)

Huddleston, Summer 2009 © UCB

Stages of the Datapath (3/5)

- **Stage 3: ALU (Arithmetic-Logic Unit)**
 - the real work of most instructions is done here: arithmetic (+, -, *, /), shifting, logic (&, !), comparisons (`slt`)
 - what about loads and stores?
 - `lw $t0, 40($t1)`
 - the address we are accessing in memory = the value in `$t1` PLUS the value 40
 - so we do this addition in this stage



CS61CL L09 Single Cycle CPU Design (15)

Huddleston, Summer 2009 © UCB

Stages of the Datapath (4/5)

- **Stage 4: Memory Access**
 - actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
 - since these instructions have a unique step, we need this extra stage to account for them
 - as a result of the cache system, this stage is expected to be fast



CS61CL L09 Single Cycle CPU Design (16)

Huddleston, Summer 2009 © UCB

Stages of the Datapath (5/5)


- **Stage 5: Register Write**
 - most instructions write the result of some computation into a register
 - examples: arithmetic, logical, shifts, loads, `slt`
 - what about stores, branches, jumps?
 - don't write anything into a register at the end
 - these remain idle during this fifth stage or skip it all together



CS61CL L09 Single Cycle CPU Design (17)

Huddleston, Summer 2009 © UCB

Generic Steps of Datapath

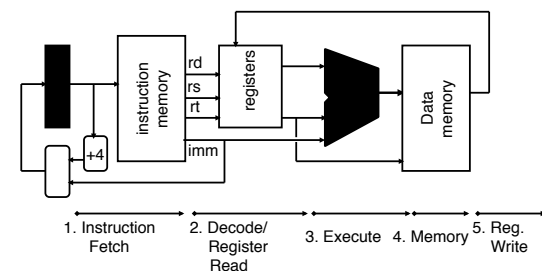

CS61CL L09 Single Cycle CPU Design (18)

Huddleston, Summer 2009 © UCB

Datapath Walkthroughs (1/3)


- `add $r3,$r1,$r2 # r3 = r1+r2`
- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's an add, then read registers `$r1` and `$r2`
- Stage 3: add the two values retrieved in Stage 2
- Stage 4: idle (nothing to write to memory)
- Stage 5: write result of Stage 3 into register `$r3`



CS61CL L09 Single Cycle CPU Design (19)

Huddleston, Summer 2009 © UCB

Example: add Instruction

 

CS61CL L09 Single Cycle CPU Design (20)

Huddleston, Summer 2009 © UCB

Datapath Walkthroughs (3/3)


- `sw $r3, 17($r1)`
- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's a `sw`, then read registers `$r1` and `$r3`
- Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
- Stage 4: write value in register `$r3` (retrieved in Stage 2) into memory address computed in Stage 3
- Stage 5: idle (nothing to write into a register)



CS61CL L09 Single Cycle CPU Design (21)

Huddleston, Summer 2009 © UCB

Example: sw Instruction

 

CS61CL L09 Single Cycle CPU Design (22)

Huddleston, Summer 2009 © UCB

Why Five Stages? (1/2)

- Could we have a different number of stages?
 - Yes, and other architectures do
- So why does MIPS have five if instructions tend to idle for at least one stage?
 - The five stages are the union of all the operations needed by all the instructions.
 - There is one type of instruction that uses all five stages: the load



CS61CL L09 Single Cycle CPU Design (23)

Huddleston, Summer 2009 © UCB

Why Five Stages? (2/2)


- `lw $r3, 17($r1)`
- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's a `lw`, then read register `$r1`
- Stage 3: add 17 to value in register `$r1` (retrieved in Stage 2)
- Stage 4: read value from memory address compute in Stage 3
- Stage 5: write value found in Stage 4 into register `$r3`



CS61CL L09 Single Cycle CPU Design (24)

Huddleston, Summer 2009 © UCB

Example: lw Instruction

 


CS61CL L09 Single Cycle CPU Design (25)

Huddleston, Summer 2009 © UCB

Datapath Summary

 - The datapath based on data transfers required to perform instructions
- A controller causes the right transfers to happen




CS61CL L09 Single Cycle CPU Design (26)

Huddleston, Summer 2009 © UCB

CPU clocking (1/2) For each instruction, how do we control the flow of information through the datapath?

 - Single Cycle CPU: All stages of an instruction are completed within one long clock cycle.
 - The clock cycle is made sufficient long to allow each instruction to complete all stages without interruption and within one cycle.




CS61CL L09 Single Cycle CPU Design (27)

Huddleston, Summer 2009 © UCB

CPU clocking (2/2) For each instruction, how do we control the flow of information through the datapath?

Multiple-cycle CPU: Only one stage of instruction per clock cycle.

 - The clock is made as long as the slowest stage.



- Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped).



How to Design a Processor: step-by-step


- Analyze instruction set architecture (ISA)
 - ⇒ datapath requirements
 - meaning of each instruction is given by the register transfers
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- Select set of datapath components and establish clocking methodology
- Assemble datapath meeting requirements
- Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- Assemble the control logic (hard part!)




Review: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:


R-type

 

I-type

 

J-type

 

- The different fields are:


- op: operation ("opcode") of the instruction
- rs, rt, rd: the source and destination register specifiers
- shamt: shift amount
- funct: selects the variant of the operation in the "op" field
- address / immediate: address offset or immediate value
- target address: target address of jump instruction



The MIPS-lite Subset for today


ADDU and SUBU

- addu rd,rs,rt
- subu rd,rs,rt

 

OR Immediate:

- ori rt,rs,imm16

 


LOAD and STORE Word

- lw rt,rs,imm16
- sw rt,rs,imm16



BRANCH:

- beq rs,rt,imm16

 

ALU Needs for MIPS-lite + Rest of MIPS

Addition, subtraction, logical OR, ==:

```
ADDU  R[rd] = R[rs] + R[rt]; ...
SUBU  R[rd] = R[rs] - R[rt]; ...
ORI   R[rt] = R[rs] | zero_ext(Imm16) ...
BEQ   if ( R[rs] == R[rt] ) ...
```

- Test to see if output == 0 for any ALU operation gives == test. How?

- P&H also adds AND, Set Less Than (1 if A < B, 0 otherwise)



ALU follows chap 5

How to Design a Processor: step-by-step

- Analyze instruction set architecture (ISA)
 - ⇒ datapath requirements
 - meaning of each instruction is given by the register transfers
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- Select set of datapath components and establish clocking methodology
- Assemble datapath meeting requirements
- Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- Assemble the control logic (hard part!)



What Hardware Is Needed? (1/2)

- PC: a register which keeps track of memory addr of the next instruction
- General Purpose Registers
 - used in Stages 2 (Read) and 5 (Write)
 - MIPS has 32 of these
- Memory
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average



What Hardware Is Needed? (2/2)

ALU

- used in Stage 3
- something that performs all necessary functions: arithmetic, logicals, etc.
- we'll design details later


Miscellaneous Registers

- In implementations with only one stage per clock cycle, registers are inserted between stages to hold intermediate data and control signals as they travels from stage to stage.
- Note: Register is a general purpose term meaning something that stores bits. Not all registers are in the "register file".




Combinational Logic Elements (Building Blocks)


Adder

 

MUX

 


ALU

 

Storage Element: Idealized Memory

Memory (idealized)

 - One input bus: Data In
- One output bus: Data Out



Memory word is found by:

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus

Clock input (CLK)


- The CLK input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - Address valid \Rightarrow Data Out valid after "access time."



Storage Element: Register (Building Block)

Similar to D Flip Flop except

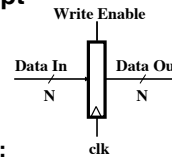- N-bit input and output
- Write Enable input



Write Enable:


- negated (or deasserted) (0): Data Out will not change
- asserted (1): Data Out will become Data In on positive edge of clock



Storage Element: Register File

Register File consists of 32 registers:

 - Two 32-bit output buses: busA and busB
- One 32-bit input bus: busW



Register is selected by:

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

Clock input (clk)

- The clk input is a factor ONLY during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after "access time."



How to Design a Processor: step-by-step

1. Analyze instruction set architecture (ISA)

\Rightarrow datapath requirements

- meaning of each instruction is given by the register transfers
- datapath must include storage element for ISA registers
- datapath must support each register transfer

2. Select set of datapath components and establish clocking methodology

3. Assemble datapath meeting requirements

4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.

5. Assemble the control logic (hard part!)




Overview of the Instruction Fetch Unit

The common RTL operations

Fetch the Instruction: mem[PC]

Update the program counter:

 - Sequential Code: $PC \leftarrow PC + 4$
- Branch and Jump: $PC \leftarrow$ "something else"




Add & Subtract


$R[rd] = R[rs] \text{ op } R[rt]$ Ex.: addU rd,rs,rt

- Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields

 - ALUctr and RegWr: control logic after decoding the instruction




 ... Already defined the register file & ALU




Logical Operations with Immediate

 $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$




But we're writing to Rt register??

 


Logical Operations with Immediate

 $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$



What about Rt register read??

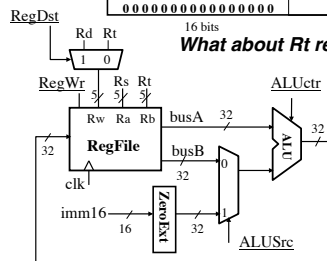



• Already defined 32-bit MUX; Zero Ext?



Load Operations


$R[rt] = \text{Mem}[R[rs] + \text{SignExt}[imm16]]$

Example: lw rt,rs,imm16

  

Load Operations

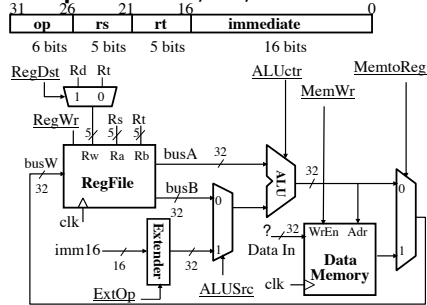- $R[rt] = Mem[R[rs] + SignExt[imm16]]$
- Example: `lw rt, rs, imm16`




Cal

CS61CL L09 Single Cycle CPU Design (46)

Huddleston, Summer 2009 © UCB

Store Operations

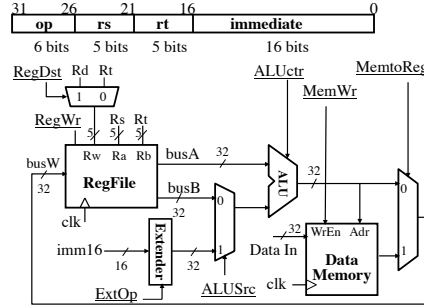- $Mem[R[rs] + SignExt[imm16]] = R[rt]$
- Ex.: `sw rt, rs, imm16`




Cal

CS61CL L09 Single Cycle CPU Design (47)

Huddleston, Summer 2009 © UCB

Store Operations

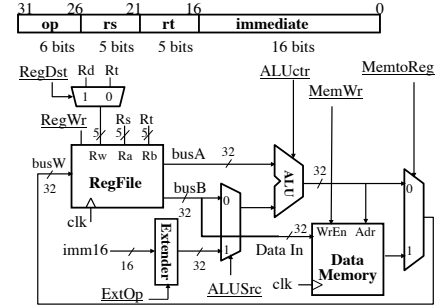- $Mem[R[rs] + SignExt[imm16]] = R[rt]$
- Ex.: `sw rt, rs, imm16`




Cal

CS61CL L09 Single Cycle CPU Design (48)

Huddleston, Summer 2009 © UCB

The Branch Instruction

 

`beq rs, rt, imm16`

- `mem[PC]` Fetch the instruction from memory
- `Equal = R[rs] == R[rt]` Calculate branch condition
- if (Equal) Calculate the next instruction's address
 - `PC = PC + 4 + (SignExt(imm16) x 4)`
- else
 - `PC = PC + 4`


Cal

CS61CL L09 Single Cycle CPU Design (49)

Huddleston, Summer 2009 © UCB

Datapath for Branch Operations

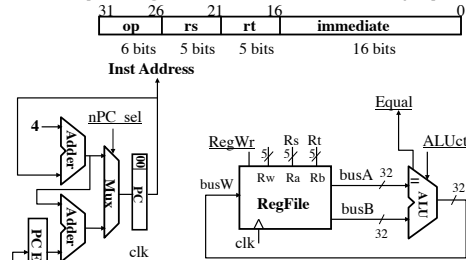- `beq rs, rt, imm16`
- Datapath generates condition (equal)




Cal

CS61CL L09 Single Cycle CPU Design (50)

Huddleston, Summer 2009 © UCB

Already have mux, adder, need special sign extender for PC, need equal compare (sub?)

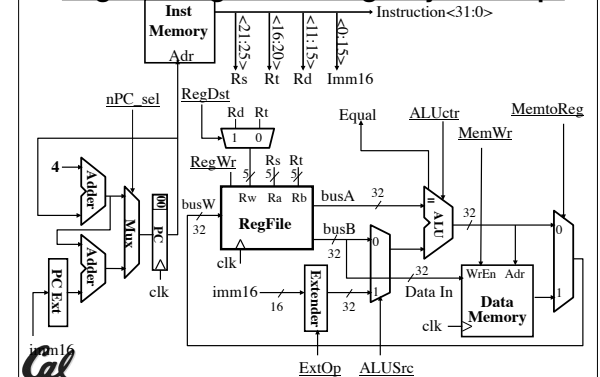Putting it All Together: A Single Cycle Datapath




Cal

CS61CL L09 Single Cycle CPU Design (51)

Huddleston, Summer 2009 © UCB

An Abstract View of the Implementation

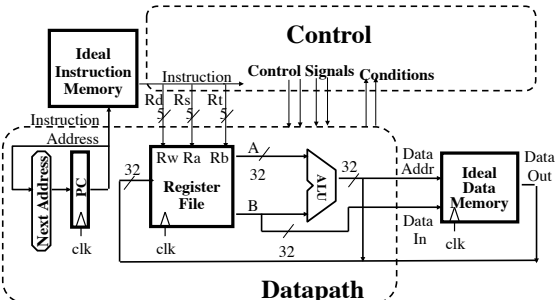


Cal

CS61CL L09 Single Cycle CPU Design (52)

Huddleston, Summer 2009 © UCB

Summary: A Single Cycle Datapath

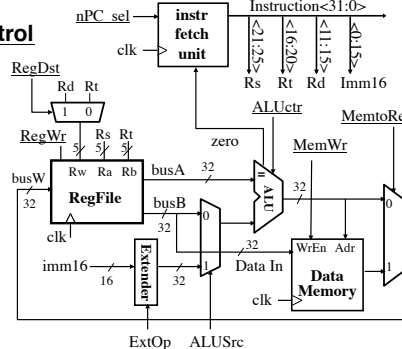- We have everything except control signals



Cal

CS61CL L09 Single Cycle CPU Design (53)

Huddleston, Summer 2009 © UCB

“And In conclusion...”

- N-bit adder-subtractor done using N-bit adders with XOR gates on input
 - XOR serves as conditional inverter
- CPU design involves Datapath, Control
 - Datapath in MIPS involves 5 CPU stages
 1. Instruction Fetch
 2. Instruction Decode & Register Read
 3. ALU (Execute)
 4. Memory
 5. Register Write

Cal

CS61CL L09 Single Cycle CPU Design (54)

Huddleston, Summer 2009 © UCB

Bonus slides

- These are extra slides that used to be included in lecture notes, but have been moved to this, the “bonus” area to serve as a supplement.
- The slides will appear in the order they would have in the normal presentation

Bonus



CS61CL L09 Single Cycle CPU Design (55)

Huddleston, Summer 2009 © UCB

Review of Timing Terms

- Clock (CLK) - steady square wave that synchronizes system
- Setup Time - when the input must be stable before the rising edge of the CLK
- Hold Time - when the input must be stable after the rising edge of the CLK
- “CLK-to-Q” Delay - how long it takes the output to change, measured from the rising edge
- Flip-flop - one bit of state that samples every rising edge of the CLK
- Register - several bits of state that samples on rising edge of CLK or on LOAD




CS61CL L09 Single Cycle CPU Design (56)

Huddleston, Summer 2009 © UCB

What about overflow?

 - Consider a 2-bit signed # & overflow:
 - 10 = -2 + -2 or -1
 - 11 = -1 + -2 only
 - 00 = 0 NOTHING!
 - 01 = 1 + 1 only



Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!

What C_{in} and $C_{out} \Rightarrow$ NO overflow!

- op? • C_{in} but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} but no $C_{in} \Rightarrow$ A,B both < 0, overflow!




CS61CL L09 Single Cycle CPU Design (57)

Huddleston, Summer 2009 © UCB

What about overflow?

- Consider a 2-bit signed # & overflow:

10 = -2
11 = -1
00 = 0
01 = 1

 

- Overflows when...

- C_{in} , but no $C_{out} \Rightarrow$ A,B both > 0, overflow!
- C_{out} , but no $C_{in} \Rightarrow$ A,B both < 0, overflow!


$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$



CS61CL L09 Single Cycle CPU Design (58)

Huddleston, Summer 2009 © UCB

Extremely Clever Subtractor

 

CS61CL L09 Single Cycle CPU Design (59)

Huddleston, Summer 2009 © UCB

Datapath Walkthroughs (2/3)


- `s1ti $r3, $r1, 17`
- Stage 1: fetch this instruction, inc. PC
- Stage 2: decode to find it's an `s1ti`, then read register `$r1`
- Stage 3: compare value retrieved in Stage 2 with the integer 17
- Stage 4: idle
- Stage 5: write the result of Stage 3 in register `$r3`



CS61CL L09 Single Cycle CPU Design (60)

Huddleston, Summer 2009 © UCB


Example: `s1ti` Instruction

 

CS61CL L09 Single Cycle CPU Design (61)

Huddleston, Summer 2009 © UCB

Clocking Methodology

 

- Storage elements clocked by same edge
- Being physical devices, flip-flops (FF) and combinational logic have some delays
 - Gates: delay from input change to output change
 - Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay
- “Critical path” (longest path through logic) determines length of clock period




CS61CL L09 Single Cycle CPU Design (62)

Huddleston, Summer 2009 © UCB

An Abstract View of the Critical Path

Critical Path (Load Instruction) =
Delay clock through PC (FFs) +
Instruction Memory's Access Time +
Register File's Access Time, +
ALU to Perform a 32-bit Add +
Data Memory Access Time +
Stable Time for Register File Write

(Assumes a fast controller)

 

CS61CL L09 Single Cycle CPU Design (63)

Huddleston, Summer 2009 © UCB