

`inst.eecs.berkeley.edu/~cs61c`
CS61CL : Machine Structures

Lecture #9 – Single Cycle CPU Design

2009-07-22




Jeremy Huddleston




Finite State Machine Example: 3 ones...

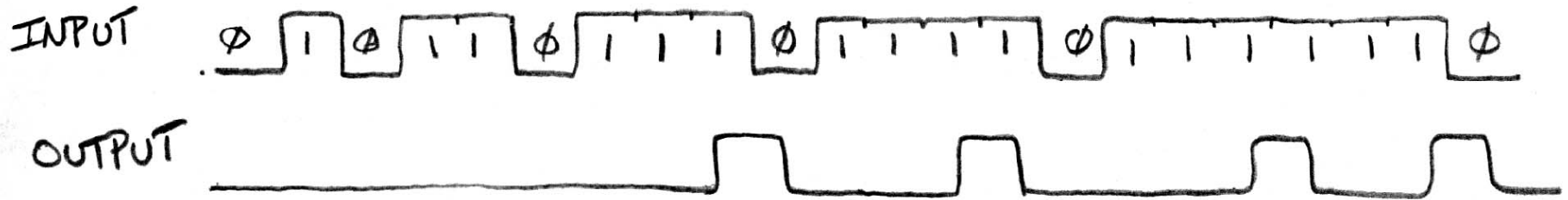FSM to detect the occurrence of 3 consecutive 1's in the input.



Draw the FSM...

 


Assume state transitions are controlled by the clock:
on each clock cycle the machine checks the inputs and moves
to a new state and produces a new output...




Hardware Implementation of FSM

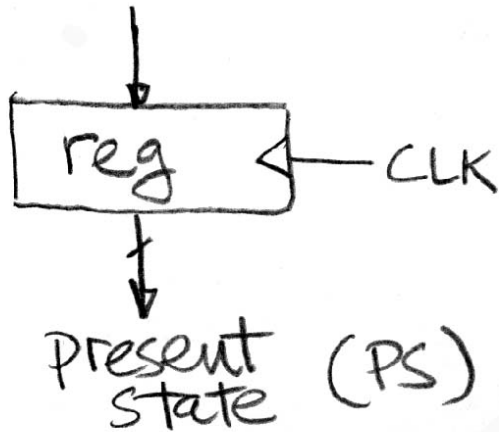
... Therefore a register is needed to hold the a representation of which state the machine is in. Use a unique bit pattern for each state.



+

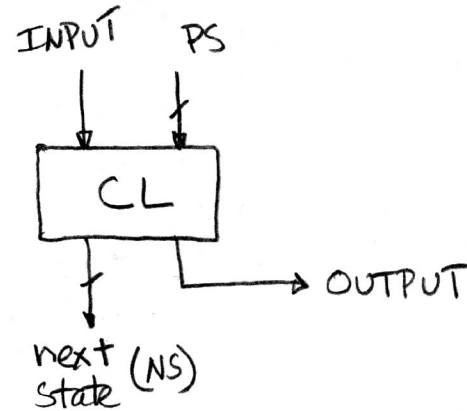


=

 

Combinational logic circuit is used to implement a function maps from *present state and input* to *next state and output*.



Register Details...What's inside?

 

- n instances of a “Flip-Flop”
- Flip-flop name because the output flips and flops between and 0,1
- D is “data”, Q is “output”
- Also called “d-type Flip-Flop”



Adder/Subtractor – One-bit adder LSB...

$$\begin{array}{rcccc} & a_3 & a_2 & a_1 & a_0 \\ + & b_3 & b_2 & b_1 & b_0 \\ \hline s_3 & s_2 & s_1 & s_0 & \end{array}$$

a_0	b_0	s_0	c_1
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$s_0 =$$

$$c_1 =$$



Adder/Subtractor – One-bit adder (1/2)...



				a_i	b_i	c_i	S_i	C_{i+1}
				0	0	0	0	0
				0	0	1	1	0
				0	1	0	1	0
+	a_3	a_2	a_1	a_0	0	1	1	0
	b_3	b_2	b_1	b_0	0	1	0	1
	s_3	s_2	s_1	s_0	1	0	0	1
				1	0	1	0	1
				1	1	0	0	1
				1	1	1	1	1

$$S_i =$$

$$C_{i+1} =$$




  Adder/Subtractor – One-bit adder (2/2)...




$$s_i = \text{XOR}(a_i, b_i, c_i)$$
$$c_{i+1} = \text{MAJ}(a_i, b_i, c_i) = a_i b_i + a_i c_i + b_i c_i$$

N 1-bit adders \Rightarrow 1 N-bit adder

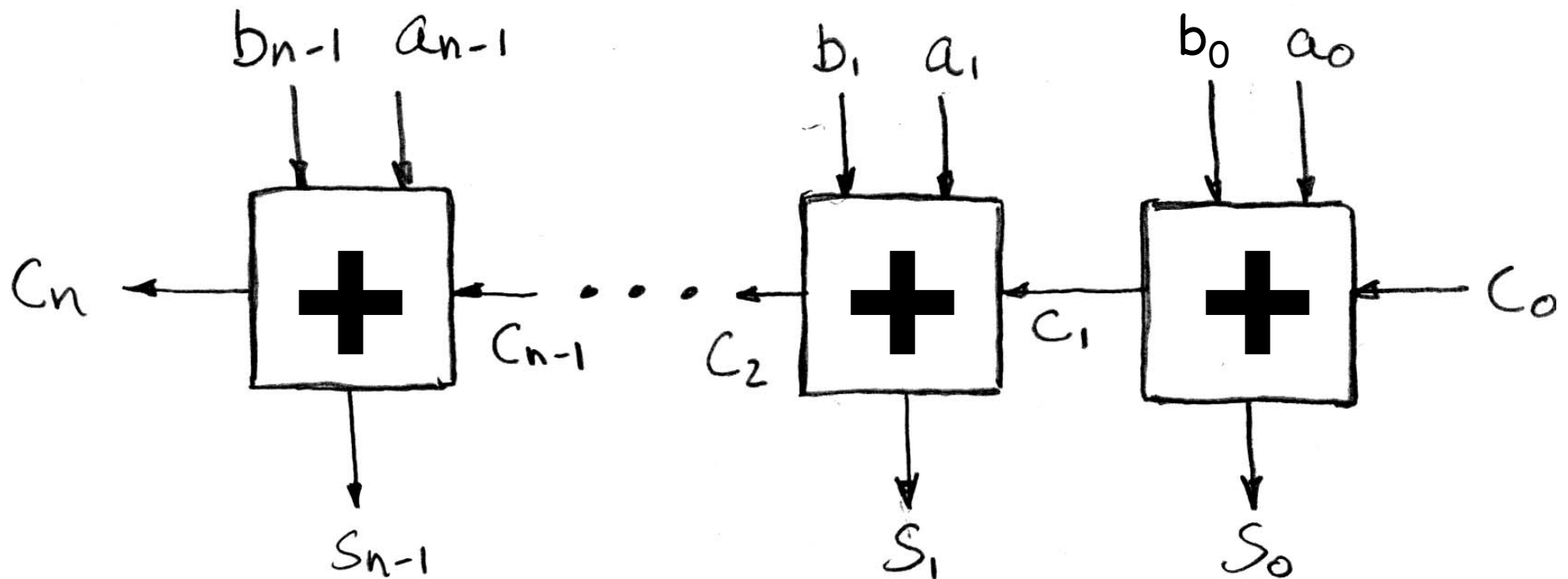


Administrivia

- Midterm handed back today

 

Five Components of a Computer

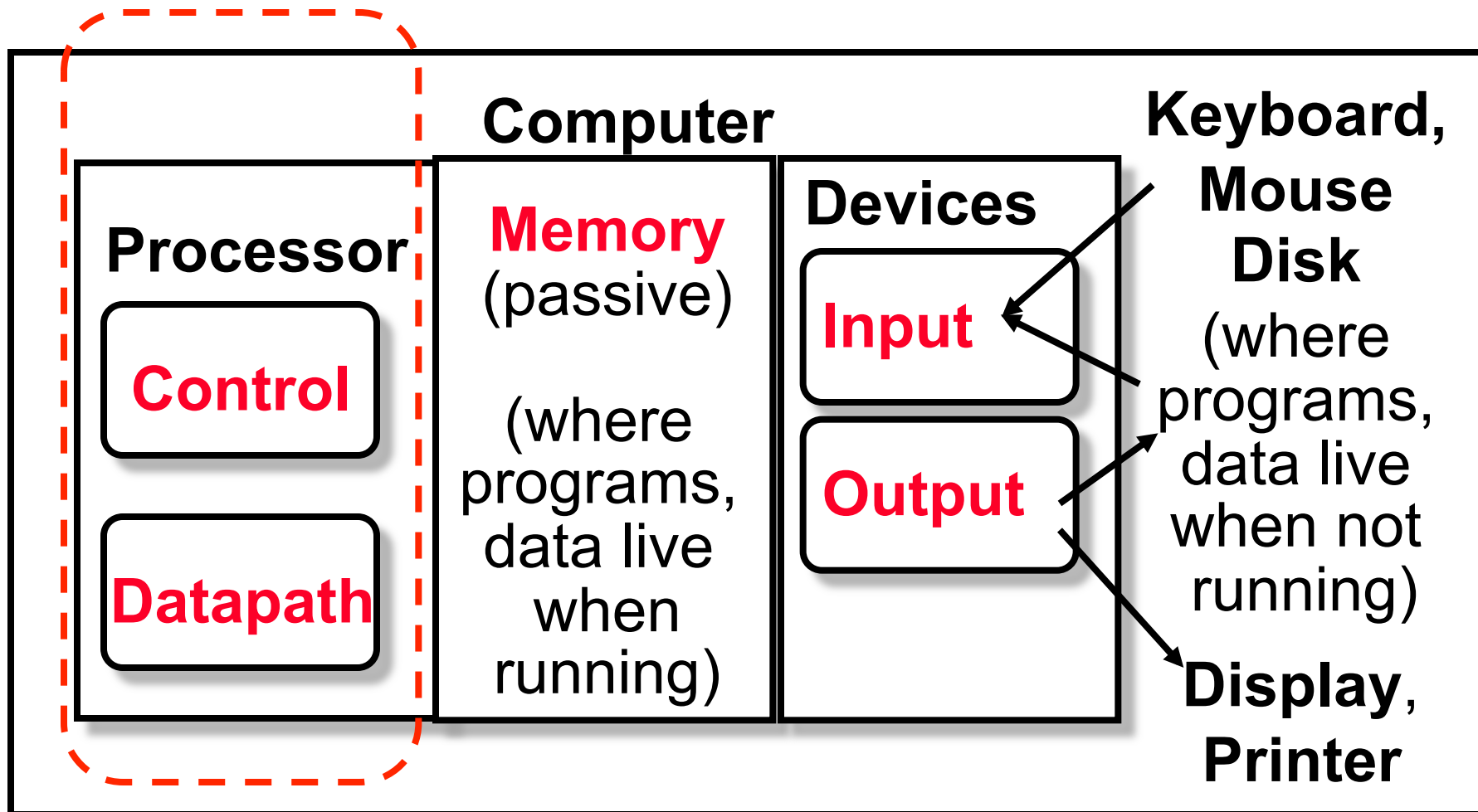

The CPU

- **Processor (CPU)**: the active part of the computer, which does all the work (data manipulation and decision-making)
- **Datapath**: portion of the processor which contains hardware necessary to perform operations required by the processor (the brawn)
- **Control**: portion of the processor (also in hardware) which tells the datapath what needs to be done (the brain)



Stages of the Datapath : Overview

- **Problem: a single, atomic block which “executes an instruction” (performs all necessary operations beginning with fetching the instruction) would be too bulky and inefficient**
- **Solution: break up the process of “executing an instruction” into **stages**, and then connect the stages to create the whole datapath**
 - **smaller stages are easier to design**
 - **easy to optimize (change) one stage without touching the others**



Stages of the Datapath (1/5)

- There is a wide variety of MIPS instructions: so what general steps do they have in common?
- Stage 1: **Instruction Fetch**
 - no matter what the instruction, the 32-bit instruction must first be fetched from memory (the cache-memory hierarchy)
 - also, this is where we **Increment PC** (that is, $PC = PC + 4$, to point to the next instruction: byte addressing so + 4)



Stages of the Datapath (2/5)

- **Stage 2: Instruction Decode**
 - upon fetching the instruction, we next gather data from the fields (decode all necessary instruction data)
 - first, read the opcode to determine instruction type and field lengths
 - second, read in data from all necessary registers
 - for add, read two registers
 - for addi, read one register
 - for jal, no reads necessary



Stages of the Datapath (3/5)

- **Stage 3: ALU (Arithmetic-Logic Unit)**
 - the real work of most instructions is done here: arithmetic (+, -, *, /), shifting, logic (&, |), comparisons (slt)
 - what about loads and stores?
 - `lw $t0, 40($t1)`
 - the address we are accessing in memory = the value in \$t1 PLUS the value 40
 - so we do this addition in this stage



Stages of the Datapath (4/5)

- **Stage 4: Memory Access**
 - actually only the load and store instructions do anything during this stage; the others remain idle during this stage or skip it all together
 - since these instructions have a unique step, we need this extra stage to account for them
 - as a result of the cache system, this stage is expected to be fast




Stages of the Datapath (5/5)

- **Stage 5: Register Write**
 - most instructions write the result of some computation into a register
 - examples: arithmetic, logical, shifts, loads, slt
 - what about stores, branches, jumps?
 - don't write anything into a register at the end
 - these remain idle during this fifth stage or skip it all together



Generic Steps of Datapath

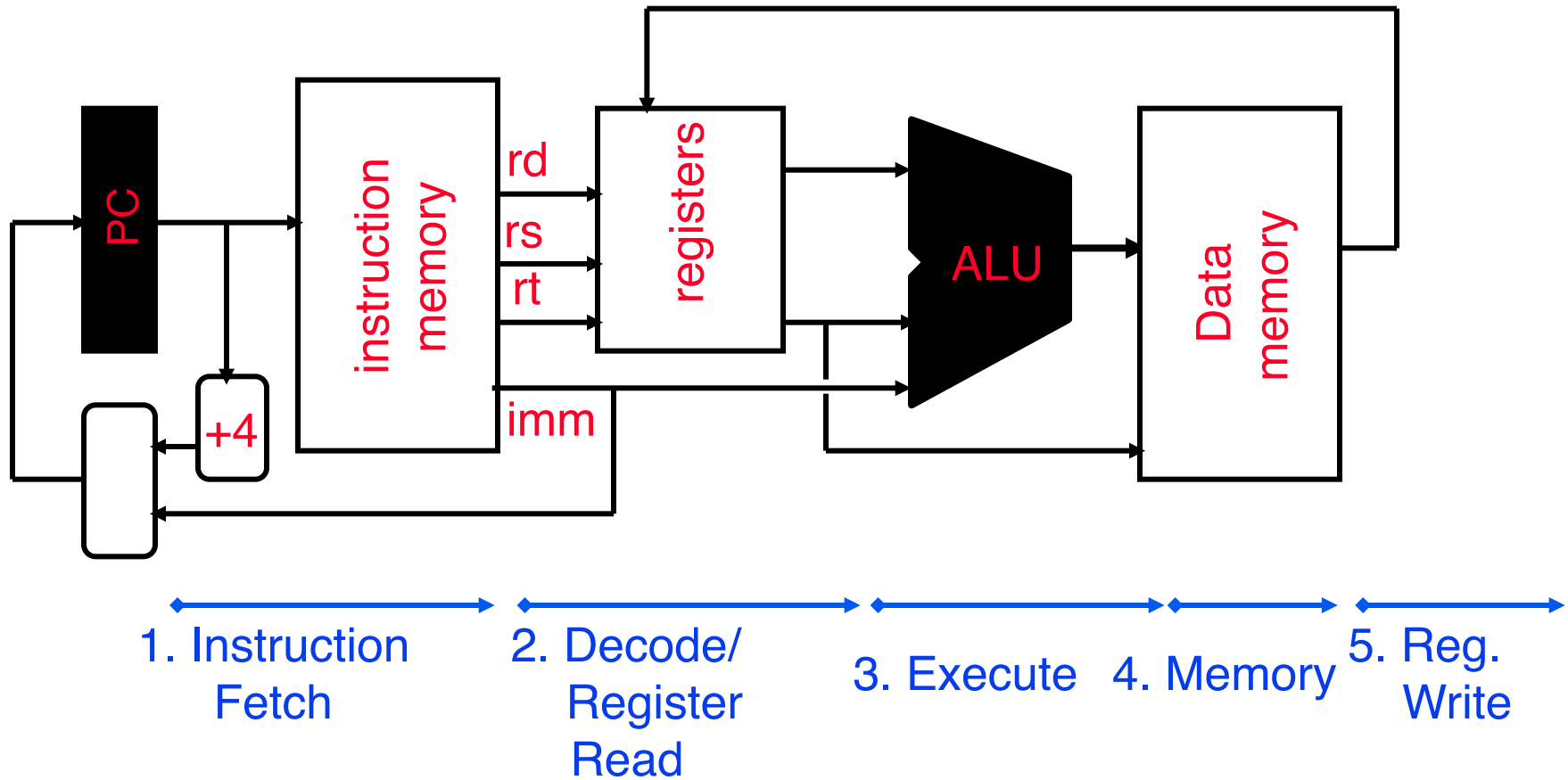


Datapath Walkthroughs (1/3)

- `add $r3, $r1, $r2 # r3 = r1+r2`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's an add, then read registers `$r1` and `$r2`
 - Stage 3: add the two values retrieved in Stage 2
 - Stage 4: idle (nothing to write to memory)
 - Stage 5: write result of Stage 3 into register `$r3`



Example: add Instruction

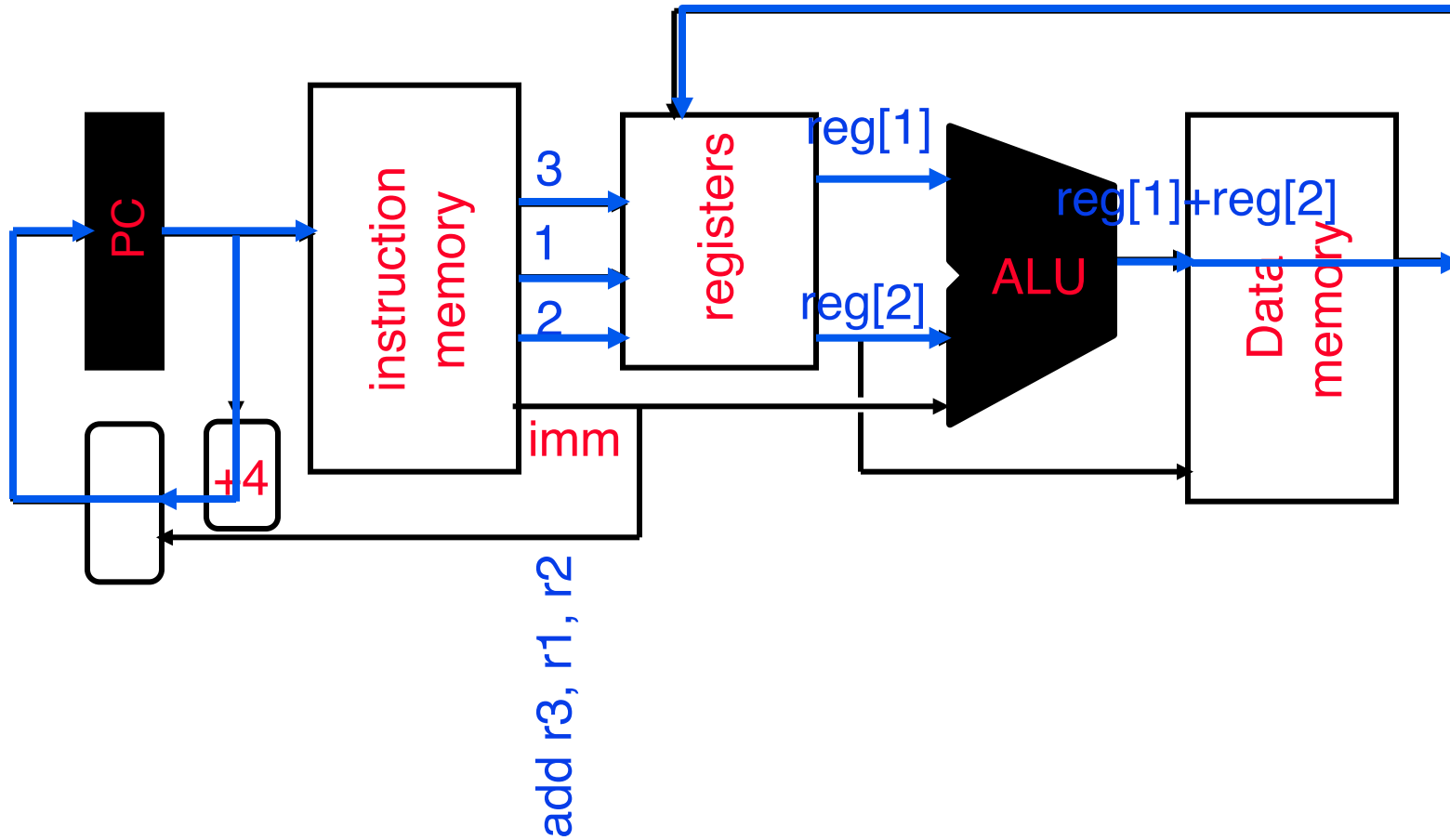


Datapath Walkthroughs (3/3)

- **sw \$r3, 17(\$r1)**
 - **Stage 1: fetch this instruction, inc. PC**
 - **Stage 2: decode to find it's a sw, then read registers \$r1 and \$r3**
 - **Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2)**
 - **Stage 4: write value in register \$r3 (retrieved in Stage 2) into memory address computed in Stage 3**
 - **Stage 5: idle (nothing to write into a register)**



Example: sw Instruction

 

Why Five Stages? (1/2)

- **Could we have a different number of stages?**
 - Yes, and other architectures do
- **So why does MIPS have five if instructions tend to idle for at least one stage?**
 - The five stages are the union of all the operations needed by all the instructions.
 - There is one type of instruction that uses all five stages: the **load**




Why Five Stages? (2/2)

- **lw \$r3, 17(\$r1)**
 - **Stage 1: fetch this instruction, inc. PC**
 - **Stage 2: decode to find it's a lw, then read register \$r1**
 - **Stage 3: add 17 to value in register \$r1 (retrieved in Stage 2)**
 - **Stage 4: read value from memory address compute in Stage 3**
 - **Stage 5: write value found in Stage 4 into register \$r3**




Example: lw Instruction

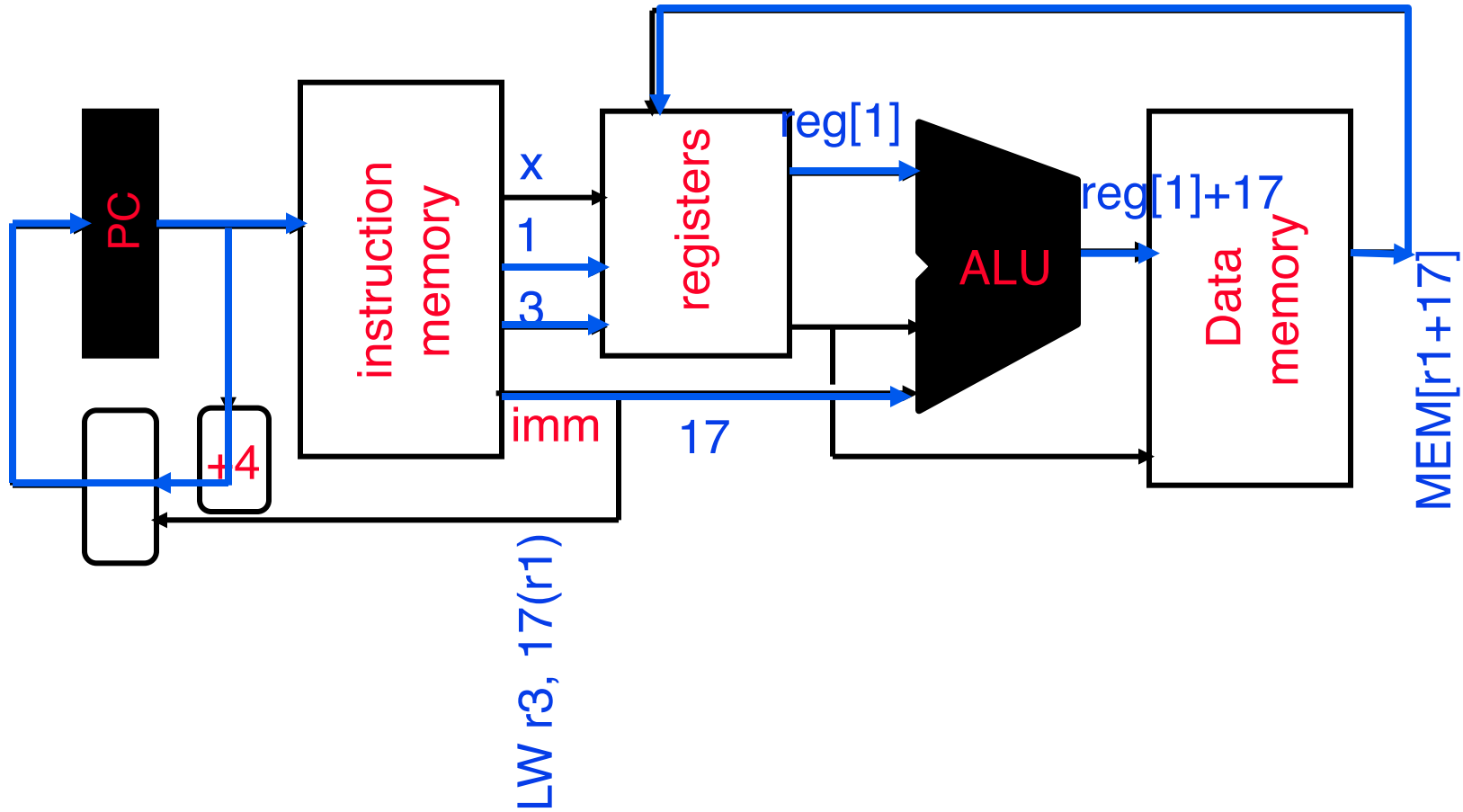

Datapath Summary

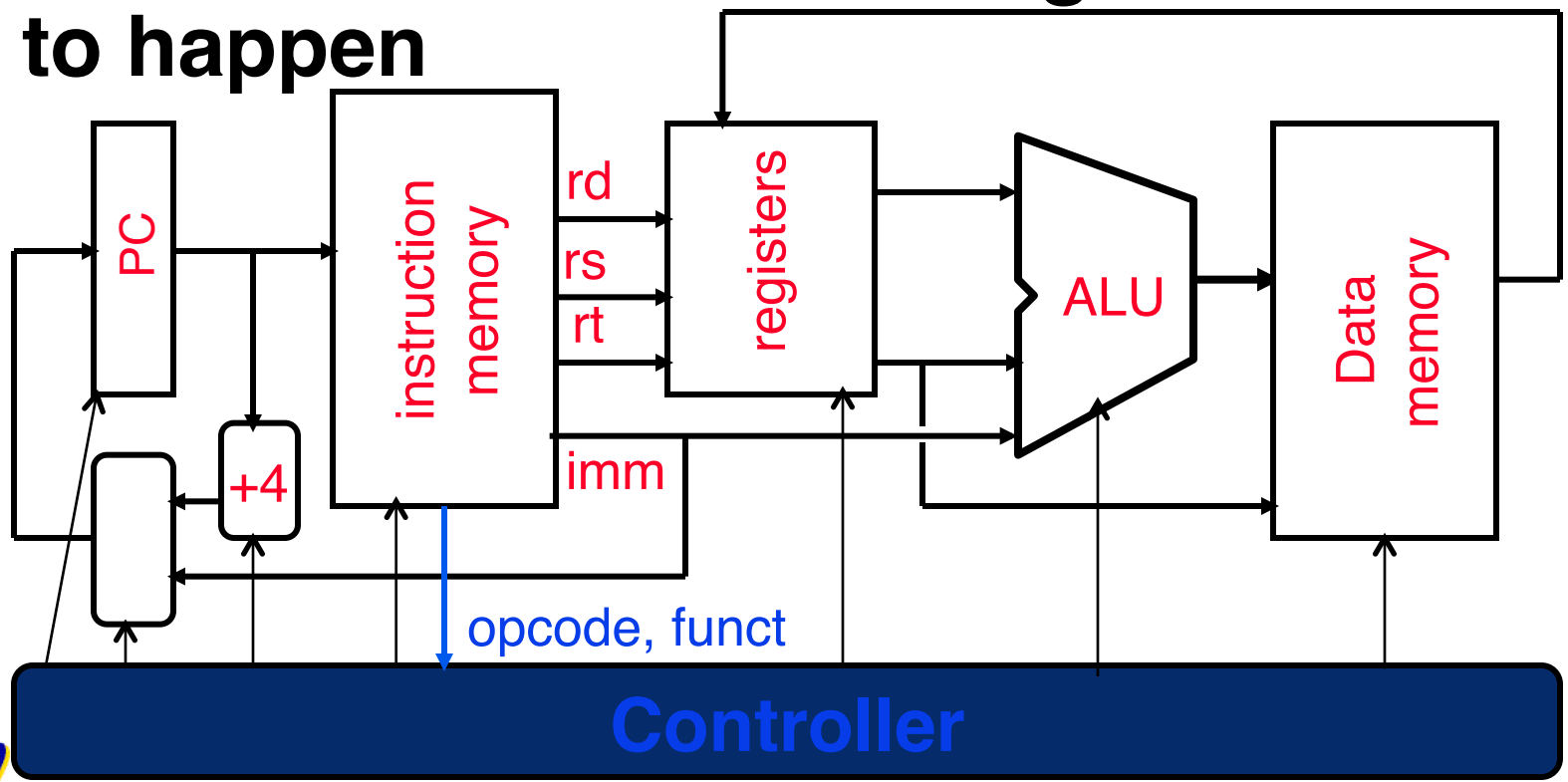
- The datapath based on data transfers required to perform instructions
- A controller causes the right transfers to happen



CPU clocking (1/2)

For each instruction, how do we control the flow of information through the datapath?

 
- **Single Cycle CPU: All stages of an instruction are completed within one long clock cycle.**
 - **The clock cycle is made sufficient long to allow each instruction to complete all stages without interruption and within one cycle.**



CPU clocking (2/2)

For each instruction, how do we control the flow of information through the datapath?

 - **Multiple-cycle CPU: Only one stage of instruction per clock cycle.**
 - The clock is made as long as the **slowest** stage.



- **Several significant advantages over single cycle execution: Unused stages in a particular instruction can be skipped OR instructions can be pipelined (overlapped).**




How to Design a Processor: step-by-step

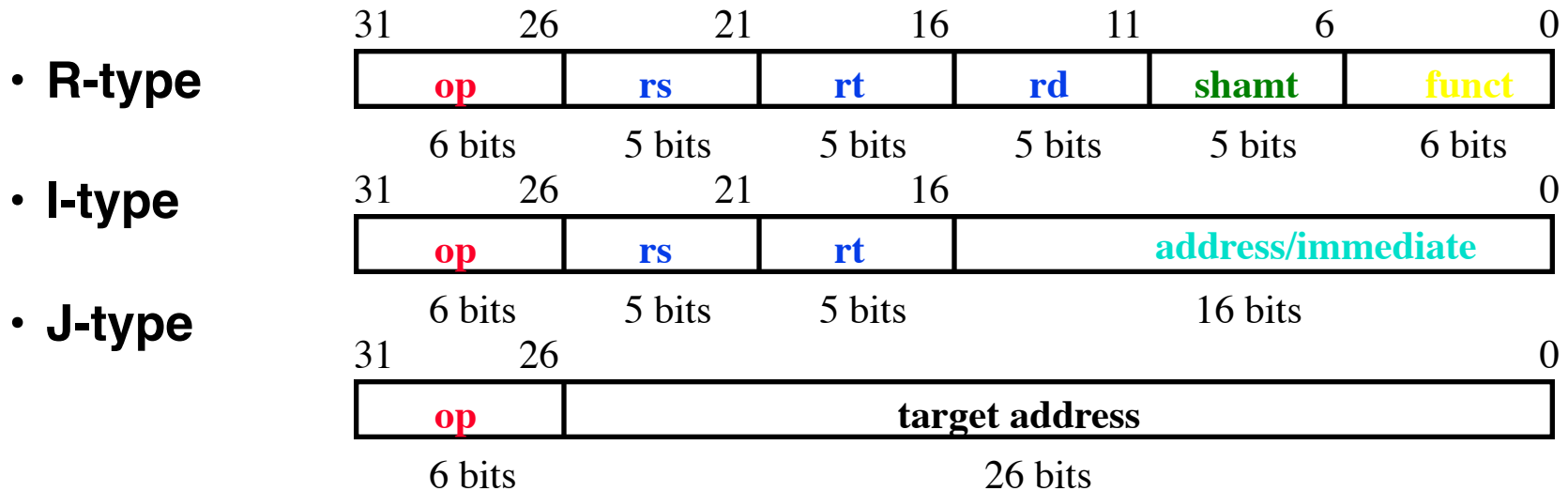- **1. Analyze instruction set architecture (ISA)**
⇒ datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic (hard part!)



Review: The MIPS Instruction Formats

- All MIPS instructions are 32 bits long. 3 formats:



- The different fields are:
 - op**: operation (“opcode”) of the instruction
 - rs, rt, rd**: the source and destination register specifiers
 - shamt**: shift amount
 - funct**: selects the variant of the operation in the “op” field
 - address / immediate**: address offset or immediate value
 - target address**: target address of jump instruction




The MIPS-lite Subset for today

- **ADDU and SUBU**


- `addu rd,rs,rt`

- `subu rd,rs,rt`

 

- **OR Immediate:**


- `ori rt,rs,imm16`

 

- **LOAD and STORE Word**


- `lw rt,rs,imm16`

- `sw rt,rs,imm16`

 

- **BRANCH:**

- `beq rs,rt,imm16`

 

ALU Needs for MIPS-lite + Rest of MIPS

- **Addition, subtraction, logical OR, ==:**

ADDU `R[rd] = R[rs] + R[rt]; ...`

SUBU `R[rd] = R[rs] - R[rt]; ...`

ORI `R[rt] = R[rs] | zero_ext(Imm16) ...`

BEQ `if (R[rs] == R[rt]) ...`

- **Test to see if output == 0 for any ALU operation gives == test. How?**
- **P&H also adds AND,
Set Less Than (1 if $A < B$, 0 otherwise)**



ALU follows chap 5

How to Design a Processor: step-by-step

- 1. Analyze instruction set architecture (ISA)
⇒ datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. **Select set of datapath components and establish clocking methodology**
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic (hard part!)



What Hardware Is Needed? (1/2)

- **PC: a register which keeps track of memory addr of the next instruction**
- **General Purpose Registers**
 - used in Stages 2 (Read) and 5 (Write)
 - MIPS has 32 of these
- **Memory**
 - used in Stages 1 (Fetch) and 4 (R/W)
 - cache system makes these two stages as fast as the others, on average




What Hardware Is Needed? (2/2)

- **ALU**
 - used in Stage 3
 - something that performs all necessary functions: arithmetic, logicals, etc.
 - we'll design details later
- **Miscellaneous Registers**
 - In implementations with only one stage per clock cycle, registers are inserted between stages to hold intermediate data and control signals as they travel from stage to stage.
 - Note: Register is a general purpose term meaning something that stores bits. Not all registers are in the “register file”.




Combinational Logic Elements (Building Blocks)


- Adder

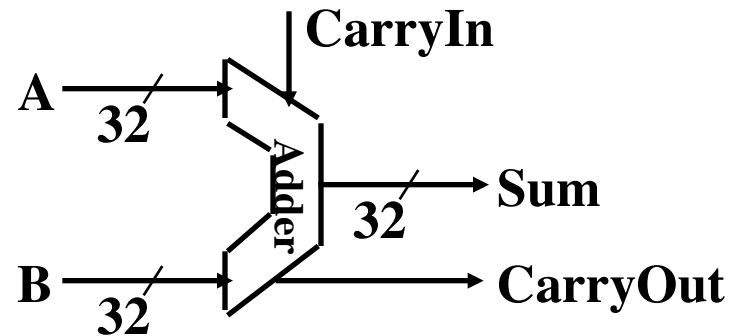

- MUX

 

- ALU

 

Storage Element: Idealized Memory

- **Memory (idealized)**

- One input bus: Data In
- One output bus: Data Out


- **Memory word is found by:**

- Address selects the word to put on Data Out
- Write Enable = 1: address selects the memory word to be written via the Data In bus

- **Clock input (CLK)**

- The CLK input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:

 - Address valid \Rightarrow Data Out valid after “access time.”




Storage Element: Register (Building Block)

- **Similar to D Flip Flop except**

- N-bit input and output
- Write Enable input

- **Write Enable:**

 
- negated (or deasserted) (0):
Data Out will not change
- asserted (1):
Data Out will become Data In on positive edge of clock



Storage Element: Register File

- **Register File consists of 32 registers:**

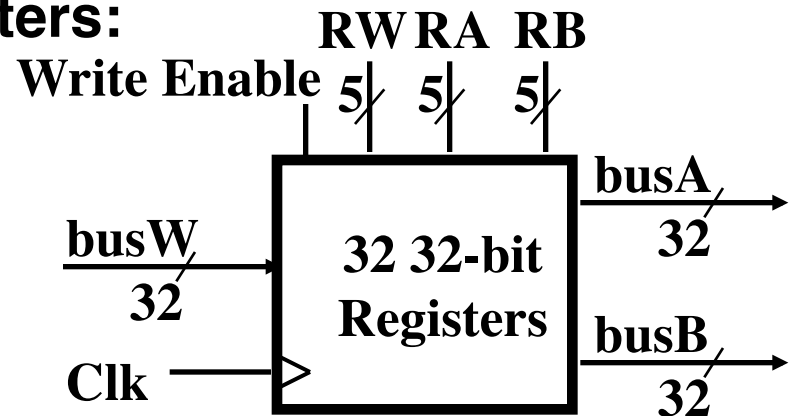- Two 32-bit output busses:
busA and busB
- One 32-bit input bus: busW



- **Register is selected by:**

- RA (number) selects the register to put on busA (data)
- RB (number) selects the register to put on busB (data)
- RW (number) selects the register to be written via busW (data) when Write Enable is 1

- **Clock input (clk)**

- The clk input is a factor **ONLY** during write operation
- During read operation, behaves as a combinational logic block:
 - RA or RB valid \Rightarrow busA or busB valid after “access time.”




How to Design a Processor: step-by-step

 - 1. Analyze instruction set architecture (ISA)
⇒ datapath requirements
 - meaning of each instruction is given by the *register transfers*
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. **Assemble** datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic (hard part!)




Overview of the Instruction Fetch Unit

- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump: $\text{PC} \leftarrow \text{“something else”}$




Add & Subtract

 - $R[rd] = R[rs] \text{ op } R[rt]$ Ex.: `addU rd,rs,rt`
 - Ra, Rb, and Rw come from instruction's Rs, Rt, and Rd fields
 - ALUctr and RegWr: control logic after decoding the instruction




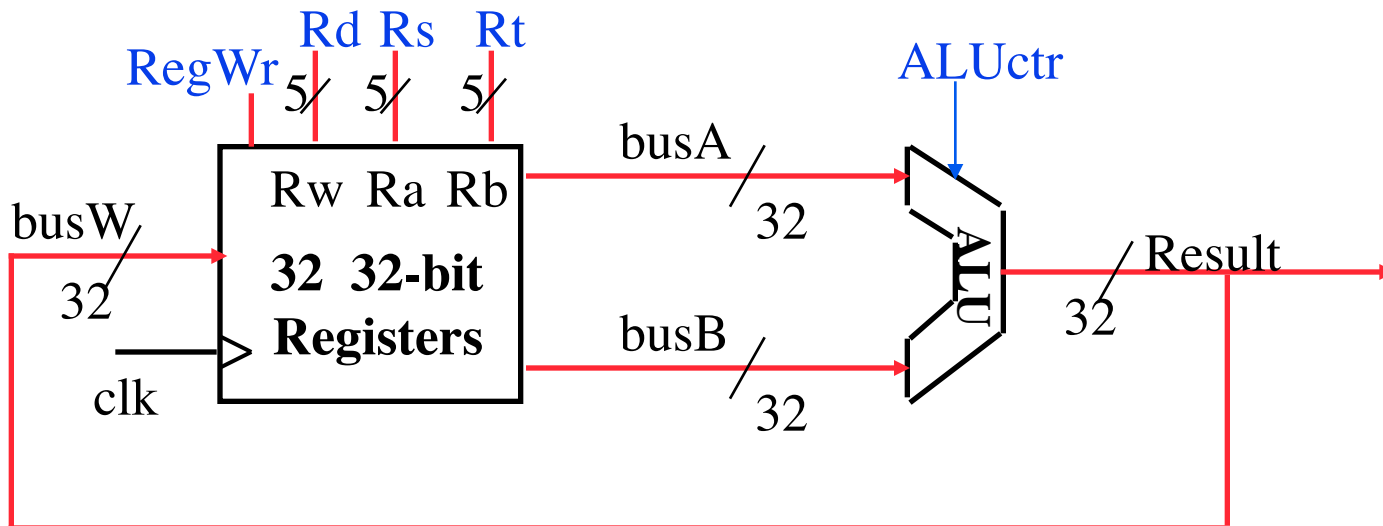- ... Already defined the register file & ALU




Logical Operations with Immediate

 - $R[rt] = R[rs] \text{ op ZeroExt}[imm16]$




But we're writing to Rt register??

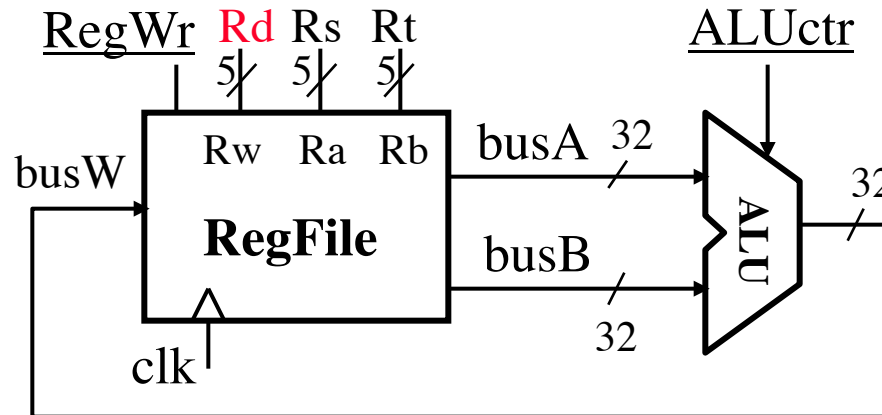


Logical Operations with Immediate

 - $R[rt] = R[rs] \text{ op } \text{ZeroExt}[\text{imm16}]$



What about Rt register read??


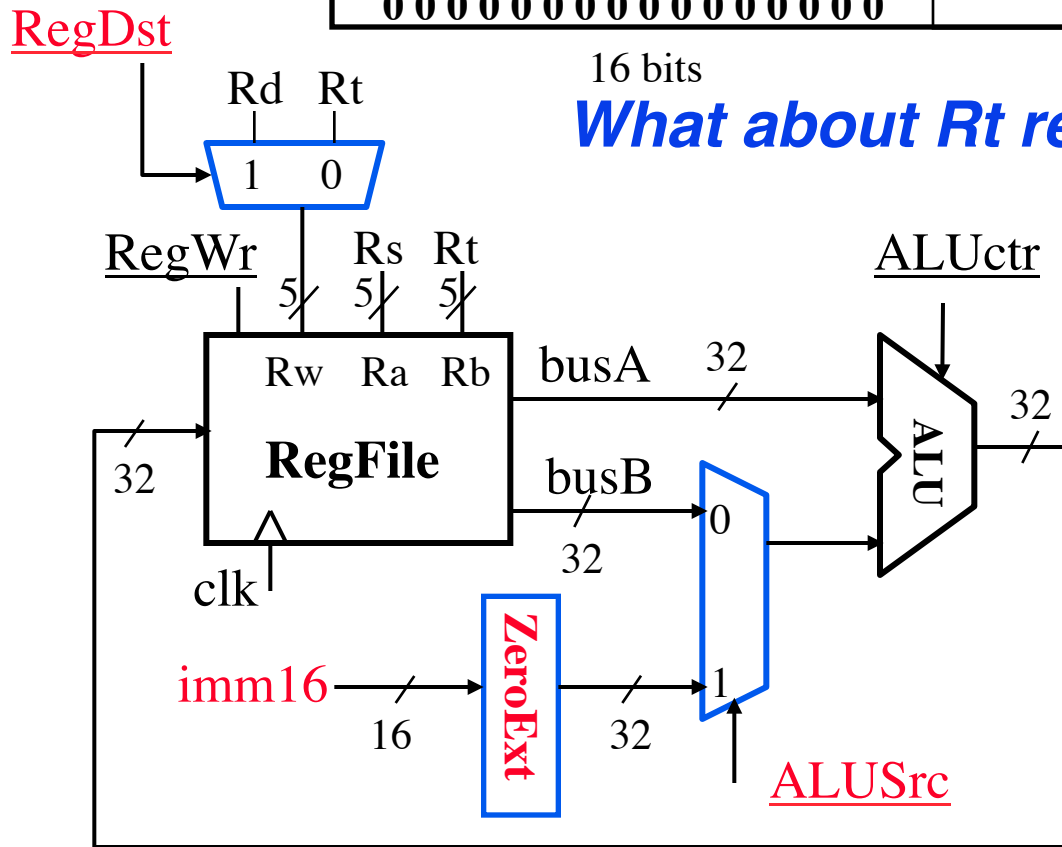


- **Already defined 32-bit MUX; Zero Ext?**





Load Operations

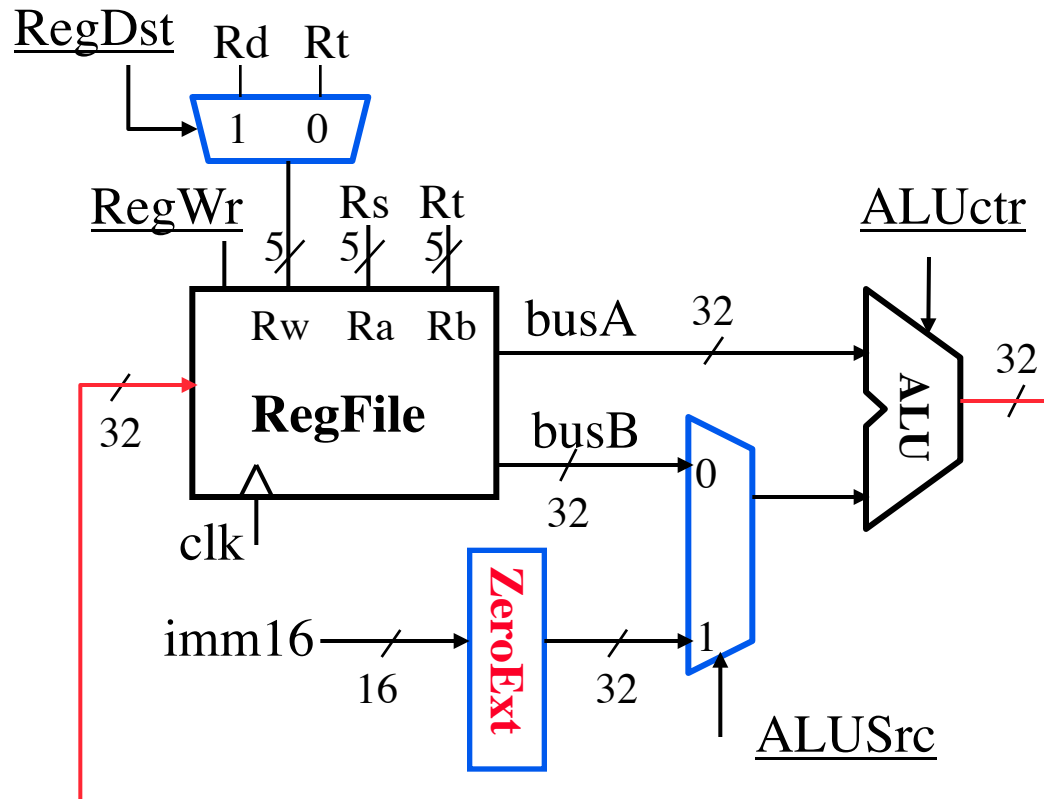 - $R[rt] = \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$
Example: lw rt, rs, imm16





Load Operations

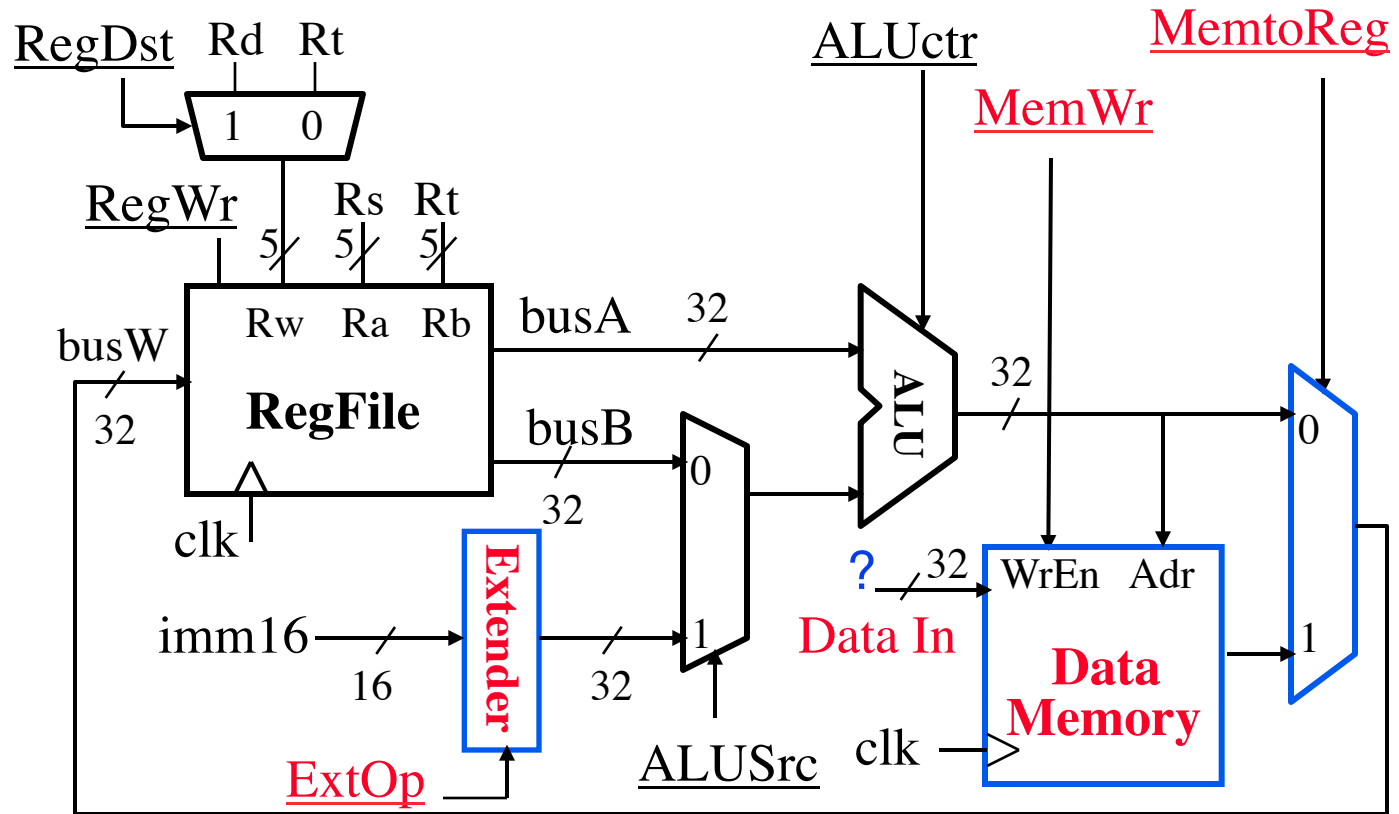 - $R[rt] = Mem[R[rs] + SignExt[imm16]]$
Example: lw rt, rs, imm16





Store Operations

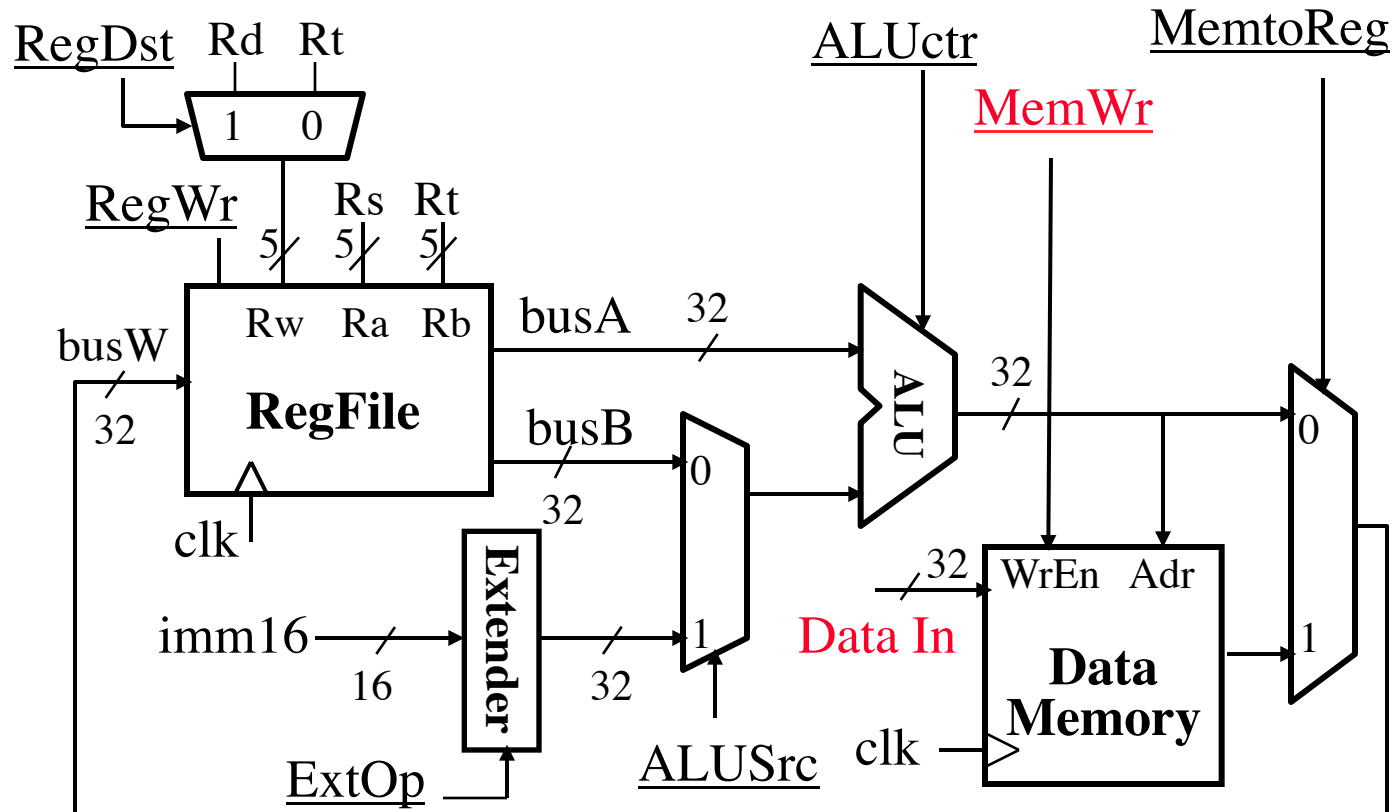 - $\text{Mem}[\text{R}[\text{rs}] + \text{SignExt}[\text{imm16}]] = \text{R}[\text{rt}]$
Ex.: sw rt, rs, imm16




Store Operations

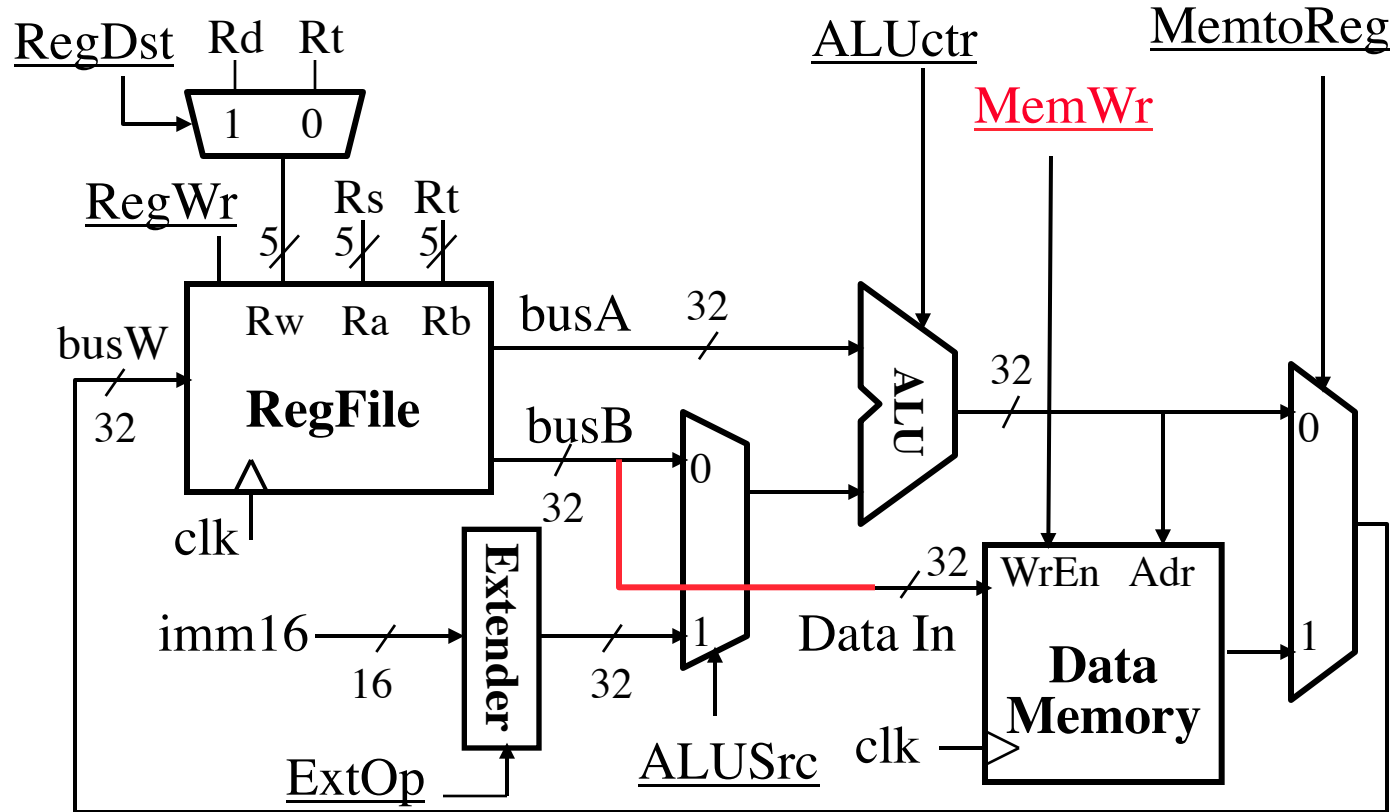 - $\text{Mem}[R[\text{rs}] + \text{SignExt}[\text{imm16}]] = R[\text{rt}]$
Ex.: sw rt, rs, imm16



The Branch Instruction

 

beq rs, rt, imm16

- **mem[PC] Fetch the instruction from memory**
- **Equal = R[rs] == R[rt] Calculate branch condition**
- **if (Equal) Calculate the next instruction's address**
 - **PC = PC + 4 + (SignExt(imm16) x 4)**


else

- **PC = PC + 4**




Datapath for Branch Operations

 - **beq** rs, rt, imm16
Datapath generates condition (equal)




Inst Address

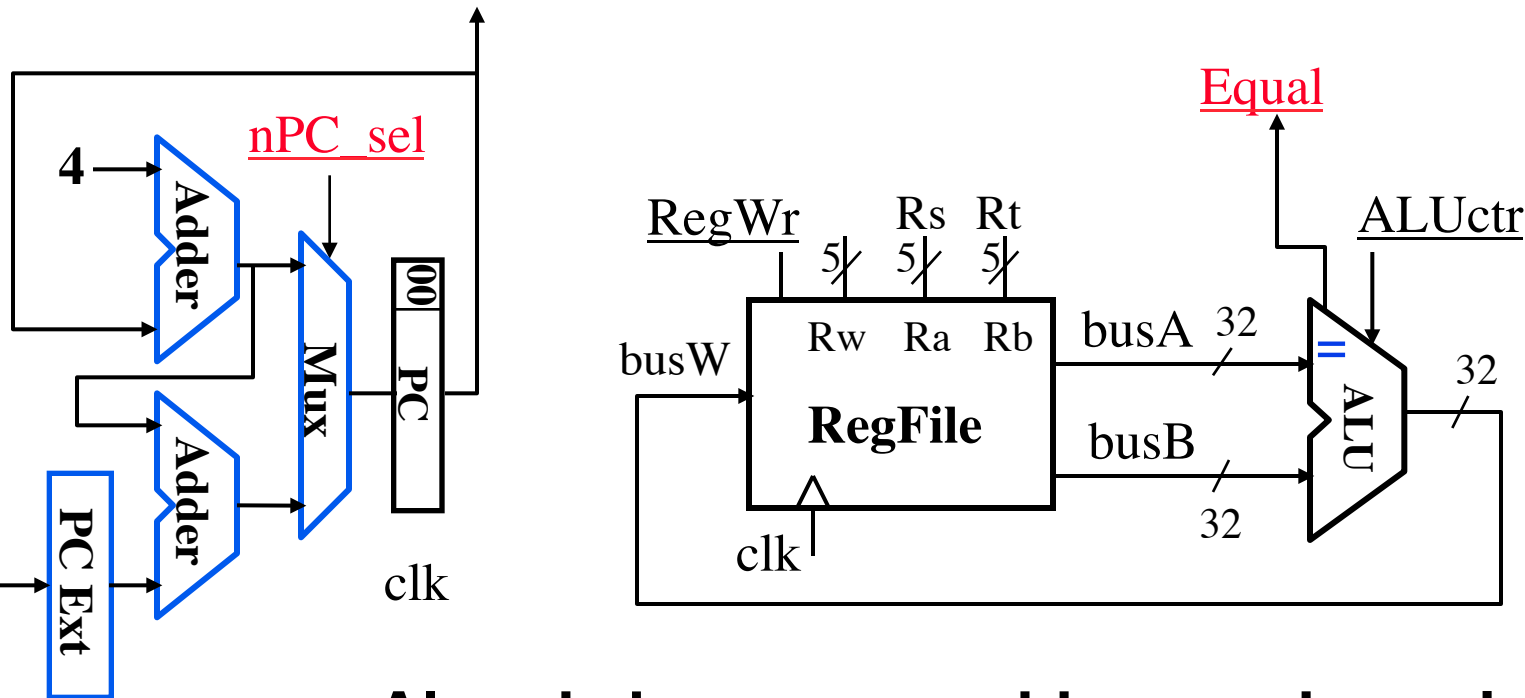


Already have mux, adder, need special sign extender for PC, need equal compare (sub?)



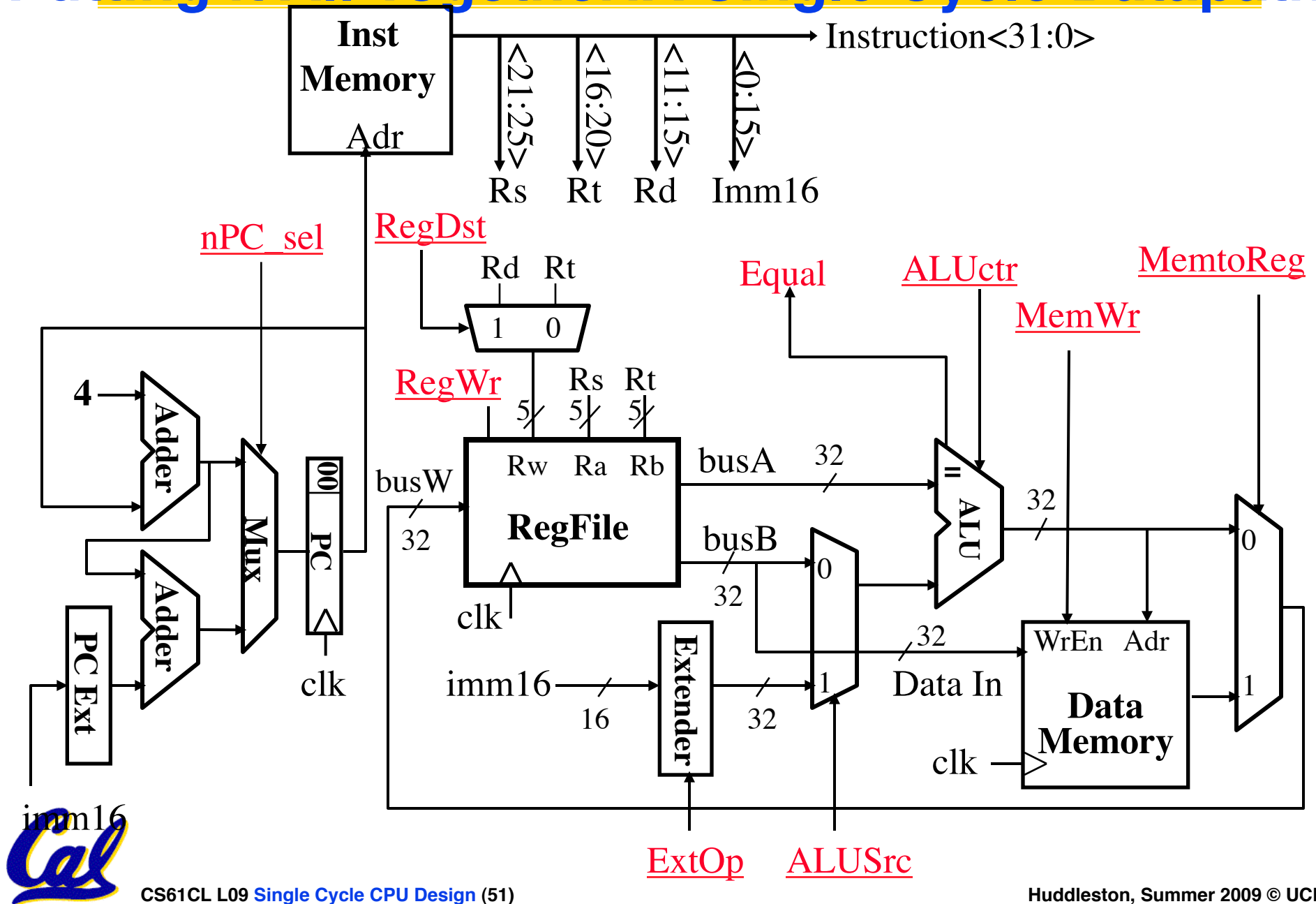Putting it All Together: A Single Cycle Datapath




An Abstract View of the Implementation

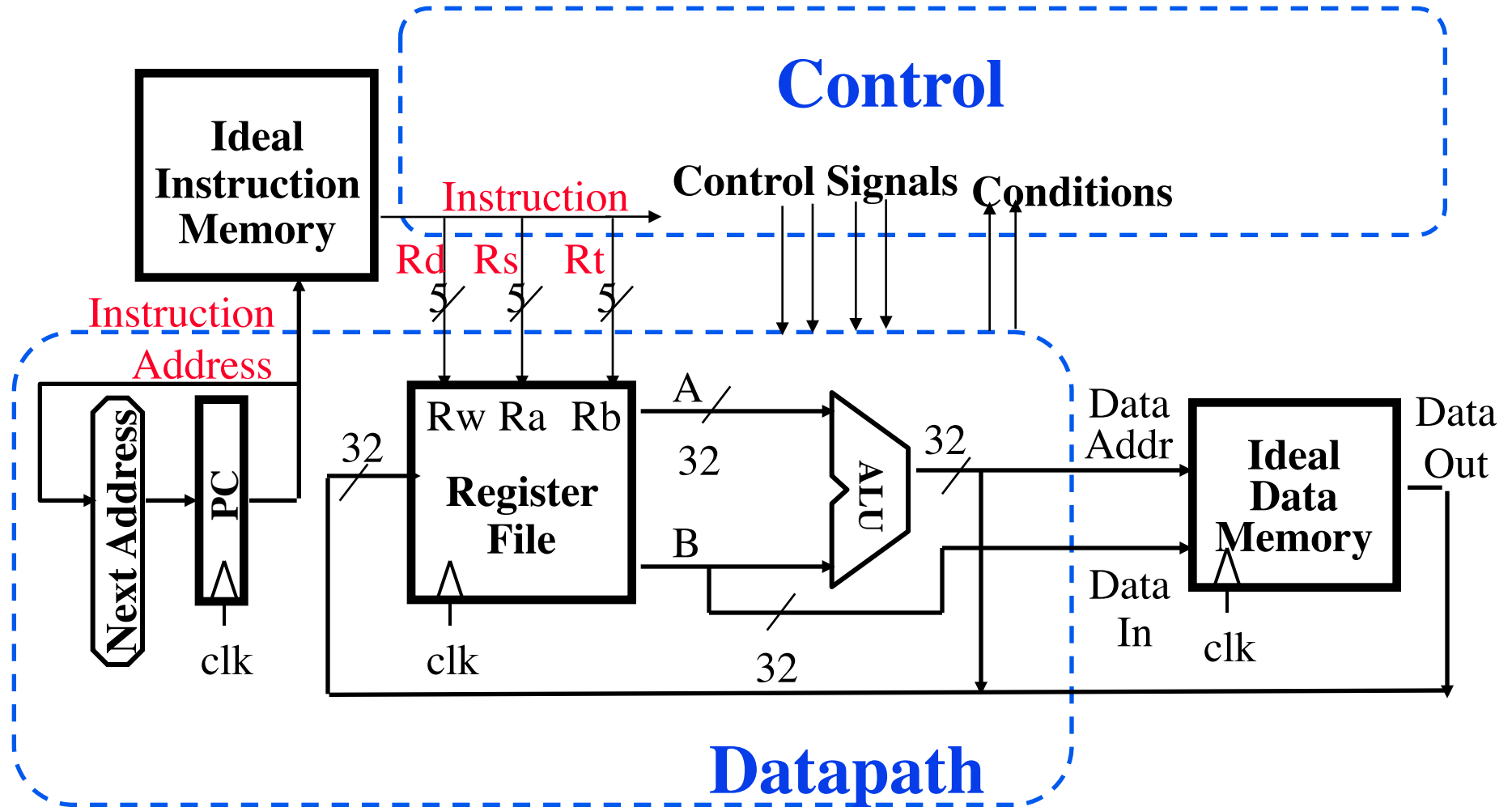

Summary: A Single Cycle Datapath

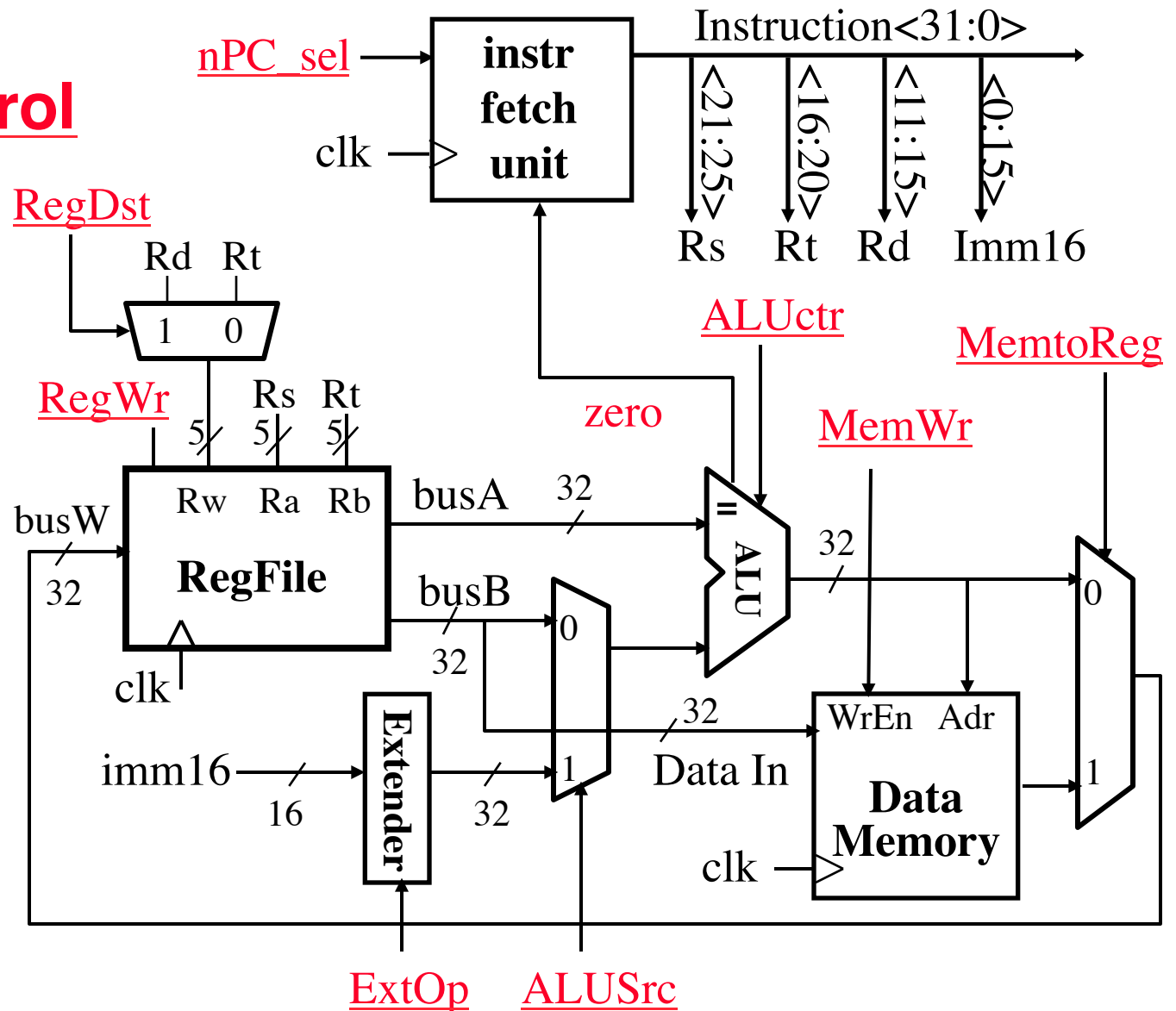- We have everything except control signals



“And In conclusion...”

- **N-bit adder-subtractor done using N 1-bit adders with XOR gates on input**
 - **XOR serves as conditional inverter**
- **CPU design involves Datapath, Control**
 - **Datapath in MIPS involves 5 CPU stages**
 1. **Instruction Fetch**
 2. **Instruction Decode & Register Read**
 3. **ALU (Execute)**
 4. **Memory**
 5. **Register Write**



Bonus slides

- **These are extra slides that used to be included in lecture notes, but have been moved to this, the “bonus” area to serve as a supplement.**
- **The slides will appear in the order they would have in the normal presentation**

Bonus



Review of Timing Terms


- **Clock (CLK)** - steady square wave that synchronizes system
- **Setup Time** - when the input must be stable before the rising edge of the CLK
- **Hold Time** - when the input must be stable after the rising edge of the CLK
- **“CLK-to-Q” Delay** - how long it takes the output to change, measured from the rising edge
- **Flip-flop** - one bit of state that samples every rising edge of the CLK
- **Register** - several bits of state that samples on rising edge of CLK or on LOAD



What about overflow?

- Consider a 2-bit signed # & overflow:

 - 10 = -2 + -2 or -1
- 11 = -1 + -2 only
- 00 = 0 NOTHING!
- 01 = 1 + 1 only



- Highest adder

- $C_1 = \text{Carry-in} = C_{in}$, $C_2 = \text{Carry-out} = C_{out}$
- No C_{out} or $C_{in} \Rightarrow$ NO overflow!

What op? • C_{in} and $C_{out} \Rightarrow$ NO overflow!

• C_{in} but no $C_{out} \Rightarrow A, B$ both > 0 , overflow!


• C_{out} but no $C_{in} \Rightarrow A, B$ both < 0 , overflow!



What about overflow?

- Consider a 2-bit signed # & overflow:

10 = -2
11 = -1
00 = 0
01 = 1

 


- Overflows when...

- C_{in} , but no $C_{out} \Rightarrow A, B$ both > 0 , overflow!
- C_{out} , but no $C_{in} \Rightarrow A, B$ both < 0 , overflow!

$$\text{overflow} = c_n \text{ XOR } c_{n-1}$$



Extremely Clever Subtractor

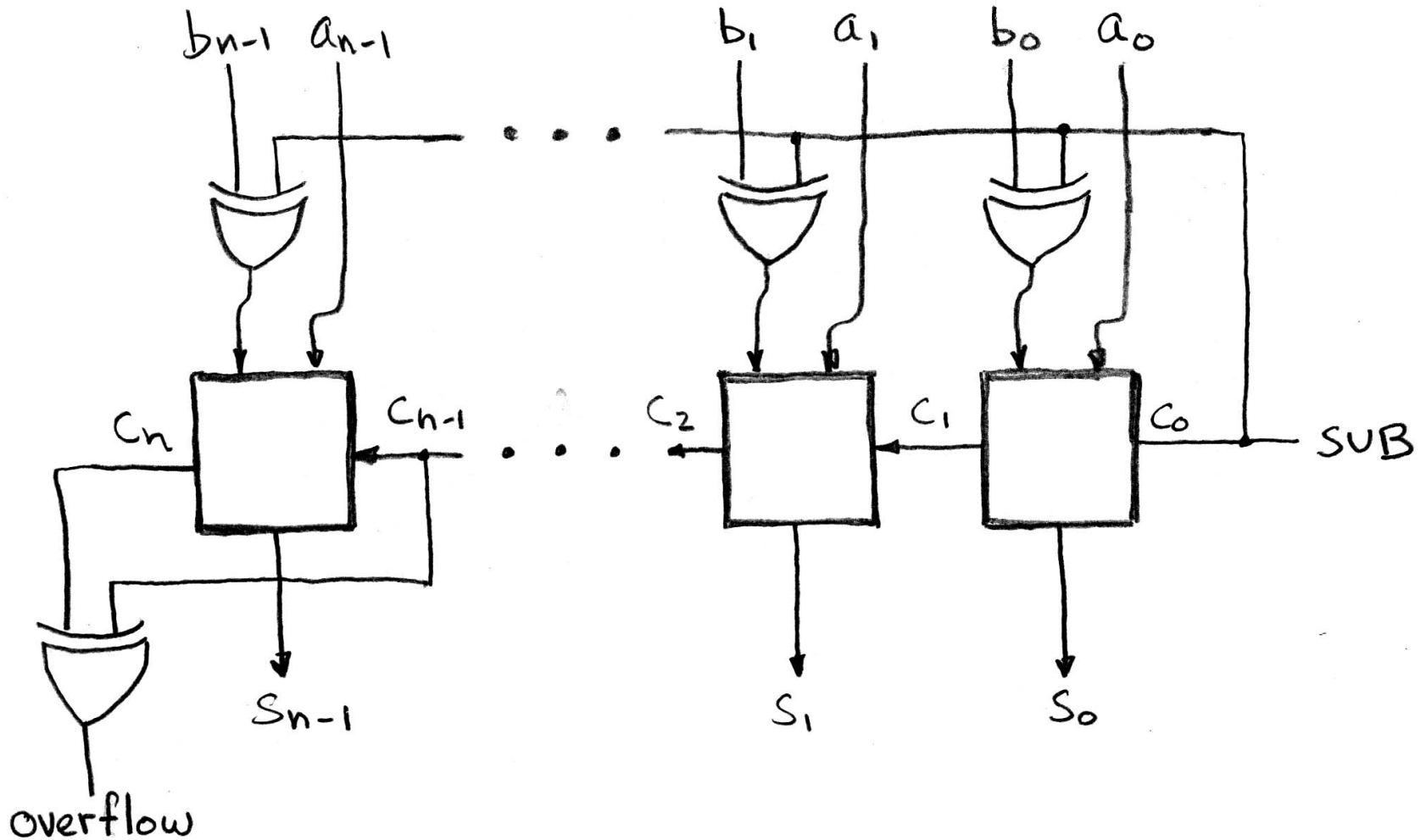


Datapath Walkthroughs (2/3)


- `slti $r3, $r1, 17`
 - Stage 1: fetch this instruction, inc. PC
 - Stage 2: decode to find it's an `slt`, then read register `$r1`
 - Stage 3: compare value retrieved in Stage 2 with the integer 17
 - Stage 4: idle
 - Stage 5: write the result of Stage 3 in register `$r3`



Example: `slti` Instruction

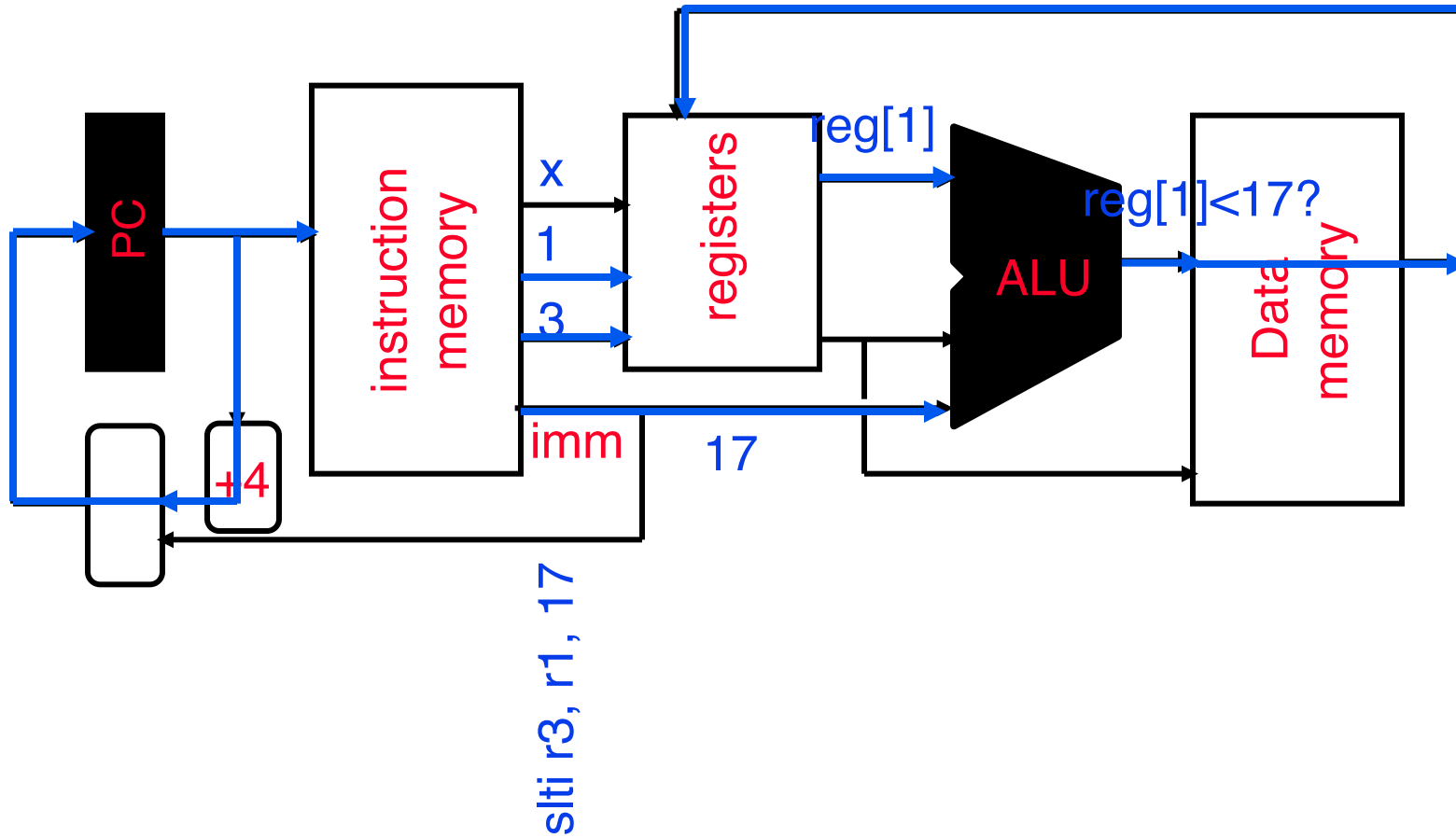

Clocking Methodology

 

- **Storage elements clocked by same edge**
- **Being physical devices, flip-flops (FF) and combinational logic have some delays**
 - **Gates: delay from input change to output change**
 - **Signals at FF D input must be stable before active clock edge to allow signal to travel within the FF (set-up time), and we have the usual clock-to-Q delay**
- **“Critical path” (longest path through logic) determines length of clock period**



An Abstract View of the Critical Path

**Critical Path (Load Instruction) =
Delay clock through PC (FFs) +
Instruction Memory's Access Time +
Register File's Access Time, +
ALU to Perform a 32-bit Add +
Data Memory Access Time +
Stable Time for Register File Write**

(Assumes a fast controller)

