

Lecture #9 – Single Cycle CPU Design

2009-07-22




Jeremy Huddleston




Review: A Single Cycle Datapath

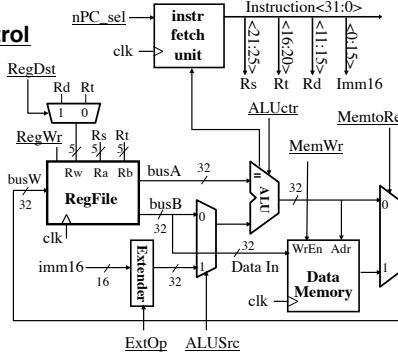- We have everything except control signals




Recap: Meaning of the Control Signals

 - nPC_sel: “n”=next
 “+4” 0 ⇒ PC ← PC + 4
 “br” 1 ⇒ PC ← PC + 4 + {SignExt(Imm16), 00}
- Later in lecture: higher-level connection between mux and branch condition




Recap: Meaning of the Control Signals

 - ExtOp: “zero”, “sign”
- ALUSrc: 0 ⇒ regB; 1 ⇒ immed
- ALUctr: “ADD”, “SUB”, “OR”
- MemWr: 1 ⇒ write memory
- MemtoReg: 0 ⇒ ALU; 1 ⇒ Mem
- RegDst: 0 ⇒ “rt”; 1 ⇒ “rd”
- RegWr: 1 ⇒ write register




Instruction Fetch Unit at the Beginning of Add

 - Fetch the instruction from Instruction memory: Instruction = MEM[PC]
- same for all instructions




The Single Cycle Datapath during Add

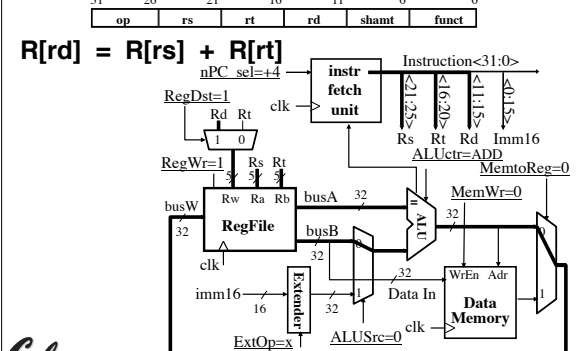


Instruction Fetch Unit at the End of Add

 - PC = PC + 4
- This is the same for all instructions except: Branch and Jump




Single Cycle Datapath during Or Immediate?

- R[rt] = R[rs] OR ZeroExt[Imm16]

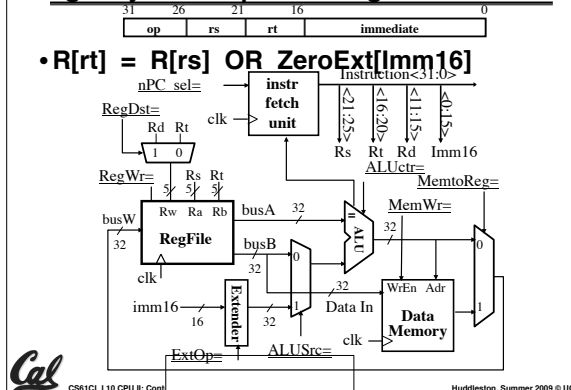


Single Cycle Datapath during Or Immediate?

- R[rt] = R[rs] OR ZeroExt[Imm16]

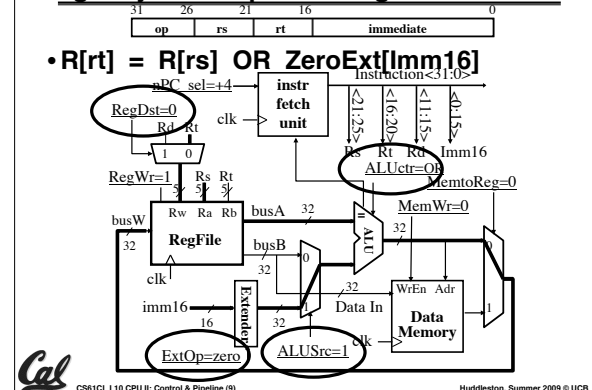

The Single Cycle Datapath during Load?

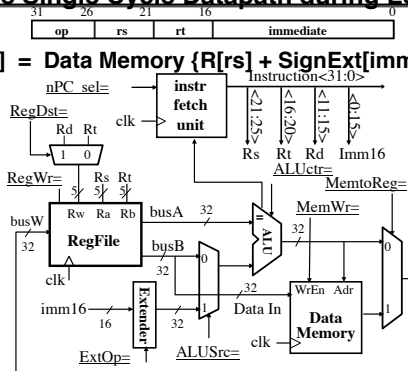- $R[rt] = \text{Data Memory}\{R[rs] + \text{SignExt}[\text{imm16}]\}$




Cal

CS61CL L10 CPU II: Control & Pipeline (10)

Huddleston, Summer 2009 © UCB

The Single Cycle Datapath during Load

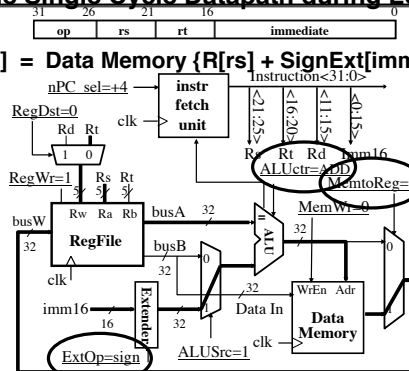- $R[rt] = \text{Data Memory}\{R[rs] + \text{SignExt}[\text{imm16}]\}$




Cal

CS61CL L10 CPU II: Control & Pipeline (11)

Huddleston, Summer 2009 © UCB

The Single Cycle Datapath during Store?

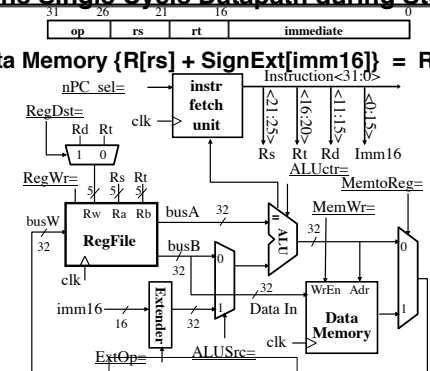- $\text{Data Memory}\{R[rs] + \text{SignExt}[\text{imm16}]\} = R[rt]$




Cal

CS61CL L10 CPU II: Control &

Huddleston, Summer 2009 © UCB

The Single Cycle Datapath during Store

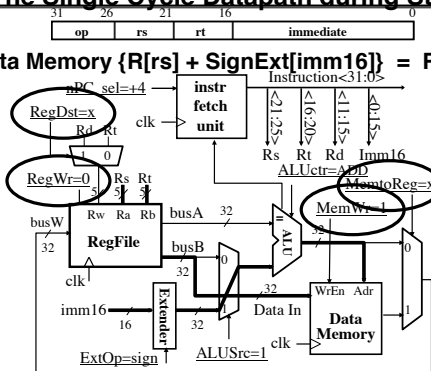- $\text{Data Memory}\{R[rs] + \text{SignExt}[\text{imm16}]\} = R[rt]$




Cal

CS61CL L10 CPU II: Control & Pipeline (13)

Huddleston, Summer 2009 © UCB

The Single Cycle Datapath during Branch?

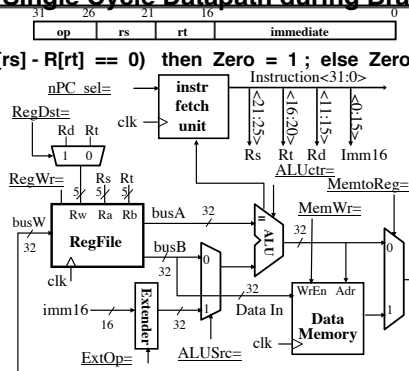- if $(R[rs] - R[rt]) == 0$ then Zero = 1 ; else Zero = 0




Cal

CS61CL L10 CPU II: Control & Pipeline (14)

Huddleston, Summer 2009 © UCB

The Single Cycle Datapath during Branch

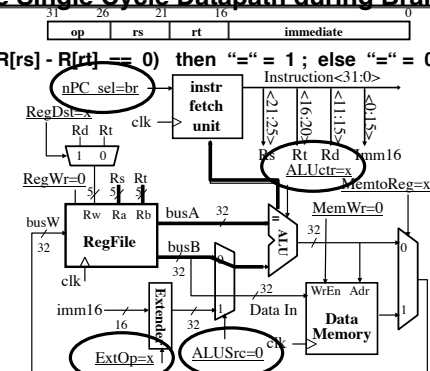- if $(R[rs] - R[rt]) == 0$ then "=" = 1 ; else "=" = 0




Cal

CS61CL L10 CPU II: Control & Pipeline (15)

Huddleston, Summer 2009 © UCB

Instruction Fetch Unit at the End of Branch

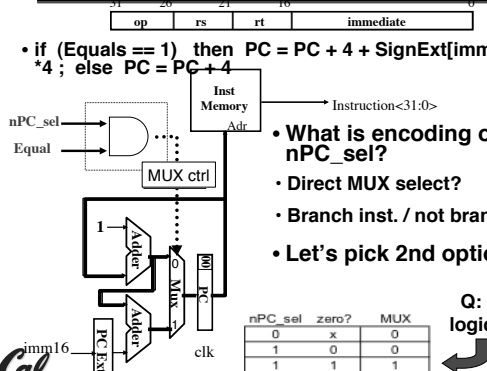- if $(\text{Equals} == 1)$ then $\text{PC} = \text{PC} + 4 + \text{SignExt}[\text{imm16}] * 4$; else $\text{PC} = \text{PC} + 4$



- What is encoding of nPC_sel?
- Direct MUX select?
- Branch inst. / not branch
- Let's pick 2nd option

Q: What logic gate?

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1

Cal

CS61CL L10 CPU II: Control & Pipeline (16)

Huddleston, Summer 2009 © UCB

How to Design a Processor: step-by-step


1. Analyze instruction set architecture (ISA)
 - ⇒ datapath requirements
 - meaning of each instruction is given by the register transfers
 - datapath must include storage element for ISA registers
 - datapath must support each register transfer
2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic (hard part!)

Cal

CS61CL L10 CPU II: Control & Pipeline (17)

Huddleston, Summer 2009 © UCB

Step 4: Given Datapath: RTL → Control

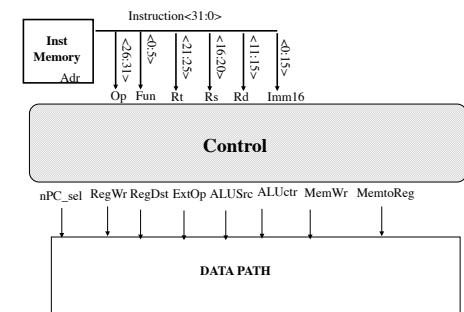

Cal

CS61CL L10 CPU II: Control & Pipeline (18)

Huddleston, Summer 2009 © UCB

A Summary of the Control Signals

See Appendix A

	func	10 0000	10 0010	We Don't Care :-)				00 0010	00 0010
op		00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010	
		add	sub	ori	lw	sw	beq	jump	
RegDst		1	1	0	0	x	x	x	
ALUSrc		0	0	1	1	1	0	x	
MemoReg		0	0	0	1	x	x	x	
RegWrite		1	1	1	1	0	0	0	
MemWrite		0	0	0	0	1	0	0	
nPCsel		0	0	0	0	0	1	?	
Jump		0	0	0	0	0	0	1	
ExtOp		x	x	x	0	1	x	x	
ALUctr<2:0>		Add	Subtract	Or	Add	Add	Subtract	x	

R-type	op	rs	rt	rd	shamt	funct	add, sub
I-type	op	rs	rt	immediate			ori, lw, sw, beq
J-type	op	target address					jump



Boolean Expressions for Controller

RegDst = add + sub
 ALUSrc = ori + lw + sw
 MemoReg = lw
 RegWrite = add + sub + ori + lw
 MemWrite = sw
 nPCsel = beq
 Jump = jump
 ExtOp = lw + sw
 ALUctr[0] = sub + beq (assume ALUctr is 0 ADD, 01: SUB, 10: OR)
 ALUctr[1] = or

where,


$rtype = \sim op_5 * \sim op_4 * \sim op_3 * \sim op_2 * \sim op_1 * \sim op_0$
 $ori = \sim op_5 * \sim op_4 * op_3 * op_2 * \sim op_1 * op_0$
 $lw = op_5 * \sim op_4 * \sim op_3 * \sim op_2 * op_1 * op_0$
 $sw = op_5 * \sim op_4 * op_3 * \sim op_2 * op_1 * op_0$
 $beq = \sim op_5 * \sim op_4 * \sim op_3 * op_2 * \sim op_1 * \sim op_0$
 $jump = \sim op_5 * \sim op_4 * \sim op_3 * \sim op_2 * op_1 * \sim op_0$

$add = rtype * func_5 * \sim func_4 * \sim func_3 * \sim func_2 * \sim func_1 * \sim func_0$
 $sub = rtype * func_5 * \sim func_4 * \sim func_3 * \sim func_2 * func_1 * \sim func_0$

How do we implement this in gates?



Controller Implementation

 

Processor Performance

• Can we estimate the clock rate (frequency) of our single-cycle processor? We know:

- 1 cycle per instruction
- lw is the most demanding instruction.
- Assume these delays for major pieces of the datapath:
 - Instr. Mem, ALU, Data Mem : 2 ns each, regfile 1 ns
 - Instruction execution requires: 2 + 1 + 2 + 2 + 1 = 8 ns
 - ⇒ 125 MHz

• What can we do to improve clock rate?

• Will this improve performance as well?

- We want increases in clock rate to result in programs executing quicker.



Gotta Do Laundry


• Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, fold, and put away



- Washer takes 30 minutes
- Dryer takes 30 minutes
- “Folder” takes 30 minutes
- “Stasher” takes 30 minutes to put clothes into drawers




Sequential Laundry

 

• Sequential laundry takes 8 hours for 4 loads



Pipelined Laundry

 

• Pipelined laundry takes 3.5 hours for 4 loads!



General Definitions


• **Latency:** time to completely execute a certain task

- for example, time to read a sector from disk is disk access time or disk latency

• **Throughput:** amount of work that can be done over a period of time



Pipelining Lessons (1/2)

 

• Pipelining doesn't help latency of single task, it helps throughput of entire workload


• Multiple tasks operating simultaneously using different resources

• Potential speedup = Number pipe stages

• Time to “fill” pipeline and time to “drain” it reduces speedup: 2.3X v. 4X in this example



Pipelining Lessons (2/2)

 

- Suppose new Washer takes 20 minutes, new Stasher takes 20 minutes. How much faster is pipeline?
- Pipeline rate limited by slowest pipeline stage
- Unbalanced lengths of pipe stages reduces speedup




Steps in Executing MIPS

- 1) **IFtch**: **I**nstruction **F**etch, Increment PC
- 2) **Dcd**: **I**nstruction **D**ecode, Read **R**egisters
- 3) **Exec**:
Mem-ref: Calculate Address
Arith-log: Perform Operation
- 4) **Mem**:
Load: Read Data from Memory
Store: Write Data to Memory
- 5) **WB**: **W**rite Data **B**ack to Register




Pipelined Execution Representation

 


- Every instruction must take same number of steps, also called pipeline “stages”, so some will go idle sometimes



Review: Datapath for MIPS

 


 - Use datapath figure to represent pipeline



Graphical Pipeline Representation

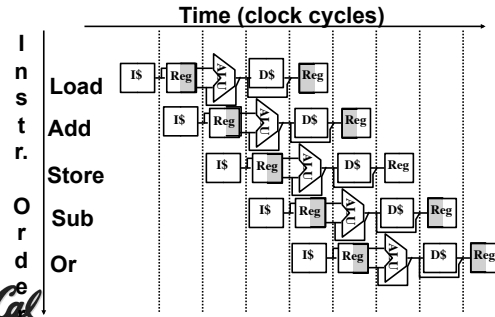(In Reg, right half highlight read, left half write)




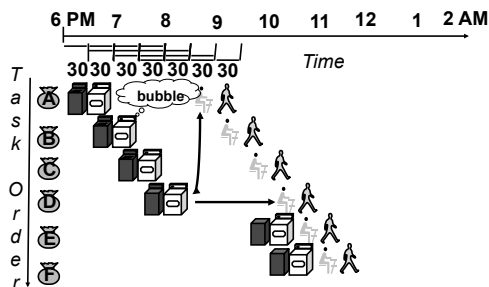Example

- Suppose 2 ns for memory access, 2 ns for ALU operation, and 1 ns for register file read or write; compute instruction rate
- Nonpipelined Execution:
 - lw : IF + Read Reg + ALU + Memory + Write Reg = 2 + 1 + 2 + 2 + 1 = 8 ns
 - add: IF + Read Reg + ALU + Write Reg = 2 + 1 + 2 + 1 = 6 ns (recall 8ns for single-cycle processor)
- Pipelined Execution:
 - Max(IF,Read Reg,ALU,Memory,Write Reg) = 2 ns



Pipeline Hazard: Matching socks in later load



Administrivia

- Midterm Solutions
- Regrade Requests
- HW7 (Design Document)




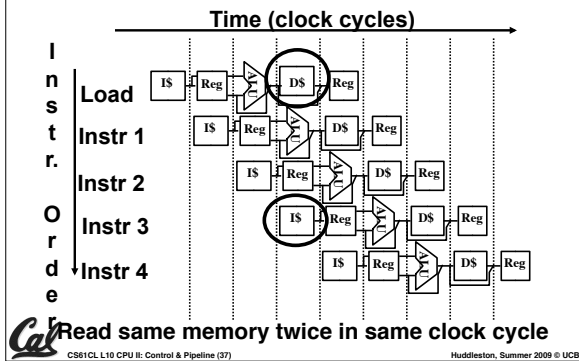Problems for Pipelining CPUs

- Limits to pipelining: Hazards prevent next instruction from executing during its designated clock cycle
 - **Structural hazards**: HW cannot support some combination of instructions (single person to fold and put clothes away)
 - **Control hazards**: Pipelining of branches causes later instruction fetches to wait for the result of the branch
 - **Data hazards**: Instruction depends on result of prior instruction still in the pipeline (missing sock)
- These might result in pipeline stalls or “bubbles” in the pipeline.



Structural Hazard #1: Single Memory (1/2)



Structural Hazard #1: Single Memory (2/2)

• Solution:


- infeasible and inefficient to create second memory
- (We'll learn about this more next week)
- so simulate this by having two Level 1 Caches (a temporary smaller [of usually most recently used] copy of memory)
- have both an L1 Instruction Cache and an L1 Data Cache
- need more complex hardware to control when both caches miss



CS61CL L10 CPU II: Control & Pipeline (38)

Huddleston, Summer 2009 © UCB

Structural Hazard #2: Registers (1/2)

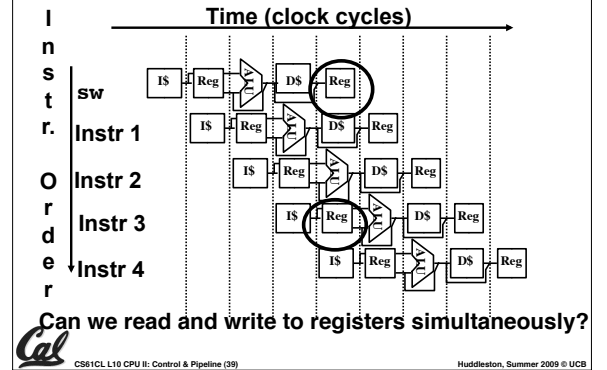

Structural Hazard #2: Registers (2/2)

• Two different solutions have been used:

1) RegFile access is *VERY* fast: takes less than half the time of ALU stage

- Write to Registers during first half of each clock cycle
- Read from Registers during second half of each clock cycle

2) Build RegFile with independent read and write ports


• Result: can perform Read and Write during same clock cycle



CS61CL L10 CPU II: Control & Pipeline (40)

Huddleston, Summer 2009 © UCB

Control Hazard: Branching (1/8)

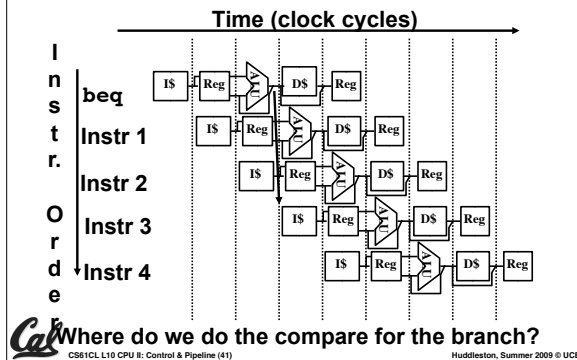

Control Hazard: Branching (2/8)

• We had put branch decision-making hardware in ALU stage

- therefore two more instructions after the branch will always be fetched, whether or not the branch is taken

• Desired functionality of a branch

- if we do not take the branch, don't waste any time and continue executing normally
- if we take the branch, don't execute any instructions after the branch, just go to the desired label



CS61CL L10 CPU II: Control & Pipeline (42)

Huddleston, Summer 2009 © UCB

Control Hazard: Branching (3/8)

• Initial Solution: Stall until decision is made

- insert "no-op" instructions (those that accomplish nothing, just take time) or hold up the fetch of the next instruction (for 2 cycles).
- Drawback: branches take 3 clock cycles each (assuming comparator is put in ALU stage)



CS61CL L10 CPU II: Control & Pipeline (43)

Huddleston, Summer 2009 © UCB

Control Hazard: Branching (4/8)

• Optimization #1:


- insert special branch comparator in Stage 2
- as soon as instruction is decoded (Opcode identifies it as a branch), immediately make a decision and set the new value of the PC
- Benefit: since branch is complete in Stage 2, only one unnecessary instruction is fetched, so only one no-op is needed
- Side Note: This means that branches are idle in Stages 3, 4 and 5.



CS61CL L10 CPU II: Control & Pipeline (44)


Huddleston, Summer 2009 © UCB

Control Hazard: Branching (5/8)

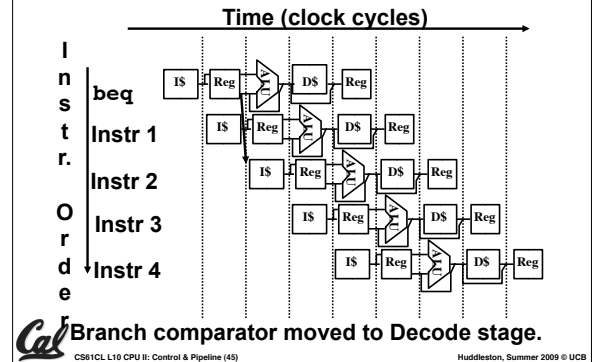


Control Hazard: Branching (6a/8)

- User inserting no-op instruction

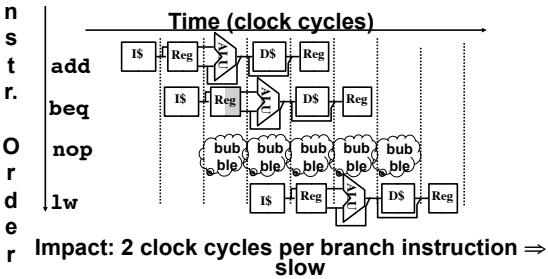

Control Hazard: Branching (6b/8)

- Controller inserting a single bubble

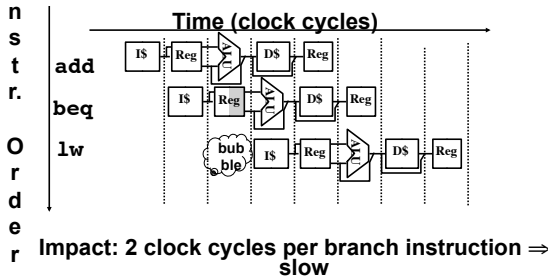

Control Hazard: Branching (7/8)

- Optimization #2: Redefine branches
 - Old definition: if we take the branch, none of the instructions after the branch get executed by accident
 - New definition: whether or not we take the branch, the single instruction immediately following the branch gets executed (called the branch-delay slot)
- The term "Delayed Branch" means we always execute inst after branch
- This optimization is used with MIPS




Control Hazard: Branching (8/8)

- Notes on Branch-Delay Slot

- Worst-Case Scenario: can always put a no-op in the branch-delay slot
- Better Case: can find an instruction preceding the branch which can be placed in the branch-delay slot without affecting flow of the program
 - re-ordering instructions is a common method of speeding up programs
 - compiler/assembler must be very smart in order to find instructions to do this
 - usually can find such an instruction at least 50% of the time
 - Jumps also have a delay slot...



Example: Nondelayed vs. Delayed Branch

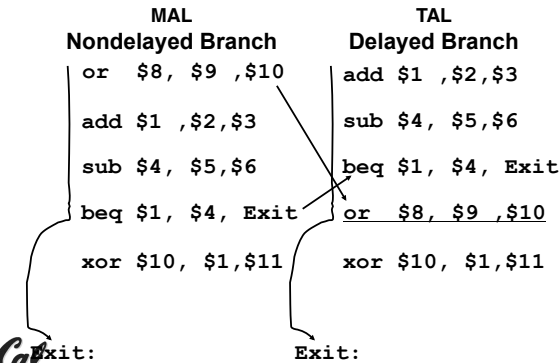

Data Hazards (1/2)


- Consider the following sequence of instructions

```
add $t0, $t1, $t2
sub $t4, $t0, $t3
and $t5, $t0, $t6
or $t7, $t0, $t8
xor $t9, $t0, $t10
```




Data Hazards (2/2)

- Data-flow backward in time are hazards

 

Data Hazard Solution: Forwarding

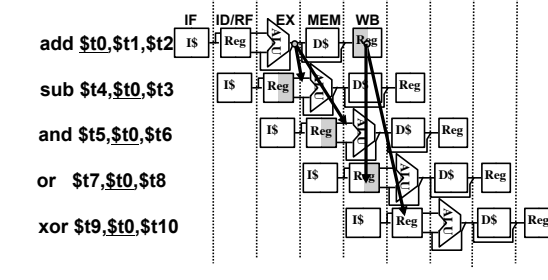- Forward result from one stage to another



Data Hazard: Loads (1/4)

- Dataflow backwards in time are hazards


```
lw $t0, 0($t1)
sub $t3, $t0, $t2
```

- Can't solve all cases with forwarding
- Must stall instruction dependent on load, then forward (more hardware)



Data Hazard: Loads (2/4)

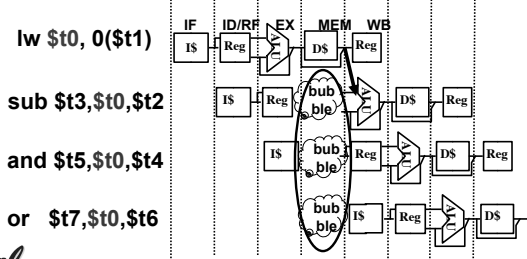- Hardware stalls pipeline
- Called "interlock"



Cal

CS61CL L10 CPU II: Control & Pipeline (55)

Huddleston, Summer 2009 © UCB

Data Hazard: Loads (3/4)

- Instruction slot after a load is called "load delay slot"
- If that instruction uses the result of the load, then the hardware interlock will stall it for one cycle.
- If the compiler puts an unrelated instruction in that slot, then no stall
- Letting the hardware stall the instruction in the delay slot is equivalent to putting a nop in the slot (except the latter uses more code space)


Cal

CS61CL L10 CPU II: Control & Pipeline (56)

Huddleston, Summer 2009 © UCB

Data Hazard: Loads (4/4)

- Stall is equivalent to nop

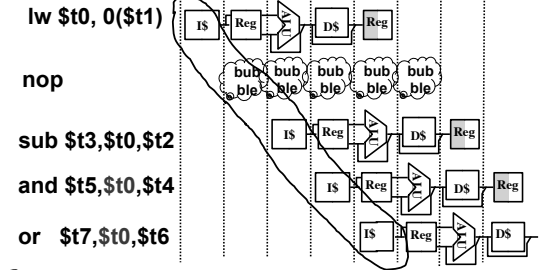

Cal


CS61CL L10 CPU II: Control & Pipeline (57)

Huddleston, Summer 2009 © UCB

Summary: Single-cycle Processor

5 steps to design a processor

 - Analyze instruction set → datapath requirements
- Select set of datapath components & establish clock methodology
- Assemble datapath meeting the requirements
- Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- Assemble the control logic
 - Formulate Logic Equations
 - Design Circuits



Cal

CS61CL L10 CPU II: Control & Pipeline (58)

Huddleston, Summer 2009 © UCB

Things to Remember

- Optimal Pipeline
 - Each stage is executing part of an instruction each clock cycle.
 - One instruction finishes during each clock cycle.
 - On average, execute far more quickly.
- What makes this work?
 - Similarities between instructions allow us to use same stages for all instructions (generally).
 - Each stage takes about the same amount of time as all others: little wasted time.

Cal

CS61CL L10 CPU II: Control & Pipeline (59)

Huddleston, Summer 2009 © UCB

"And in Conclusion.."

- Pipeline challenge is hazards
 - Forwarding helps w/many data hazards
 - Delayed branch helps with control hazard in 5 stage pipeline
 - Load delay slot / interlock necessary
- More aggressive performance:
 - Superscalar
 - Out-of-order execution

Cal

CS61CL L10 CPU II: Control & Pipeline (60)

Huddleston, Summer 2009 © UCB

Bonus slides

- These are extra slides that used to be included in lecture notes, but have been moved to this, the "bonus" area to serve as a supplement.
- The slides will appear in the order they would have in the normal presentation


Bonus

Cal

CS61CL L10 CPU II: Control & Pipeline (61)

Huddleston, Summer 2009 © UCB

RTL: The Add Instruction

 

add rd, rs, rt

- MEM[PC] Fetch the instruction from memory
- $R[rd] = R[rs] + R[rt]$ The actual operation
- $PC = PC + 4$ Calculate the next instruction's address

Cal

CS61CL L10 CPU II: Control & Pipeline (62)

Huddleston, Summer 2009 © UCB





A Summary of the Control Signals (1/2)

	inst	Register Transfer
	add	$R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$ ALUsrc = RegB, ALUctr = "ADD", RegDst = rd, RegWr, nPC_sel = "+4"
	sub	$R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4$ ALUsrc = RegB, ALUctr = "SUB", RegDst = rd, RegWr, nPC_sel = "+4"
	ori	$R[rt] \leftarrow R[rs] + \text{zero_ext}(Imm16); PC \leftarrow PC + 4$ ALUsrc = Im, Extop = "Z", ALUctr = "OR", RegDst = rt, RegWr, nPC_sel = "+4"
lw		$R[rt] \leftarrow MEM[R[rs] + \text{sign_ext}(Imm16)]; PC \leftarrow PC + 4$ ALUsrc = Im, Extop = "sn", ALUctr = "ADD", MemtoReg, RegDst = rt, RegWr, nPC_sel = "+4"
sw		$MEM[R[rs] + \text{sign_ext}(Imm16)] \leftarrow R[rs]; PC \leftarrow PC + 4$ ALUsrc = Im, Extop = "sn", ALUctr = "ADD", MemWr, nPC_sel = "+4"
	beq if ($R[rs] == R[rt]$) then $PC \leftarrow PC + \text{sign_ext}(Imm16) 00$ else $PC \leftarrow PC + 4$ nPC_sel = "br", ALUctr = "SUB"	

Cal

CS61CL L10 CPU II: Control & Pipeline (63)

Huddleston, Summer 2009 © UCB

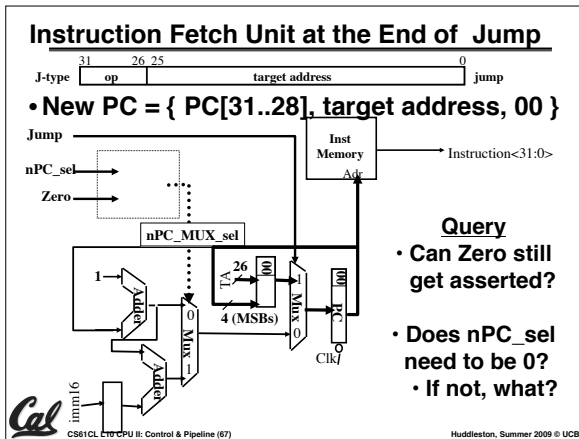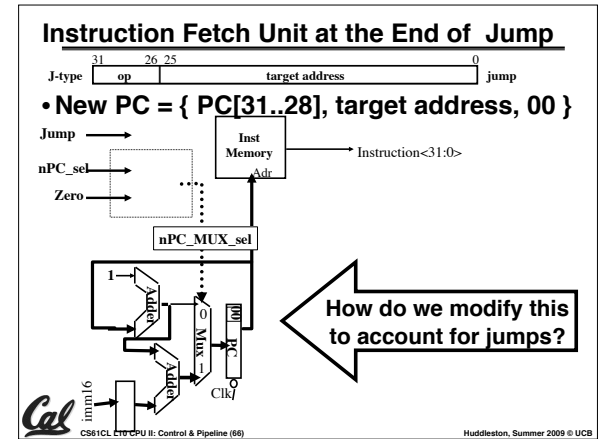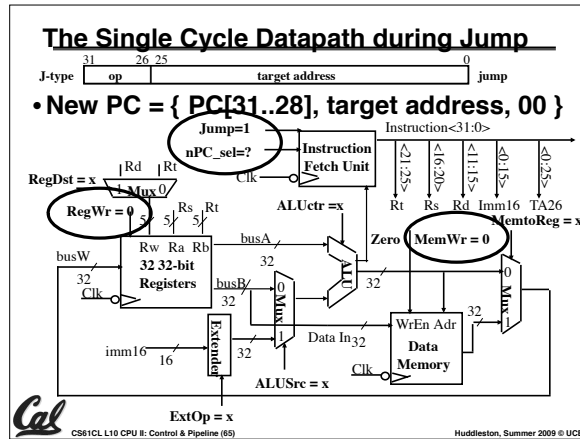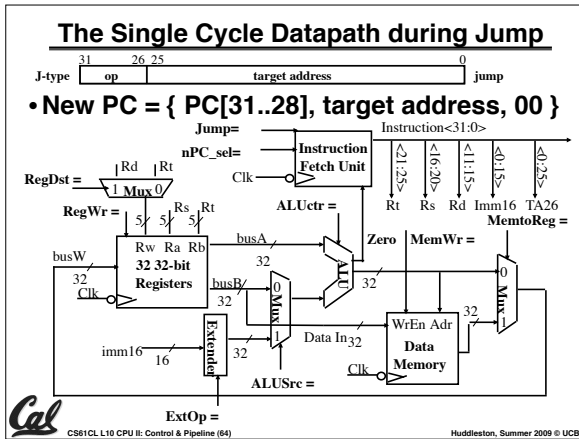

Historical Trivia

- First MIPS design did not interlock and stall on load-use data hazard
- Real reason for name behind MIPS: **Microprocessor without Interlocked Pipeline Stages**
 - Word Play on acronym for Millions of Instructions Per Second, also called MIPS

CS61CL L10 CPU II: Control & Pipeline (68) Huddleston, Summer 2009 © UCB

