

`inst.eecs.berkeley.edu/~cs61c`  
**CS61CL : Machine Structures**

**Lecture #9 – Single Cycle CPU Design**

**2009-07-22**




**Jeremy Huddleston**


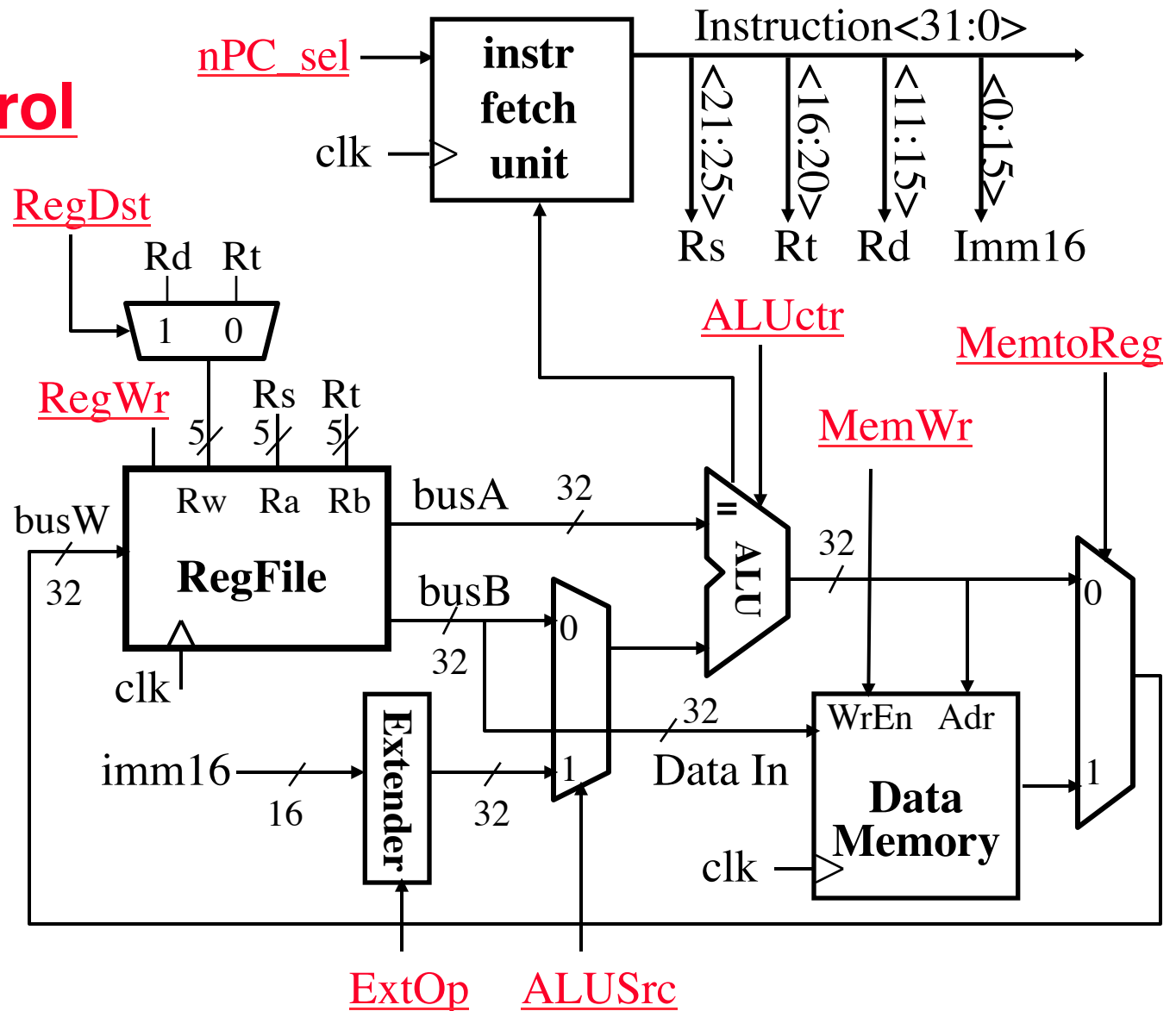
# Review: A Single Cycle Datapath

- We have everything except **control signals**




# Recap: Meaning of the Control Signals

- **nPC\_sel:** “n”=next

“+4” 0  $\Rightarrow$   $PC \leftarrow PC + 4$


“br” 1  $\Rightarrow$   $PC \leftarrow PC + 4 + \{ \text{SignExt}(Im16), 00 \}$

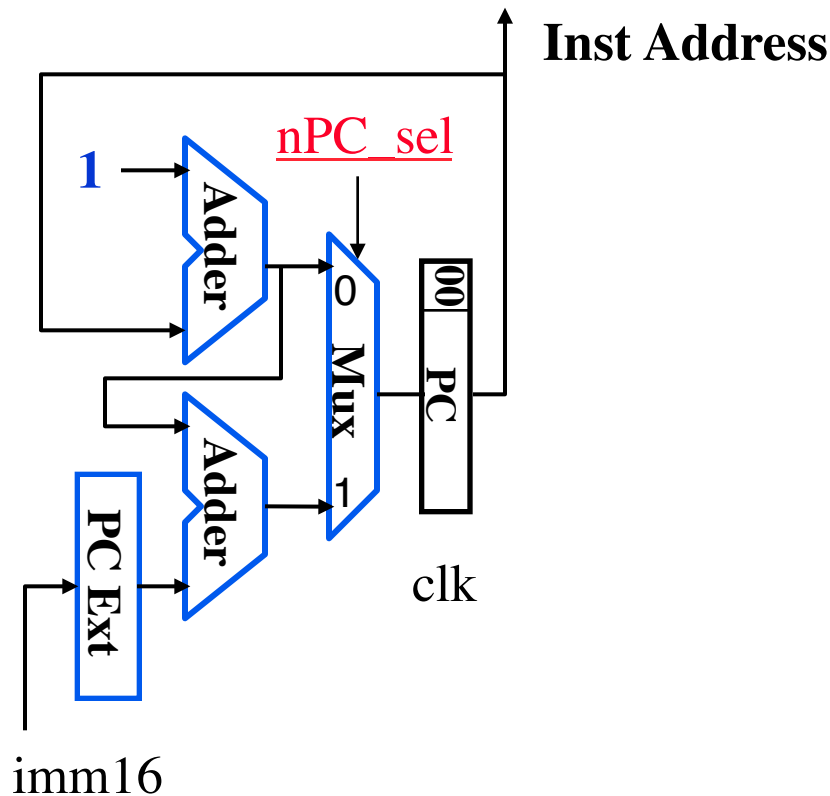- Later in lecture: higher-level connection between mux and branch condition


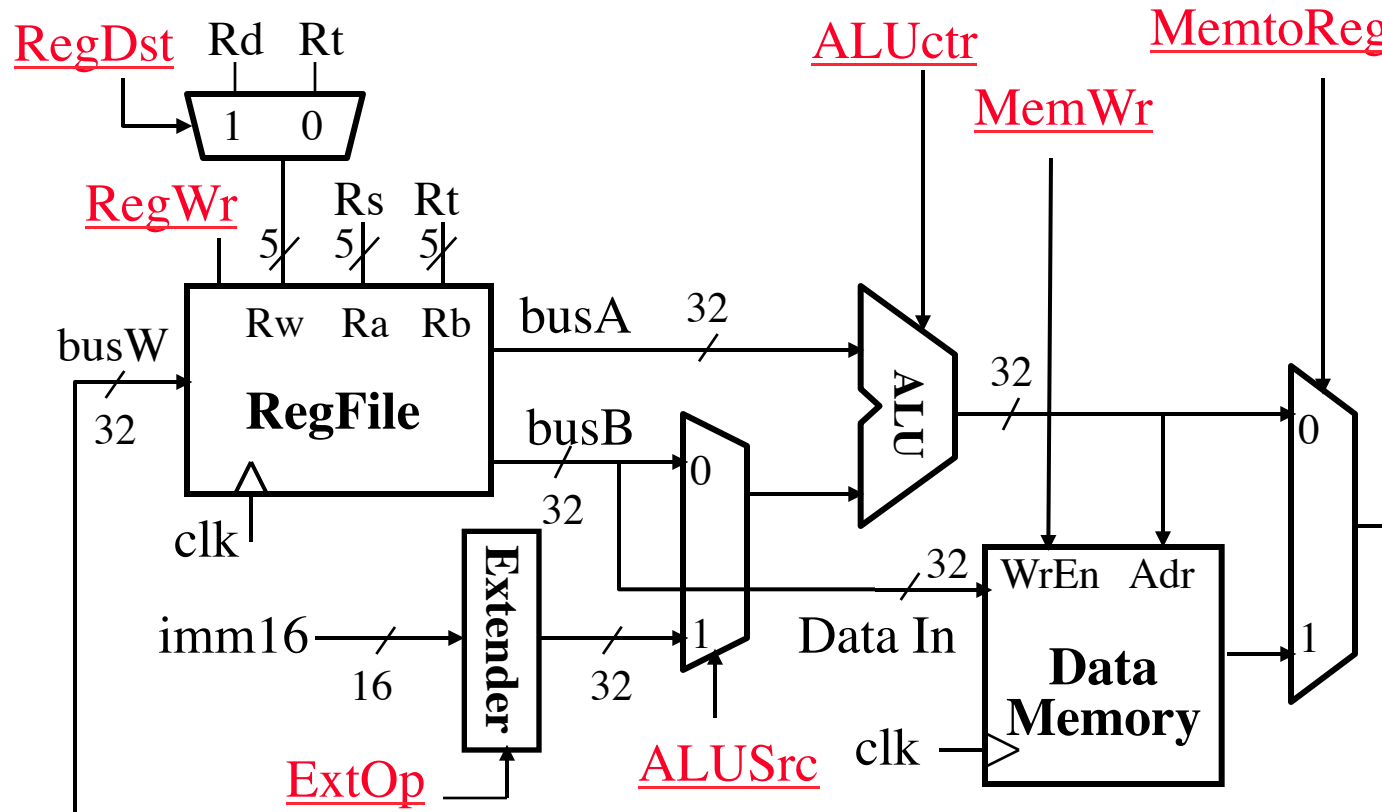
# Recap: Meaning of the Control Signals


- **ExtOp:** “zero”, “sign”
- **ALUsrc:** 0  $\Rightarrow$  regB;  
1  $\Rightarrow$  immedi
- **ALUctr:** “ADD”, “SUB”, “OR”
- **MemWr:** 1  $\Rightarrow$  write memory
- **MemtoReg:** 0  $\Rightarrow$  ALU; 1  $\Rightarrow$  Mem
- **RegDst:** 0  $\Rightarrow$  “rt”; 1  $\Rightarrow$  “rd”
- **RegWr:** 1  $\Rightarrow$  write register




# Instruction Fetch Unit at the Beginning of Add

- Fetch the instruction from Instruction memory:  $\text{Instruction} = \text{MEM}[\text{PC}]$


- same for all instructions

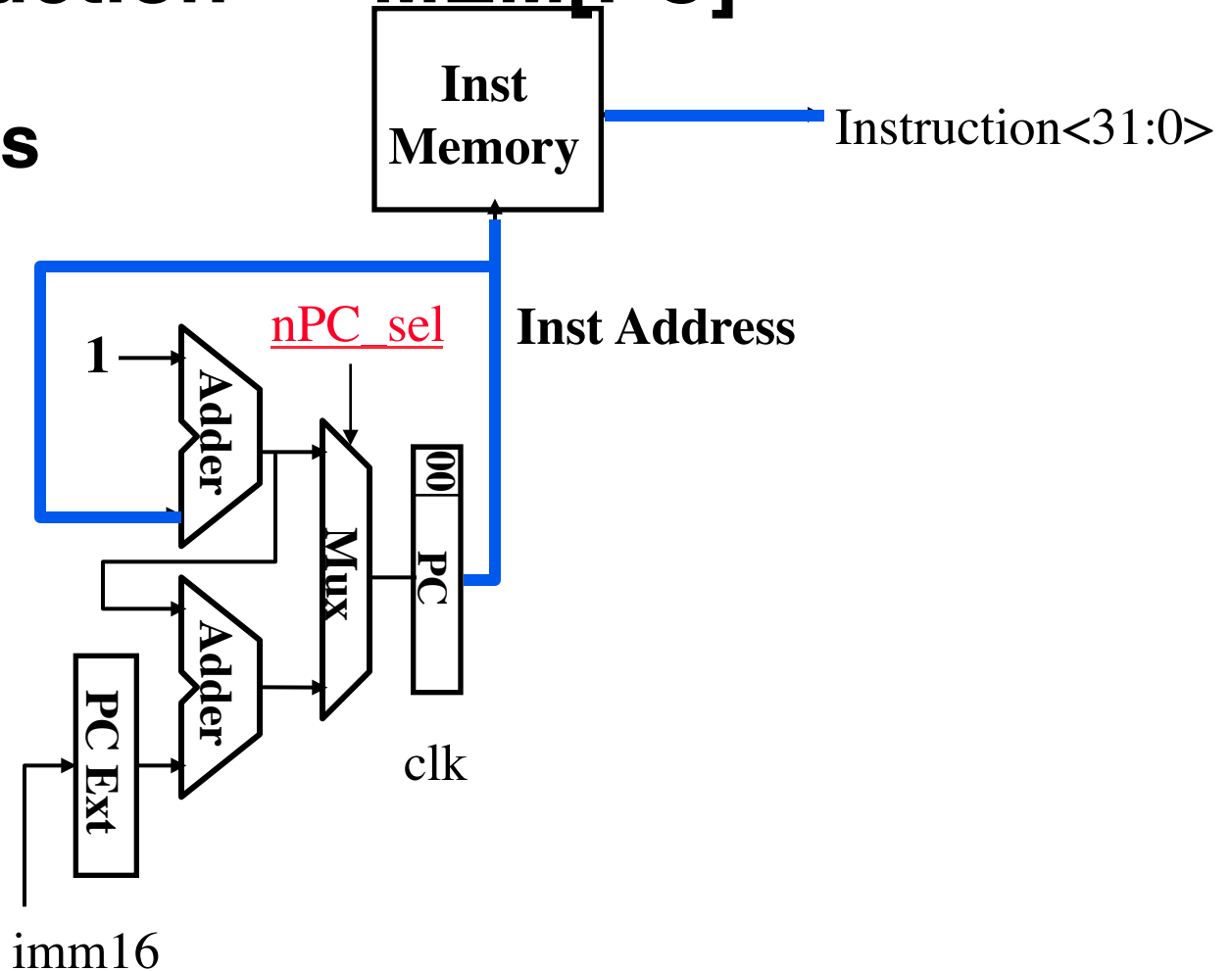

# The Single Cycle Datapath during Add

 


$$R[rd] = R[rs] + R[rt]$$

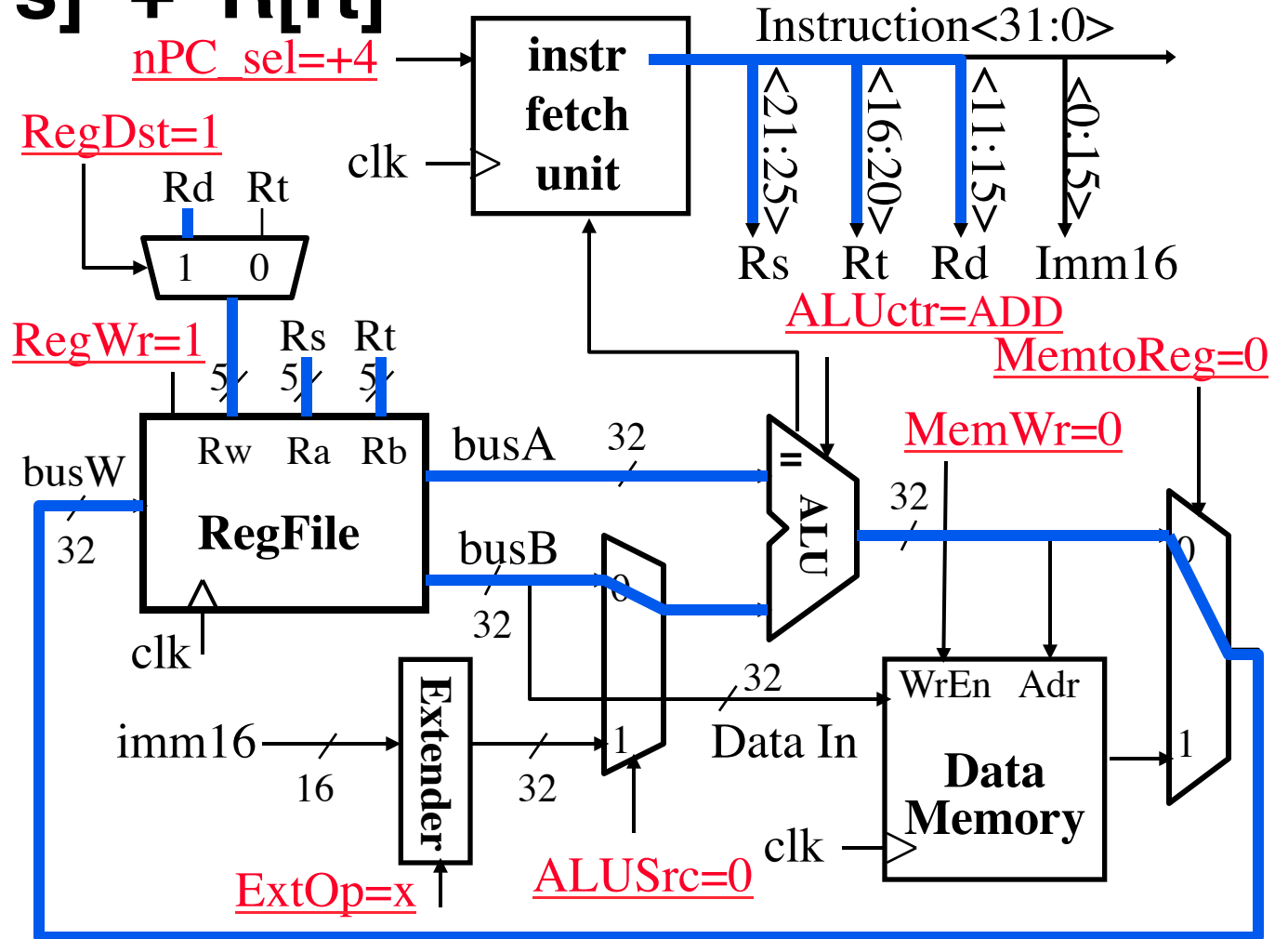

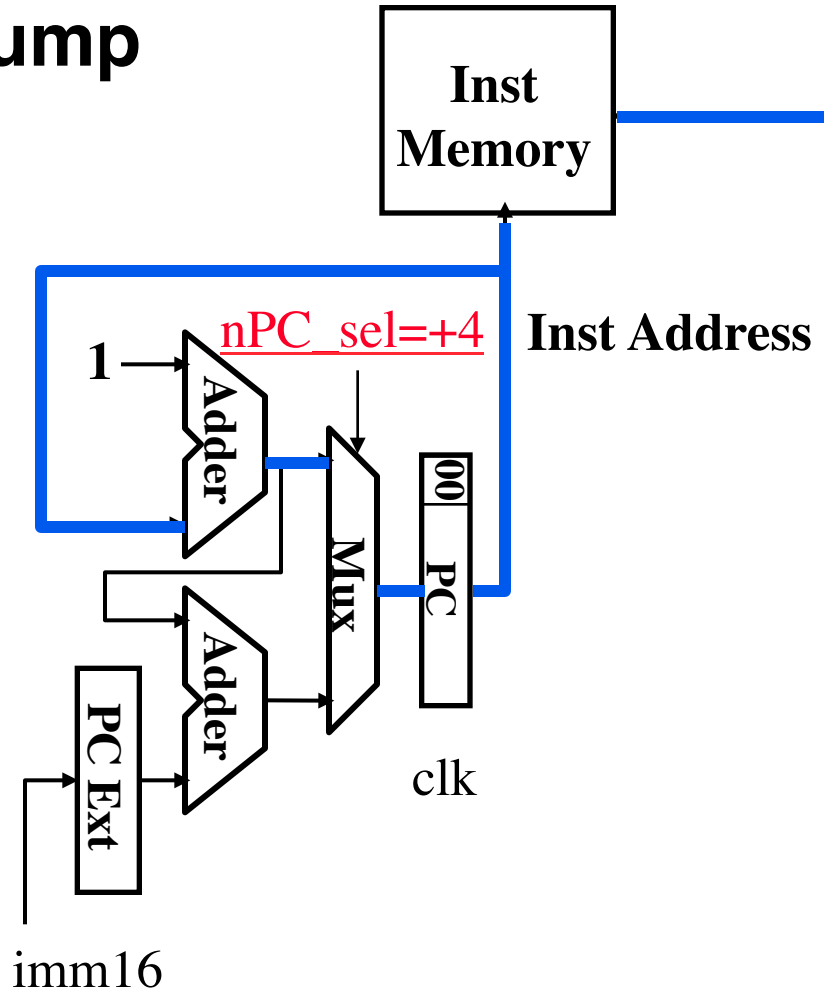
# Instruction Fetch Unit at the End of Add


- **PC = PC + 4**
  - This is the same for all instructions except:  
**Branch and Jump**


 
# Single Cycle Datapath during Or Immediate?




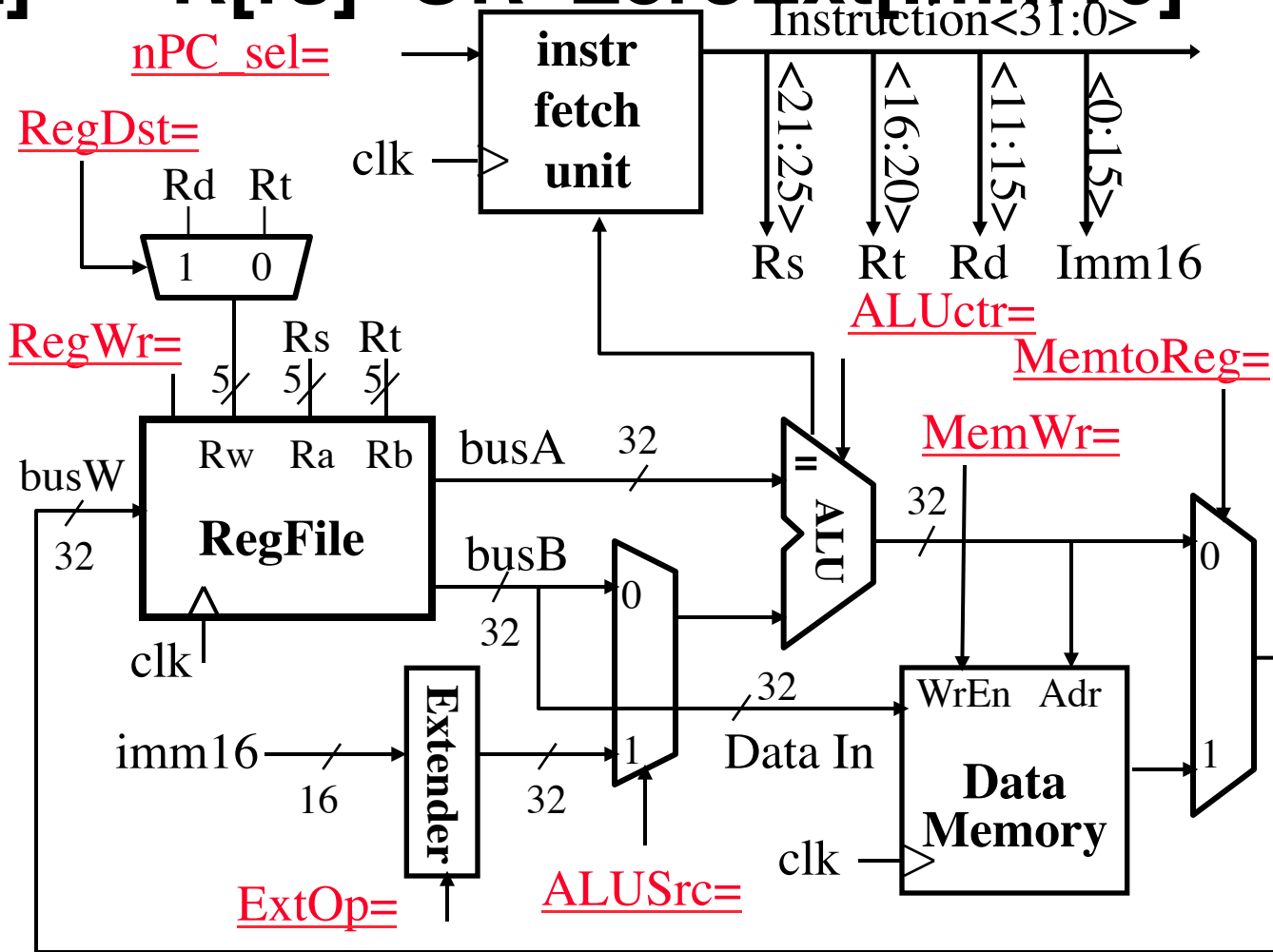•  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$






 
# Single Cycle Datapath during Or Immediate?



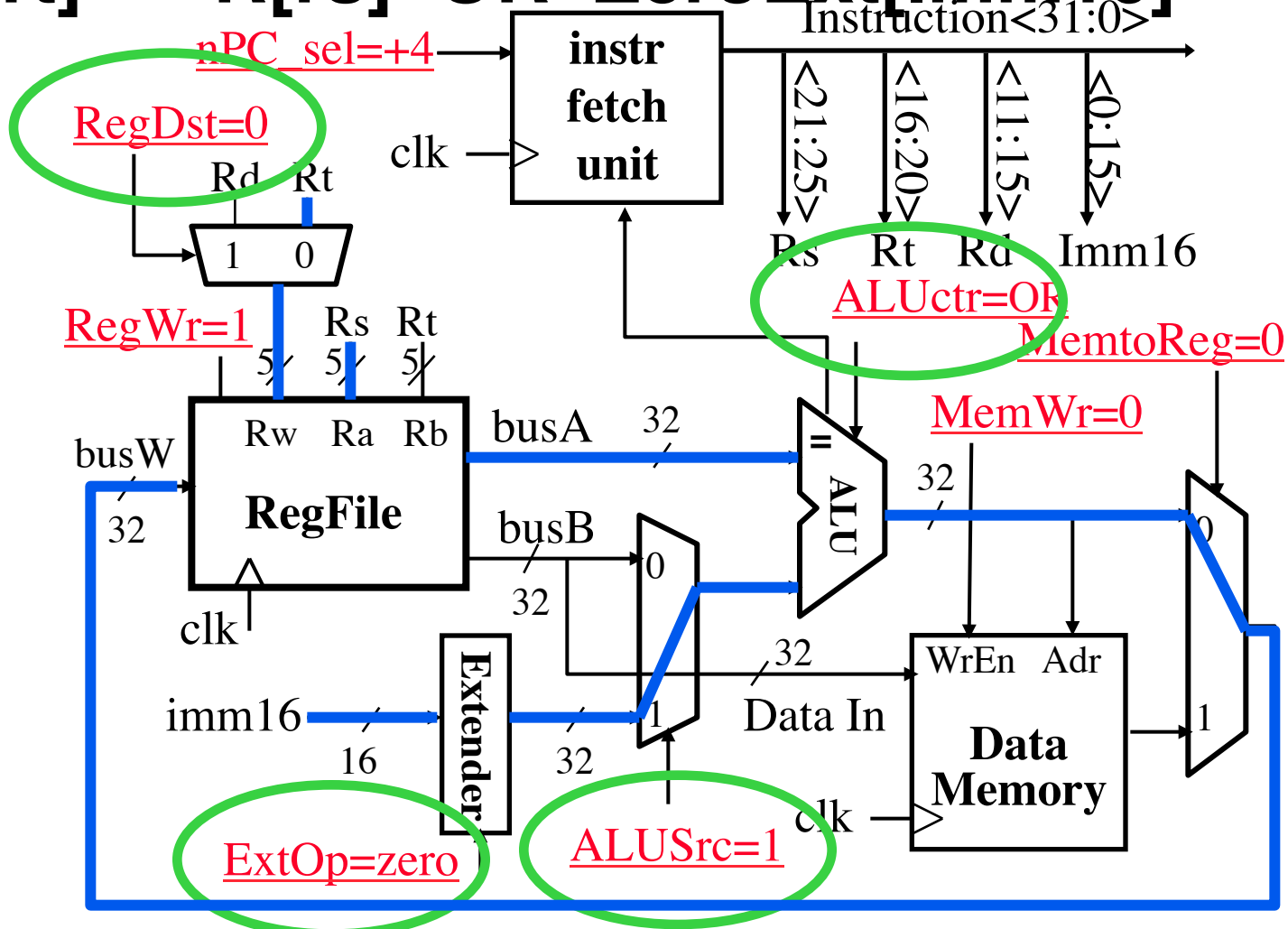
•  $R[rt] = R[rs] \text{ OR } \text{ZeroExt}[\text{Imm16}]$




# The Single Cycle Datapath during Load?

 

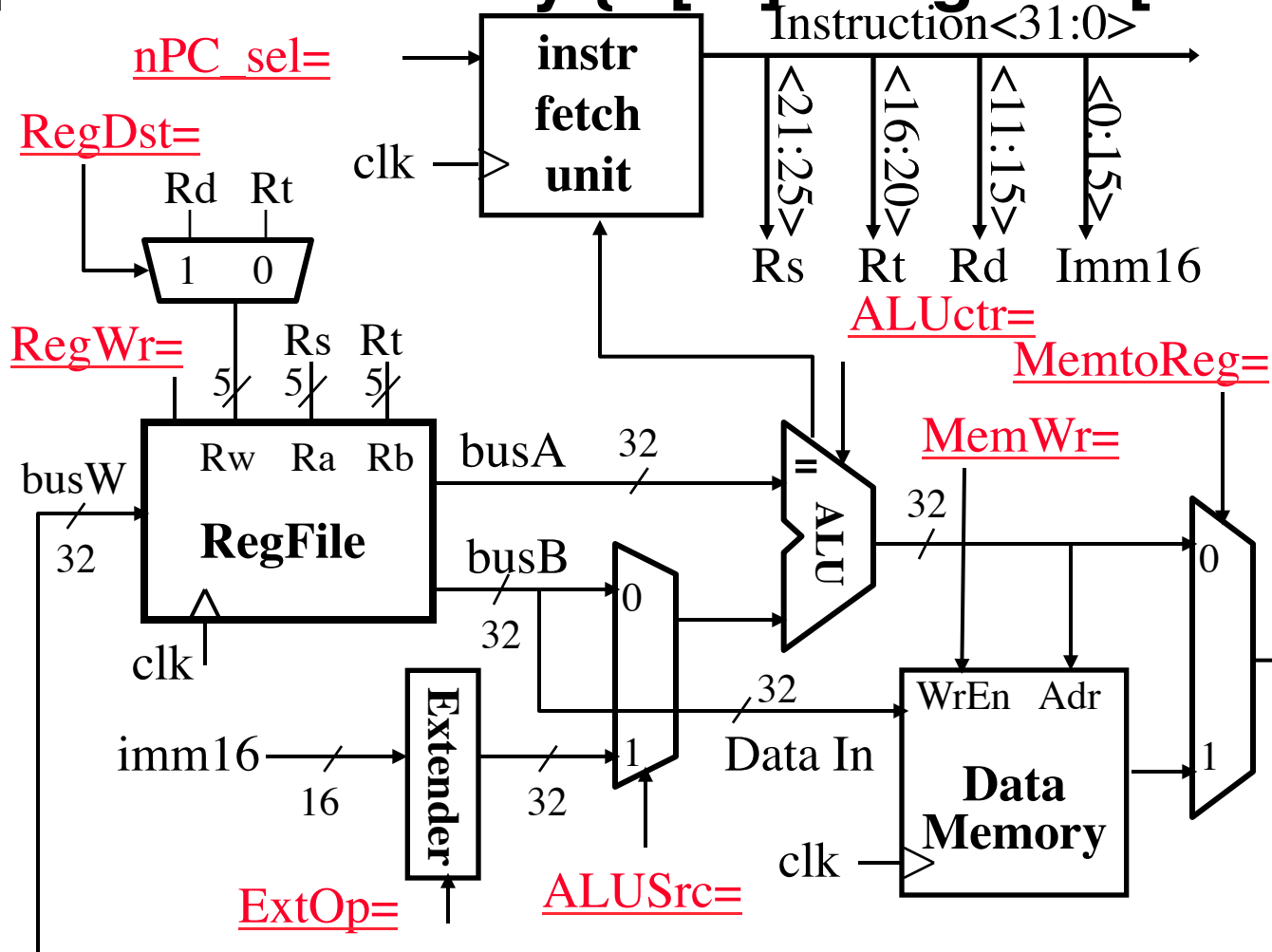
- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[\text{imm16}]\}$




# The Single Cycle Datapath during Load

 

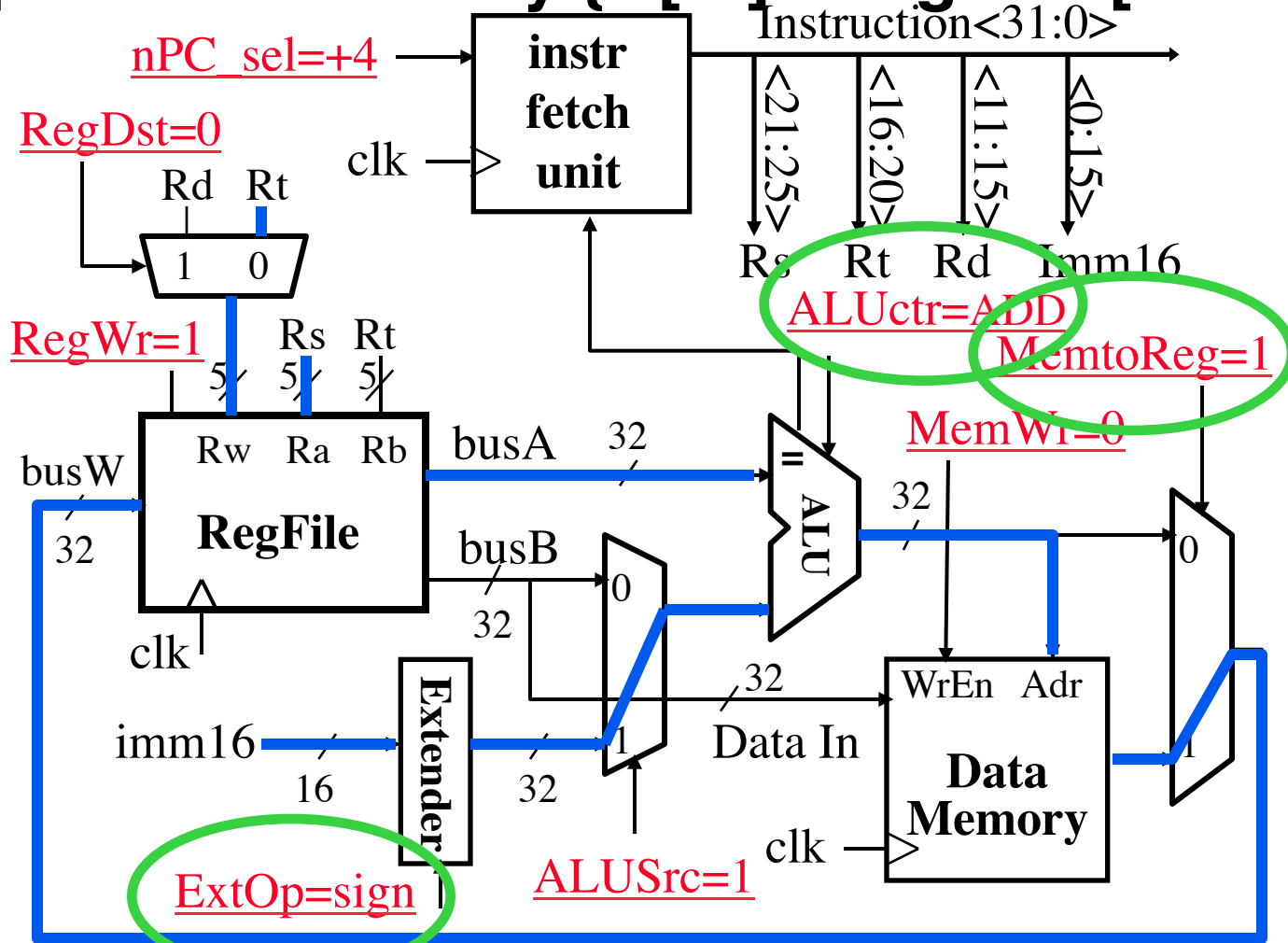
- $R[rt] = \text{Data Memory} \{R[rs] + \text{SignExt}[imm16]\}$



 
# The Single Cycle Datapath during Store?



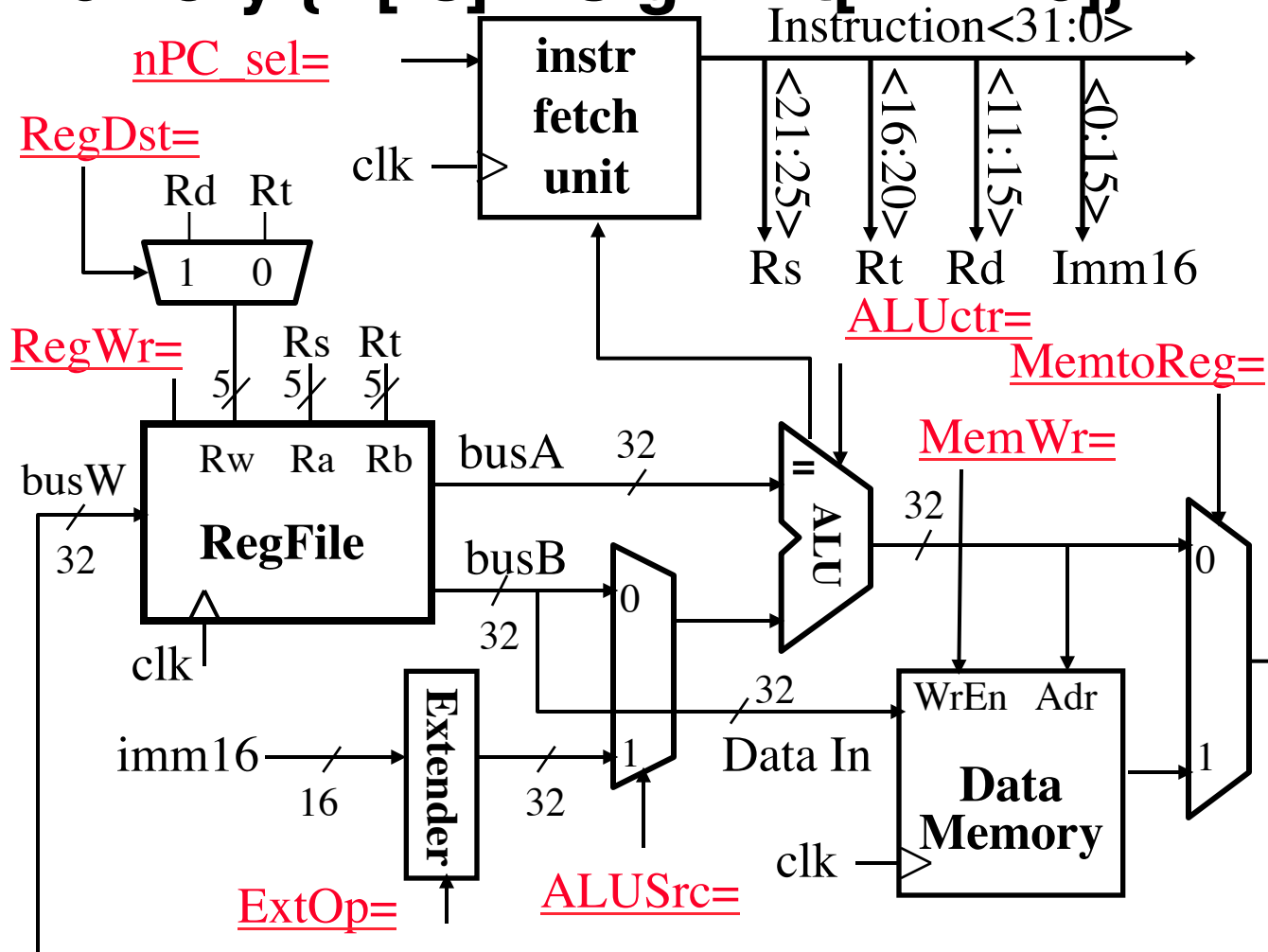
- Data Memory {R[rs] + SignExt[imm16]} = R[rt]




# The Single Cycle Datapath during Store

 

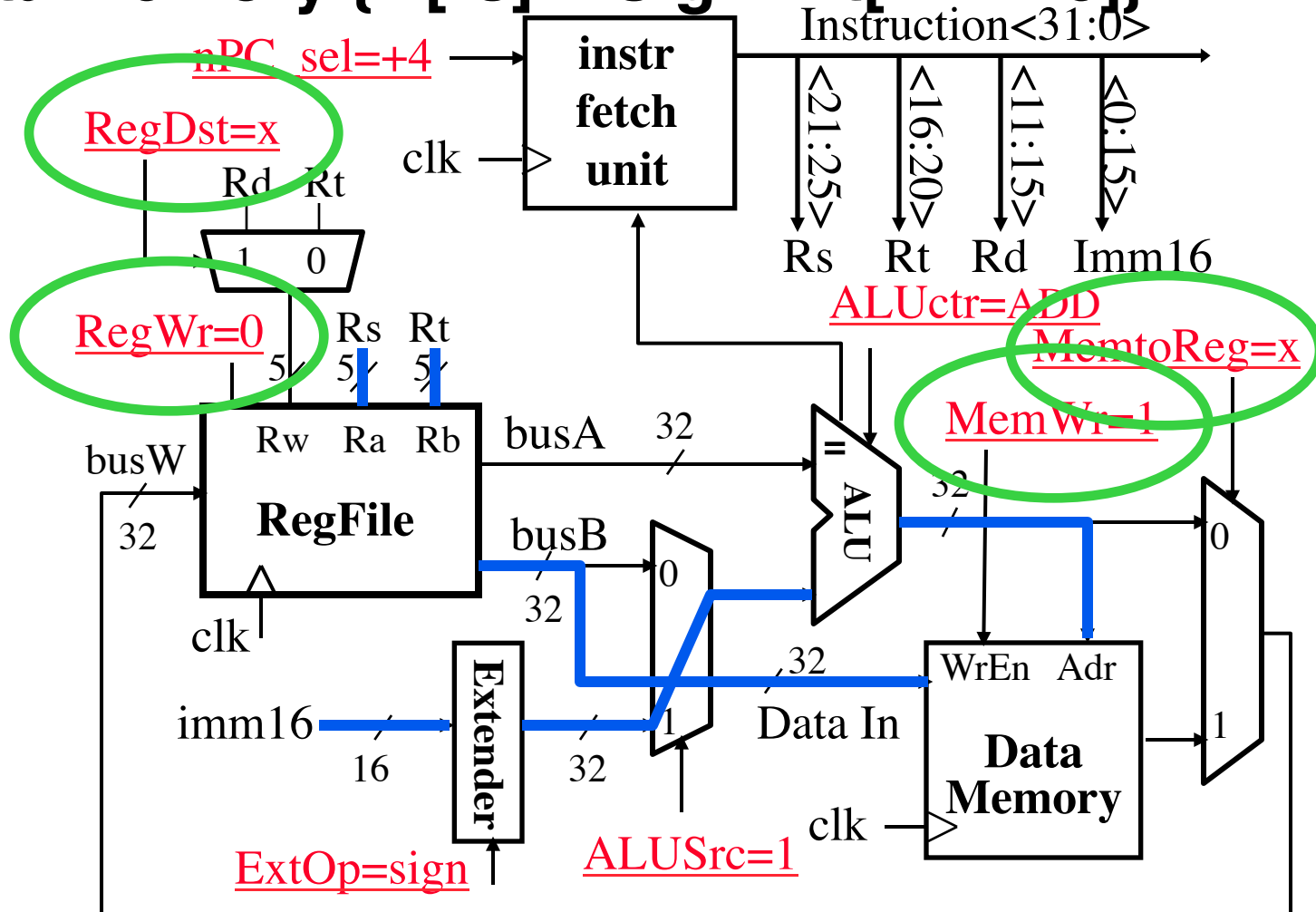
- Data Memory {R[rs] + SignExt[imm16]} = R[rt]



 
# The Single Cycle Datapath during Branch?



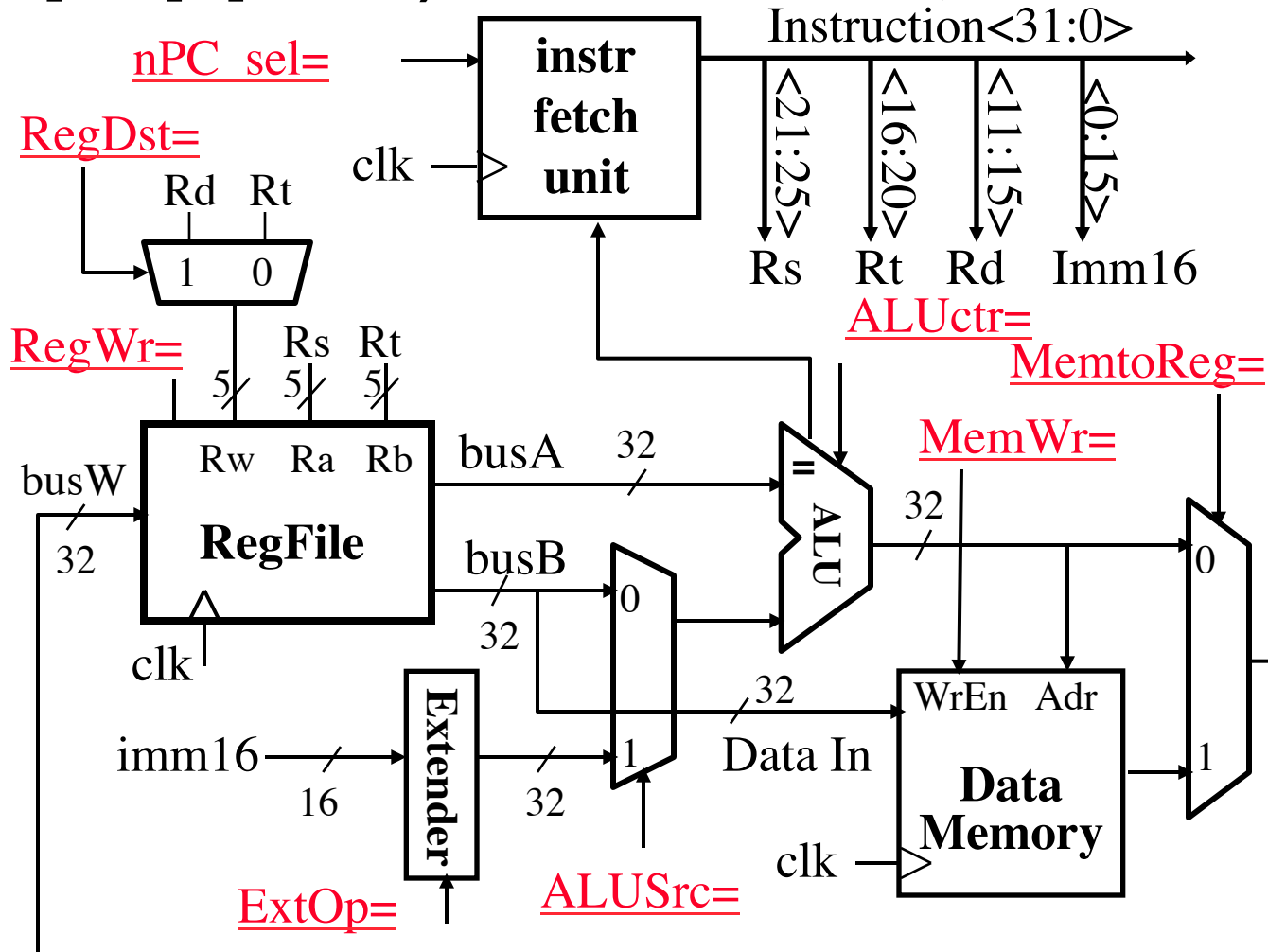
- if  $(R[rs] - R[rt] == 0)$  then Zero = 1 ; else Zero = 0



 
# The Single Cycle Datapath during Branch



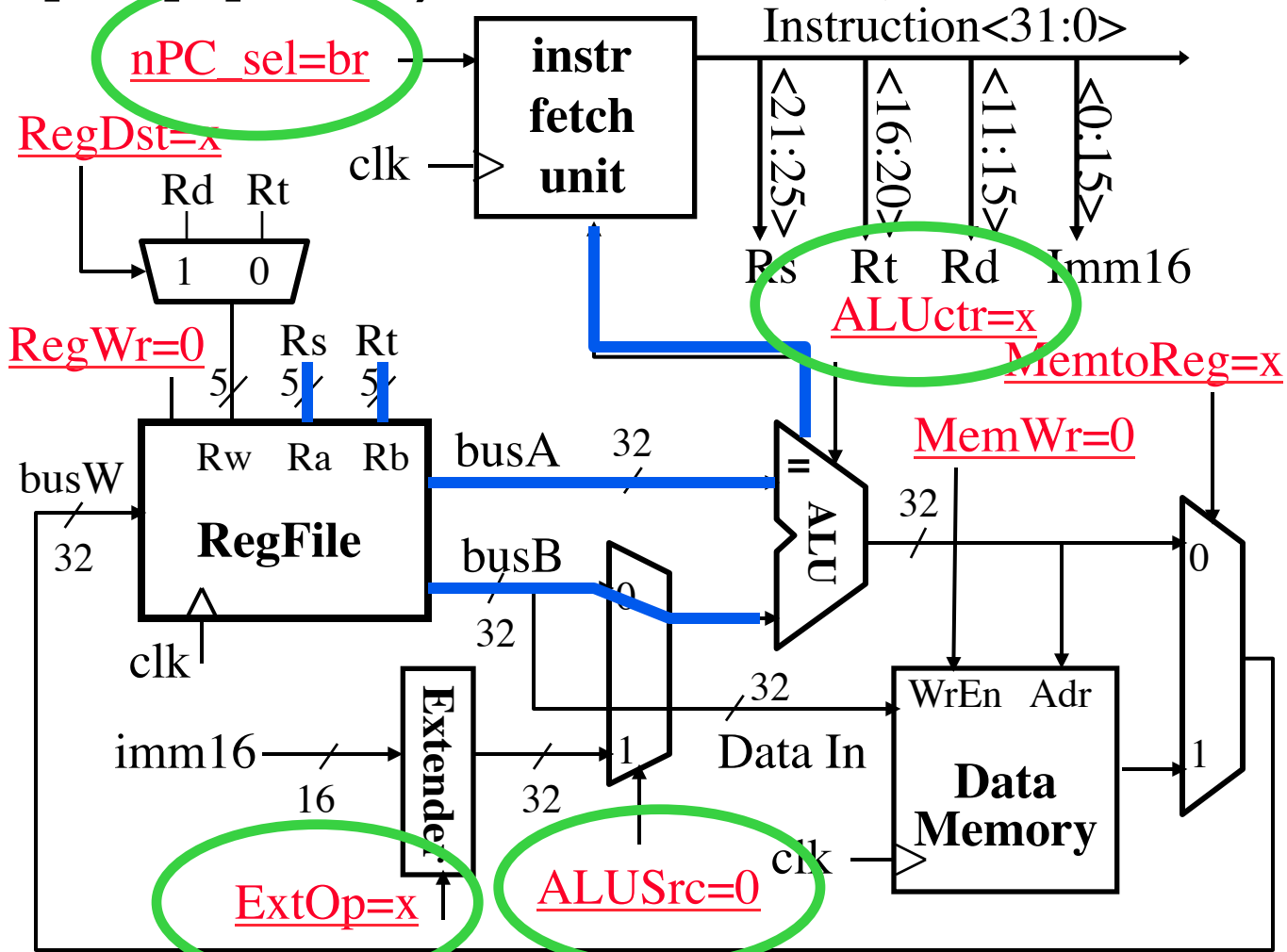
• if  $(R[rs] - R[rt] == 0)$  then "=" = 1 ; else "=" = 0


 
# Instruction Fetch Unit at the End of Branch



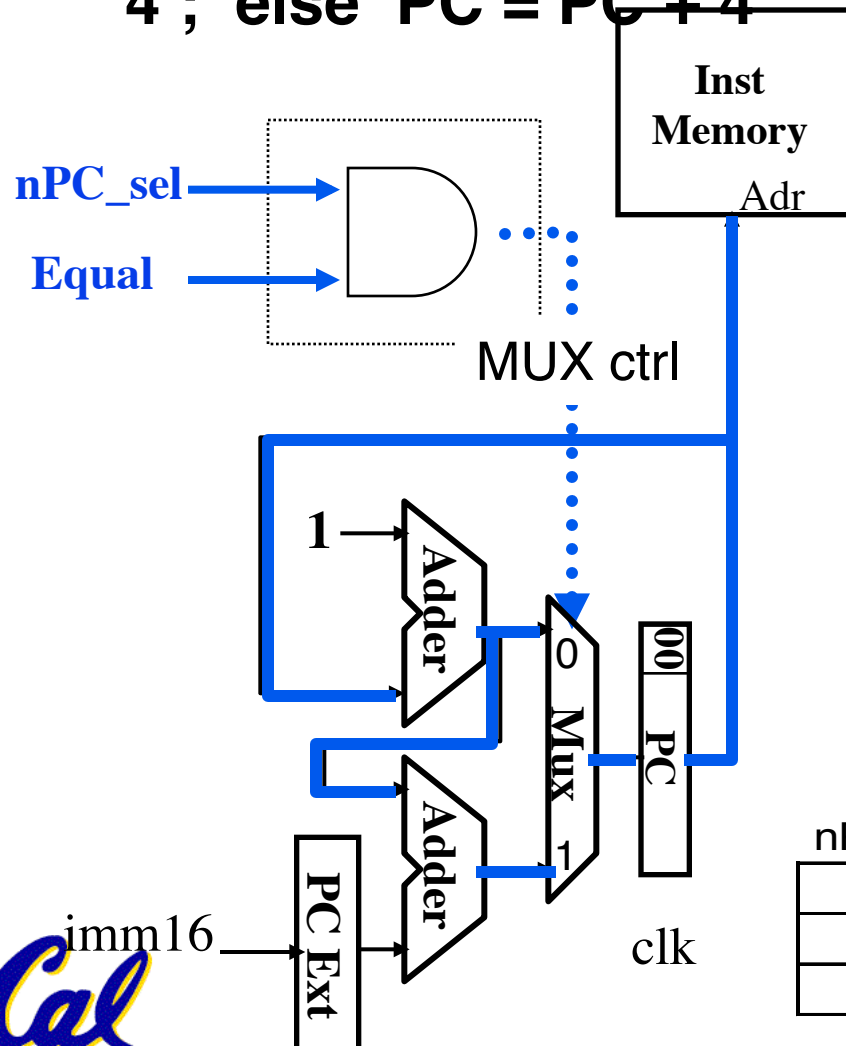- if (Equals == 1) then  $PC = PC + 4 + \text{SignExt}[\text{imm16}] * 4$ ; else  $PC = PC + 4$



- What is encoding of nPC\_sel?
- Direct MUX select?
- Branch inst. / not branch
- Let's pick 2nd option

nPC_sel	zero?	MUX
0	x	0
1	0	0
1	1	1

Q: What logic gate?






# How to Design a Processor: step-by-step

- 1. Analyze instruction set architecture (ISA)  
⇒ datapath requirements
  - meaning of each instruction is given by the *register transfers*
  - datapath must include storage element for ISA registers
  - datapath must support each register transfer
- 2. Select set of datapath components and establish clocking methodology
- 3. Assemble datapath meeting requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic (hard part!)




# Step 4: Given Datapath: RTL → Control

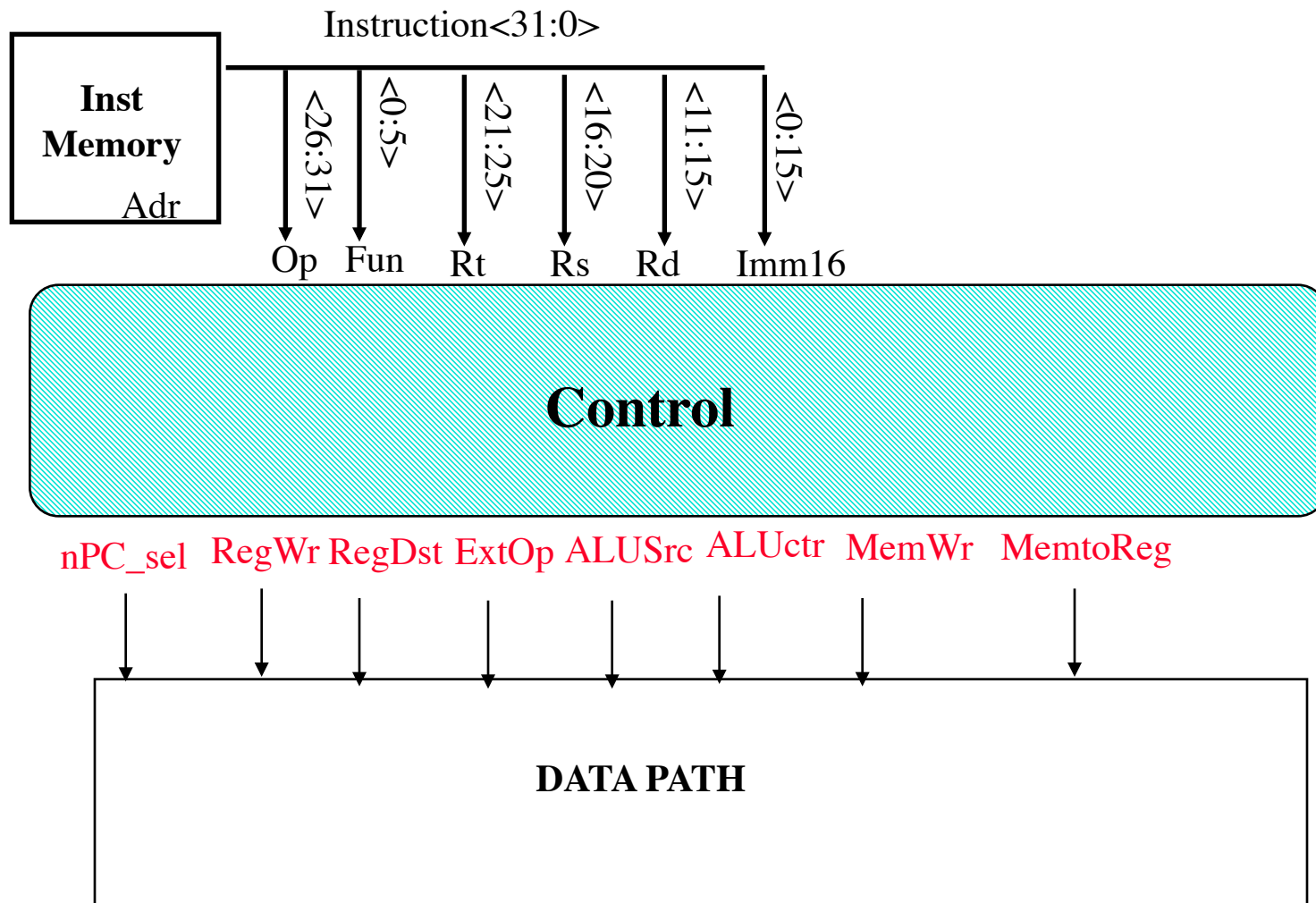

# A Summary of the Control Signals

See Appendix A → **func**  
 → **op**

	10 0000	10 0010	We Don't Care :-)				
	00 0000	00 0000	00 1101	10 0011	10 1011	00 0100	00 0010
	<b>add</b>	<b>sub</b>	<b>ori</b>	<b>lw</b>	<b>sw</b>	<b>beq</b>	<b>jump</b>
<b>RegDst</b>	1	1	0	0	x	x	x
<b>ALUSrc</b>	0	0	1	1	1	0	x
<b>MemtoReg</b>	0	0	0	1	x	x	x
<b>RegWrite</b>	1	1	1	1	0	0	0
<b>MemWrite</b>	0	0	0	0	1	0	0
<b>nPCsel</b>	0	0	0	0	0	1	?
<b>Jump</b>	0	0	0	0	0	0	1
<b>ExtOp</b>	x	x	0	1	1	x	x
<b>ALUctr&lt;2:0&gt;</b>	Add	Subtract	Or	Add	Add	Subtract	x

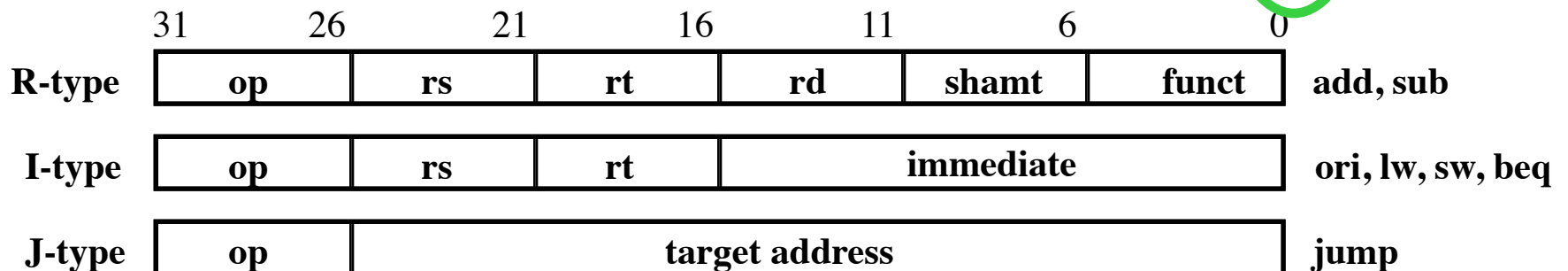

# Boolean Expressions for Controller

**RegDst** = add + sub

**ALUSrc** = ori + lw + sw

**MemtoReg** = lw

**RegWrite** = add + sub + ori + lw

**MemWrite** = sw

**nPCsel** = beq

**Jump** = jump

**ExtOp** = lw + sw

**ALUctr[0]** = sub + beq (assume ALUctr is 0 ADD, 01: SUB, 10: OR)

**ALUctr[1]** = or

*where,*

$rtype = \sim op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot \sim op_2 \cdot \sim op_1 \cdot \sim op_0$ ,

$ori = \sim op_5 \cdot \sim op_4 \cdot op_3 \cdot op_2 \cdot \sim op_1 \cdot op_0$

$lw = op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot \sim op_2 \cdot op_1 \cdot op_0$

$sw = op_5 \cdot \sim op_4 \cdot op_3 \cdot \sim op_2 \cdot op_1 \cdot op_0$

$beq = \sim op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot op_2 \cdot \sim op_1 \cdot \sim op_0$

$jump = \sim op_5 \cdot \sim op_4 \cdot \sim op_3 \cdot \sim op_2 \cdot op_1 \cdot \sim op_0$


How do we  
implement this in  
gates?

$add = rtype \cdot func_5 \cdot \sim func_4 \cdot \sim func_3 \cdot \sim func_2 \cdot \sim func_1 \cdot \sim func_0$

$sub = rtype \cdot func_5 \cdot \sim func_4 \cdot \sim func_3 \cdot \sim func_2 \cdot func_1 \cdot \sim func_0$



# Controller Implementation

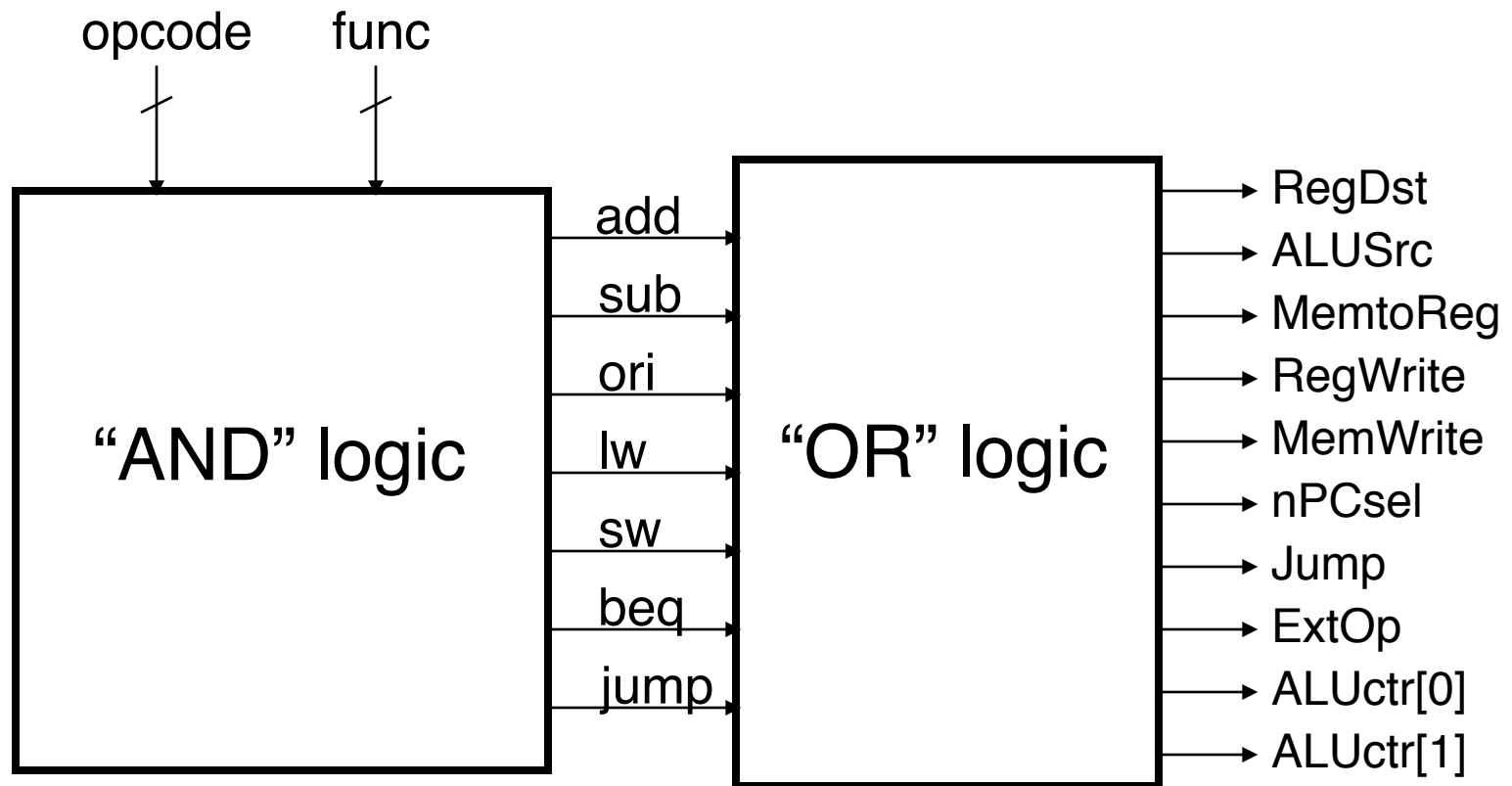

# Processor Performance

---





- Can we estimate the clock rate (frequency) of our single-cycle processor? We know:
  - 1 cycle per instruction
  - **lw** is the most demanding instruction.
  - Assume these delays for major pieces of the datapath:
    - Instr. Mem, ALU, Data Mem : 2 ns each, regfile 1 ns
    - Instruction execution requires:  $2 + 1 + 2 + 2 + 1 = 8$  ns
    - $\Rightarrow$  125 MHz
- What can we do to improve clock rate?
- Will this improve performance as well?
  - We want increases in clock rate to result in programs executing quicker.



    
# Gotta Do Laundry

---

- **Ann, Brian, Cathy, Dave each have one load of clothes to wash, dry, fold, and put away**
  - **Washer takes 30 minutes**
  - **Dryer takes 30 minutes**
  - **“Folder” takes 30 minutes**
  - **“Stasher” takes 30 minutes to put clothes into drawers**



# Sequential Laundry

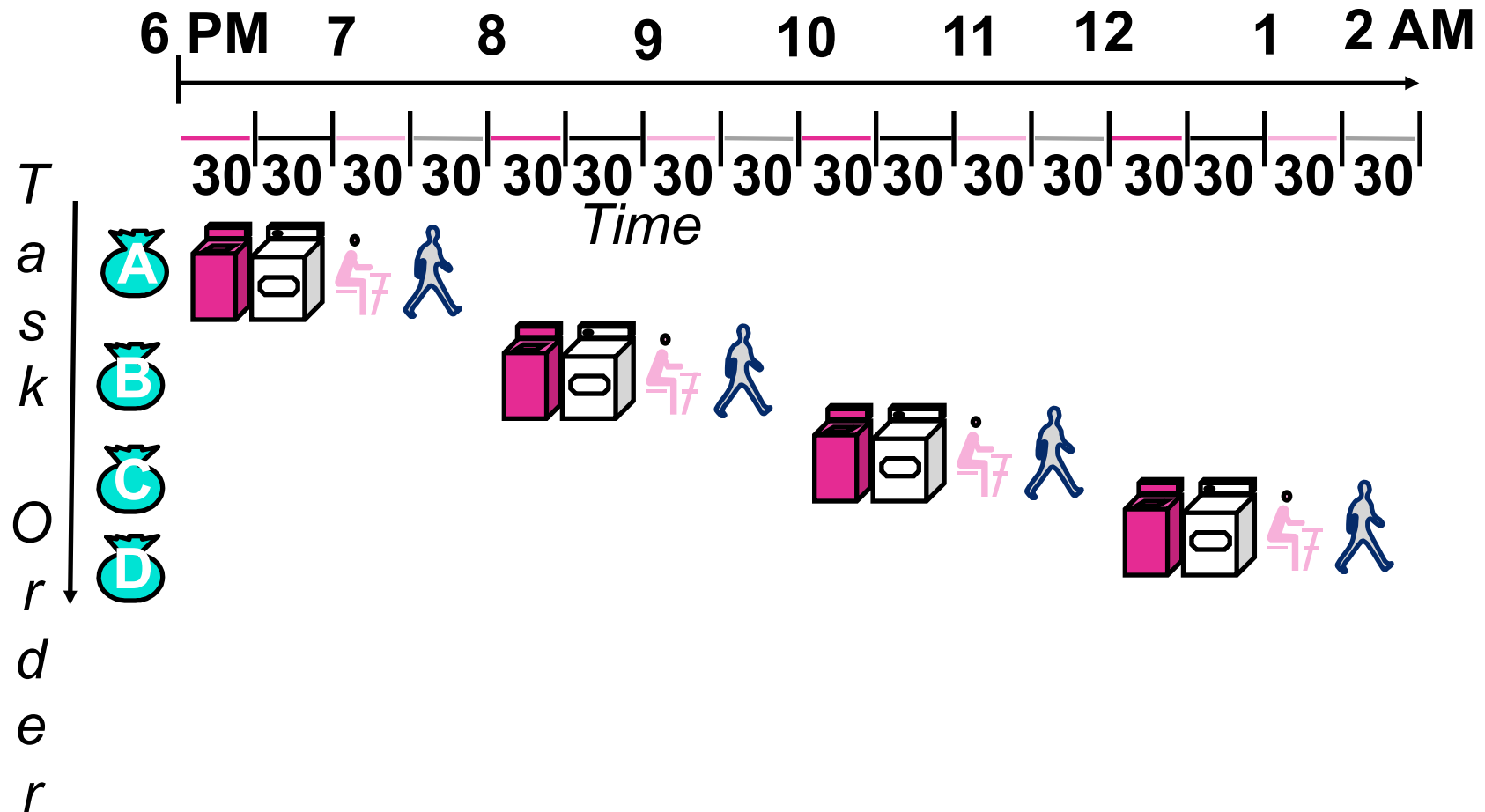


- Sequential laundry takes 8 hours for 4 loads





# Pipelined Laundry

 

• Pipelined laundry takes 3.5 hours for 4 loads!




# General Definitions

---

- **Latency**: time to completely execute a certain task
  - for example, time to read a sector from disk is disk access time or disk latency
- **Throughput**: amount of work that can be done over a period of time




# Pipelining Lessons (1/2)

 

- Pipelining doesn't help **latency** of single task, it helps **throughput** of entire workload
- **Multiple** tasks operating simultaneously using different resources
- Potential speedup = **Number pipe stages**
- Time to “**fill**” pipeline and time to “**drain**” it reduces speedup: 2.3X v. 4X in this example

# Pipelining Lessons (2/2)

 


- Suppose new Washer takes 20 minutes, new Stasher takes 20 minutes. How much faster is pipeline?
- Pipeline rate limited by **slowest** pipeline stage
- Unbalanced lengths of pipe stages reduces speedup

# Steps in Executing MIPS

- 1) **IFtch**: Instruction Fetch, Increment PC
- 2) **Dcd**: Instruction Decode, Read Registers
- 3) **Exec**:  
Mem-ref: Calculate Address  
Arith-log: Perform Operation
- 4) **Mem**:  
Load: Read Data from Memory  
Store: Write Data to Memory
- 5) **WB**: Write Data Back to Register




# Pipelined Execution Representation

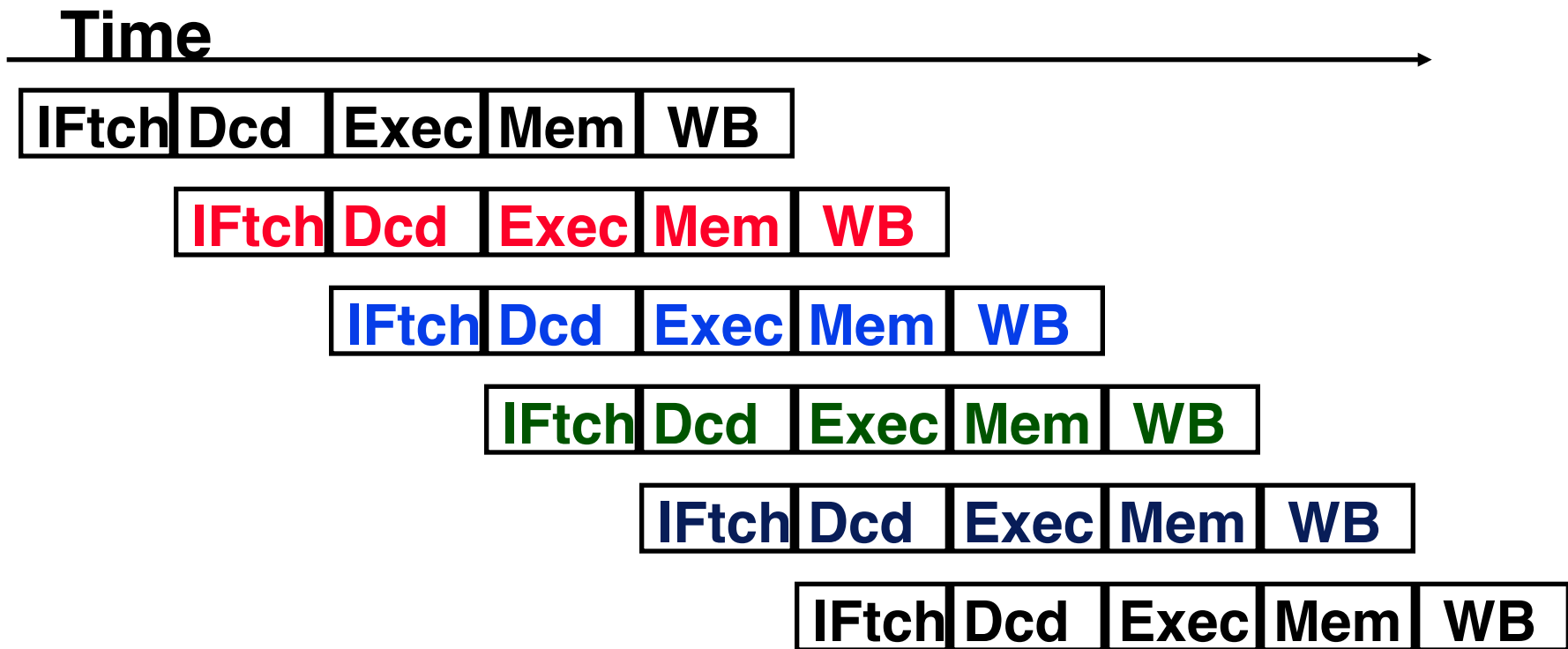


- Every instruction must take same number of steps, also called pipeline “stages”, so some will go idle sometimes



# Review: Datapath for MIPS

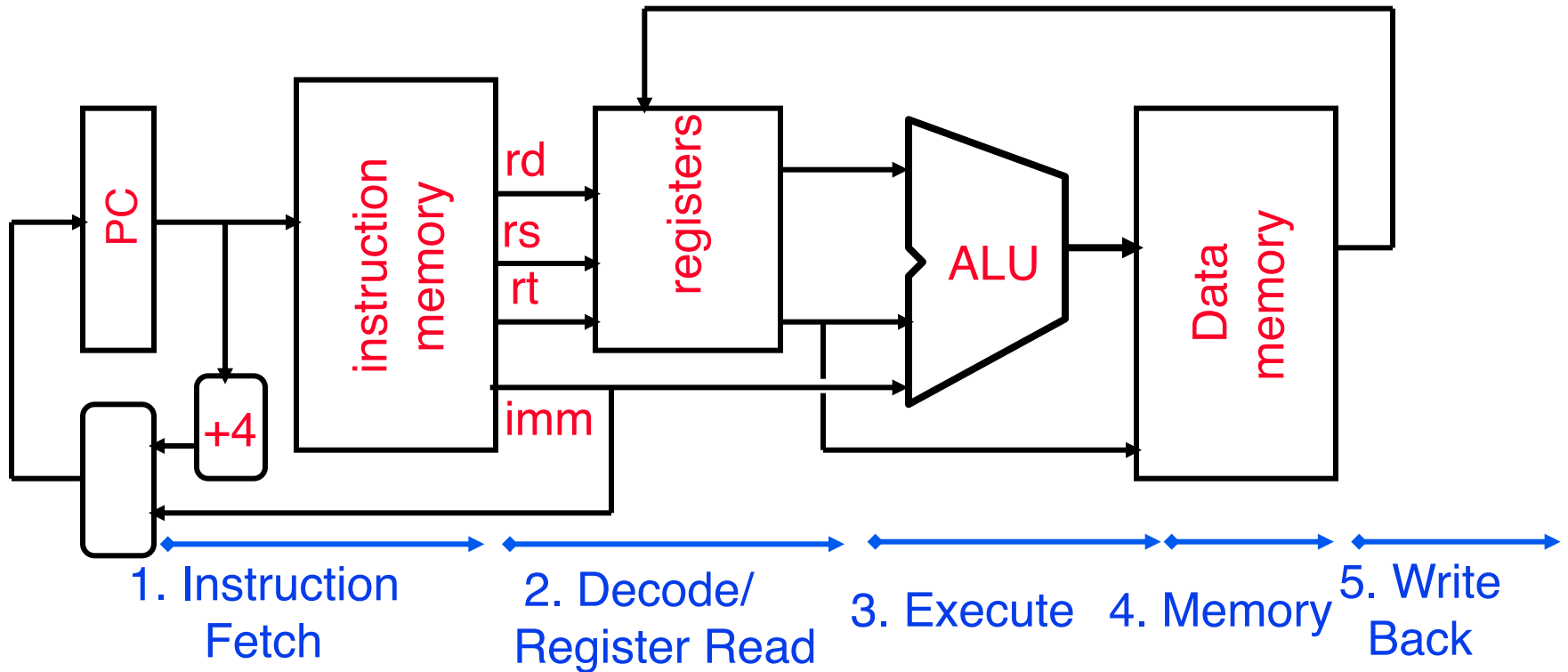

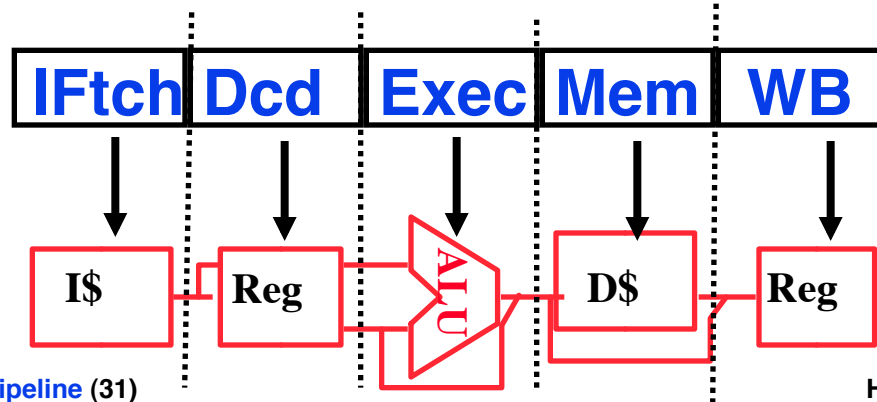• Use datapath figure to represent pipeline




# Graphical Pipeline Representation

(In Reg, right half highlight read, left half write)

Time (clock cycles)

I  
n  
s  
t  
r.  
O  
r  
d  
e  
r

Load  
Add  
Store  
Sub  
Or

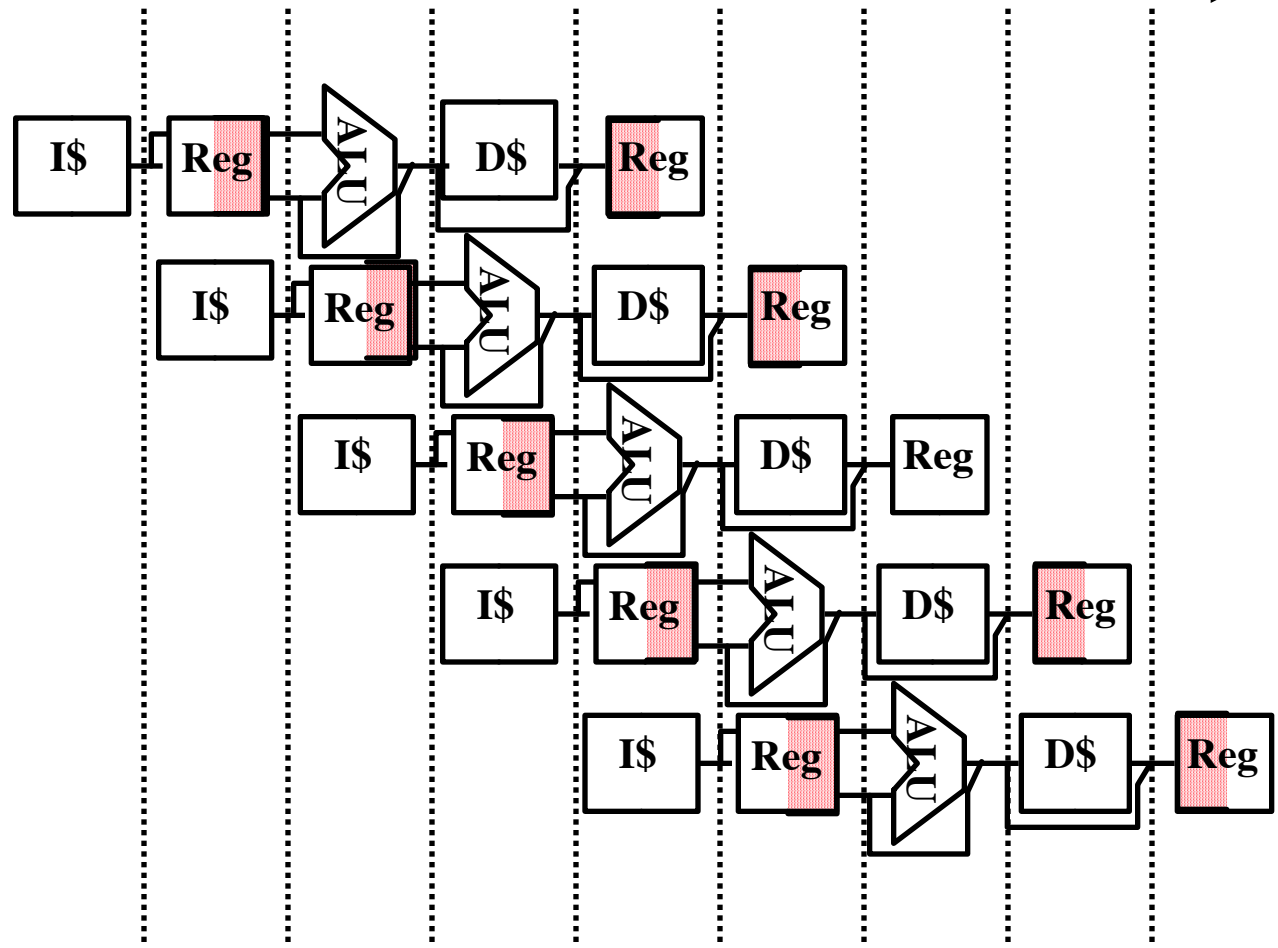




# Example

---

- Suppose 2 ns for memory access, 2 ns for ALU operation, and 1 ns for register file read or write; compute instruction rate
- Nonpipelined Execution:
  - **lw** : IF + Read Reg + ALU + Memory + Write Reg  
= 2 + 1 + 2 + 2 + 1 = **8 ns**
  - **add**: IF + Read Reg + ALU + Write Reg  
= 2 + 1 + 2 + 1 = **6 ns**  
(recall **8ns** for single-cycle processor)
- Pipelined Execution:
  - $\text{Max}(\text{IF}, \text{Read Reg}, \text{ALU}, \text{Memory}, \text{Write Reg}) = 2 \text{ ns}$


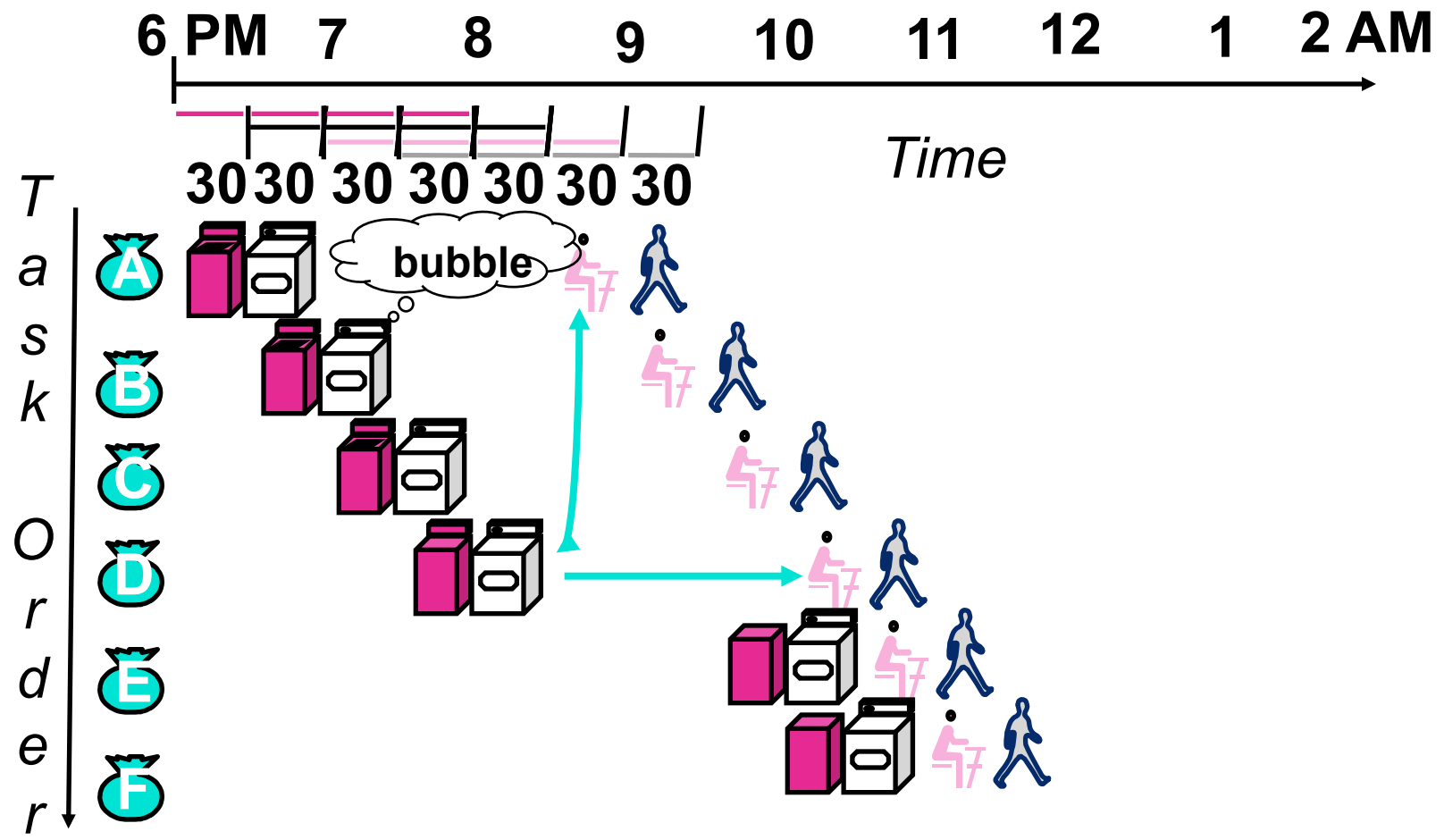
# Pipeline Hazard: Matching socks in later load



# Administrivia

---

- **Midterm Solutions**
- **Regrade Requests**
- **HW7 (Design Document)**




# Problems for Pipelining CPUs

- Limits to pipelining: **Hazards** prevent next instruction from executing during its designated clock cycle
  - **Structural hazards**: HW cannot support some combination of instructions (single person to fold and put clothes away)
  - **Control hazards**: Pipelining of branches causes later instruction fetches to wait for the result of the branch
  - **Data hazards**: Instruction depends on result of prior instruction still in the pipeline (missing sock)
- These might result in pipeline **stalls** or **“bubbles”** in the pipeline.


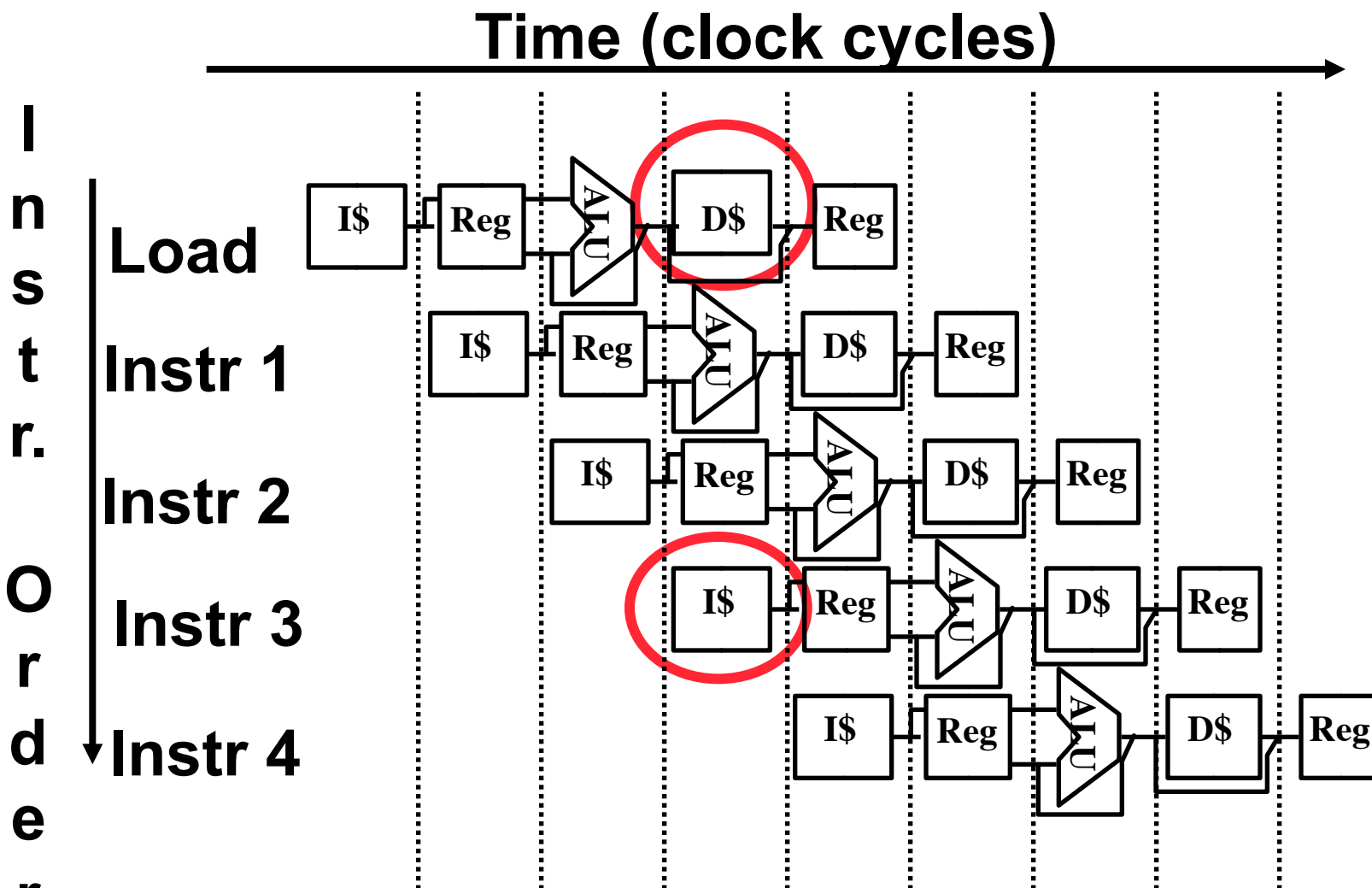
# Structural Hazard #1: Single Memory (1/2)



**Read same memory twice in same clock cycle**




# Structural Hazard #1: Single Memory (2/2)

- **Solution:**
  - infeasible and inefficient to create second memory
  - (We'll learn about this more next week)
  - so simulate this by having **two Level 1 Caches** (a temporary smaller [of usually most recently used] copy of memory)
  - have both an **L1 Instruction Cache** and an **L1 Data Cache**
  - need more complex hardware to control when both caches miss



# Structural Hazard #2: Registers (1/2)

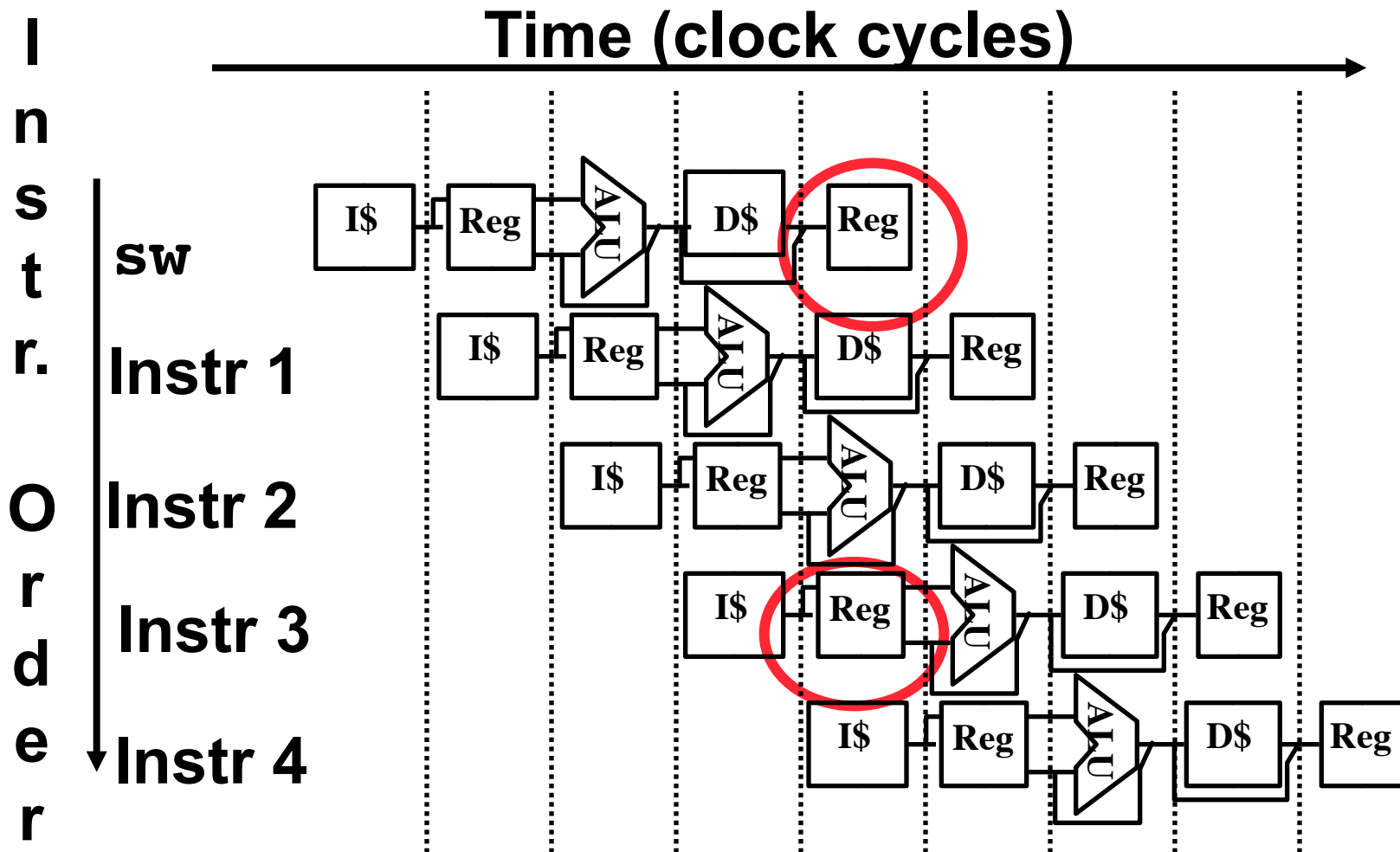

Can we read and write to registers simultaneously?




## Structural Hazard #2: Registers (2/2)

- **Two different solutions have been used:**
  - 1) **RegFile access is *VERY* fast: takes less than half the time of ALU stage**
    - Write to Registers during first half of each clock cycle
    - Read from Registers during second half of each clock cycle
  - 2) **Build RegFile with independent read and write ports**
- **Result: can perform Read and Write during same clock cycle**





# Control Hazard: Branching (1/8)

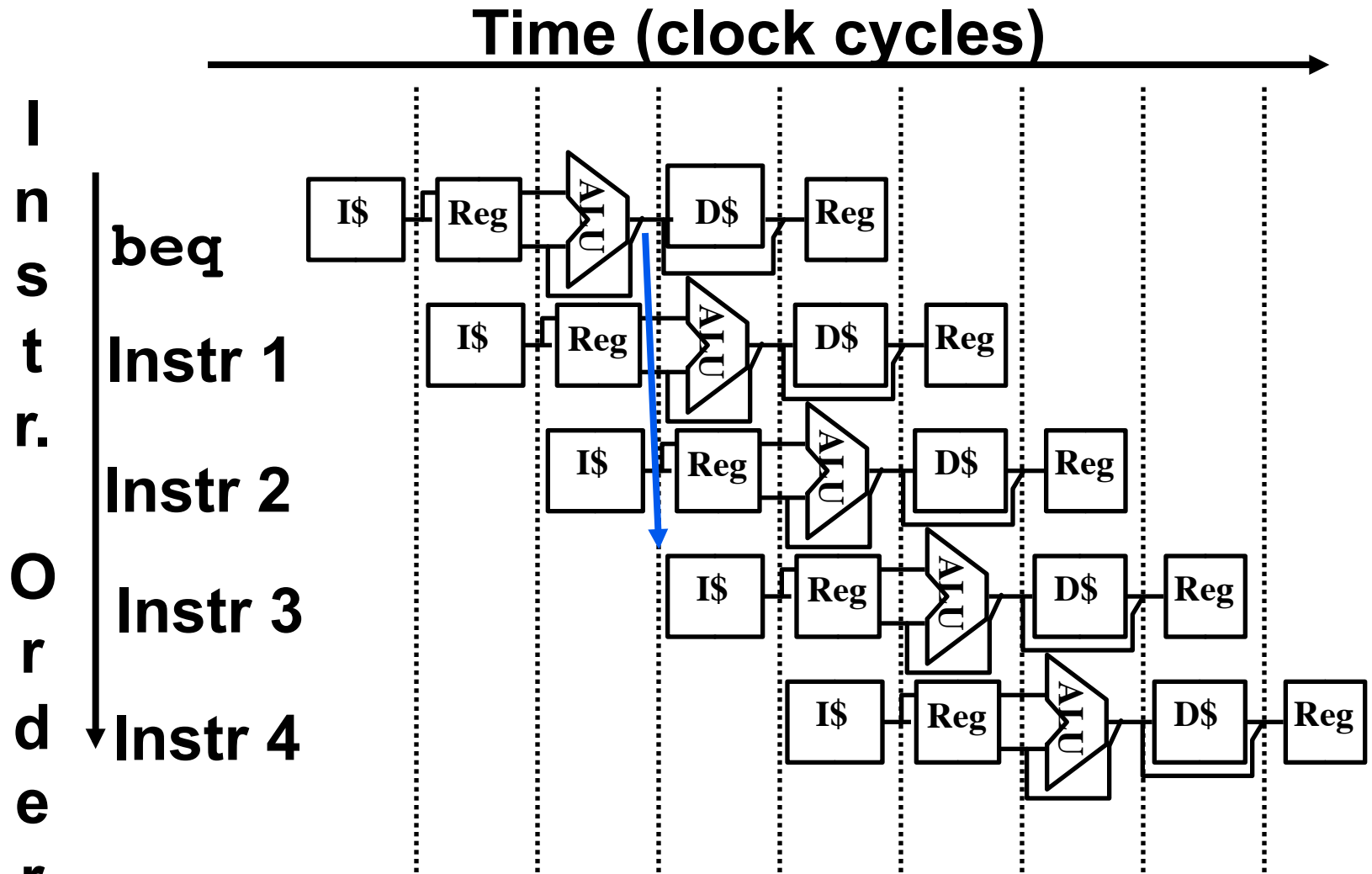

Where do we do the compare for the branch?

## **Control Hazard: Branching (2/8)**

---

- **We had put branch decision-making hardware in ALU stage**
  - therefore two more instructions after the branch will always be fetched, whether or not the branch is taken
- **Desired functionality of a branch**
  - if we do not take the branch, don't waste any time and continue executing normally
  - if we take the branch, don't execute any instructions after the branch, just go to the desired label



## **Control Hazard: Branching (3/8)**

---

- **Initial Solution: Stall until decision is made**
  - **insert “no-op” instructions (those that accomplish nothing, just take time) or hold up the fetch of the next instruction (for 2 cycles).**
  - **Drawback: branches take 3 clock cycles each (assuming comparator is put in ALU stage)**




# Control Hazard: Branching (4/8)

---

- **Optimization #1:**
  - insert **special branch comparator** in Stage 2
  - as soon as instruction is decoded (Opcode identifies it as a branch), immediately make a decision and set the new value of the PC
  - **Benefit:** since branch is complete in Stage 2, only one unnecessary instruction is fetched, so only one no-op is needed
  - **Side Note:** This means that branches are idle in Stages 3, 4 and 5.



# Control Hazard: Branching (5/8)

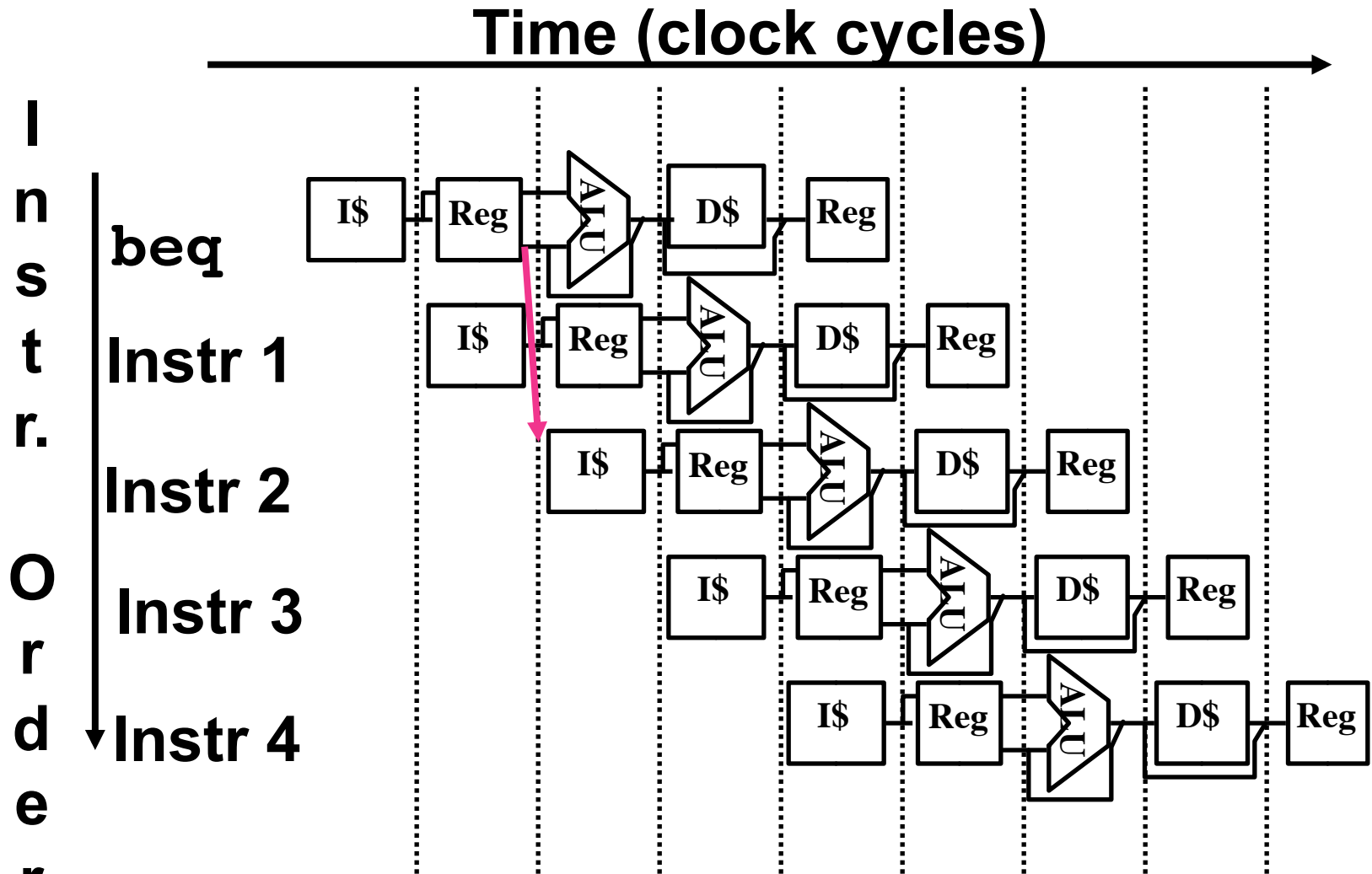


Branch comparator moved to Decode stage.



# Control Hazard: Branching (6a/8)

- User inserting no-op instruction

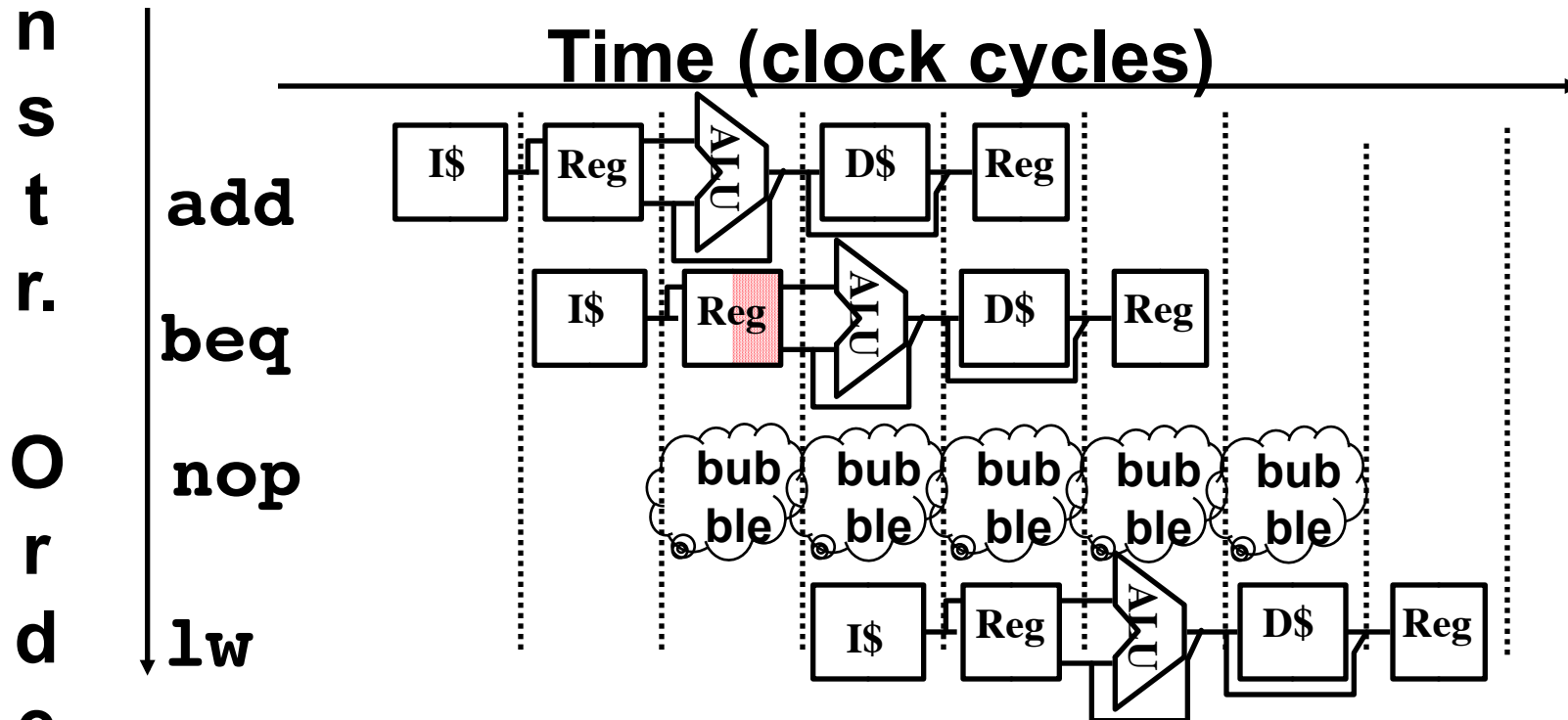


**Impact: 2 clock cycles per branch instruction  $\Rightarrow$  slow**



# Control Hazard: Branching (6b/8)

- Controller inserting a single bubble

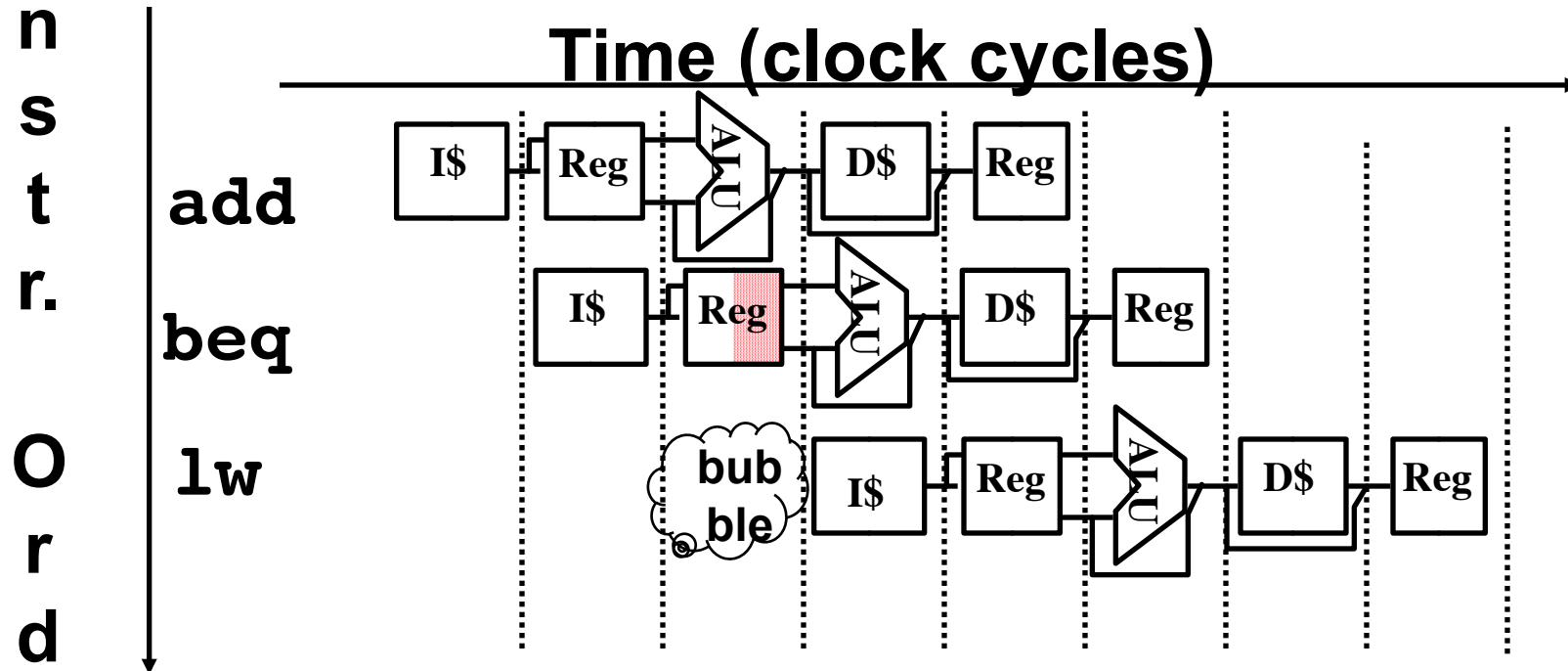

**Impact: 2 clock cycles per branch instruction ⇒ slow**



## **Control Hazard: Branching (7/8)**

---

- **Optimization #2: Redefine branches**
  - **Old definition: if we take the branch, none of the instructions after the branch get executed by accident**
  - **New definition: whether or not we take the branch, the single instruction immediately following the branch gets executed (called the **branch-delay slot**)**
- **The term “**Delayed Branch**” means **we always execute inst after branch****
- **This optimization is used with MIPS**





# Control Hazard: Branching (8/8)

---

- **Notes on Branch-Delay Slot**
  - **Worst-Case Scenario:** can always put a no-op in the branch-delay slot
  - **Better Case:** can find an instruction preceding the branch which can be placed in the branch-delay slot without affecting flow of the program
    - re-ordering instructions is a common method of speeding up programs
    - compiler/assembler must be very smart in order to find instructions to do this
    - usually can find such an instruction at least 50% of the time
    - Jumps also have a delay slot...



# Example: Nondelayed vs. Delayed Branch

**MAL**

**Nondelayed Branch**

or \$8, \$9, \$10

add \$1, \$2, \$3

sub \$4, \$5, \$6

beq \$1, \$4, Exit

xor \$10, \$1, \$11

Exit:

**TAL**

**Delayed Branch**

add \$1, \$2, \$3

sub \$4, \$5, \$6

beq \$1, \$4, Exit

or \$8, \$9, \$10

xor \$10, \$1, \$11

Exit:



## Data Hazards (1/2)

---

- Consider the following sequence of instructions

add \$t0, \$t1, \$t2

sub \$t4, \$t0, \$t3

and \$t5, \$t0, \$t6


or \$t7, \$t0, \$t8

xor \$t9, \$t0, \$t10




# Data Hazards (2/2)

- Data-flow backward in time are hazards

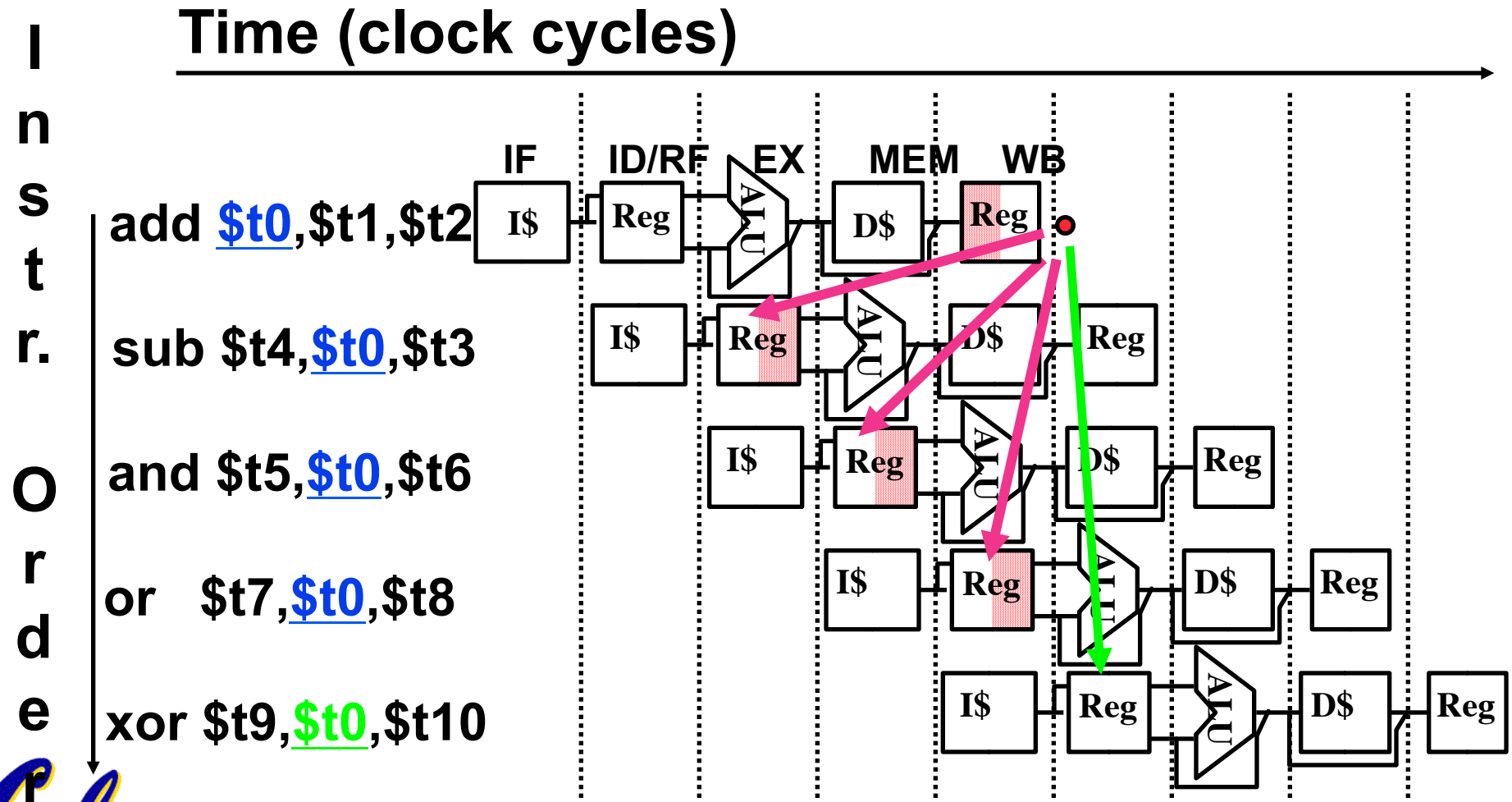
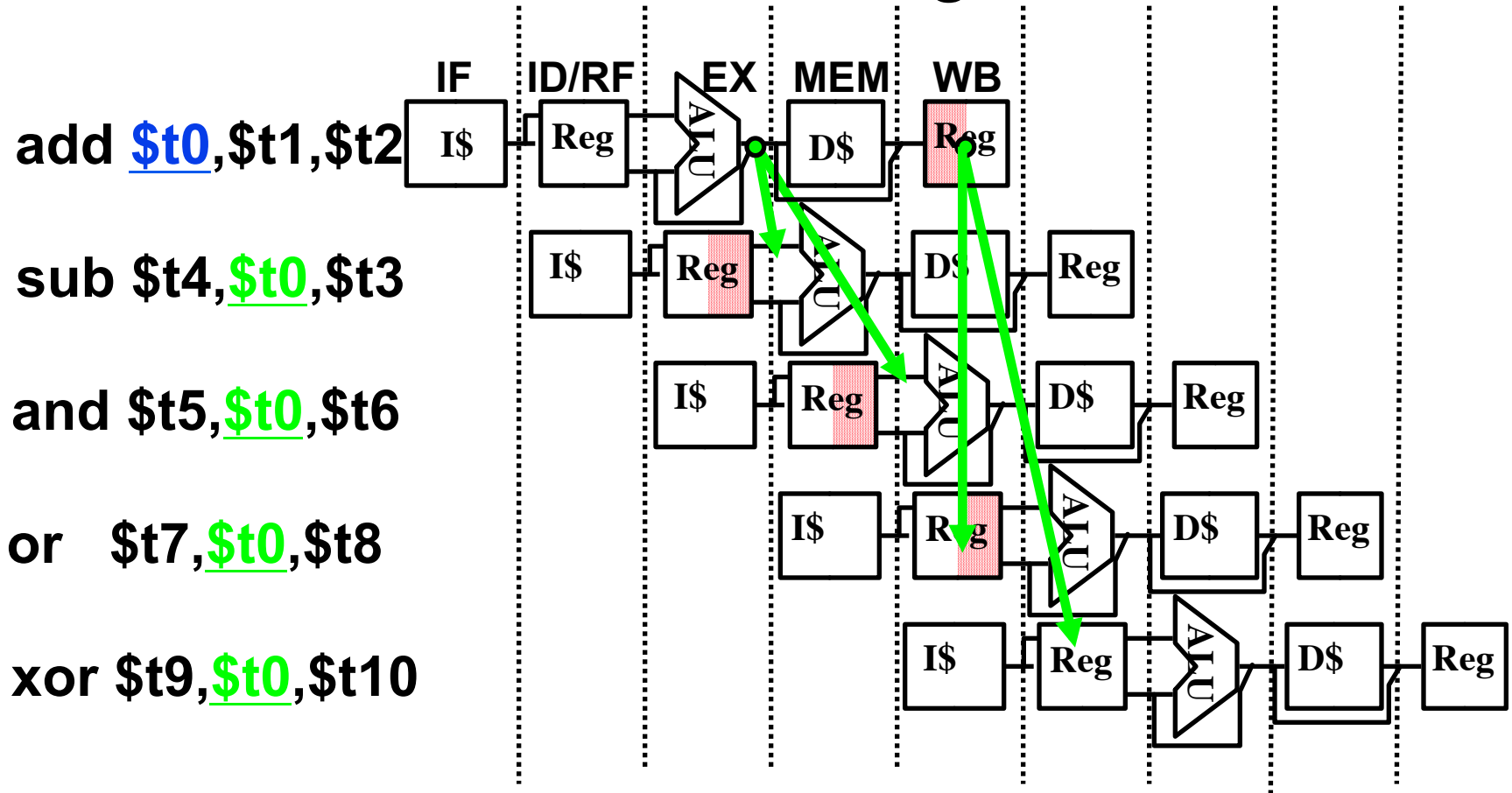
# Data Hazard Solution: Forwarding


- Forward result from one stage to another



“or” hazard solved by register hardware

# Data Hazard: Loads (1/4)

- Dataflow backwards in time are hazards

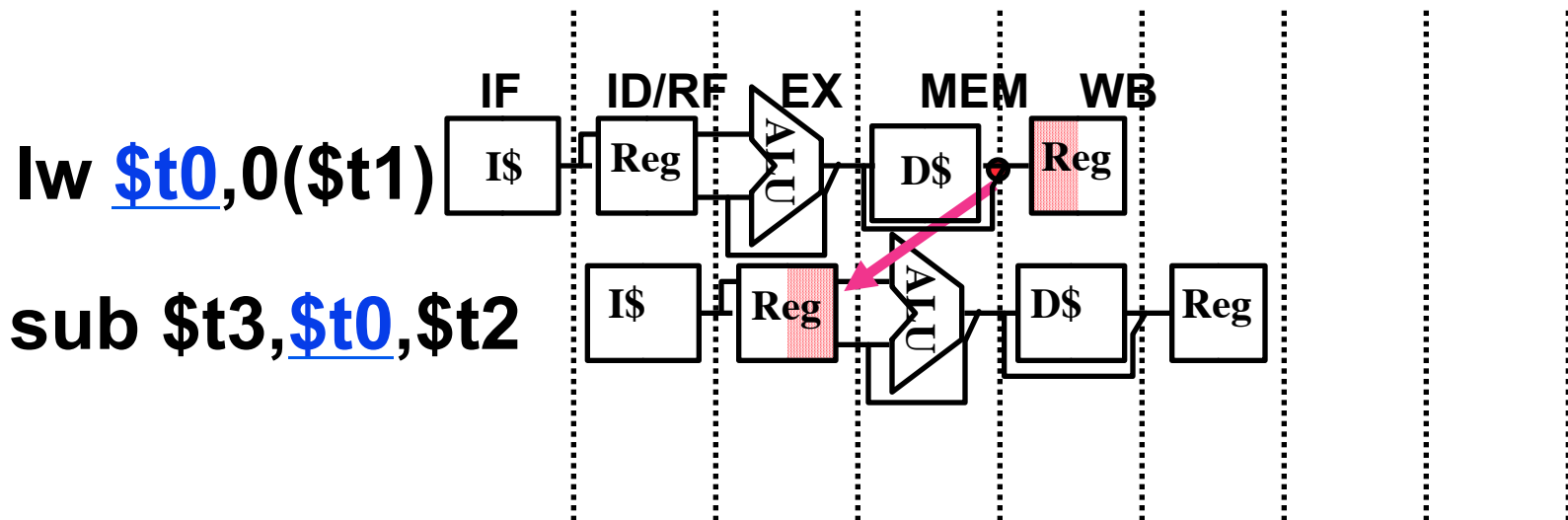

- Can't solve all cases with forwarding
- Must stall instruction dependent on load, then forward (more hardware)



# Data Hazard: Loads (2/4)


- Hardware stalls pipeline
  - Called “interlock”

lw \$t0, 0(\$t1)

sub \$t3, \$t0, \$t2

and \$t5, \$t0, \$t4

or \$t7, \$t0, \$t6

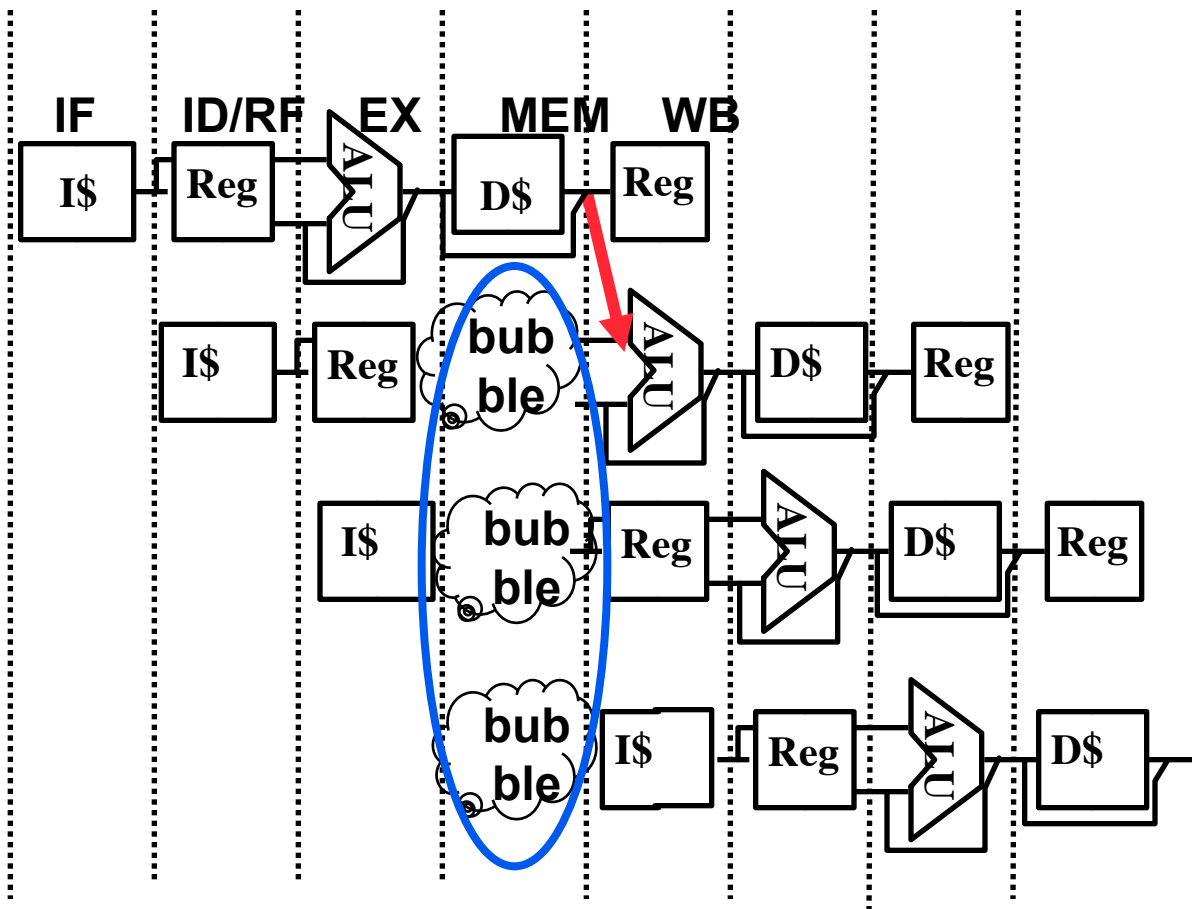

## Data Hazard: Loads (3/4)

- Instruction slot after a load is called **“load delay slot”**
- If that instruction uses the result of the load, then the hardware interlock will stall it for one cycle.
- If the compiler puts an unrelated instruction in that slot, then no stall
- Letting the hardware stall the instruction in the delay slot is equivalent to putting a nop in the slot (except the latter uses more code space)





# Data Hazard: Loads (4/4)

- Stall is equivalent to nop


lw \$t0, 0(\$t1)

nop

sub \$t3, \$t0, \$t2

and \$t5, \$t0, \$t4


or \$t7, \$t0, \$t6

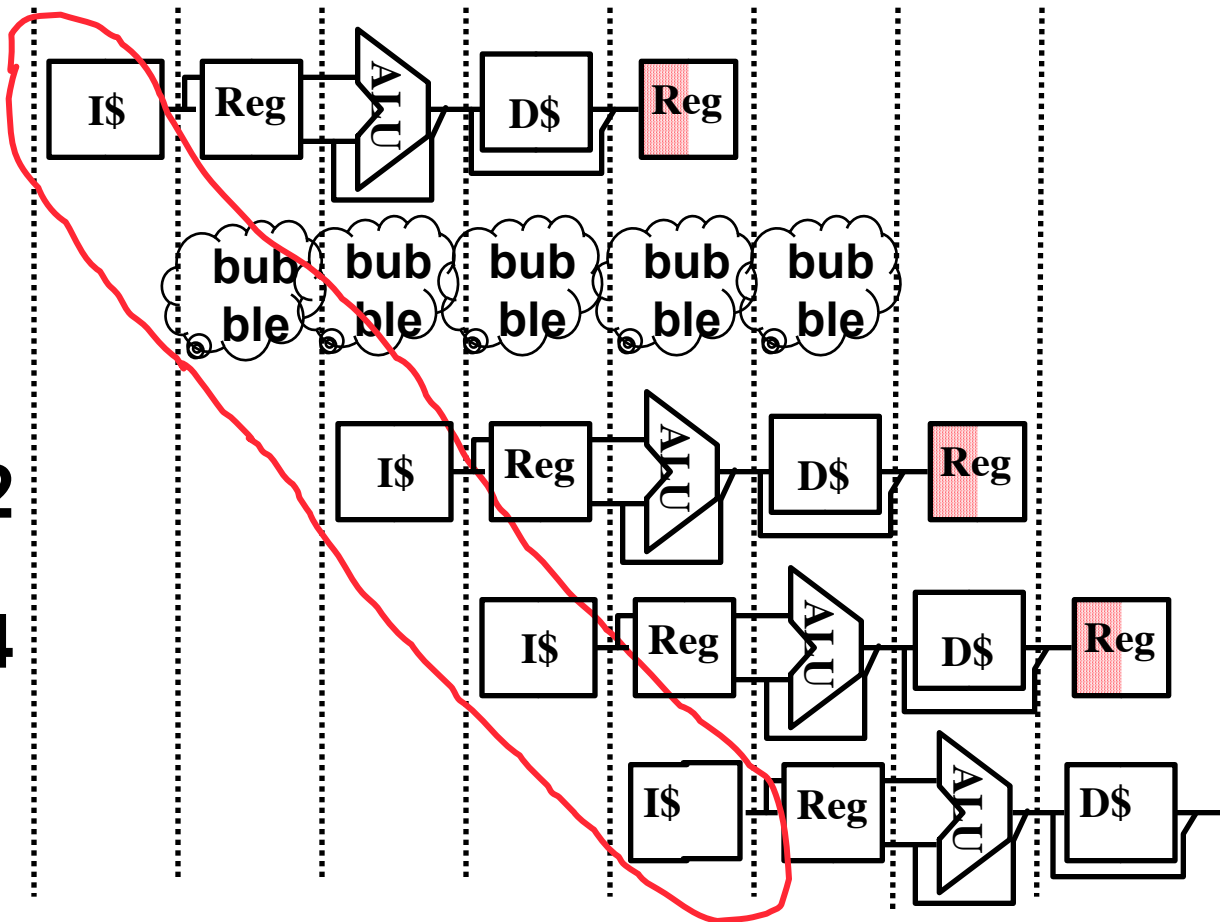

# Summary: Single-cycle Processor

## ◦ 5 steps to design a processor

 - 1. Analyze instruction set → datapath requirements
- 2. Select set of datapath components & establish clock methodology
- 3. Assemble datapath meeting the requirements
- 4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
- 5. Assemble the control logic
  - Formulate Logic Equations
  - Design Circuits



# Things to Remember

---

- **Optimal Pipeline**
  - **Each stage is executing part of an instruction each clock cycle.**
  - **One instruction finishes during each clock cycle.**
  - **On average, execute far more quickly.**
- **What makes this work?**
  - **Similarities between instructions allow us to use same stages for all instructions (generally).**
  - **Each stage takes about the same amount of time as all others: little wasted time.**



## **“And in Conclusion..”**

---

- **Pipeline challenge is hazards**
  - Forwarding helps w/many data hazards
  - Delayed branch helps with control hazard in 5 stage pipeline
  - Load delay slot / interlock necessary
- **More aggressive performance:**
  - Superscalar
  - Out-of-order execution



## Bonus slides


---

- **These are extra slides that used to be included in lecture notes, but have been moved to this, the “bonus” area to serve as a supplement.**
- **The slides will appear in the order they would have in the normal presentation**

# Bonus



# RTL: The Add Instruction

 

**add rd, rs, rt**

- **MEM[PC]**      **Fetch the instruction from memory**
- **$R[rd] = R[rs] + R[rt]$**       **The actual operation**
- **$PC = PC + 4$**       **Calculate the next instruction's address**



# A Summary of the Control Signals (1/2)

## inst                      Register Transfer

**add**                                       $R[rd] \leftarrow R[rs] + R[rt]; PC \leftarrow PC + 4$

**ALUsrc = RegB, ALUctr = "ADD", RegDst = rd, RegWr, nPC\_sel = "+4"**

**sub**                                       $R[rd] \leftarrow R[rs] - R[rt]; PC \leftarrow PC + 4$

**ALUsrc = RegB, ALUctr = "SUB", RegDst = rd, RegWr, nPC\_sel = "+4"**

**ori**                                       $R[rt] \leftarrow R[rs] + \text{zero\_ext}(\text{Imm16}); \quad PC \leftarrow PC + 4$

**ALUsrc = Im, Extop = "Z", ALUctr = "OR", RegDst = rt, RegWr, nPC\_sel = "+4"**

**lw**                                       $R[rt] \leftarrow \text{MEM}[R[rs] + \text{sign\_ext}(\text{Imm16})]; \quad PC \leftarrow PC + 4$

**ALUsrc = Im, Extop = "sn", ALUctr = "ADD",  
MemtoReg, RegDst = rt, RegWr,                      nPC\_sel = "+4"**

**sw**                                       $\text{MEM}[R[rs] + \text{sign\_ext}(\text{Imm16})] \leftarrow R[rs]; \quad PC \leftarrow PC + 4$

**ALUsrc = Im, Extop = "sn", ALUctr = "ADD", MemWr, nPC\_sel = "+4"**

**beq if (  $R[rs] == R[rt]$  ) then  $PC \leftarrow PC + \text{sign\_ext}(\text{Imm16}) \parallel 00$  else  $PC \leftarrow PC + 4$**


**nPC\_sel = "br", ALUctr = "SUB"**


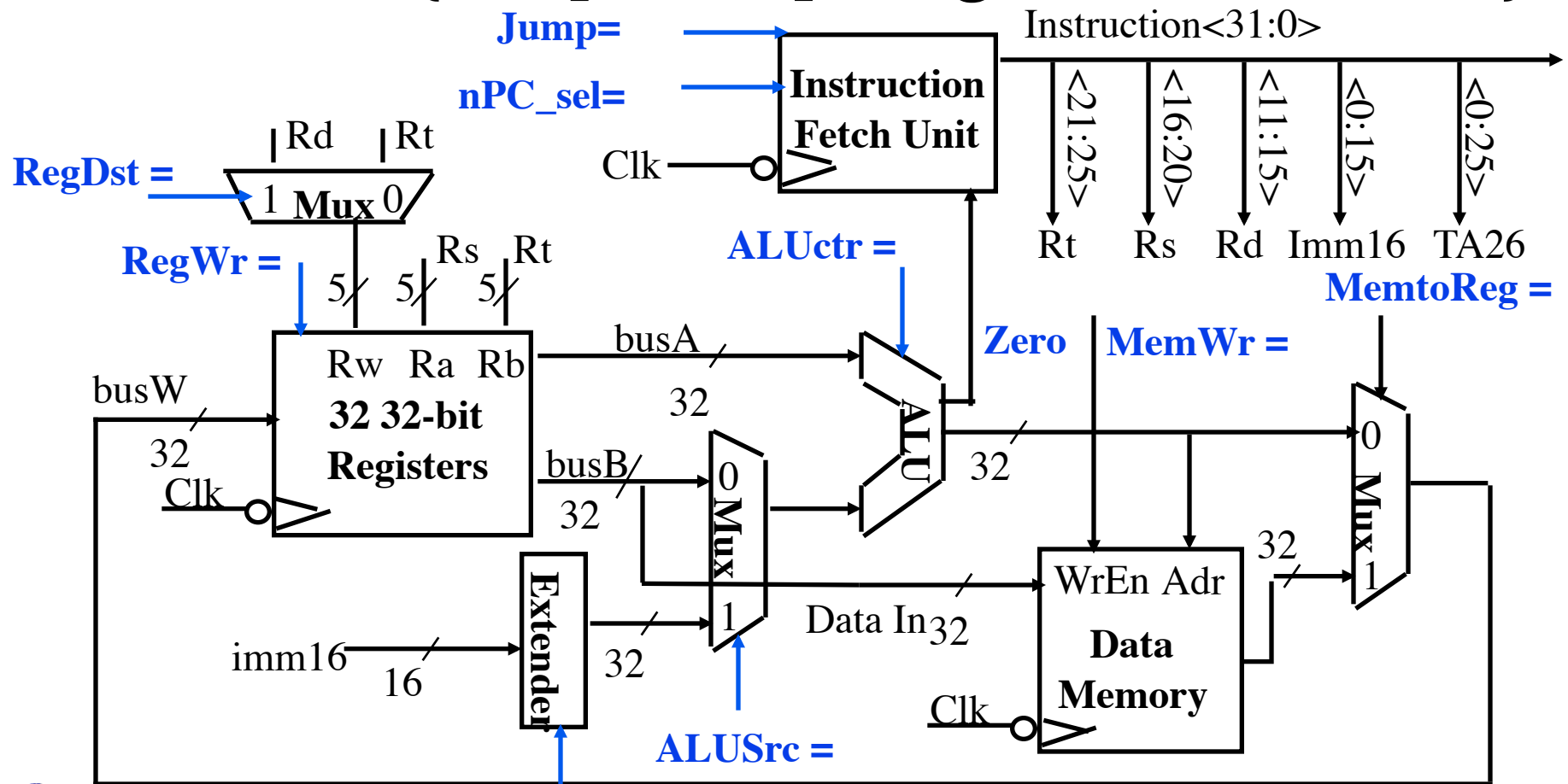
# The Single Cycle Datapath during Jump



- **New PC = { PC[31..28], target address, 00 }**





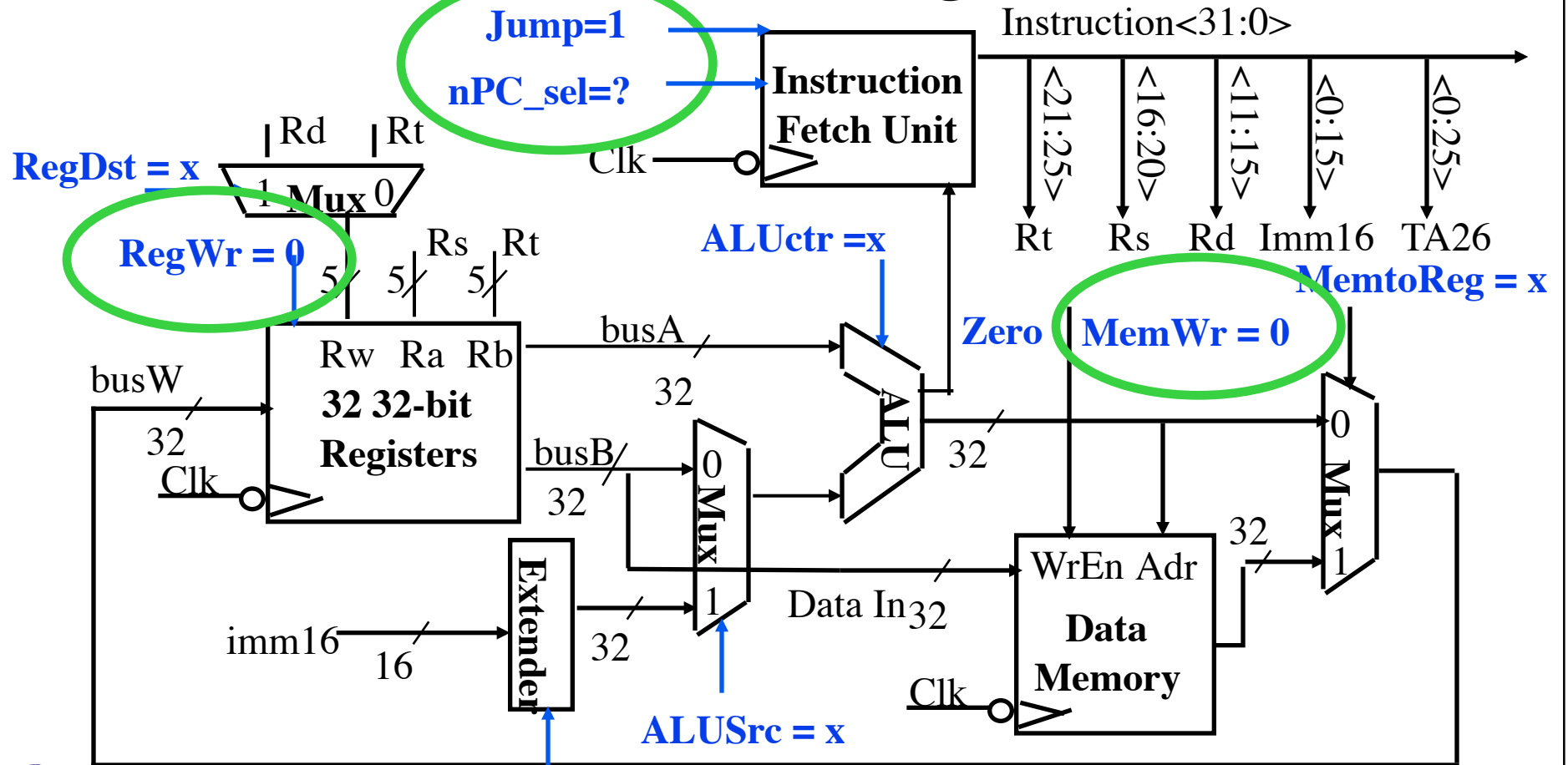
# The Single Cycle Datapath during Jump





• **New PC = { PC[31..28], target address, 00 }**


  
# Instruction Fetch Unit at the End of Jump



• **New PC = { PC[31..28], target address, 00 }**




How do we modify this to account for jumps?


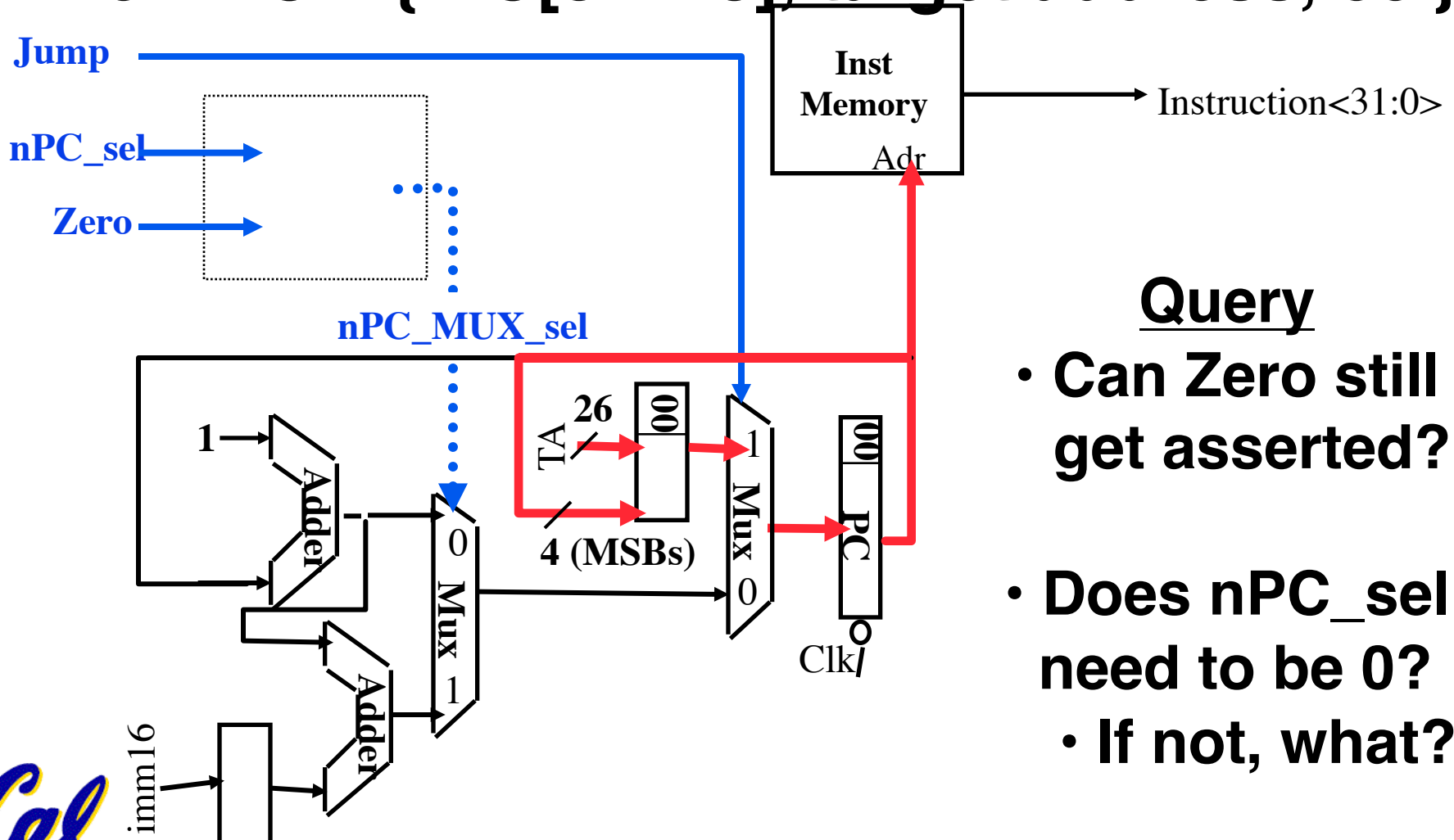
# Instruction Fetch Unit at the End of Jump



• **New PC = { PC[31..28], target address, 00 }**



## Query

- Can Zero still get asserted?
- Does nPC\_sel need to be 0?
  - If not, what?




# Historical Trivia

---

- **First MIPS design did not interlock and stall on load-use data hazard**
- **Real reason for name behind MIPS:**  
**M**icroprocessor without  
**I**nterlocked  
**P**ipeline  
**S**tages
  - **Word Play on acronym for Millions of Instructions Per Second, also called MIPS**



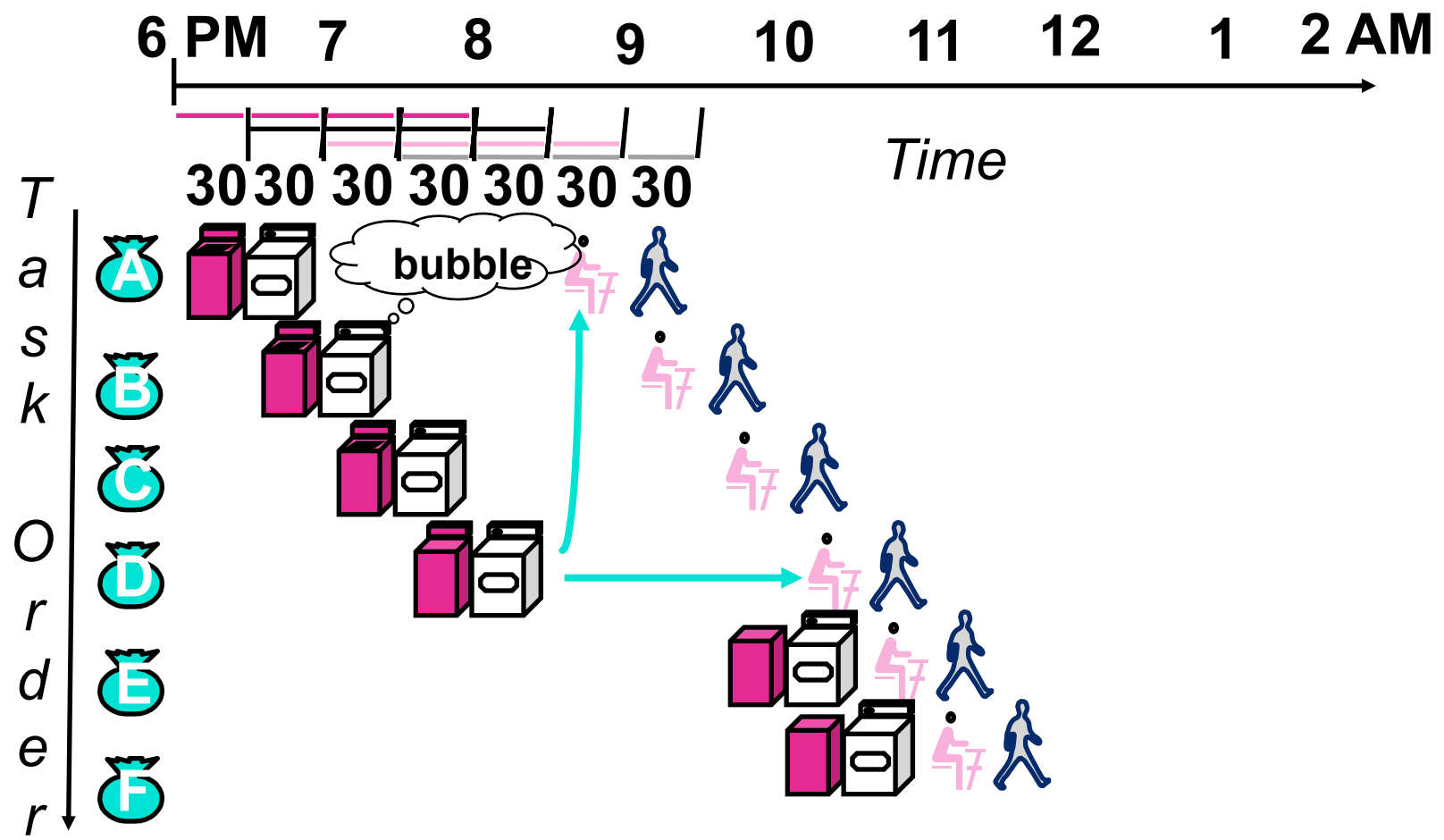
# Pipeline Hazard: Matching socks in later load




A depends on D; stall since folder tied up; Note this is much different from processor cases so far. We have not had an earlier instruction depend on a later one.

# Out-of-Order Laundry: Don't Wait

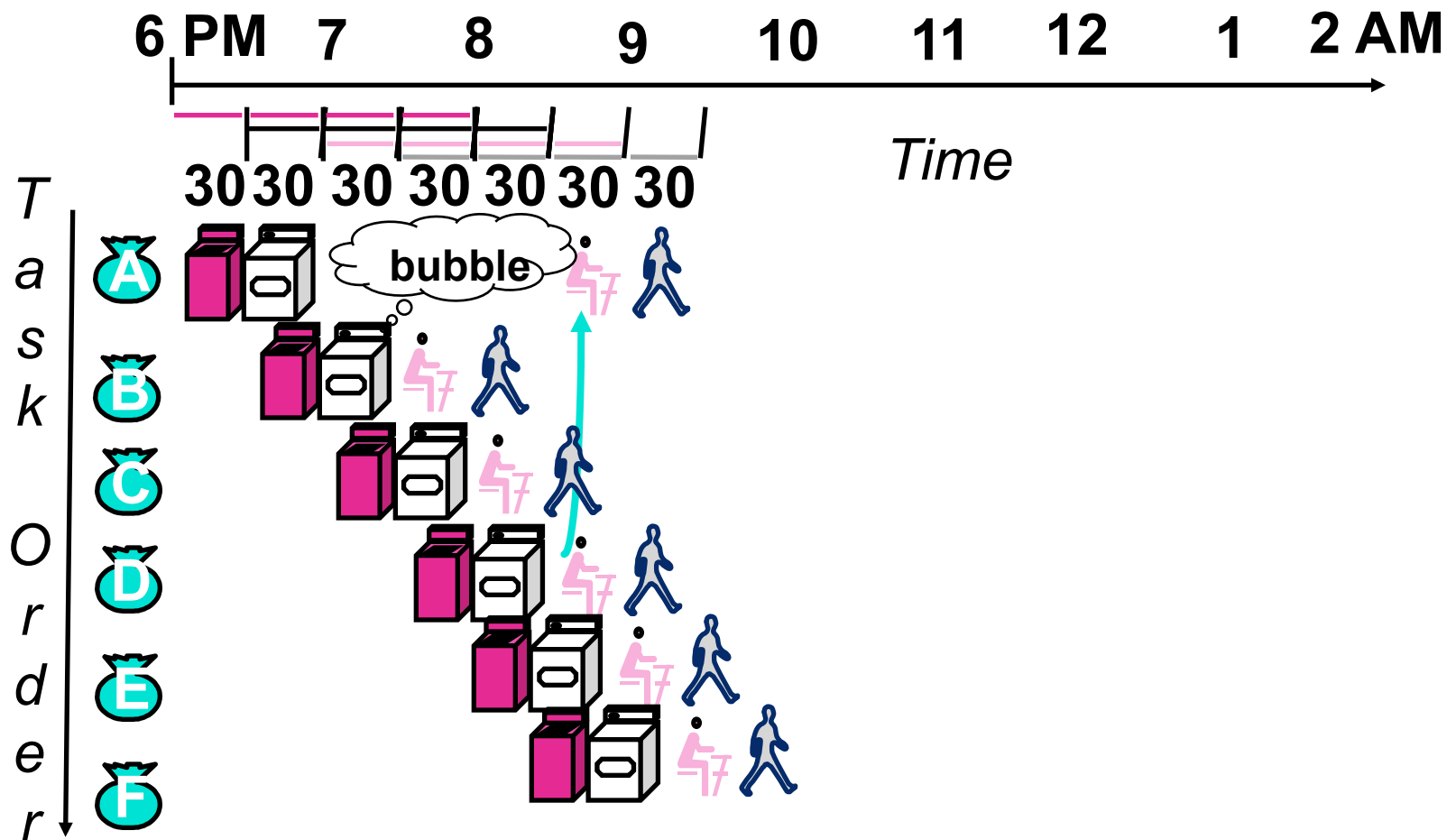

- A depends on D: rest continue: need more
 
# Superscalar Laundry: Parallel per stage



- More resources. HW to match mix of parallel

# Superscalar Laundry: Mismatch Mix

