

**Fill out information below and attach this cover sheet to the FRONT of your HW.
If you do not (or enter incorrect information) you WILL loose 10 points on the HW.**

NAME: _____

SID #: _____

Circle One: EE42 / EE100

If EE100, Lab Day: _____, **Time:** _____

EE 100

Homework # 6

L. Chua

Issued : Oct. 3

Fall 2008

Due : Oct. 10

1. Problem 5.2

p.176

2. Problem 5.5

p.176

3. (a) Apply *load line analysis* to find the *operating point* voltage v_D of the ideal diode circuit in Fig.1 with $v_i = 10$ V. Show your graphical constructions.

(b) Apply *load line analysis* to find the *operating point* current i_D of the ideal diode circuit in Fig.2 with $v_i = 5$ V. Show your graphical constructions.

(c) Derive and sketch the *transfer characteristic plot* (TC plot) of the *ideal diode* circuits shown in Figs. 1 and 2.

(d) Sketch the output voltage $v_o(t)$ of Figs. 1 and 2 with $v_i(t) = 30 \sin t$ volts.

 


Fig. 1

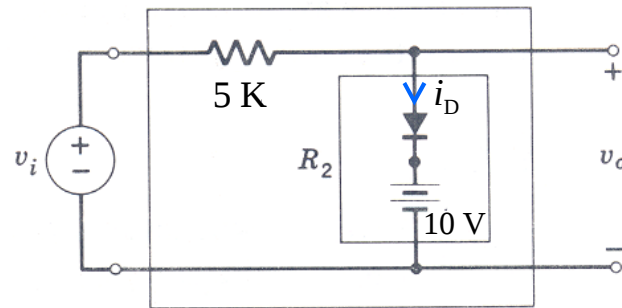


Fig. 2

4. (a) Assuming the nonlinear ideal op-amp model with $E_{sat} = 15$ V, derive and sketch the driving-point characteristic for the one-port shown in Fig. P4.14.

(b) Connect a linear resistor R_1 across the one-port, and find the maximum value of the resistance for which the one-port functions as an independent current source.

 


Figure P4.14