

Fill out information below and attach this cover sheet to the FRONT of your HW.  
If you do not (or enter incorrect information) you WILL loose 10 points on the HW.

NAME: \_\_\_\_\_

SID #: \_\_\_\_\_

Circle One: EE42 / EE100

If EE100, Lab Day: \_\_\_\_\_, Time: \_\_\_\_\_

## EE 100

### Homework # 7

L. Chua

Issued : Oct. 10

Fall 2008

Due : Oct. 17

1. Problem 5.2 p.176

2. Problem 5.5 p.176

3.(a) Assuming the nonlinear ideal op-amp model with  $E_{\text{sat}} = 15 \text{ V}$ , derive and sketch the driving-point characteristic for the one-port shown in Fig. P4.14.

(b) Connect a linear resistor  $R_1$  across the one-port, and find the maximum value of the resistance for which the one-port functions as an independent current source.

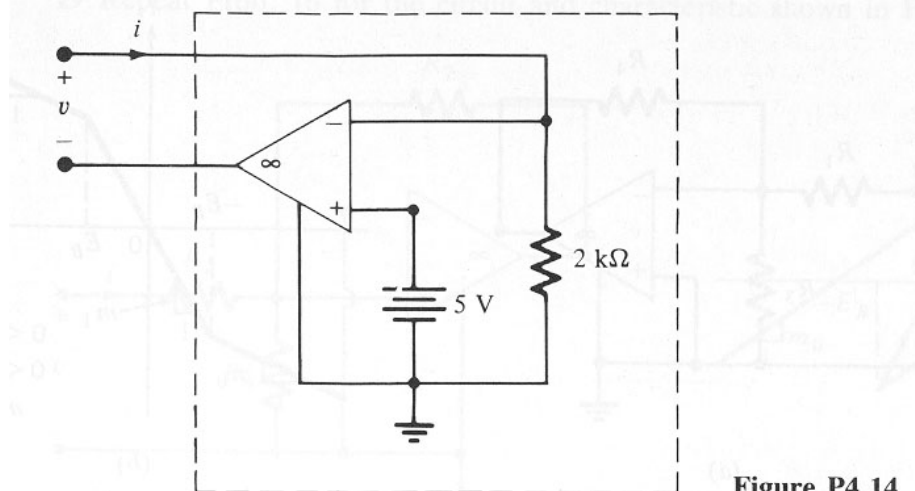


Figure P4.14