

Fill out information below and attach this cover sheet to the FRONT of your HW.
 If you do not (or enter incorrect information) you WILL loose 10 points on the HW.

NAME: _____

SID #: _____

Circle One: EE42 / EE100

If EE100, Lab Day: _____, Time: _____

EE 100

Homework # 12



L. Chua

Fall 2008



Issued : Nov. 14

Due : Nov. 21

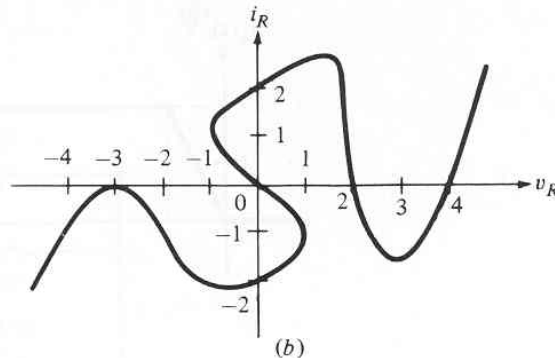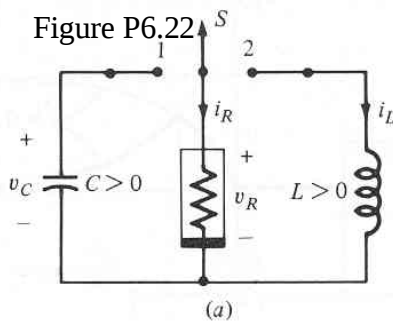1. For the circuit shown in Fig. P6.22a with the nonlinear resistor as in Fig. P6.22b, find all equilibrium states and classify each as stable or unstable:
- When switch S is in position 1.
 - When switch S is in position 2.



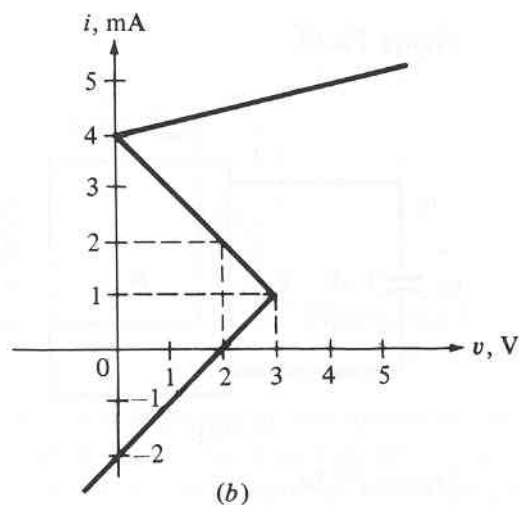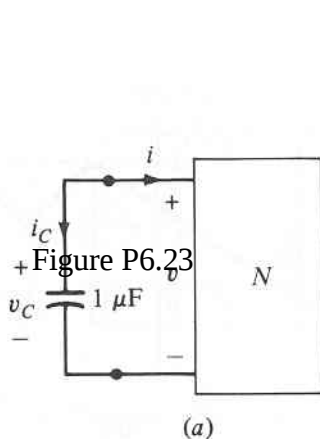2. Consider the circuit and characteristic shown in Fig. P6.23a and b.
- Sketch the dynamic route.
 - If $v_c(0) = 2 \text{ V}$ and $i_c(0) = -2 \text{ mA}$, calculate and sketch $i(t)$ and $v(t)$ for $t \geq 0$.



3. Consider the circuit shown in Fig. P6.25a where the one-port is described by the v - i characteristic in Fig. P6.25b.
- Sketch the dynamic route.
 - If $i_L(0) = -15$ mA, find and sketch $i(t)$ and $v(t)$ for $t \geq 0$.
 - Determine all switching times.
 - Calculate the period of oscillation.

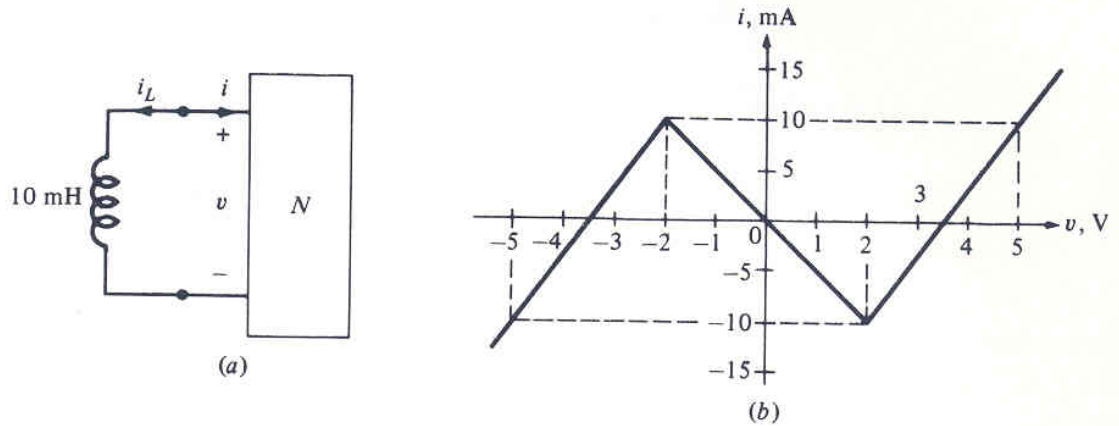


Figure P6.25

4. Do the assessment problem on page 342 of the textbook.