

Power in Sinusoidal Signal

$$\begin{aligned} \langle P \rangle &= \\ & \frac{1}{T} \int_0^T V_0 \cos(\omega t + \phi_1) I_0 \cos(\omega t + \phi_2) dt \\ &= V_0 I_0 \frac{1}{T} \int_0^T \left(\cos^2(\omega t) \cos(\phi_1) \cos(\phi_2) \right. \\ & \quad \left. + \sin^2(\omega t) \sin(\phi_2) \sin(\phi_1) \right. \\ & \quad \left. + \dots \cos(\omega t) \sin(\omega t) \right) dt \end{aligned}$$

Sinusoidal Power Contd.

$$\langle P \rangle =$$

$$= \frac{1}{2} V_0 I_0 (\cos(\phi_1) \cos(\phi_2) + \sin(\phi_1) \sin(\phi_2))$$

$$= \frac{1}{2} V_0 I_0 \cos(\phi_1 - \phi_2)$$

$$= V_{RMS} I_{RMS} \cos(\Delta\phi)$$

Phasor Form of Power

$$\mathbf{V} = V_0 e^{j\phi_1}$$


$$\mathbf{I} = I_0 e^{j\phi_2}$$

$$P = \frac{1}{2} V_0 I_0 \cos(\phi_1 - \phi_2)$$

$$= \frac{1}{2} V_0 I_0 \Re e [e^{j(\phi_1 - \phi_2)}]$$

$$= \frac{1}{2} \Re e (\mathbf{V} \mathbf{I}^*)$$

Optimum Load: DC Case

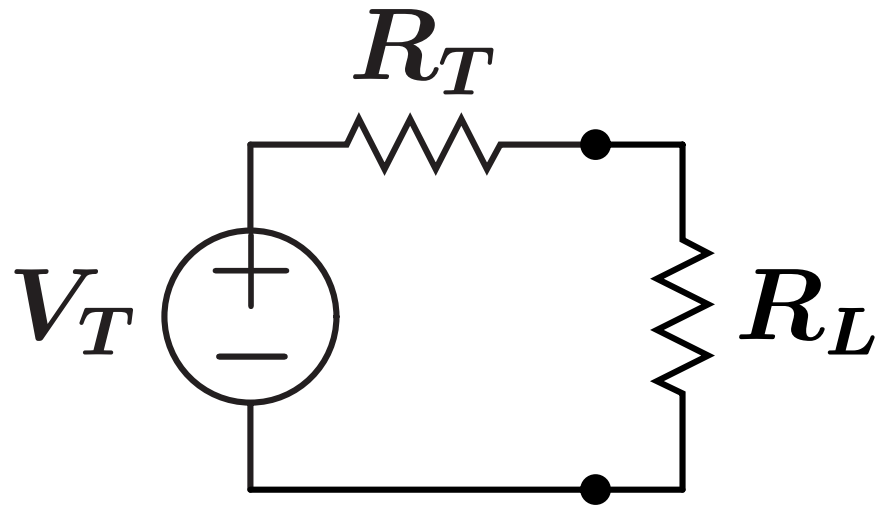

$$P_L = V_0 \left(\frac{R_L}{R_L + R_T} \right) \left(\frac{V_0}{R_L + R_T} \right)$$

DC Optimum Load Contd.

let $x = R_L/R_T$:

$$P_L = \frac{V_0^2}{R_T} \left(\frac{x}{(1+x)^2} \right)$$


$d/dx = 0$ when:

$$\frac{1-x}{(1+x)^3} = 0 \rightarrow x = 1$$

Optimum Load is when

$$R_L = R_T$$

Optimum Load: AC Case

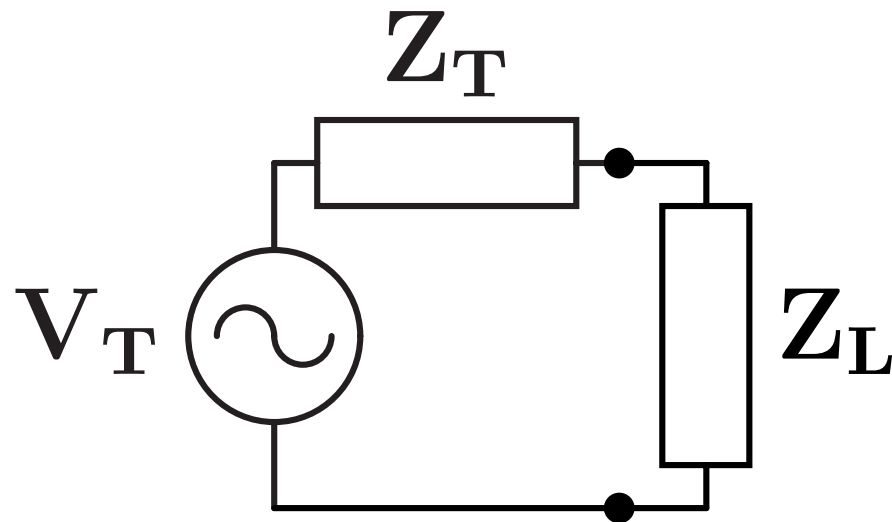

$$P_L = \Re e \left[\frac{V_T}{2} \left(\frac{Z_L}{Z_L + Z_T} \right) \left(\frac{V_T}{Z_L + Z_T} \right)^* \right]$$

AC Optimum Load Contd.

$$P_L = (1/2)|V_T|^2 \left(\frac{R_L}{(R_L + R_T)^2 + (X_L + X_T)^2} \right)$$

Maximum when:

$$X_L = -X_T$$

Optimum Load is when

$$R_L = R_T$$

Conjugate Match Maximizes Power

$$X_L(\textit{opt}) = -X_T$$

$$R_L(\textit{opt}) = R_T$$

$$Z_L(\textit{opt}) = Z_T^*$$

$$P_{max} = \frac{|V_T|^2}{8R_T}$$