

Solutions Prepared by Lynn Wang
ting 0918@eecs.berkeley.edu.

2. Hambley 3rd Ed, P12.4

$$V_{t0} = 3V$$

$$K = 0.5 \text{ mA}/V^2$$


$$V_{GS} = 5V$$

Triode Region $V_{GS} - V_{t0} \geq V_{DS} \Rightarrow 5 - 3 \geq V_{DS}$

$$\boxed{2V \geq V_{DS}}$$

Saturation Region $V_{GS} - V_{t0} \leq V_{DS} \Rightarrow 5 - 3 < V_{DS}$

$$\boxed{2V < V_{DS}}$$

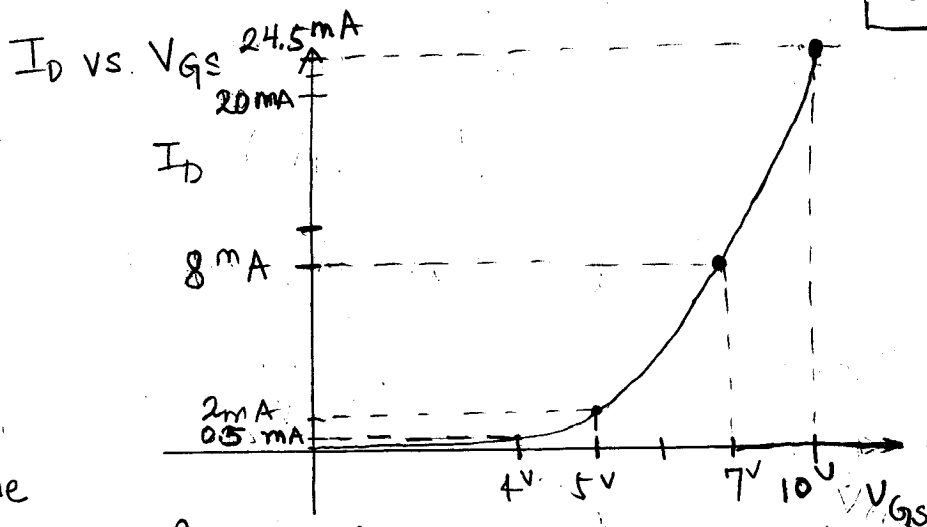

Assume

Saturation region:

$$V_{GS} = 5 \quad I_D = \frac{K}{2} (V_{GS} - V_t)^2 = 0.5 \text{ m} (5 - 3)^2 = 0.5 \text{ m} (4) = 2 \text{ mA}$$

$$V_{GS} = 10 \quad I_D = \frac{0.5 \text{ m}}{2} (10 - 3)^2 = \frac{0.5}{2} (7)^2 = 49 \left(\frac{1}{2}\right) = 24.5 \text{ mA}$$

$$V_{GS} = 7 \quad I_D = \frac{1}{2} (7 - 3)^2 = \frac{1}{2} (4)^2 = \frac{16}{2} = 8 \text{ mA}$$

$$V_{GS} = 4 \quad I_D = \frac{1}{2} (4 - 3)^2 = 0.5 \text{ mA}$$

3. Hambley 3rd Ed. P.12.9

$$i_D = 0.5 \text{ mA}$$

$$V_{GS} = V_{DS} = 5 \text{ V}$$

$$K_p = 50 \mu\text{A}/\text{V}^2$$

$$V_{t0} = 1 \text{ V}$$

$$V_{GS} - V_{t0} = 5 \text{ V} - 1 = 4 \text{ V} \leq V_{DS} = 5 \text{ V}$$

$\Rightarrow V_{DS} \geq V_{GS} - V_{t0} \Rightarrow \text{saturat}^n \text{ reg}^n.$

$$I_d = K (V_{GS} - V_{t0})^2 = \frac{1}{2} K_p \left(\frac{W}{L}\right) (V_{GS} - V_{t0})^2$$

Solving for $\left(\frac{W}{L}\right)$ ratio:

$$\left(\frac{W}{L}\right) = \frac{2 I_d}{K_p (V_{GS} - V_{t0})^2} = \frac{2 (0.5 \text{ mA})}{50 \mu\text{A}/\text{V}^2 (5 - 1)^2} = \frac{1 \text{ m}}{50 \mu (4)^2} = \frac{1 \text{ m}}{50 \mu (16)}$$

$$\boxed{\left(\frac{W}{L}\right) = 1.25}$$

For $L = 2 \mu\text{m}.$

$$W = 2(1.25) = \boxed{2.5 \mu\text{m}.}$$

4. Hambley 3rd Ed, P.12.16

Why does distortion occur in FET amplifiers?

- curvature
- non-uniform spacing of characteristic curves


5. Hambley 3rd Ed, P.12.18

$i_D - v_{DS}$ axes - load lines

a. $R_D = 1\text{K}\Omega$, $V_{DD} = 5\text{V}$

b. $R_D = 1\text{K}\Omega$, $V_{DD} = 10\text{V}$

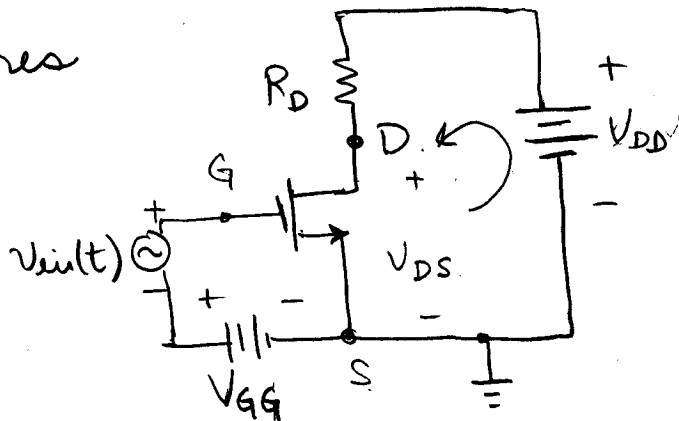c. $R_D = 1\text{K}\Omega$, $V_{DD} = 15\text{V}$



writing a KVL:

$$V_{DD} - i_D R_D - v_{DS}(t)$$

$$V_{DD} = i_D R_D + v_{DS}(t) \leftarrow \text{eqn. for the load line}$$

a. $R_D = 1\text{K}$ $5 = i_D (1\text{K}) + v_{DS}(t)$

$V_{DD} = 5\text{V}$


$$i_D (1\text{K}) = -v_{DS}(t) + 5$$


$$i_D = \frac{5 - v_{DS}}{1\text{K}} \quad \bar{i}_D (\text{mA})$$

b. $i_D = \frac{10 - v_{DS}}{1\text{K}}$

c. $i_D = \frac{15 - v_{DS}}{1\text{K}}$


shifts to the right

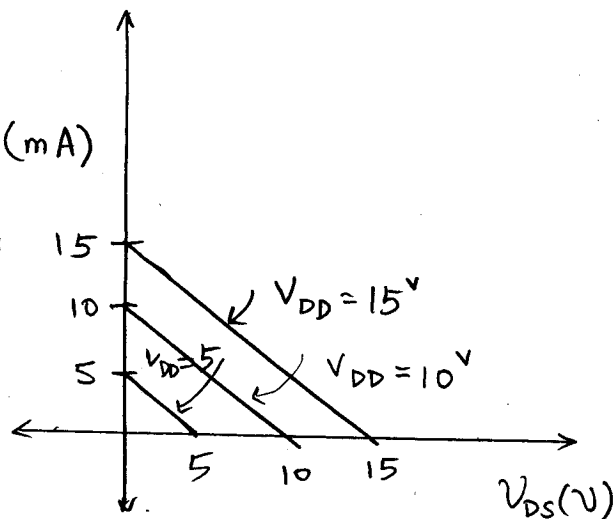

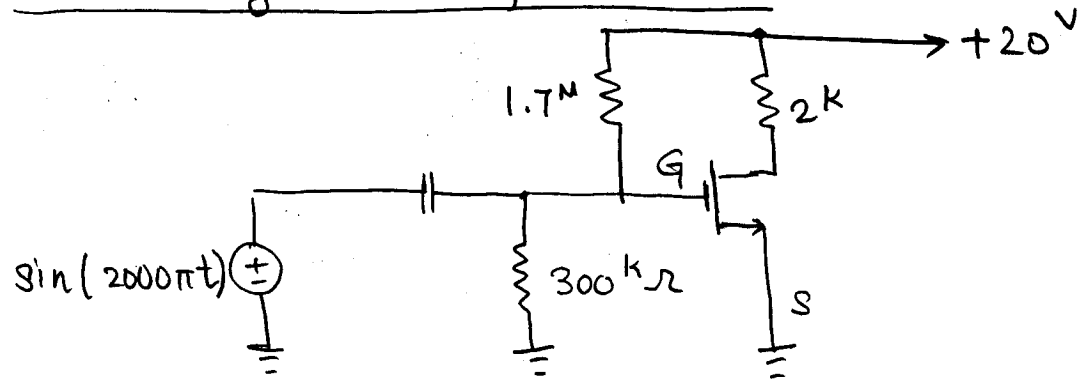


(a). Find $V_{GS}(t)$ (AC & DC).

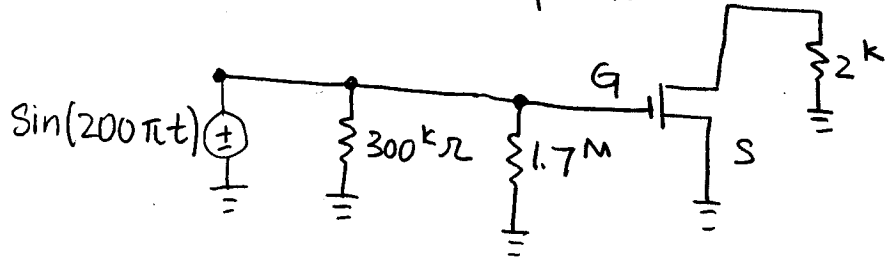AC signal (short DC voltage supplies)
Short capacitor



$$V_{GS}(t)_{AC} = \sin(200\pi t) \text{ V}$$

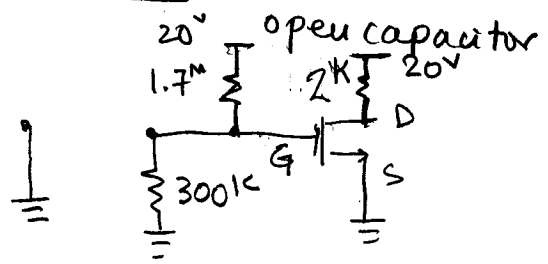DC signal (short all AC voltage supplies)



The $1.7\text{M}\Omega$ and $300\text{k}\Omega$ resistors act as voltage dividers

$$V_{GS,DC} = 20\text{V} \left(\frac{300\text{k}}{1.7\text{M} + 300\text{k}} \right) = 3\text{V}$$


$$V_{GS}(t) = V_{GS}(t)_{AC} + V_{GS,DC} = 3 + \sin(200\pi t) \text{ V}$$

(b) FET.

$$V_{to} = 1V$$

$$K = 0.5 \text{ mA/V}^2$$

$$V_{gs} = 1, 2, 3, 4V$$

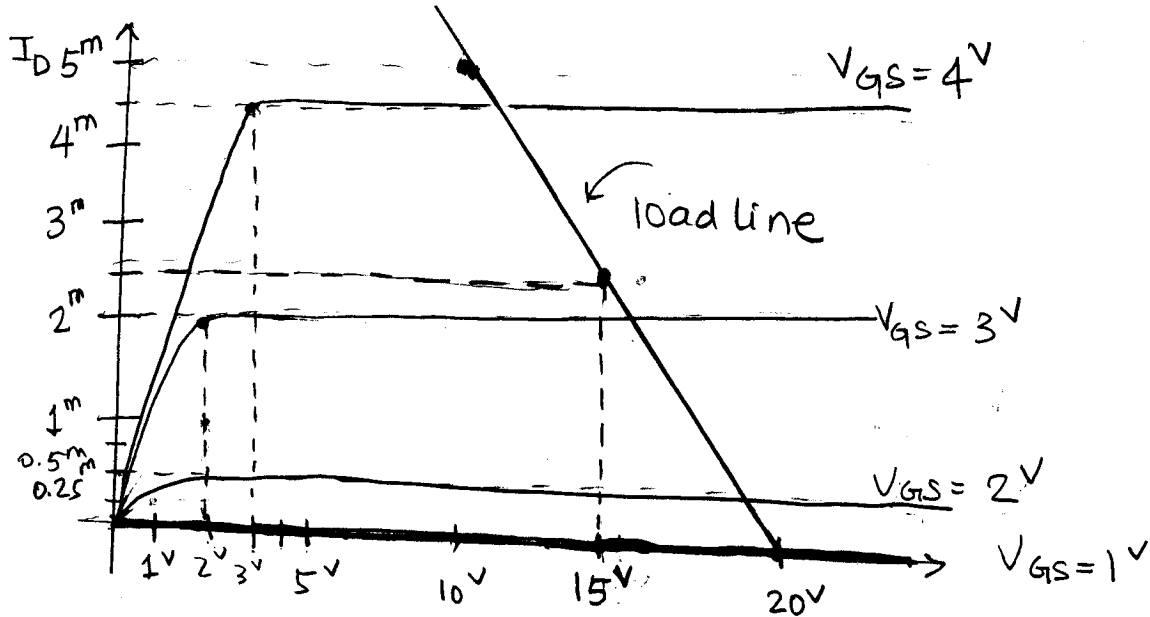

$$V_{gs} = 1$$

$$V_{gs} - V_{to} = 1 - 1 = 0 \quad \text{Device is off.}$$

$$V_{gs} = 2$$

Triode $V_{gs} - V_{to} \geq V_{DS}$
 $2 - 1 \geq V_{DS}$

$$1 \geq V_{DS}$$

$$V_{DS} \leq 1$$

saturatⁿ

$$V_{DS} \geq 1$$

$$I_D = K(V_{gs} - V_{to})^2 = 0.5 \text{ mA} (2 - 1)^2 = 0.5 \text{ mA}$$

$$V_{gs} = 3$$

$$V_{gs} - V_{to} = 3 - 1 = 2V$$

Sat.

$$V_{DS} \geq 2V$$

$$I_D = 0.5 \text{ mA} (3 - 1)^2 = 4 \cdot (0.5 \text{ mA}) = 2 \text{ mA}$$

$$V_{gs} = 4$$

$$V_{gs} - V_{to} = 4 - 1 = 3V$$

Sat. $V_{DS} \geq 3V$ $I_D = 0.5 \text{ mA} (4 - 1)^2 = \frac{9}{2} = 4.5 \text{ mA}$

V_{DS}

(c) Load line

$$V_{DS} + I_D 2K = 20V$$

$$I_D = \frac{20V - V_{DS}}{2K}$$

$$I_D = 10 \text{ mA} - \frac{V_{DS}}{2K}$$

$$\begin{cases} V_{DS} = 20V & I_D = 0 \\ V_{DS} = 15V & I_D = 2.5 \text{ mA} \\ V_{DS} = 10V & I_D = 5 \text{ mA} \end{cases}$$

$$(d) \quad V_{DSQ} (V_{GS} = 3V, V_{in}(t) = 0) \Rightarrow i_d = 2mA$$

$$2mA = 10mA - \frac{V_{DS}}{2K} \Rightarrow V_{DS} = 16V \Rightarrow \boxed{V_{DSQ} = 16V}$$

$$V_{DSmax} (i_d = 0.5mA)$$

$$9.5mA = \frac{V_{DS}}{2K} \Rightarrow V_{DS} = 19V \Rightarrow \boxed{V_{DSmax} = 19V}$$

$$V_{DSmin} (i_d = 4.5mA)$$

$$5.5 = \frac{V_{DS}}{2K} \Rightarrow V_{DS} = \boxed{V_{DSmin} = 11V}$$