

2. Relative dielectric constant for water is 78.5

The transducer consists of two capacitors in parallel
{ one above the surface of the liquid
{ one below the surface of liquid

$$C_{\text{above}} = 200 \times \frac{100 - X}{100} = 200 - 2X$$

$$C_{\text{below}} = 200 \times \frac{X}{100} \times 78.5 = 157X$$

$$C_{\text{total}} = C_{\text{above}} + C_{\text{below}} = \underline{\underline{200 + 155X}} \text{ pF}$$

Now, suppose there are 100cm of water

$$C_{\text{total}} = 200 \times 78.5 = 15700 \text{ pF}$$

However, if the top 1cm is oil rather than water


$$C_{\text{water}} = 200 \times \frac{99}{100} \times 78.5 = 15543$$

$$C_{\text{oil}} = 200 \times \frac{1}{100} \times 10 = 20$$

$$C_{\text{total}} = 15543 + 20 = 15563 \text{ pF}$$

$$\Delta C_{\text{total}} = 15700 - 15563 = \underline{\underline{137}} \text{ pF}$$


3. Find open-circuit voltage

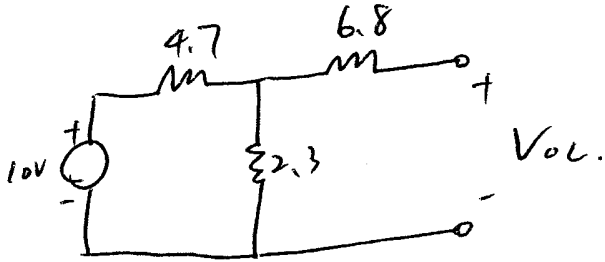

$$10 \times \frac{2.3}{4.7 + 2.3} = \frac{23}{7} = \underline{\underline{3.29 \text{ V} = V_{oc}}}$$


Find Thévenin Resistance
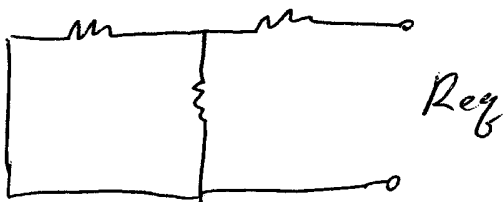
$$6.8 + \frac{1}{\frac{1}{4.7} + \frac{1}{2.3}} = \underline{\underline{8.34 \text{ k}\Omega = R_{eq}}}$$




$$I_{sc} = \frac{V_{oc}}{R_{eq}} = \underline{\underline{.39 \text{ mA}}}$$


Thévenin equivalent

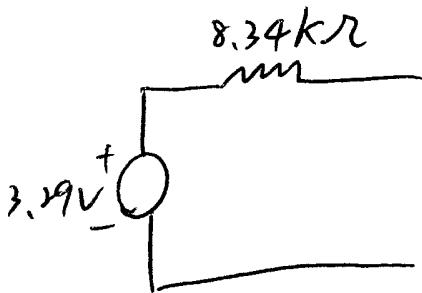


Norton equivalent

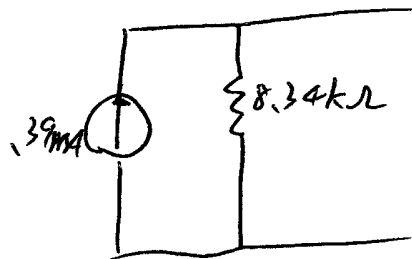

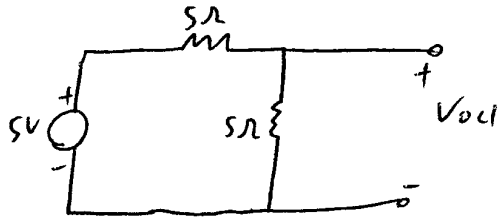4. Find open-circuit voltage through superposition




$$V_{oc1} = 2.5 \text{ V}$$

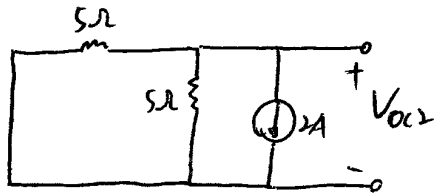


$$V_{oc2} = -5 \text{ V}$$

$$V_{oc} = V_{oc1} + V_{oc2} = \underline{\underline{-2.5 \text{ V}}}$$

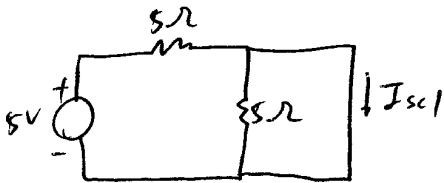Find Thévenin resistance by short-circuit current w/ superposition



$$I_{sc1} = 1 \text{ A}$$

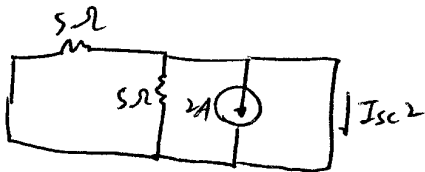


$$I_{sc2} = -2 \text{ A}$$

$$I_{sc} = I_{sc1} + I_{sc2} = \underline{\underline{-1 \text{ A}}}$$

$$R_{eq} = \frac{V_{oc}}{I_{sc}} = \underline{\underline{2.5 \Omega}}$$

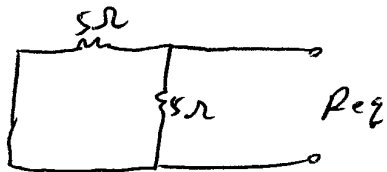Find Thévenin resistance in alternative way




$$R_{eq} = \frac{1}{\frac{1}{5} + \frac{1}{5}} = \underline{\underline{2.5 \Omega}}$$

Thévenin equivalent is below




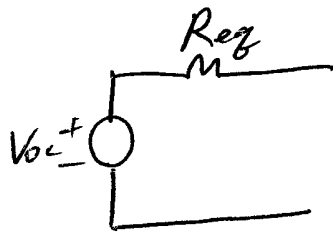5. The battery can be considered as a circuit w/ Thevenin equivalent



$$V_{oc} \text{ is } \underline{\underline{6V}} = V_T$$

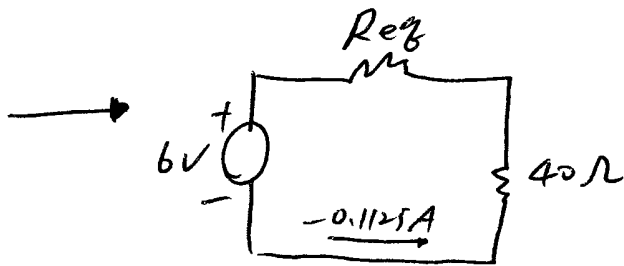
The measured current when connecting a 40Ω is -0.1125



$$R_{eq} + 40 = \frac{6}{0.1125} = 53.33$$


$$\underline{\underline{R_{eq} = 13.33\Omega}} = R_T$$

6.

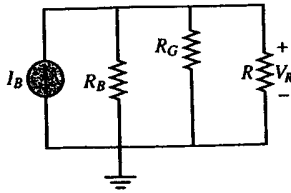

(b)

Figure 3.30 (b) Circuit obtained by suppressing the voltage source

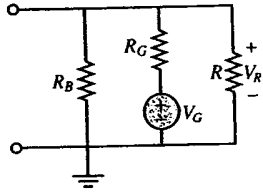

(c)

Figure 3.30 (c) Circuit obtained by suppressing the current source

Analysis: Specify a ground node and the polarity of the voltage across R . Suppress the voltage source by replacing it with a short circuit. Redraw the circuit, as shown in Figure 3.30(b), and apply KCL:

$$-I_B + \frac{V_{R-I}}{R_B} + \frac{V_{R-I}}{R_G} + \frac{V_{R-I}}{R} = 0$$

$$V_{R-I} = \frac{I_B}{1/R_B + 1/R_G + 1/R} = \frac{12}{1/1 + 1/0.3 + 1/0.23} = 1.38 \text{ V}$$

Suppress the current source by replacing it with an open circuit, draw the resulting circuit, as shown in Figure 3.30(c), and apply KCL:

$$\frac{V_{R-V}}{R_B} + \frac{V_{R-V} - V_G}{R_G} + \frac{V_{R-V}}{R} = 0$$

$$V_{R-V} = \frac{V_G/R_G}{1/R_B + 1/R_G + 1/R} = \frac{12/0.3}{1/1 + 1/0.3 + 1/0.23} = 4.61 \text{ V}$$

Finally, we compute the voltage across R as the sum of its two components:

$$V_R = V_{R-I} + V_{R-V} = 5.99 \text{ V}$$

Comments: Superposition essentially doubles the work required to solve this problem. The voltage across R can easily be determined by using a single KCL.

7.

$$C_{\text{total}} = \frac{1}{\frac{1}{0.015} + \frac{1}{0.022 + 0.01}} = \underline{\underline{0.01 \mu\text{F}}}$$

$$L_{\text{total}} = \frac{1}{\frac{1}{3} + \frac{1}{1 + 2.5}} = \underline{\underline{1.62 \text{ mH}}}$$

$$8. \quad I_0 = C \frac{d}{dt} V_C(t)$$

$$dV_C = \frac{I_0}{C} dt$$

$$\text{Integrating: } V_C = \frac{I_0}{C} \int dt \\ = \frac{I_0 t}{C} + K$$

K represents the value of V_C at time $t=0$

$$K = 0$$

$$V_C = \frac{10 \text{ mA}}{10 \mu\text{F}} t = \underline{\underline{1000 t}} \text{ volt}$$

9.

$$Q = CV = 5 \times 10^{-6} \times 10^3 = 5 \text{ mC}$$

$$W = \frac{1}{2} CV^2 = \frac{1}{2} \times 5 \times 10^{-6} \times (10^3)^2 = 2.5 \text{ J}$$

$$P = \frac{\Delta W}{\Delta t} = \frac{2.5}{10^{-6}} = 2.5 \text{ MW}$$

10、

$$\begin{aligned}i(t) &= C \frac{dv}{dt} \\&= 10^{-6} \frac{d}{dt} (100e^{-100t}) \\&= -0.01e^{-100t} \text{ A}\end{aligned}$$

$$\begin{aligned}p(t) &= v(t)i(t) \\&= -e^{-200t} \text{ W}\end{aligned}$$

$$\begin{aligned}w(t) &= \frac{1}{2} C [v(t)]^2 \\&= 5 \times 10^{-3} \times e^{-200t} \text{ J}\end{aligned}$$

