

## EE 100 Lab 3

### Pre-Lab: RC Circuits

Name: \_\_\_\_\_  
TA: \_\_\_\_\_ Section: \_\_\_\_\_

Please read the lab manual first then show your work here.


$$V = Q/C = [ \int i(t)dt ] / C$$


Differentiating this equation, we obtain  $i(t) = C(dV/dt)$

1. If a constant current of 1.0 mA were to flow into a 200  $\mu\text{F}$  (microfarad) capacitor, what would be the voltage across the capacitor after 3 seconds?

2. Describe what would happen theoretically if you were to connect an ideal current source to the following circuits. Use time plots to illustrate.

a)

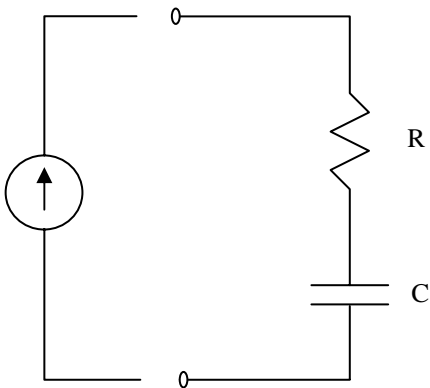

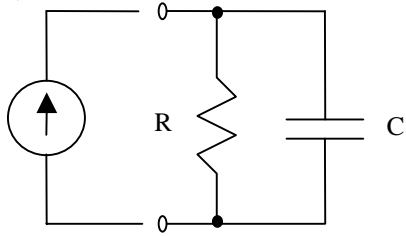**b)**

**3.** An RC (resistor + capacitor) circuit will have an exponential voltage response of the form  $v(t) = A + B e^{-t/RC}$  where A and B are constants that express the final voltage and the difference between the initial voltage and the final voltage, respectively.

**a.** Given  $R = 10 \text{ k}\Omega$  and  $C = 0.1 \text{ }\mu\text{F}$ , a starting voltage of 5 volts and an ending voltage of 0 volts, what will the voltage be at  $t = 1 \text{ ms}$ ?

**b.** At what time will the voltage be 0.5 volts?

**4.** Suppose you were given two black boxes that contain either a series or parallel combination of R and C. In the case of the series RC, you would not be able to touch a probe between the R and the C in the black box, so how would you go about determining R and C using the signal generator, the oscilloscope and an external resistance? (Hint: read the lab)