

Closed node sequence

Definition:

A sequence of node $\{ n_a, n_b, \dots n_j \dots n_k \dots, n_m \}$ is said to form a **closed node sequence** iff

1. $n_a = n_m$
2. $n_j \neq n_k$, for all $j \neq a$ and $k \neq m$

Remarks:

We do **not** require that there be a 2-terminal circuit element present between any **consecutive** pair of nodes belonging to a **closed node sequence**.

Kirchhoff Current Law (KCL)

The **algebraic sum** of **all currents leaving** a **Gaussian** surface is equal to **zero** at all times.

KCL

Corollary 1 (KCL at **nodes**)

Algebraic sum of all currents **leaving** any **node** is equal to **zero** at all times.

KCL

Corollary 2 (KCL at **cut sets**)


Algebraic sum of **all**
currents **leaving** a *cut set* is
equal to **zero** at all times.

KCL

Corollary 3

(KCL at **n-terminal device**)

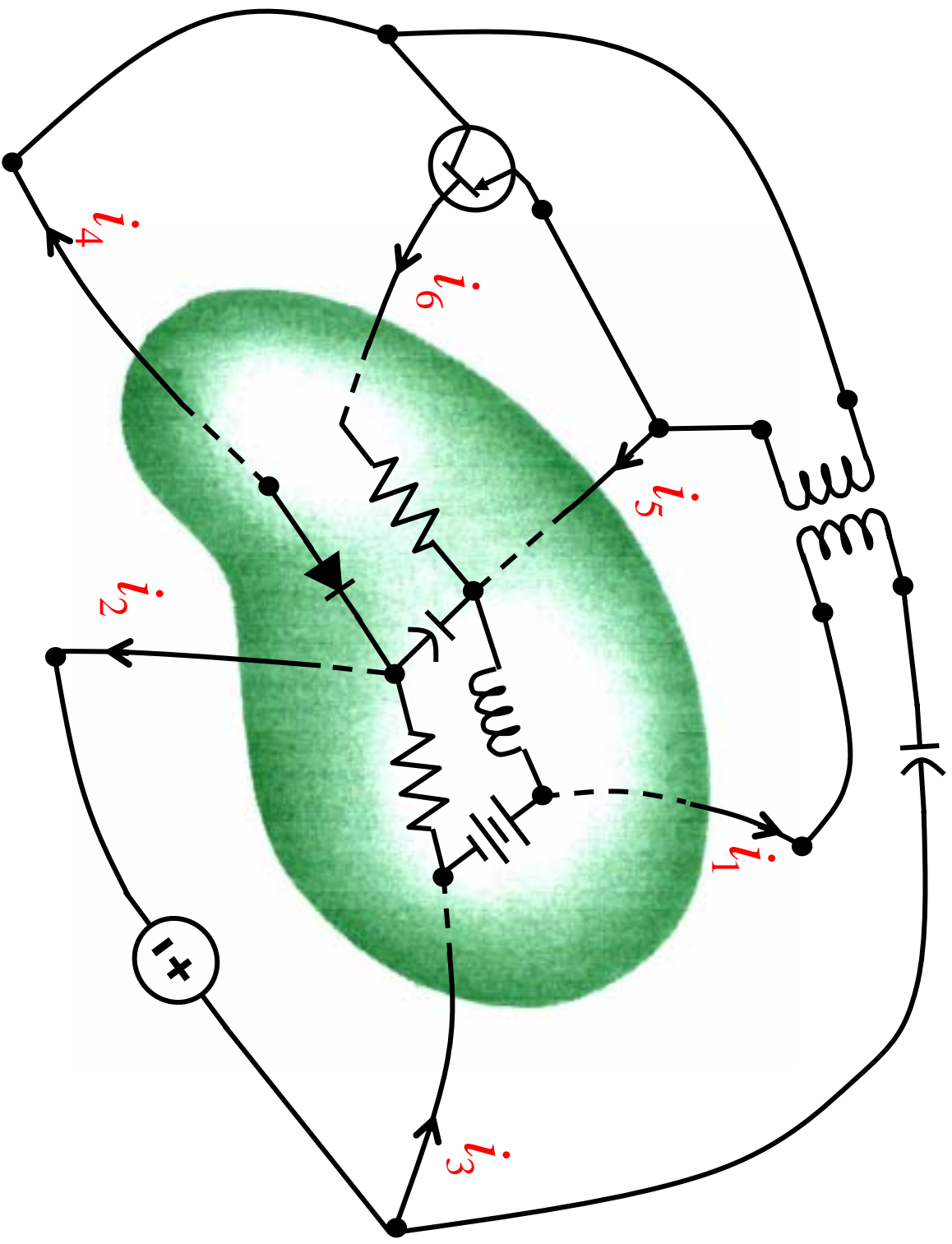Algebraic sum of **all**
currents **leaving** **all**
terminals of an **n-terminal**
device is equal to **zero** at all
times.



$$KCL \Rightarrow i_1 + i_2 - i_3 + i_4 - i_5 - i_6 = 0$$

Instantaneous Power

$$vi = \frac{dw}{dq} \frac{dq}{dt} = \frac{dw}{dt}$$

Since w represents energy, dw / dt represents the rate of change of energy, or the power p ; ∂ hence

$$P(t) = v(t)i(t) \quad , \text{ watts (W)}$$

6 Fundamental Circuit Variables

Current	$i(t) = \frac{dq(t)}{dt}$	Ampere (A)
Voltage	$v(t) = \frac{d\phi(t)}{dt}$	Volt (V)
Power	$p(t) = v(t) i(t) = \frac{dw(t)}{dt}$	Watt (W)
Energy	$w(t) = \int_{-\infty}^t p(\tau) d\tau = \int_{-\infty}^t v(\tau) i(\tau) d\tau$	Watt-Hour
Charge	$q(t) = \int_{-\infty}^t i(\tau) d\tau$	Coulomb (C)
Flux	$\phi(t) = \int_{-\infty}^t v(\tau) d\tau$	Weber