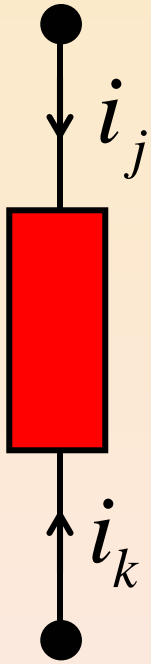



Independent Device Currents



Since **KCL** \Rightarrow

$$-i_j - i_k = 0$$

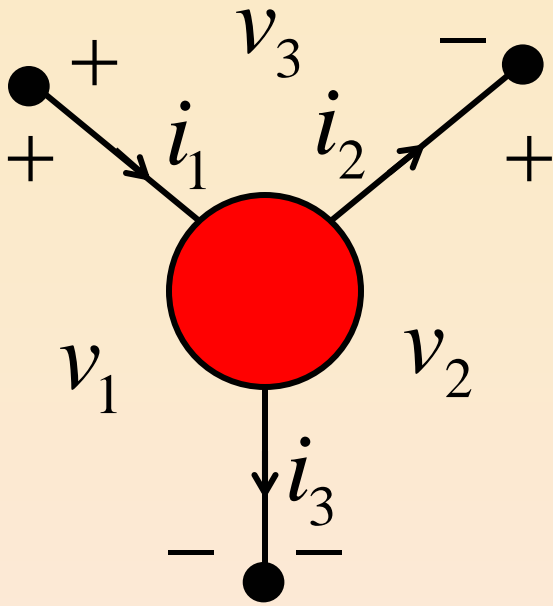Only one independent current can be defined for each **2-terminal device**.



Since **KCL** \Rightarrow

$$-i_1 + i_2 + i_3 = 0$$


Only 2 independent currents can be defined for a **3-terminal device**.

Since **KVL** $\Rightarrow v_1 - v_2 - v_3 = 0$

Only 2 independent voltages can be defined for a **3-terminal device**.


n -port device

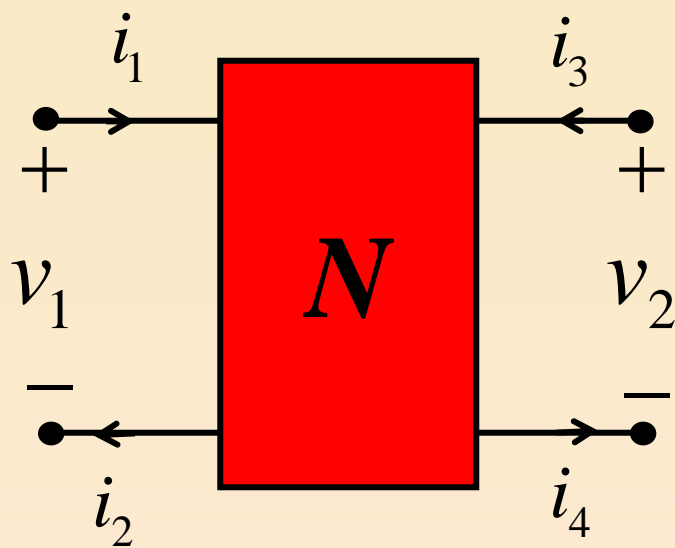There are electrical devices having an **even** number of terminals and constructed in such a way that the terminals can be grouped into pairs, called **ports**, such that the current entering one terminal of each pair is always equal to the current leaving the other terminal. A device with “ n ” pairs of such current-following terminals is called an **n -port**.



A 4-terminal device


Example of a 2-port

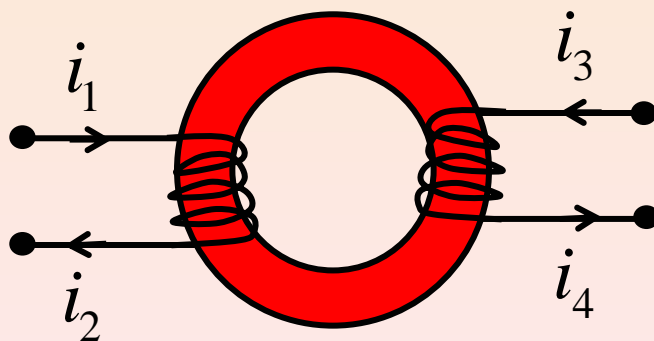

In this example, the 2 separate physical windings guarantee that :

$$i_1 = i_2 \text{ and } i_3 = i_4$$

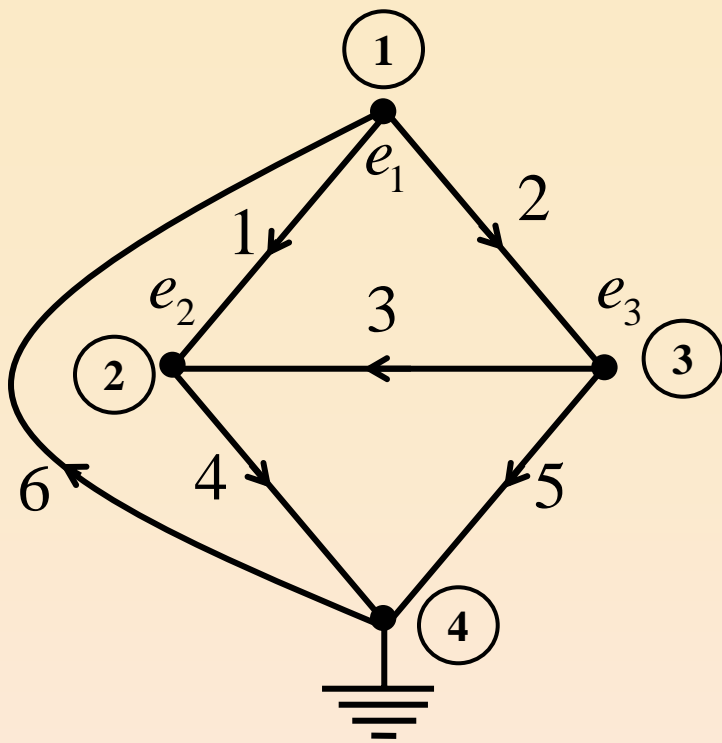In this case, only 1 current and 1 voltage needs to be defined for each pair of terminals, henceforth called ports.




KCL Equations:

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$

$$\mathbf{A} \mathbf{i} = \mathbf{0} \quad \Rightarrow \quad \begin{array}{c} \text{node} \\ \text{no.} \end{array} \begin{array}{c} \text{Branch no.} \\ 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \end{array} \begin{array}{c} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \end{array} \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

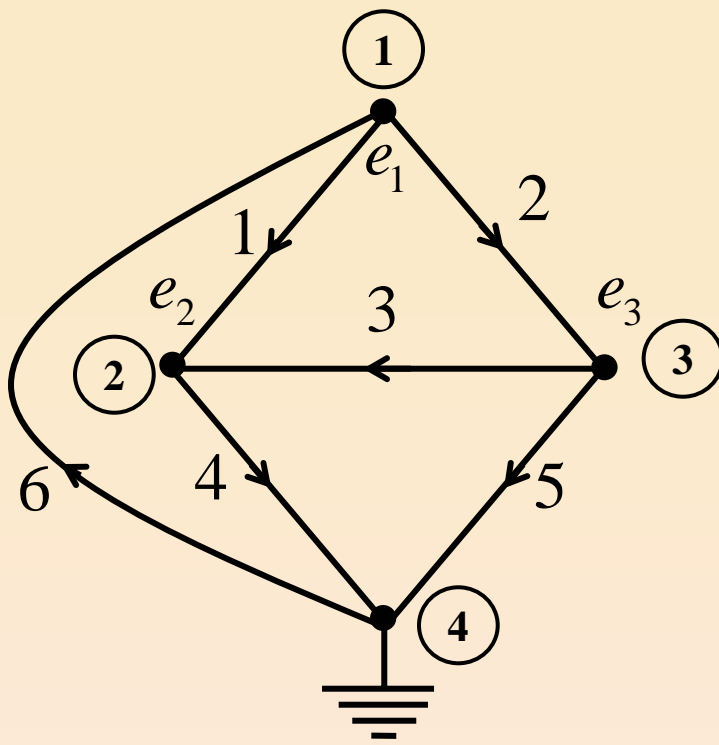

KCL Equations:

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$


$$\mathbf{A} \mathbf{i} = \mathbf{0} \quad \Rightarrow$$

node no.	Branch no.						
	1	2	3	4	5	6	
$\textcircled{1}$	1	1	0	0	0	-1	= $\begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$
$\textcircled{2}$	-1	0	-1	1	0	0	
$\textcircled{3}$	0	-1	1	0	1	0	

$\underbrace{\hspace{15em}}_{\mathbf{A}}$

\mathbf{A} is called the **reduced Incidence Matrix** of the digraph G relative to datum node $\textcircled{4}$.

KCL Node Equations:

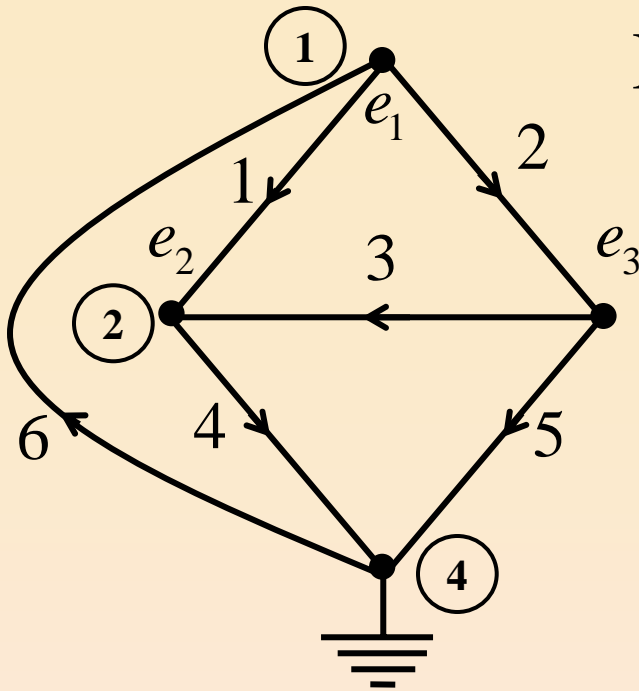

node No.

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$

$$\textcircled{4} \quad -i_4 - i_5 + i_6 = 0$$

These 4 equations are linearly-dependent.

Matrix Formulation:

node no.	Branch no.					
	1	2	3	4	5	6
$\textcircled{1}$	1	1	0	0	0	-1
$\textcircled{2}$	-1	0	-1	1	0	0
$\textcircled{3}$	0	-1	1	0	1	0
$\textcircled{4}$	0	0	0	-1	-1	1


$$\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

INCIDENCE MATRIX

→ \mathbf{A}_a

$\mathbf{i} = \mathbf{0}$
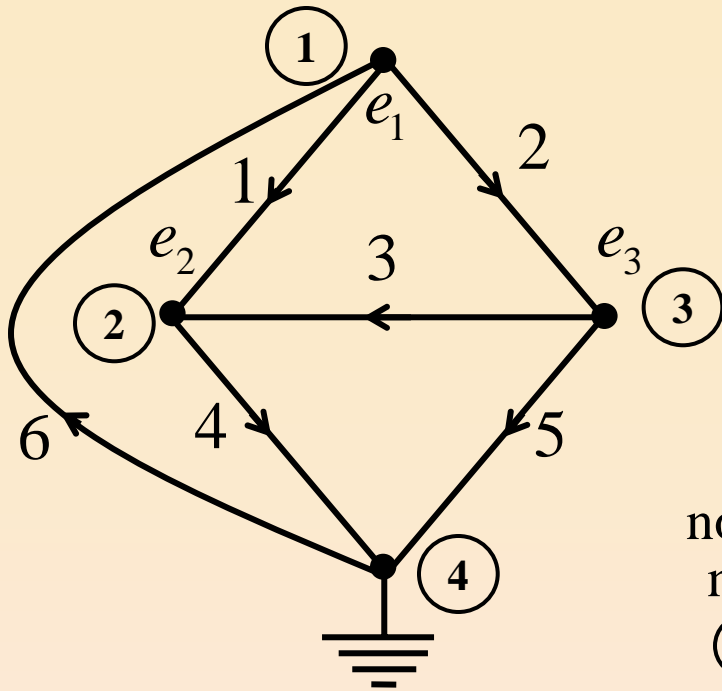
$$a_{jk} = \begin{cases} 1 & \text{if branch } k \text{ leaves node } \textcircled{j} \\ -1 & \text{if branch } k \text{ enters node } \textcircled{j} \\ 0 & \text{if branch } k \text{ is not connected to node } \textcircled{j} \end{cases}$$



KCL Equations:

$$\textcircled{1} \quad i_1 + i_2 - i_6 = 0$$

$$\textcircled{2} \quad -i_1 - i_3 + i_4 = 0$$

$$\textcircled{3} \quad -i_2 + i_3 + i_5 = 0$$

node Branch no.

no. 1 2 3 4 5 6

$$\begin{matrix} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \end{matrix} \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & -1 \\ -1 & 0 & -1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 & 1 & 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\mathbf{A} \mathbf{i} = \mathbf{0} \Rightarrow$$

$$\underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \end{bmatrix}}_{\mathbf{v}} = \underbrace{\begin{bmatrix} 1 & -1 & 0 \\ 1 & 0 & -1 \\ 0 & -1 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 0 & 0 \end{bmatrix}}_{\mathbf{A}^T} \underbrace{\begin{bmatrix} e_1 \\ e_2 \\ e_3 \end{bmatrix}}_{\mathbf{e}}$$

KVL Equations:

$$\Leftrightarrow \begin{cases} v_1 = e_1 - e_2 \\ v_2 = e_1 - e_3 \\ v_3 = e_3 - e_2 \\ v_4 = e_2 \\ v_5 = e_3 \\ v_6 = -e_1 \end{cases}$$

$$\text{KVL: } \boxed{\mathbf{v} = \mathbf{A}^T \mathbf{e}}$$

Since v_j is present only in the j th equation, these k equations are **linearly - independent**.

Theorem

$$\mathbf{A} \mathbf{i} = \mathbf{0}$$

gives the **maximum possible** number of **linearly-independent KCL equations** for a connected circuit.

Reduced Incidence Matrix

Let G be a connected **digraph** with “ n ” nodes and “ b ” branches. Let \mathbf{A}_a be the **Incidence Matrix** of G . The $(n-1) \times b$ matrix \mathbf{A} obtained by deleting any one row of \mathbf{A}_a is called a **Reduced-Incidence Matrix** of G .

Observation : The 4 KCL node equations are *not* linearly independent.

Adding the left side of the 4 KCL node equations, we obtain:

$$\underbrace{(i_1 + i_2 - i_6)}_{\textcircled{1}} + \underbrace{(-i_1 - i_3 + i_4)}_{\textcircled{2}} + \underbrace{(-i_2 + i_3 + i_5)}_{\textcircled{3}} + \underbrace{(-i_4 - i_5 + i_6)}_{\textcircled{4}} \equiv 0$$

This means we can derive any one of these 4 equations from the other 3.

Example: Derive KCL equations at node $\textcircled{4}$:

Adding the first 3 node equations gives:

$$\underbrace{(i_1 + i_2 - i_6)}_{\textcircled{1}} + \underbrace{(-i_1 - i_3 + i_4)}_{\textcircled{2}} + \underbrace{(-i_2 + i_3 + i_5)}_{\textcircled{3}} = \underbrace{i_4 + i_5 - i_6}_{\textcircled{4}}$$

Reduced Incidence Matrix

A

Let G be a connected **digraph** with “ n ” nodes and “ b ” branches, the **reduced incidence matrix** \mathbf{A} relative to **datum node** \textcircled{n} is an $(n-1) \times b$ matrix whose coefficients a_{jk} are obtained from the $(n-1)$ KCL equations written at the $n-1$ non-datum nodes:

$$a_{jk} = \begin{cases} 1 & \text{if branch } k \text{ leaves node } \textcircled{j} \\ -1 & \text{if branch } k \text{ enters node } \textcircled{j} \\ 0 & \text{if branch } k \text{ is not connected to node } \textcircled{j} \end{cases}$$

By applying the various versions of KCL, we can write many different KCL equations for each circuit. However, these equations are usually **not** linearly independent in the sense that each equation can be derived by a linear combination of the others.

How can we write a maximum set of **linearly-independent** KCL equations?




Simplest Method to write linearly-Independent KCL Equations.

Given a connected circuit with “ n ” nodes, choose an arbitrary node as **datum**. Write a KCL equation at each of the remaining $(n-1)$ nodes.

Relationship between \mathbf{A} and \mathbf{A}_a

Let \mathbf{A}_a be the $n \times b$ **Incidence matrix** of a connected digraph G with “ n ” nodes and “ b ” branches.

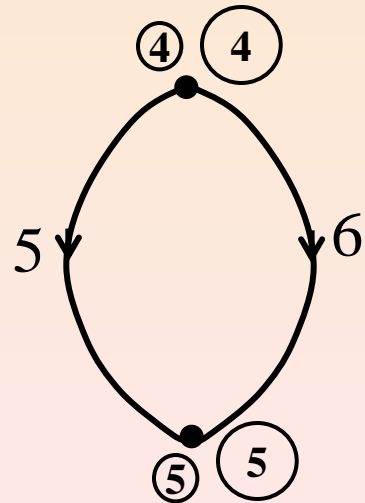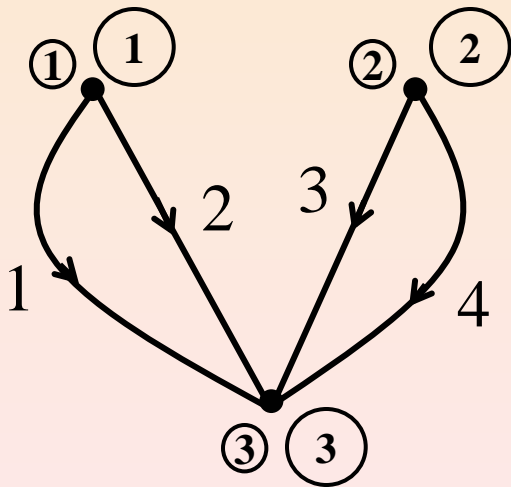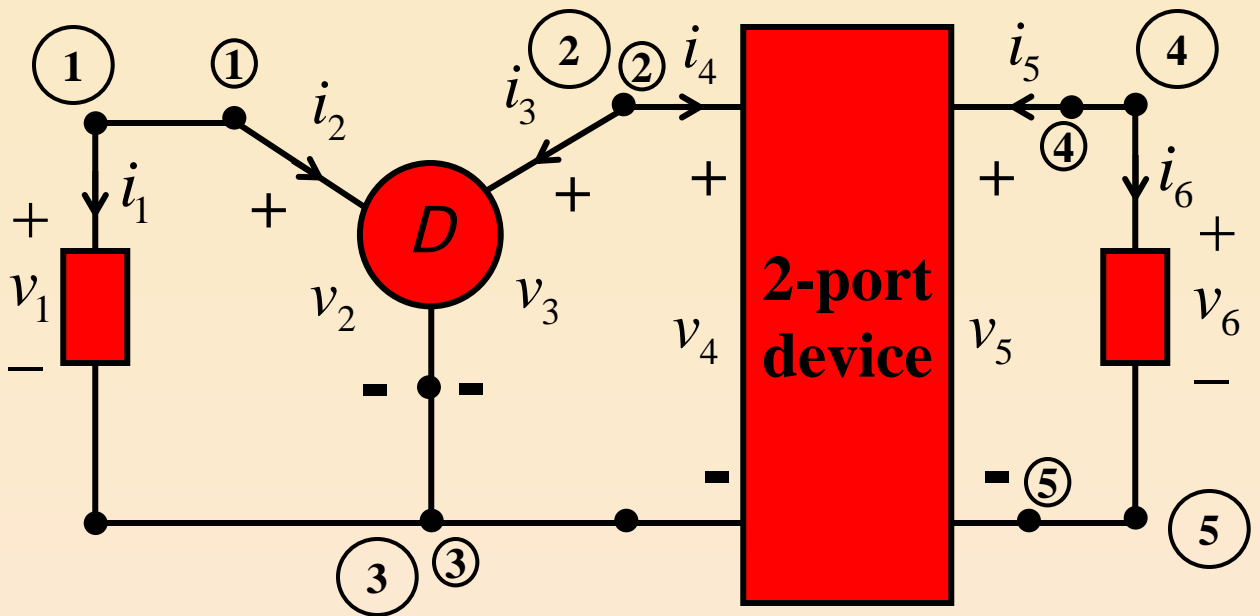By deleting any row corresponding to node \textcircled{m} from \mathbf{A}_a , we obtain the **reduced incidence matrix** \mathbf{A} of G relative to the datum node \textcircled{m} .





disconnected diagraph

$$\text{KCL at } \textcircled{2} : \quad i_3 + i_4 = 0$$



$$\text{KCL at } \textcircled{4} : \quad i_5 + i_6 = 0$$

$$\text{KVL around } \textcircled{2} - \textcircled{3} - \textcircled{2} : \quad v_4 - v_3 = 0$$

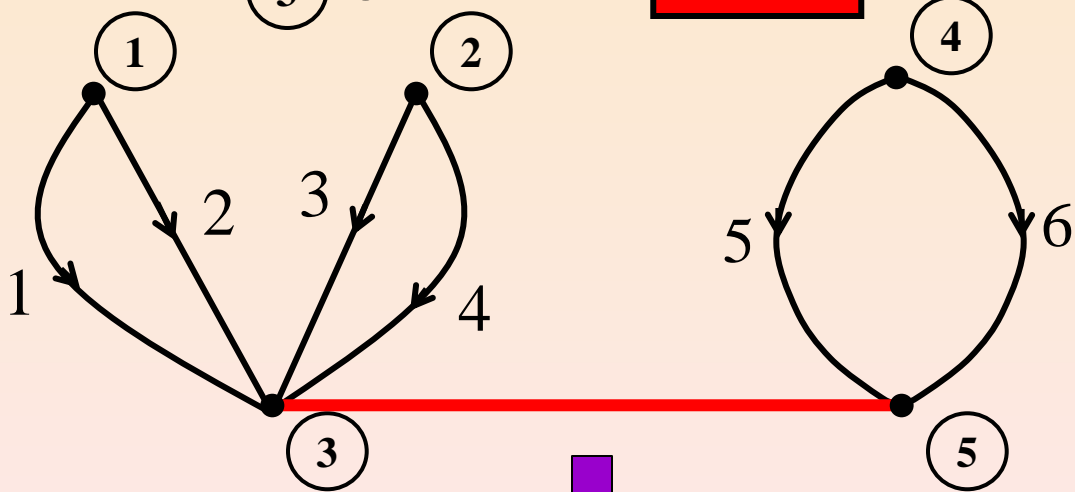
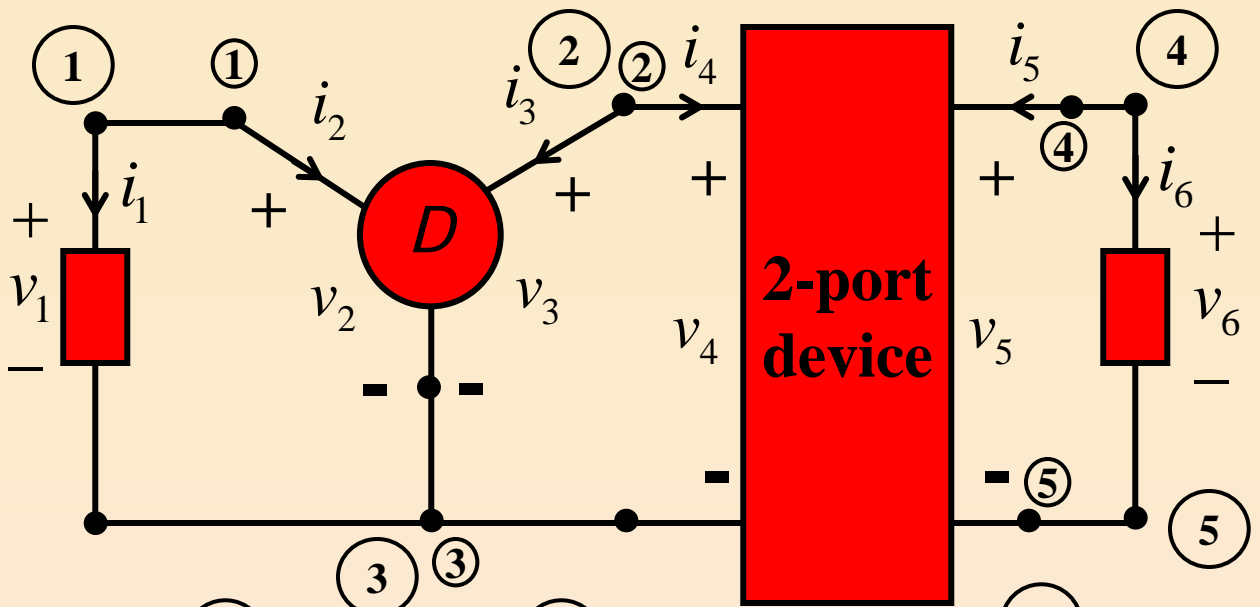
$$\text{KVL around } \textcircled{4} - \textcircled{5} - \textcircled{4} : \quad v_6 - v_5 = 0$$





HINGED DIAGRAM

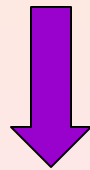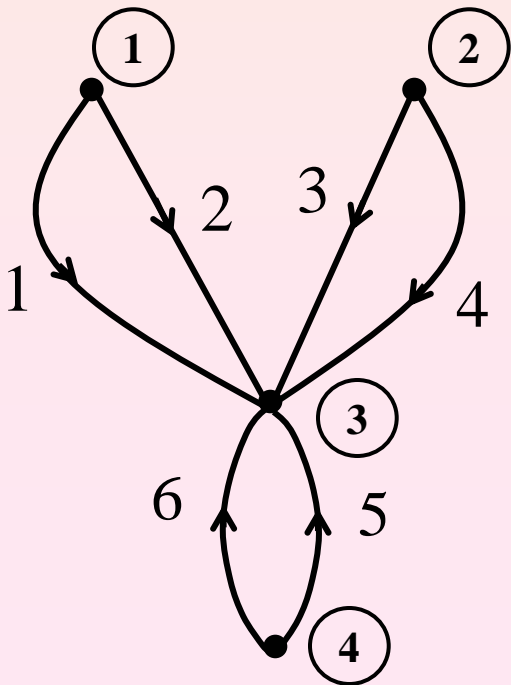

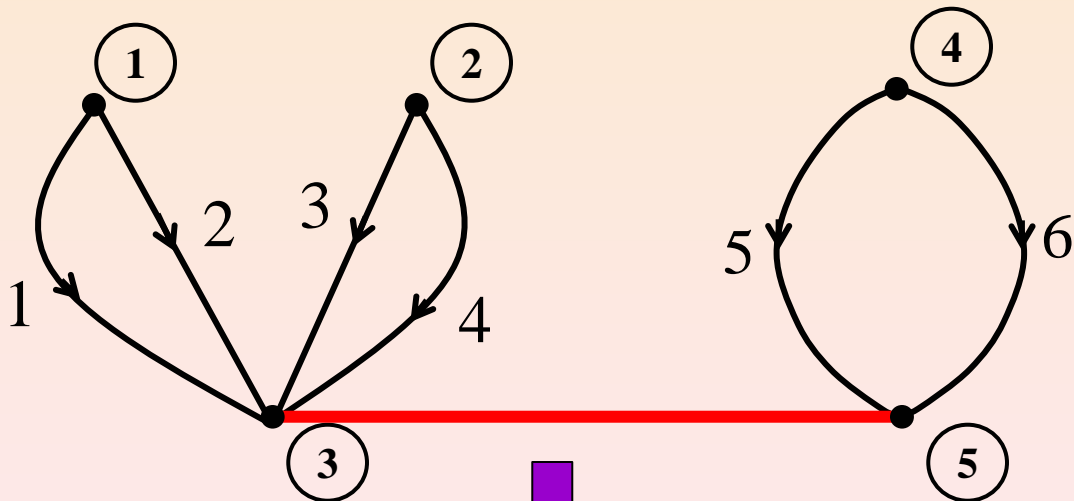
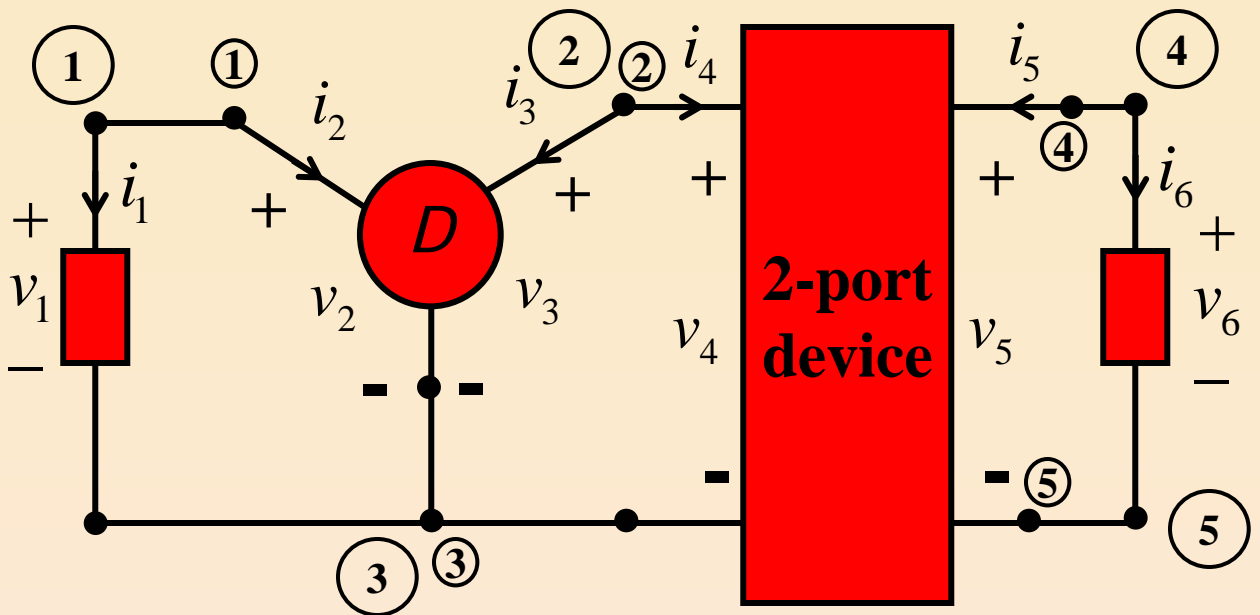
Since nodes ③ and ⑤ are now the same node, they can be combined into one node, and the redrawn diagram is called a **hinged** graph.



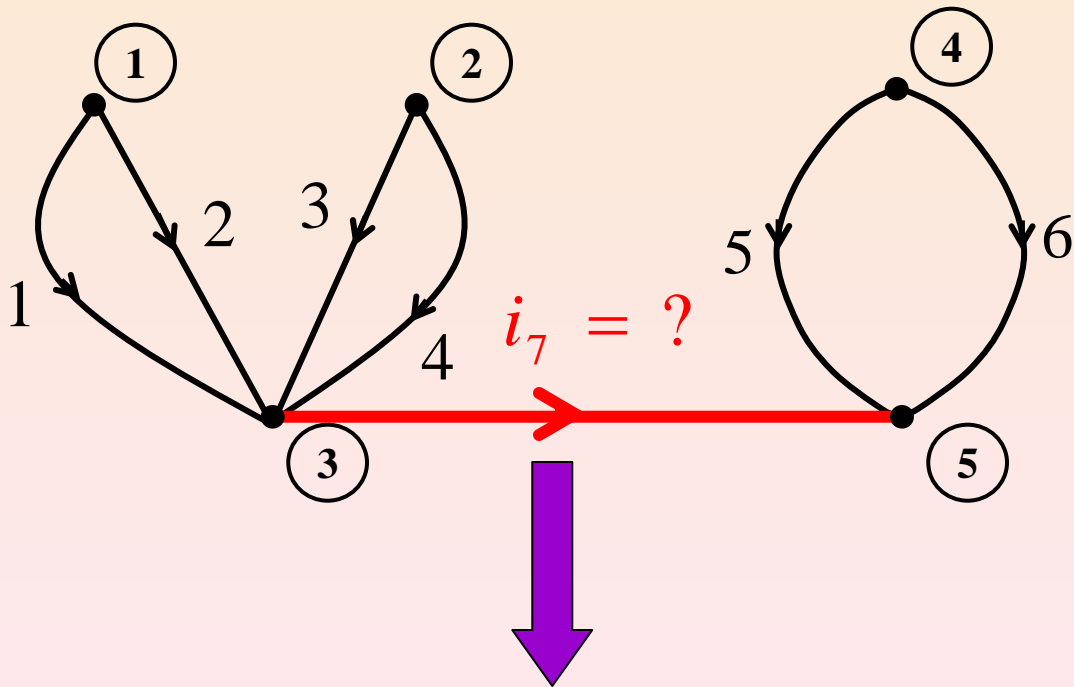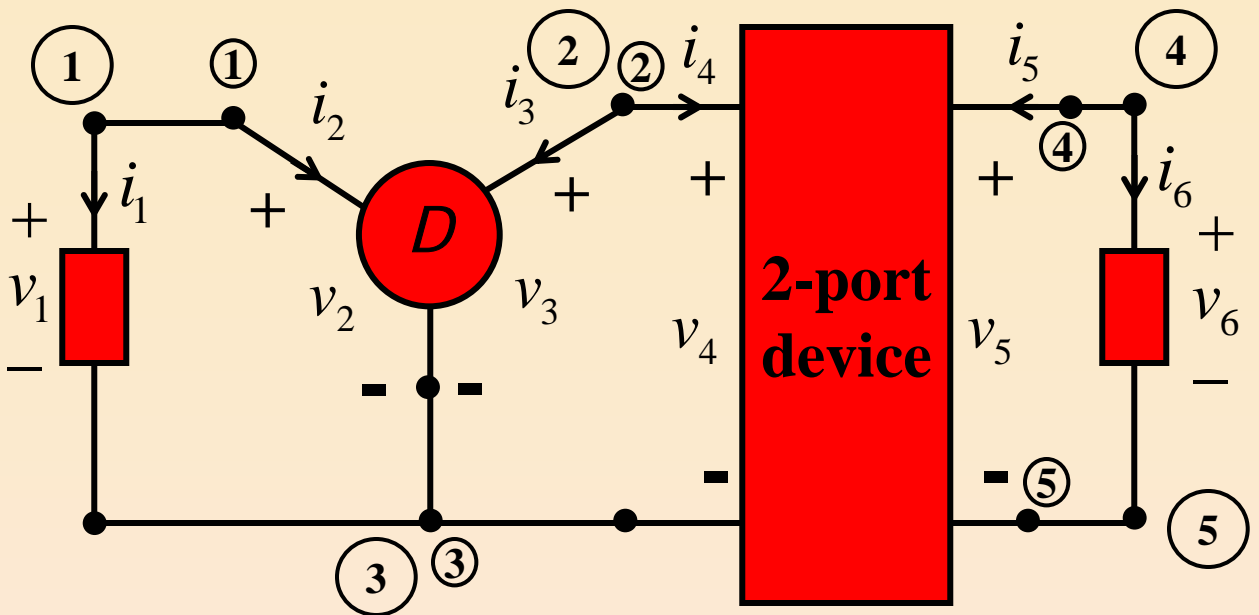Adding a wire connecting one node from each separate component does **not** change KVL or KCL equations.



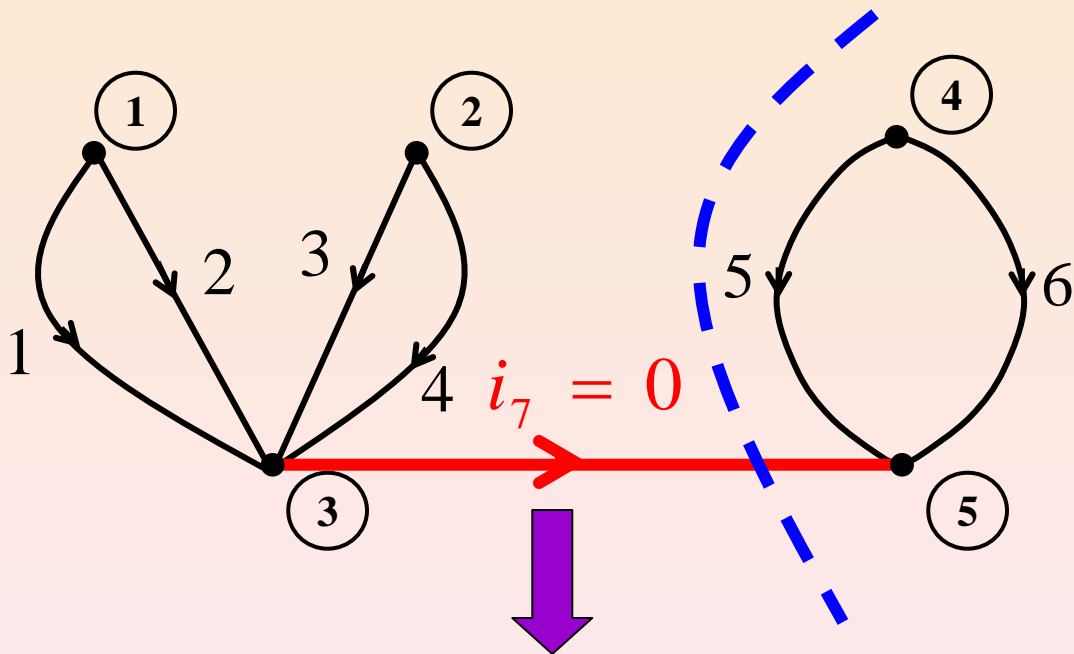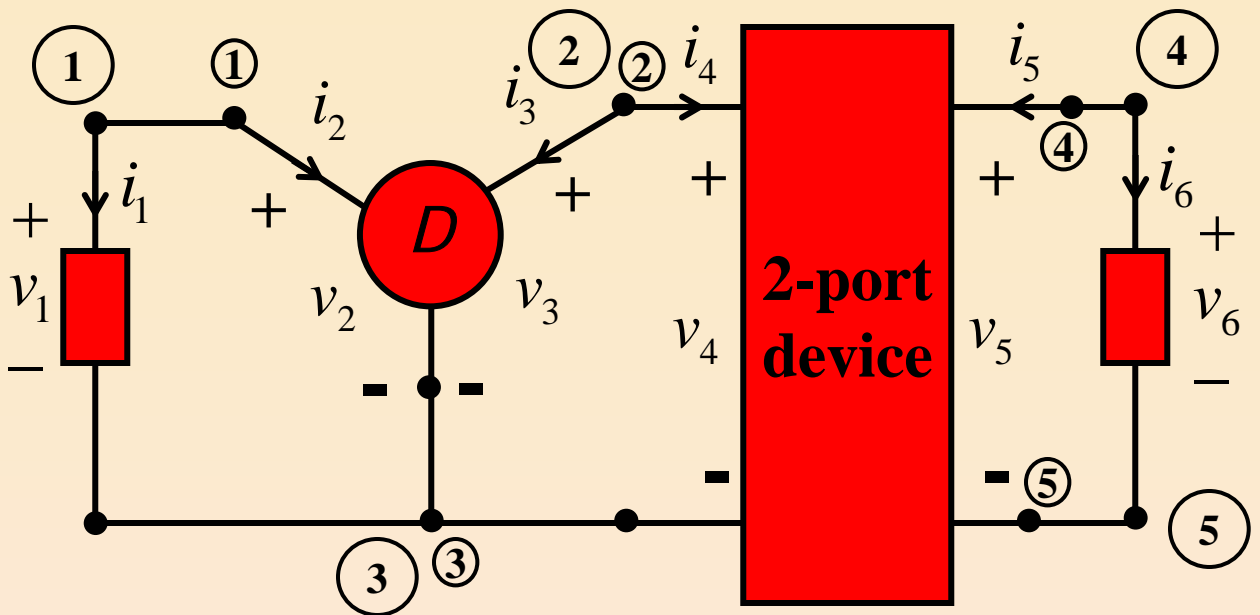
Adding a wire connecting one node from each separate component does **not** change KVL or KCL equations.




Adding a wire connecting one node from each separate component does **not** change KVL or KCL equations.

$$\{7\} \text{ is a cut set} \Rightarrow i_7 = 0$$

Associated Reference Convention :


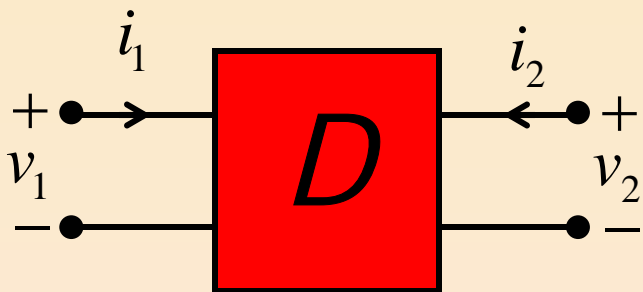



2-port Device

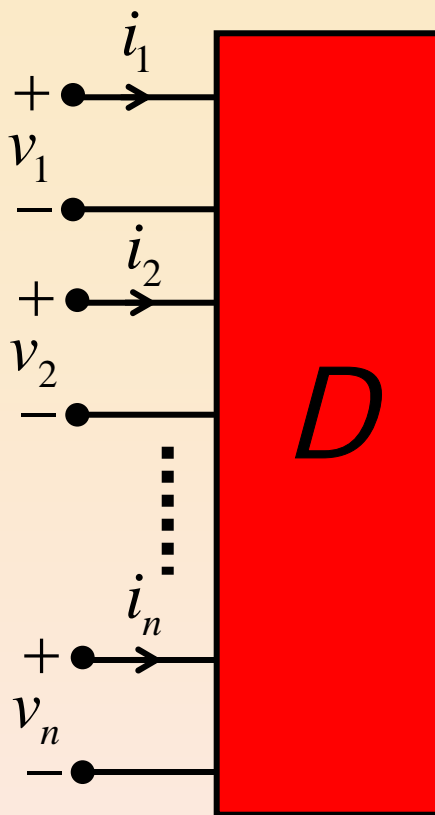

n -port Device

Device Graph

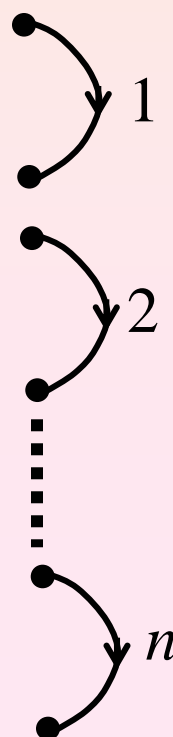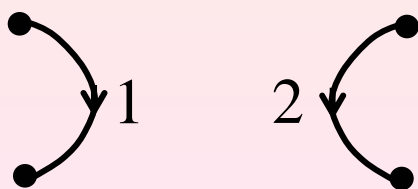

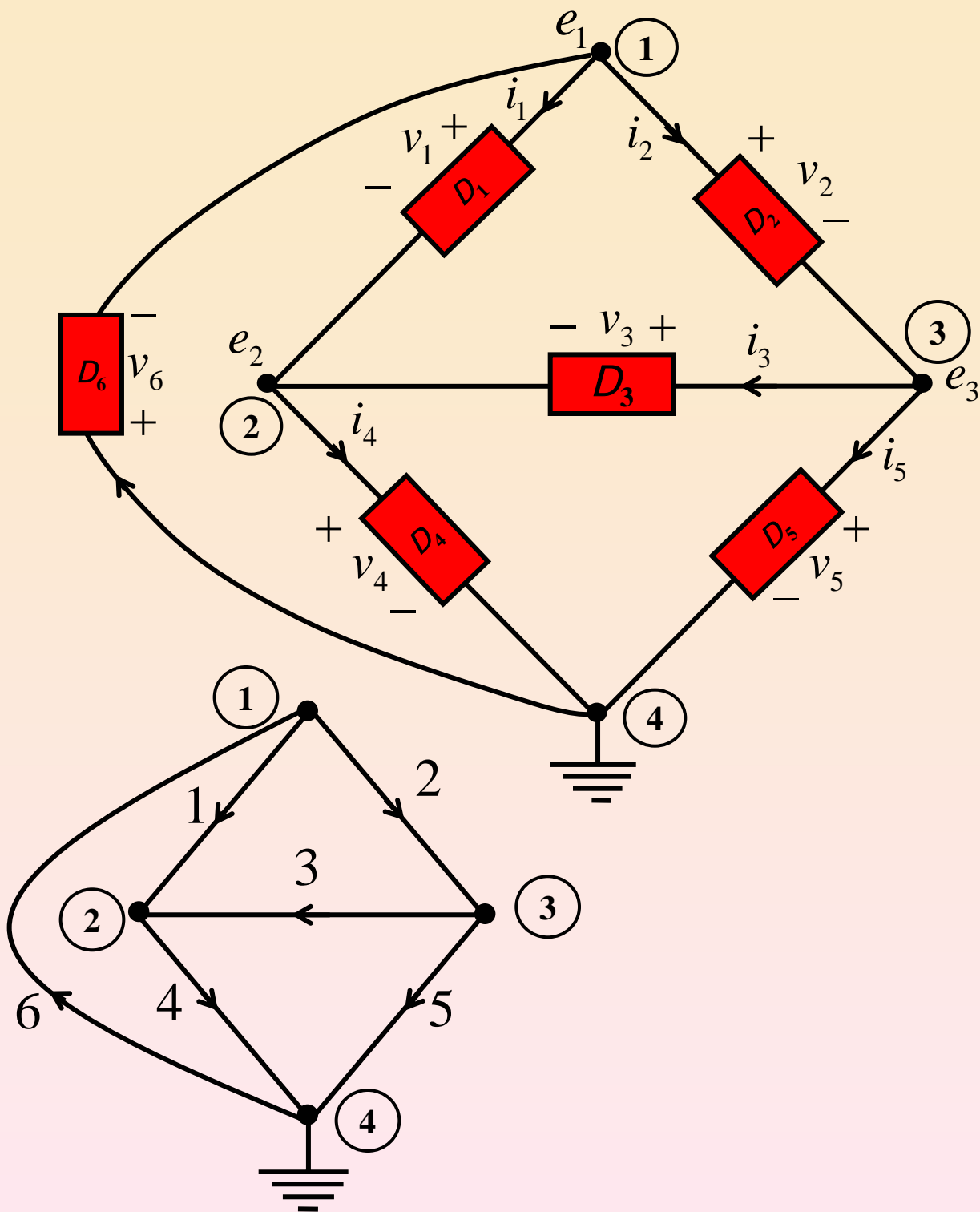


KCL at $\textcircled{1}$: $i_1 + i_2 - i_6 = 0$


KVL around $\textcircled{1}-\textcircled{3}-\textcircled{4}-\textcircled{2}-\textcircled{1}$:
 $v_2 + v_5 - v_4 - v_1 = 0$


Associated Reference Convention :

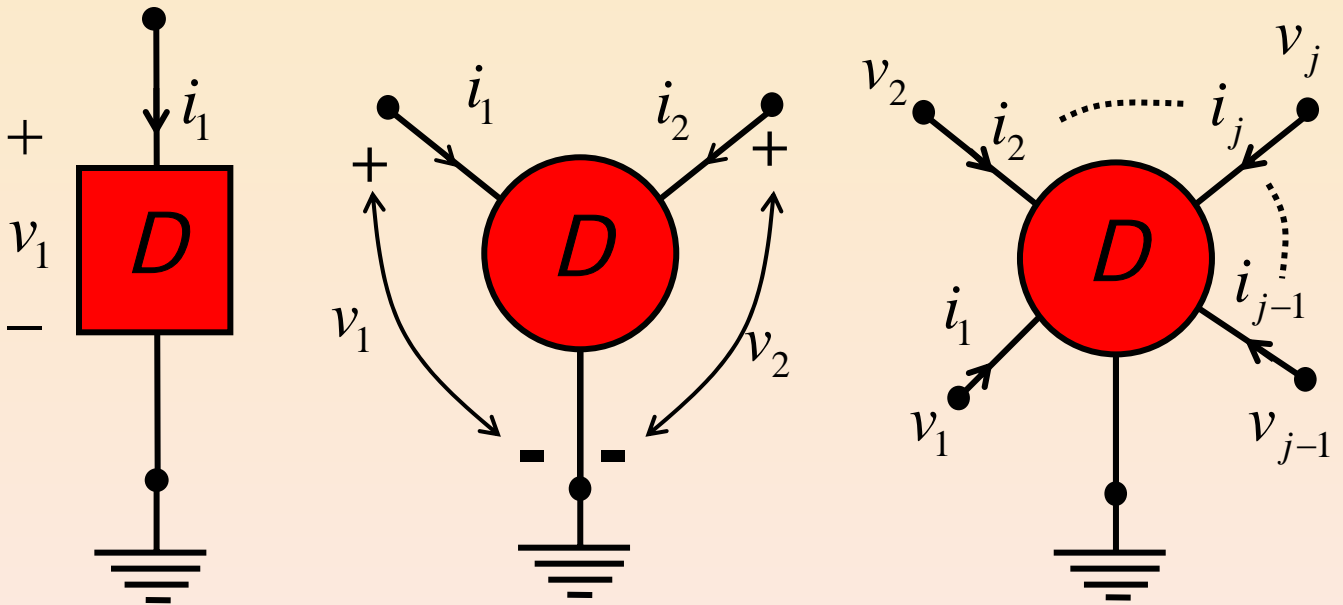A current direction is chosen entering each positively-referenced terminal.



Device Graph : DIGRAPH (Directed Graph)

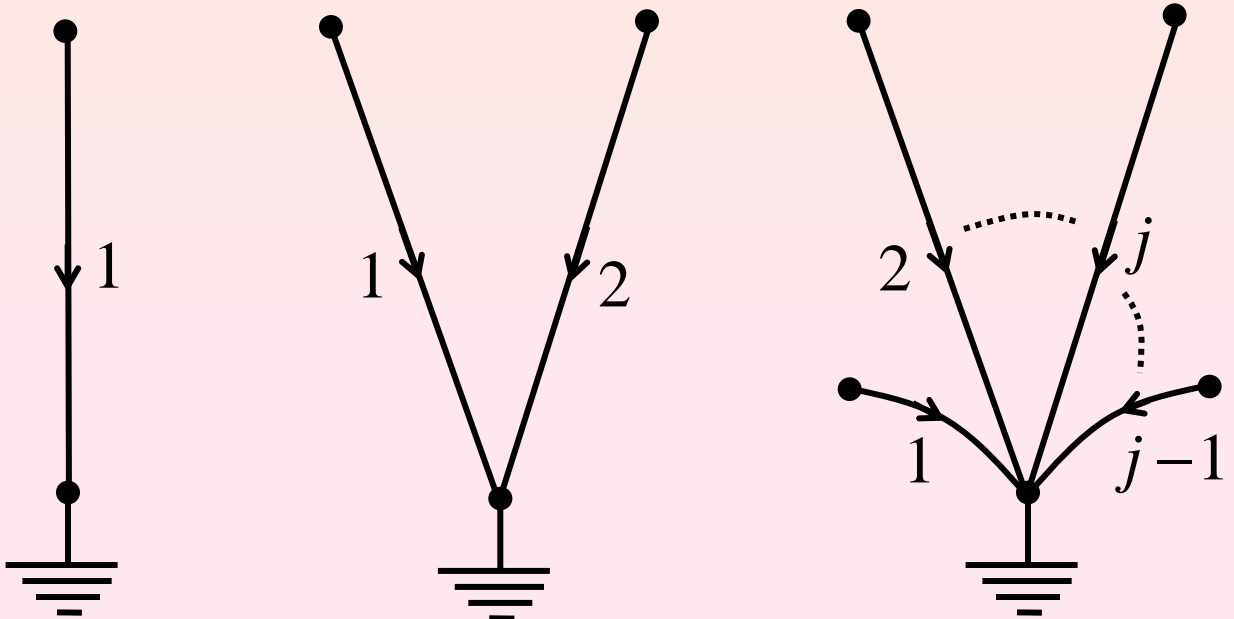

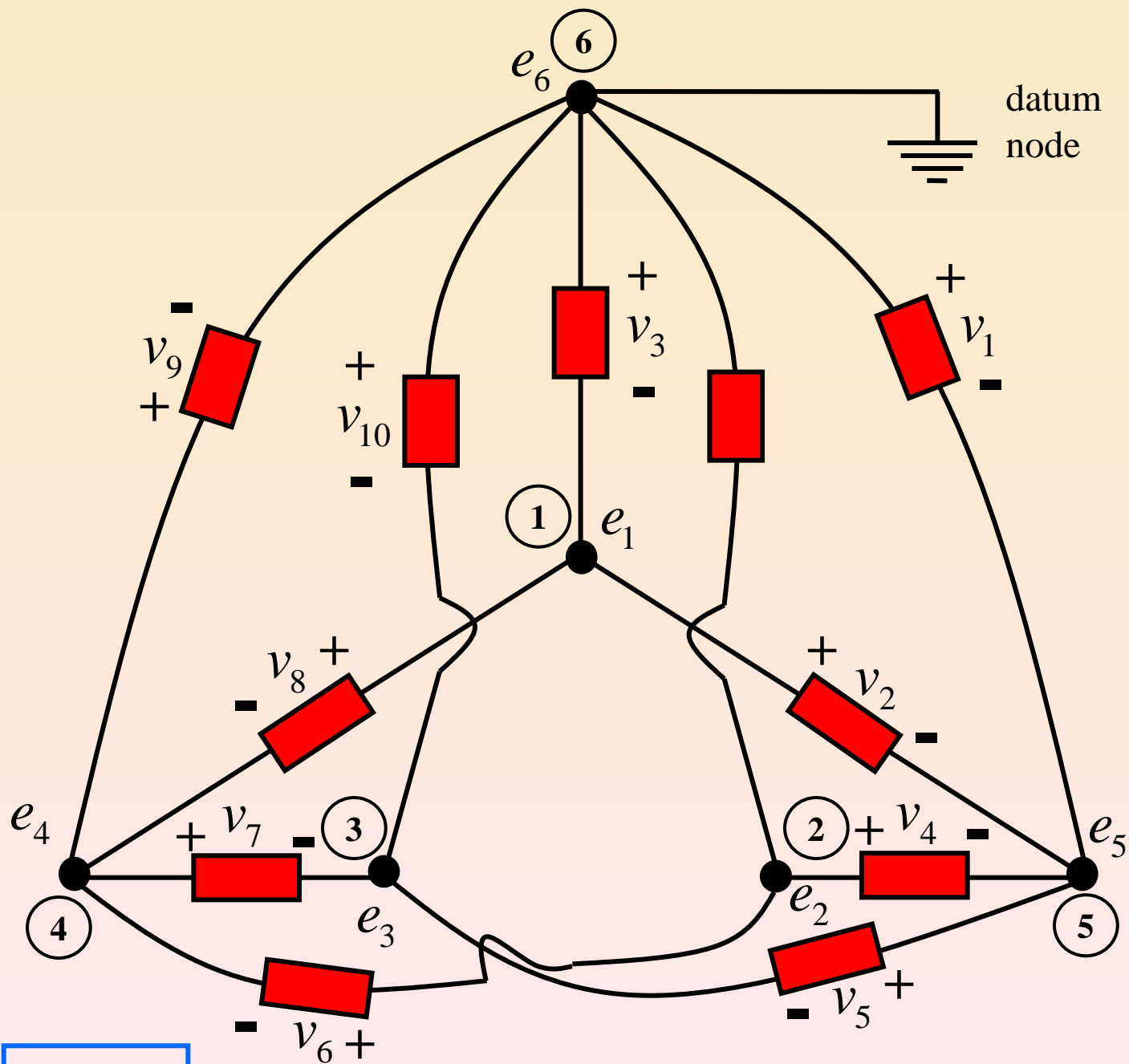


KVL

$$v_1 = e_6 - e_5 = -e_5, \quad v_4 = e_2 - e_5$$

$$v_2 = e_1 - e_5, \quad v_5 = e_5 - e_3$$

$$v_3 = e_6 - e_1 = -e_1, \quad v_6 = e_2 - e_4$$

KCL

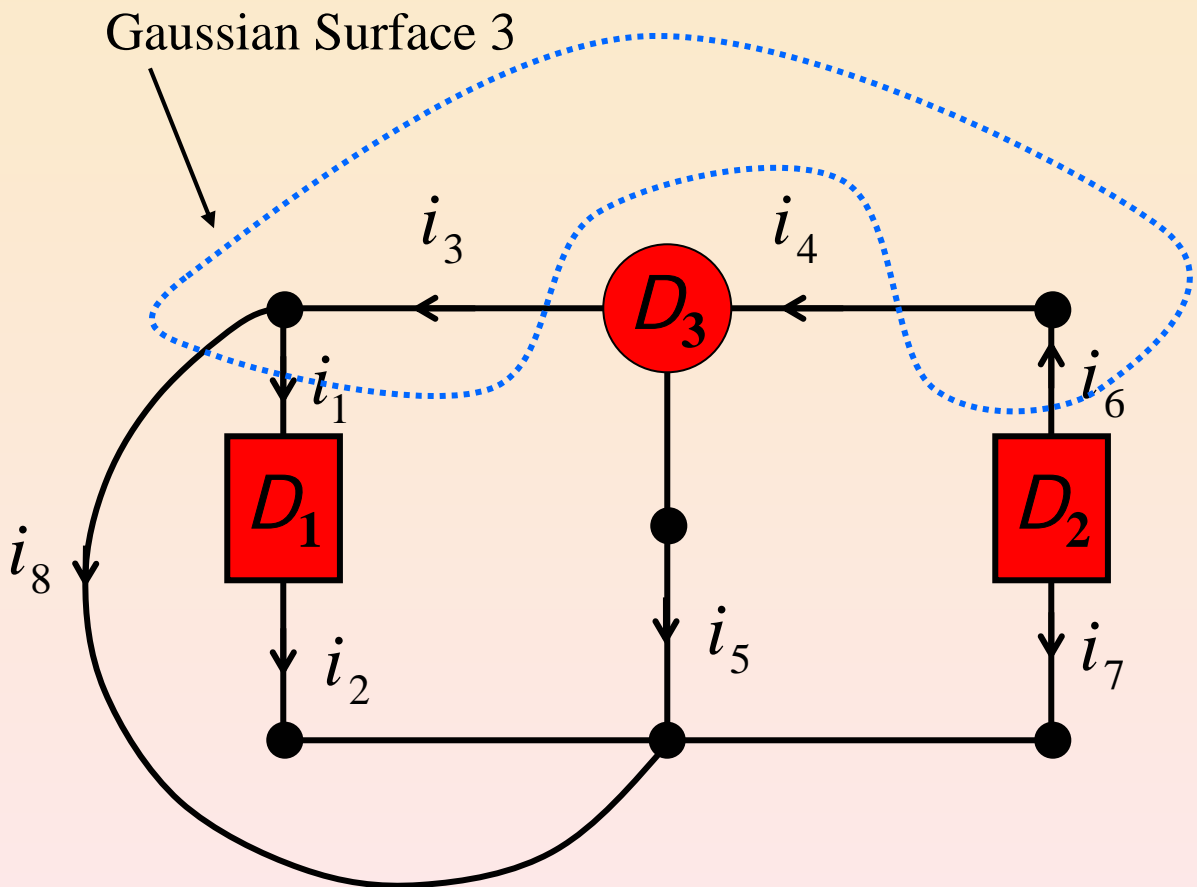

Gaussian Surface 3:

$$i_1 - i_3 + i_4 - i_6 + i_8 = 0$$

This KCL equation can be decomposed into the sum of two KCL cut set equations:

$$\text{cut set } \{4,6\} \Rightarrow i_4 - i_6 = 0$$

$$\text{cut set } \{1,3,8\} \Rightarrow i_1 - i_3 + i_8 = 0$$