

SOCCER Ball Circuit

Consider a soccer ball circuit where each edge is a resistor.

number of nodes = $n = 60$

number of branches = $b = 90$

number of meshes = $m = 32$

node-voltage analysis $\Rightarrow n - 1 = 59$

equations involving $\{e_1, e_2, \dots, e_{59}\}$

node-voltage variables.

mesh-current analysis $\Rightarrow m - 1 = 31$

equations involving $\{\hat{i}_1, \hat{i}_2, \dots, \hat{i}_{31}\}$

mesh-current variables.

A **SOCCER** ball has :

$$n = 60 \text{ vertices}$$

$$b = 90 \text{ edges}$$

$$m = 32 \text{ faces}$$


These numbers must satisfy

Euler's formula

$$m + n = b + 2$$

Check: $32 + 60 = 90 + 2$

Voltage divider

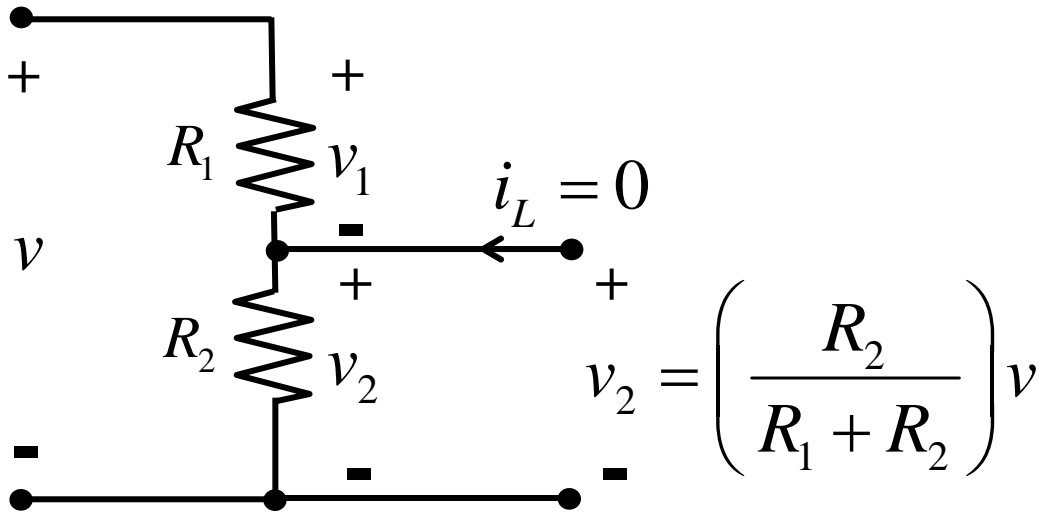

$$v_2 = \left(\frac{R_2}{R_1 + R_2} \right) v$$

warning: This formula is valid only if

$i_L = 0$ (no loading!)

How to Construct Dual Circuits


Given a **planar** circuit N with n nodes and $m-1$ meshes, draw its digraph G . Label all branches, nodes, and meshes and let node (n) be the datum node. The dual circuit N' is constructed in 2 steps:

Step 1 draw the dual digraph G' of G .

- (a) For each mesh m_j of G , draw a node **inside** mesh m_j and label it as node (j') , $j = 1, 2, \dots, m-1$.
- (b) Draw a node **outside** of G and label it as node (m') , and choose this *exterior* node (m') as the datum node of G' .
- (c) For each branch k of G belonging to 2 adjacent meshes m_j and m_k , draw a **dual** branch k' connecting node (m'_j) to node (m'_k) .
- (d) For each branch k of G belonging to only 1 mesh m_j , draw a **dual** branch k' from node (m'_j) to the *exterior* node (m') .

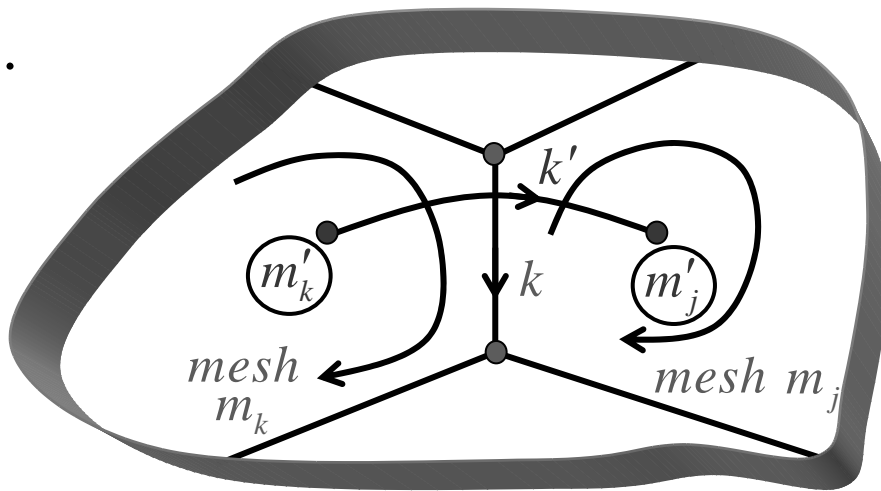(e) Draw an **arrowhead** for each branch k' of G' as follow:


The **arrowhead** of each branch k' connected to nodes (m'_j) and (m'_k) is drawn **toward** node (m'_j) if the direction of branch k of G is in a **counterclockwise** direction relative to node (m'_j) .



Step 2 For each branch k' in the dual digraph G' , draw a circuit element which is **dual** of the corresponding circuit element from N .

Examples.

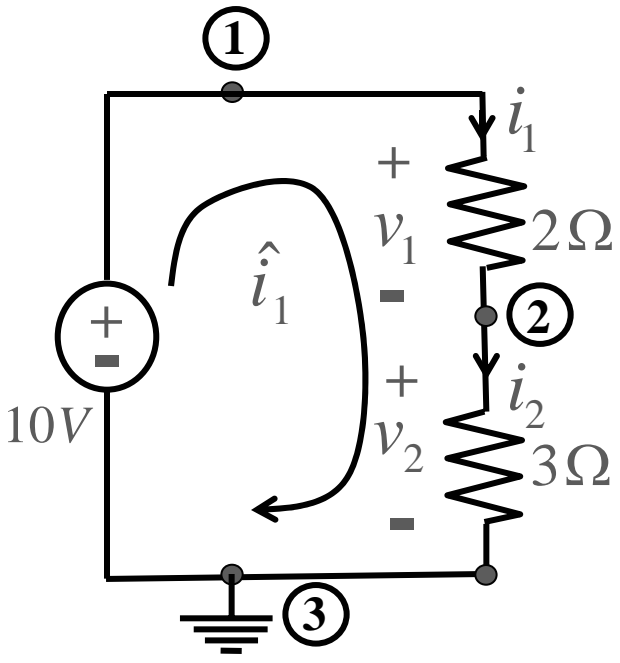1. If element k is a 5Ω linear resistor in N , then its dual is $1/5 \Omega$ (or 5 Siemen) linear resistor in N' .
2. If element k is a $2 V$ voltage source in N , then its dual is a $2 A$ current source in N' .
3. If element k is a $5 A$ current source in N , then its dual is a $5 V$ voltage source in N' .





Circuit N

Mesh-current Equation

$$5 \hat{i}_1 = 10$$



Digraph G

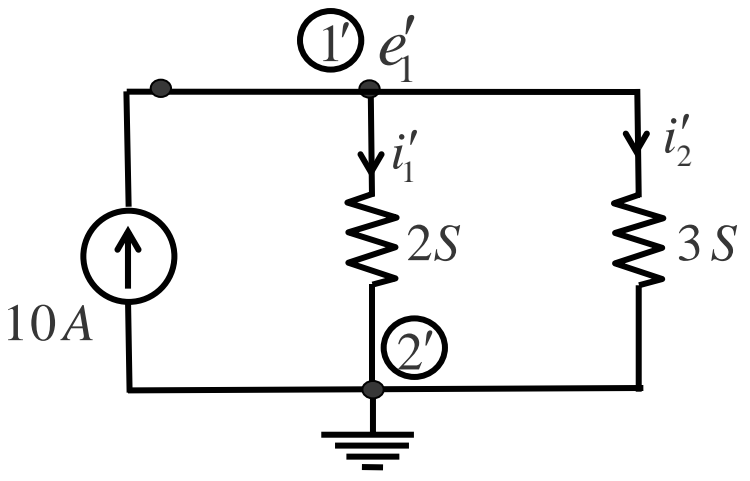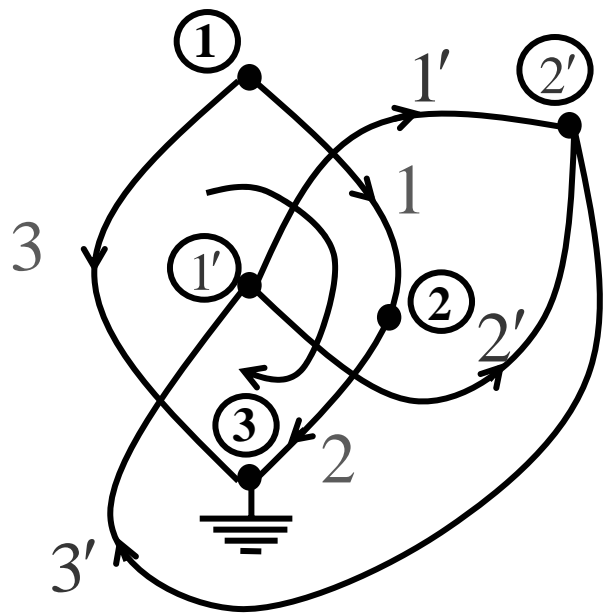



Circuit N'

Node-voltage Equation

$$5 e'_1 = 10$$



Digraph G'

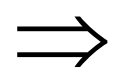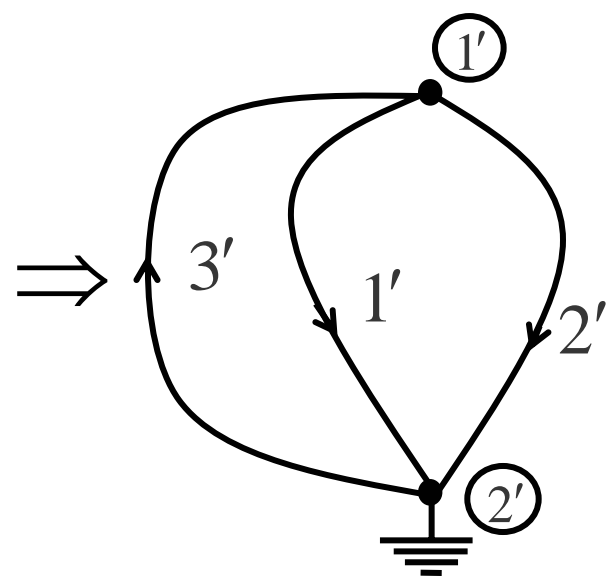

Theorem.



The **mesh-current equations** $\mathbf{Z}_m \hat{\mathbf{i}} = \mathbf{v}_s$ for a planar circuit N constitute an **independent** system of equations whose solution can be used to find *all* branch voltages and currents of N trivially via Ohm's law.

Proof.

For each planar circuit N , we can always construct its **dual** circuit N' . By the duality principle, the **node-voltage equations** $\mathbf{Y}_n \mathbf{e}' = \mathbf{i}'_s$ of N' are identical to the **mesh-current equations** of N , except for a trivial change of dual symbols

$$\text{mesh-current } \hat{i}_j \quad \rightarrow \quad \text{node-voltage } e'_j$$

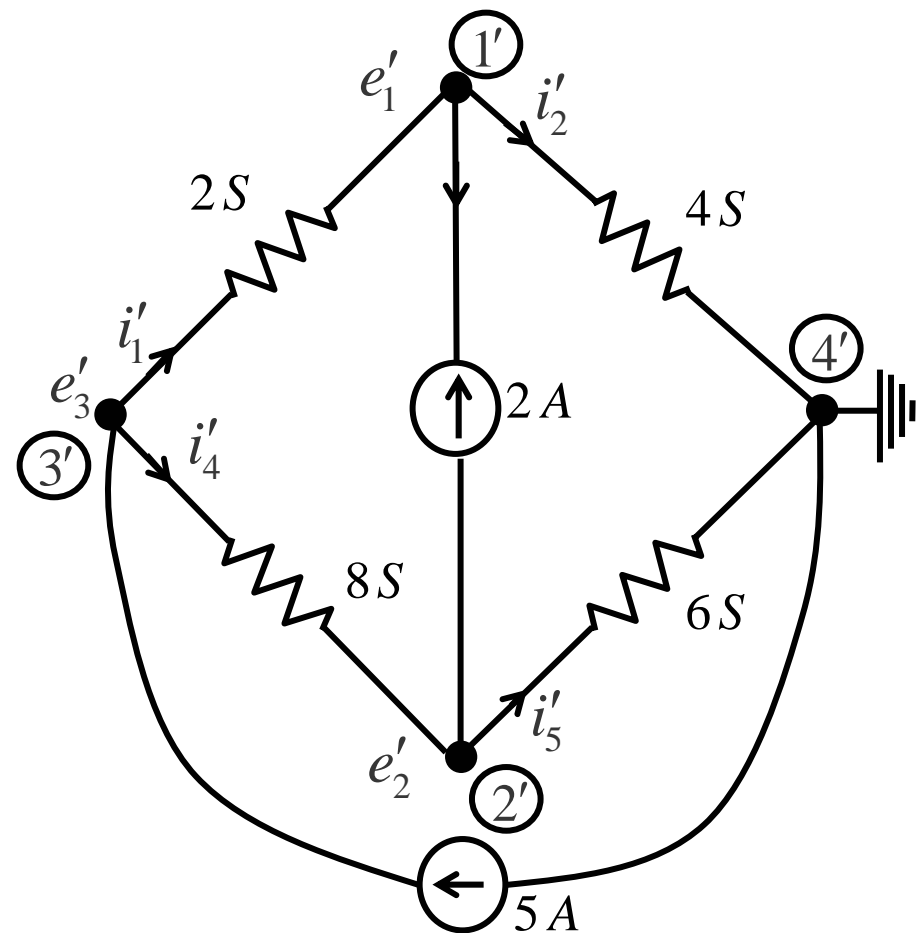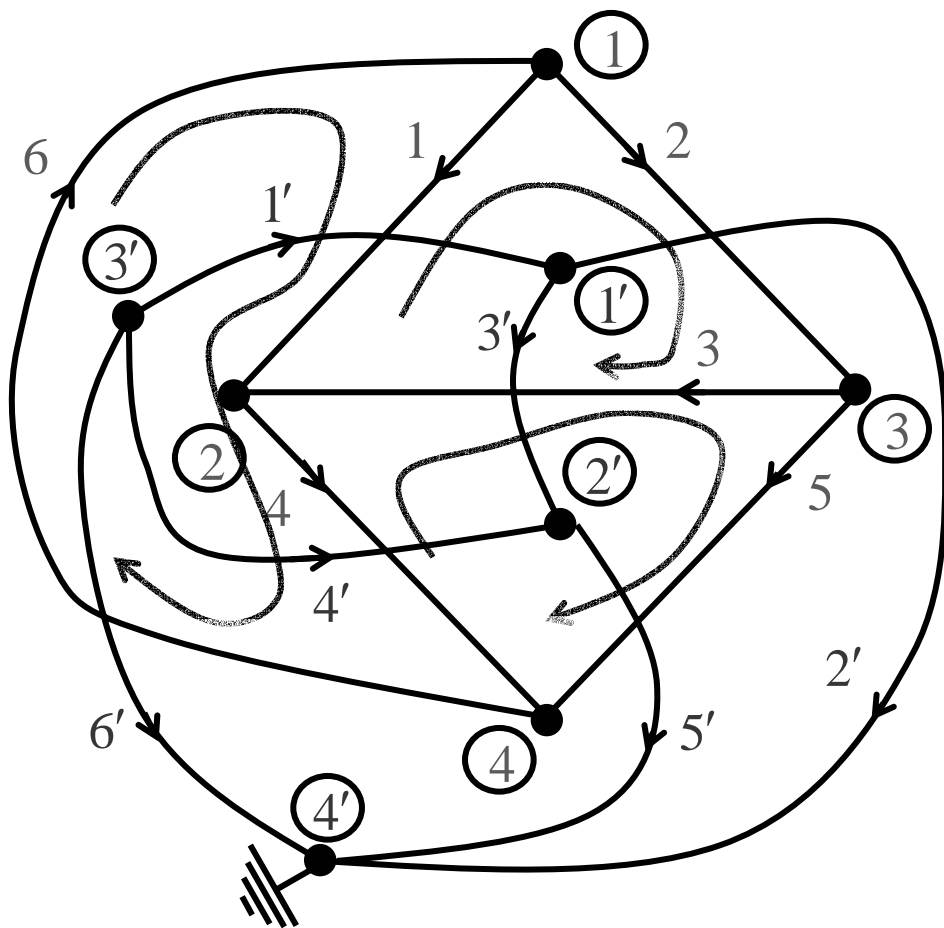But we have already proved the **node-voltage equations** constitute an **independent** system of equations whose solution can be used to find all branch voltages and currents of N' trivially via Ohm's law. ■



Mesh-current Equations

$$\begin{bmatrix} 6 & 0 & -2 \\ 0 & 14 & -8 \\ -2 & -8 & 10 \end{bmatrix} \begin{bmatrix} \hat{i}_1 \\ \hat{i}_2 \\ \hat{i}_3 \end{bmatrix} = \begin{bmatrix} 2 \\ -2 \\ 5 \end{bmatrix}$$

Node-voltage Equations

$$\begin{bmatrix} 6 & 0 & -2 \\ 0 & 14 & -8 \\ -2 & -8 & 10 \end{bmatrix} \begin{bmatrix} e'_1 \\ e'_2 \\ e'_3 \end{bmatrix} = \begin{bmatrix} 2 \\ -2 \\ 5 \end{bmatrix}$$