

$$\left[\begin{array}{cccccccccc} a_{11} & a_{12} & a_{13} & a_{14} & a_{15} & a_{16} & a_{17} & a_{18} & a_{19} & a_{1,10} \\ a_{21} & a_{22} & a_{23} & a_{24} & a_{25} & a_{26} & a_{27} & a_{28} & a_{29} & a_{2,10} \\ a_{31} & a_{32} & a_{33} & a_{34} & a_{35} & a_{36} & a_{37} & a_{38} & a_{39} & a_{3,10} \\ a_{41} & a_{42} & a_{43} & a_{44} & a_{45} & a_{46} & a_{47} & a_{48} & a_{49} & a_{4,10} \\ a_{51} & a_{52} & a_{53} & a_{54} & a_{55} & a_{56} & a_{57} & a_{58} & a_{59} & a_{5,10} \\ a_{61} & a_{62} & a_{63} & a_{64} & a_{65} & a_{66} & a_{67} & a_{68} & a_{69} & a_{6,10} \\ a_{71} & a_{72} & a_{73} & a_{74} & a_{75} & a_{76} & a_{77} & a_{78} & a_{79} & a_{7,10} \\ a_{81} & a_{82} & a_{83} & a_{84} & a_{85} & a_{86} & a_{87} & a_{88} & a_{89} & a_{8,10} \\ a_{91} & a_{92} & a_{93} & a_{94} & a_{95} & a_{96} & a_{97} & a_{98} & a_{99} & a_{9,10} \\ a_{10,1} & a_{10,2} & a_{10,3} & a_{10,4} & a_{10,5} & a_{10,6} & a_{10,7} & a_{10,8} & a_{10,9} & a_{10,10} \end{array} \right] \begin{matrix} x_1 \\ x_2 \\ x_3 \\ x_4 \\ x_5 \\ x_6 \\ x_7 \\ x_8 \\ x_9 \\ x_{10} \end{matrix} = \begin{matrix} b_1 \\ b_2 \\ b_3 \\ b_4 \\ b_5 \\ b_6 \\ b_7 \\ b_8 \\ b_9 \\ b_{10} \end{matrix}$$

A x b

CRAMER'S RULE

If $\det \mathbf{A} \neq 0$, then the solution $\mathbf{x} = [x_i]$ of the system of linear equations

$$\mathbf{Ax} = \mathbf{b}$$

is given by

$$x_i = \frac{\Delta_i}{\Delta}$$

$$i = 1, 2, \dots, n$$

where $\Delta = \det \mathbf{A}$ and $\Delta_i = \det \mathbf{A}_{(i)}$, where $\mathbf{A}_{(i)}$ is the matrix obtained by replacing the i th column of \mathbf{A} by \mathbf{b} .

Determinant of A

For a 3×3 matrix

$$\mathbf{A} = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$$

$$\begin{aligned} \det \mathbf{A} = & a_{11}(a_{22}a_{33} - a_{23}a_{32}) \\ & - a_{21}(a_{12}a_{33} - a_{13}a_{32}) \\ & + a_{31}(a_{12}a_{23} - a_{22}a_{13}) \triangleq \Delta \end{aligned}$$

Remark

An extension of the above procedure can be used to find $\det \mathbf{A}$ of any $n \times n$ matrix \mathbf{M} . However, for $n > 3$, it is too cumbersome and error prone to compute **determinants** manually. Almost every numerical analysis software includes a subroutine to compute determinants.

Determinant of A

Given

$$\mathbf{A} = \begin{bmatrix} a_{11} & a_{12} & \cdots & a_{1n} \\ a_{21} & a_{22} & \cdots & a_{2n} \\ \vdots & & & \\ a_{n1} & a_{n2} & \cdots & a_{nn} \end{bmatrix}$$

$$\det \mathbf{A} = \sum_{j=1}^n a_{jk} A_{jk}$$

for any $k = 1, 2, \dots, n$

Minor and Cofactor of a_{ij} of \mathbf{A}

Definition:

The determinant of the $(n-1) \times (n-1)$ matrix formed by deleting the i th row and the j th column of the $n \times n$ matrix \mathbf{A} is called the **minor** of element a_{ij} of \mathbf{A} , and is denoted by M_{ij} .

The number


$$A_{ij} = (-1)^{i+j} M_{ij}$$

is called the **cofactor** of a_{ij} .

Remark

The signs $(-1)^{i+j}$ form a checkerboard pattern:
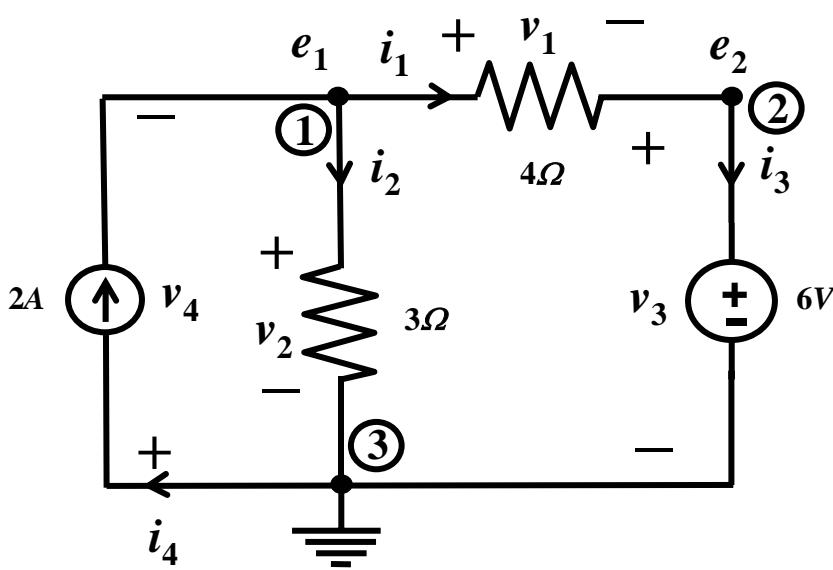
$$\begin{bmatrix} + & - & + & \dots \\ - & + & - & \dots \\ + & - & + & \dots \\ \vdots & \vdots & \vdots & \ddots \end{bmatrix}$$




Problem :

Find v_2 .

Solution-by-Inspection


Step1. Find voltage component solutions.

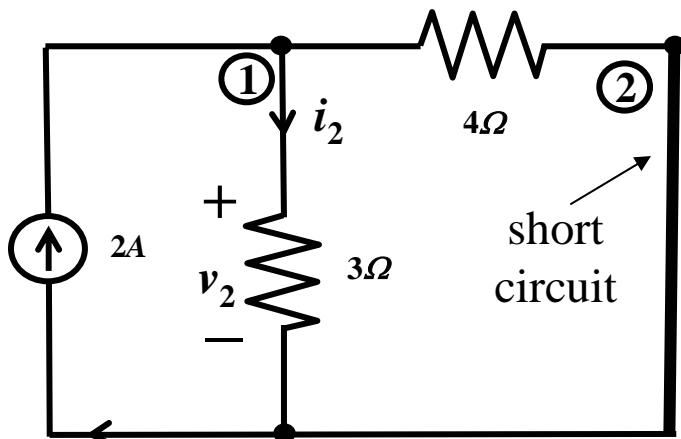

The 2 resistors in the simplified circuit are connected in parallel:

$$v'_2 = \left(\frac{3 \cdot 4}{3 + 4} \right) (2)$$

$$= \frac{24}{7} V$$

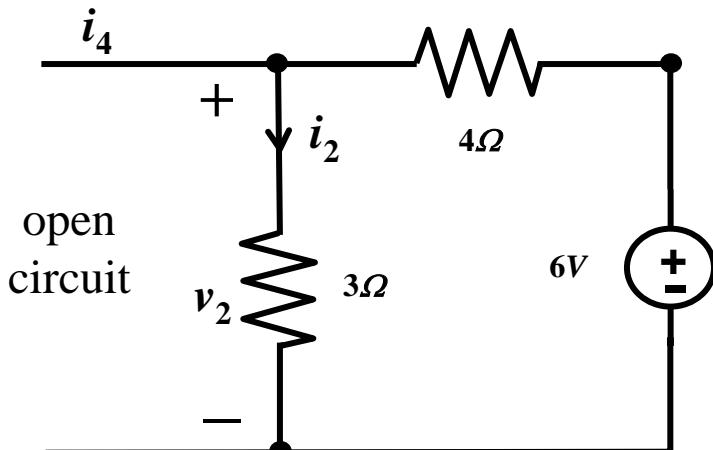

The simplified circuit is a voltage divider:

$$v''_2 = \left(\frac{3}{3 + 4} \right) (6)$$

$$= \frac{18}{7} V$$

Step2. Add voltage component solutions.

$$v_2 = v'_2 + v''_2 = \frac{24}{7} + \frac{18}{7} = \frac{42}{7} V$$

Let us rearrange all 10 independent equations as follow:

$$\left[\begin{array}{cc|ccccc|cccc} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 \\ \hline -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & -1 & 0 & 0 & 0 & 4 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & 0 & 0 & 3 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{array} \right] \begin{matrix} e_1 \\ e_2 \\ \vdots \\ v_1 \\ v_2 \\ v_3 \\ v_4 \\ \vdots \\ i_1 \\ i_2 \\ i_3 \\ i_4 \end{matrix} = \begin{matrix} 0 \\ 0 \\ \vdots \\ 0 \\ 0 \\ 0 \\ 0 \\ \vdots \\ 0 \\ 0 \\ 6 \\ 2 \end{matrix}$$

$\det \mathbf{A} =$

$$\left| \begin{array}{cc|ccccc|cccc} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 \\ \hline -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & -1 & 0 & 0 & 0 & 0 & 4 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 3 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{array} \right|$$

\mathbf{A}

$\triangleq \Delta$

$\det \mathbf{A}_1 =$

$$\left| \begin{array}{cc|ccccc|cccc} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 \\ \hline 0 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & -1 & 0 & 0 & 0 & 4 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & 0 & 0 & 3 & 0 & 0 \\ 6 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 2 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{array} \right| \triangleq \Delta_1$$

\mathbf{A}_1

$\det \mathbf{A}_4 =$

$$\left| \begin{array}{cc|cc|cc|cc} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 \\ \hline -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ \hline 0 & 0 & -1 & 0 & 0 & 0 & 4 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 3 & 0 \\ 0 & 0 & 0 & 6 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 2 & 0 & 0 & 0 & 0 & 1 \end{array} \right| \triangleq \Delta_4$$

$\underbrace{\hspace{10cm}}_{\mathbf{A}_4}$

$$\det \mathbf{A}_9 =$$

$$\left| \begin{array}{cc|ccccc|cccc} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 \\ \hline -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & -1 & 0 & 0 & 0 & 0 & 4 & 0 & 0 & 0 \\ 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 3 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 6 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 2 & 1 \end{array} \right|$$

$$\mathbf{A}_9$$

$$\triangleq \Delta_9$$

$$\begin{aligned}
e_1 &= \frac{\Delta_1}{\Delta} \\
&= \frac{1}{\Delta} \left\{ \begin{array}{l} 0 \bullet A_{11} + 0 \bullet A_{21} + 0 \bullet A_{31} + 0 \bullet A_{41} + 0 \bullet A_{51} \\ + 0 \bullet A_{61} + 0 \bullet A_{71} + 0 \bullet A_{81} + 6 \bullet A_{91} + 2 \bullet A_{10,1} \end{array} \right\} \\
&= \frac{1}{\Delta} (6 \bullet A_{91} + 2 \bullet A_{10,1}), \quad \text{because } a_{11} = a_{21} = \cdots = a_{81} = 0
\end{aligned}$$

$$\begin{aligned}
&= \underbrace{\frac{A_{91}}{\Delta}}_{k_{11}} (6) + \underbrace{\frac{A_{10,1}}{\Delta}}_{k_{12}} (2)
\end{aligned}$$

$$= k_{11} \bullet 6 + k_{12} \bullet 2$$

$$= k_{11} \bullet v_{s1} + k_{12} \bullet i_{s1}$$

$$\begin{aligned}
i_9 &= \frac{\Delta_9}{\Delta} \\
&= \frac{1}{\Delta} \left\{ \begin{array}{l} 0 \bullet A_{19} + 0 \bullet A_{29} + 0 \bullet A_{39} + 0 \bullet A_{49} + 0 \bullet A_{59} \\ + 0 \bullet A_{69} + 0 \bullet A_{79} + 0 \bullet A_{89} + 6 \bullet A_{99} + 2 \bullet A_{10,9} \end{array} \right\} \\
&= \frac{1}{\Delta} (6 \bullet A_{99} + 2 \bullet A_{10,9}) \\
&= \underbrace{\frac{A_{99}}{\Delta}}_{k''_{11}} + \underbrace{\frac{A_{10,9}}{\Delta}}_{k''_{12}} \\
&= k''_{11} \bullet v_{s1} + k''_{12} \bullet i_{s1}
\end{aligned}$$

$$\nu_2 = \frac{\Delta_4}{\Delta} \\ = \frac{1}{\Delta} \left\{ \begin{array}{l} 0 \bullet A_{14} + 0 \bullet A_{24} + 0 \bullet A_{34} + 0 \bullet A_{44} + 0 \bullet A_{54} \\ + 0 \bullet A_{64} + 0 \bullet A_{74} + 0 \bullet A_{84} + 6 \bullet A_{94} + 2 \bullet A_{10,4} \end{array} \right\}$$

$$= \frac{1}{\Delta} (6 \bullet A_{94} + 2 \bullet A_{10,4})$$

$$= \underbrace{\frac{A_{94}}{\Delta}}_{(6)} + \underbrace{\frac{A_{10,4}}{\Delta}}_{(2)}$$

$$k'_{11} \qquad \qquad k'_{12}$$

$$= k'_{11} \bullet \nu_{s1} + k'_{12} \bullet i_{s1}$$

Let us rearrange all 10 independent equations as follow:

$$\left[\begin{array}{cccccc|cccc} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 \\ \hline -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & -1 & 0 & 0 & 0 & 4\frac{d}{dt} & 0 & 0 & 0 \\ 0 & 0 & 0 & 2\frac{d}{dt} & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{array} \right] \begin{matrix} e_1 \\ e_2 \\ v_1 \\ v_2 \\ v_3 \\ v_4 \\ i_1 \\ i_2 \\ i_3 \\ i_4 \end{matrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 6\sin\omega t \\ 2\cos\omega t \end{bmatrix}$$

Let us rearrange all 10 independent equations as follow:

$$\left[\begin{array}{cc|ccccc|cccc} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & -1 & 0 & 1 & 0 \\ \hline -1 & 1 & 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & -1 & 0 & 0 & 0 & L_1 \frac{d}{dt} & 0 & 0 & 0 \\ 0 & 0 & 0 & C_2 \frac{d}{dt} & 0 & 0 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{array} \right] \begin{bmatrix} e_1 \\ e_2 \\ v_1 \\ v_2 \\ v_3 \\ v_4 \\ i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 6 \sin \omega t \\ 2 \cos \omega t \end{bmatrix}$$

$$\left[\begin{array}{cccc} -1 & 0 & 0 & 0 \\ 0 & 2\frac{d}{dt} & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{array} \right] \left[\begin{array}{cccc} 4\frac{d}{dt} & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{array} \right] \left[\begin{array}{c} v_1 \\ v_2 \\ v_3 \\ v_4 \\ i_1 \\ i_2 \\ i_3 \\ i_4 \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 6\sin\omega t \\ 2\cos\omega t \end{array} \right]$$

$\underbrace{\qquad\qquad\qquad}_{\mathbf{H}_v}$ $\underbrace{\qquad\qquad\qquad}_{\mathbf{H}_i}$ $\underbrace{\qquad\qquad\qquad}_{\mathbf{v}}$ $\underbrace{\qquad\qquad\qquad}_{\mathbf{i}}$ $\underbrace{\qquad\qquad\qquad}_{\mathbf{u}}$

↓

$\mathbf{H}_v \mathbf{v} + \mathbf{H}_i \mathbf{i} = \mathbf{u}$

↑
independent source vector

$$\underbrace{\begin{bmatrix} -1 & 0 & 0 & 0 \\ 0 & C_2 \frac{d}{dt} & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}}_{\mathbf{H}_v} \quad \underbrace{\begin{bmatrix} L_1 \frac{d}{dt} & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}}_{\mathbf{H}_i} = \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 6 \sin \omega t \\ 2 \cos \omega t \end{bmatrix}$$

u

independent
source
vector



$$\begin{bmatrix} \mathbf{v} \\ \mathbf{i} \end{bmatrix}$$

$$\boxed{\mathbf{H}_v \mathbf{v} + \mathbf{H}_i \mathbf{i} = \mathbf{u}}$$