
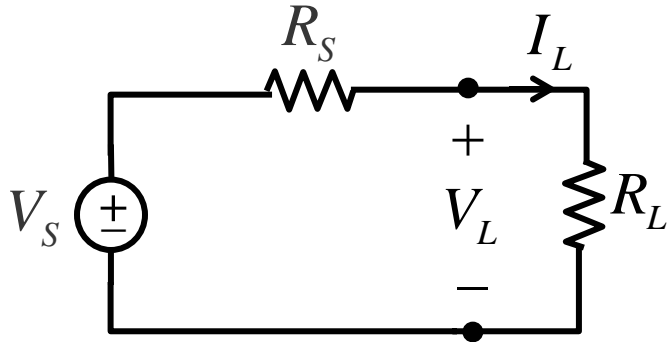


Maximum Power Transfer

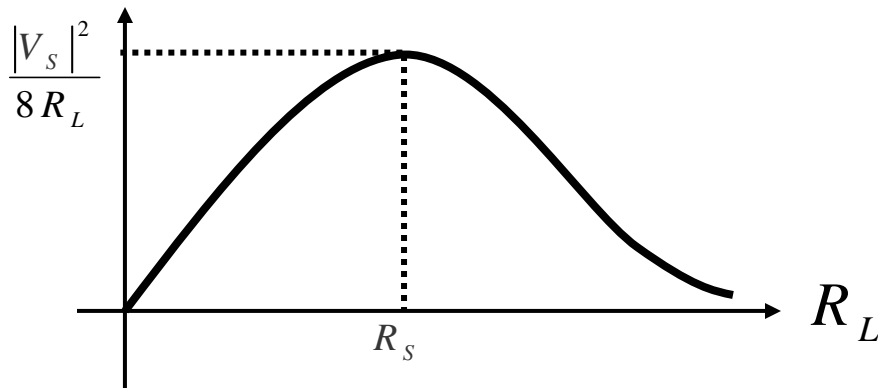

$$I_L = \frac{V_S}{R_S + R_L}$$

$$P_{av_L} = \frac{1}{2} |V_L| |I_L| = \frac{1}{2} R_L |I_L|^2 = \frac{1}{2} |V_S|^2 \frac{R_L}{(R_S + R_L)^2}$$




\therefore For fixed V_S and R_S , maximum average power transfer to load R_L occurs when

$$\frac{dP_{av_L}}{\partial R_L} = \frac{1}{2} |V_S|^2 \frac{(R_S + R_L)^2 - 2(R_S + R_L)R_L}{(R_S + R_L)^4} = 0 \Rightarrow$$

$$R_L = R_S$$

Maximum Power Transfer

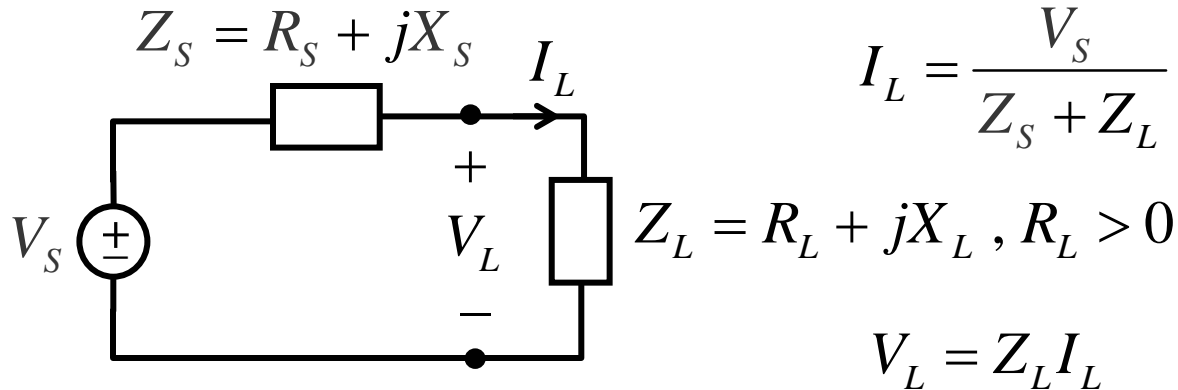

$$I_L = \frac{V_S}{Z_S + Z_L}$$

$$Z_L = R_L + jX_L, R_L > 0$$

$$V_L = Z_L I_L$$


$$P_{av_L} = \frac{1}{2} |V_L| |I_L| \cos \angle Z_L = \frac{1}{2} |Z_L| |I_L|^2 \cos \angle Z_L = \frac{1}{2} R_L |I_L|^2$$

$$= \frac{1}{2} |V_S|^2 \frac{R_L}{|Z_S + Z_L|^2} = \frac{1}{2} |V_S|^2 \frac{R_L}{(R_S + R_L)^2 + (X_S + X_L)^2}$$

To maximize P_{av_L} , necessary to set $X_L = -X_S$


$$\Rightarrow P_{av_L} = \frac{1}{2} |V_S|^2 \frac{R_L}{(R_S + R_L)^2}$$

$$\frac{dP_{av_L}}{\partial R_L} = \frac{1}{2} |V_S|^2 \frac{(R_S + R_L)^2 - 2(R_S + R_L)R_L}{(R_S + R_L)^4} = 0 \Rightarrow R_L = R_S$$

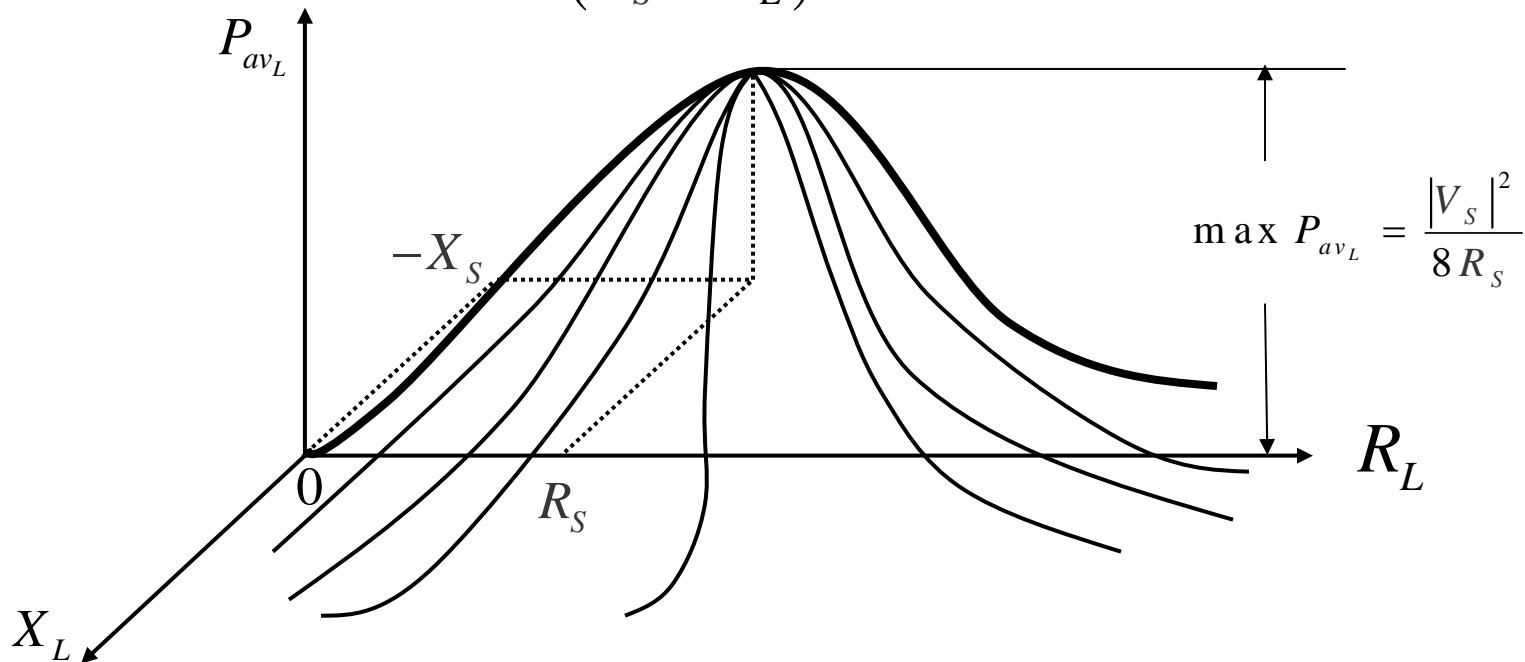

Theorem : Maximum Power Theorem

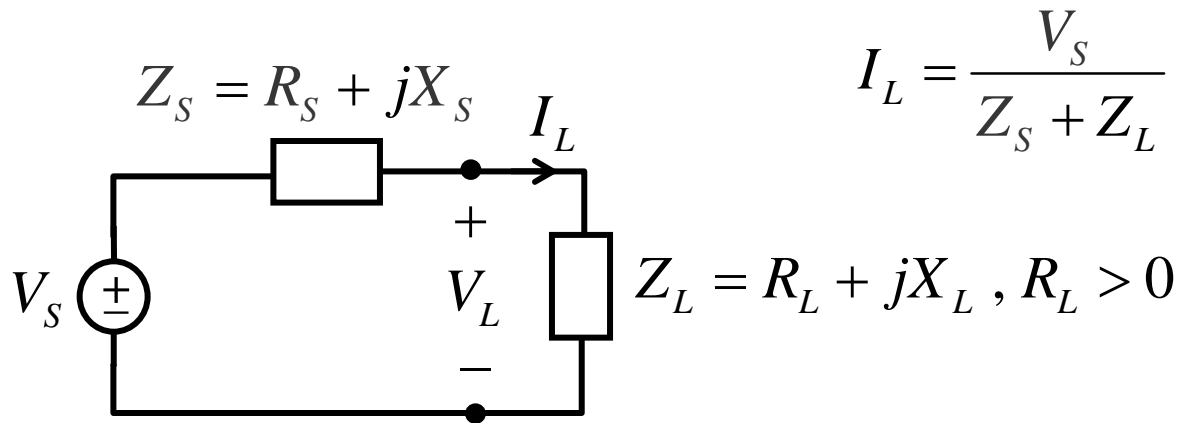Optimum Load Impedance $Z_{L_{opt}} = \bar{Z}_S$



Max. Power Theorem : $Z_{L_{opt}} = \bar{Z}_S$ **Conjugate-match condition**

$$\begin{aligned}
 P_{av_s} &= \frac{1}{2} |V_S| |I_S| \cos \angle (Z_S + Z_L) \\
 &= \frac{1}{2} (|(Z_S + Z_L)| |I_S|) |I_S| \cos \angle (Z_S + Z_L) \\
 &= \frac{1}{2} |I_S|^2 \operatorname{Re}(Z_S + Z_L) \\
 &= \frac{1}{2} |I_L|^2 \operatorname{Re}(Z_S + Z_L) \\
 &= \frac{1}{2} \frac{|V_S|^2}{|Z_S + Z_L|^2} \operatorname{Re}(Z_S + Z_L)
 \end{aligned}$$

$$\therefore P_{av_S} \Big|_{Z_L = \bar{Z}_S} = \frac{1}{2} \frac{|V_S|^2}{|Z_S + \bar{Z}_S|^2} \operatorname{Re}(Z_S + \bar{Z}_S) = \frac{1}{2} \frac{|V_S|^2}{|2R_S|^2} (2R_S)$$


$$= \frac{|V_S|^2}{4R_S} = 2P_{av_L}$$

$$\text{Efficiency} = \frac{P_{av_L}}{P_{av_S}} = \frac{P_{av_L}}{2P_{av_L}} = \frac{1}{2} \quad \text{or} \quad 50\%$$

Comments :

1. Under conjugate-match condition, 50% of the power delivered by the source is lost as heat dissipation in R_S . \therefore Power company **never** conjugates their loads!
2. **Max. Power Theorem** is used extensively in communication circuits to extract maximum power from preceding stages.

Network Functions

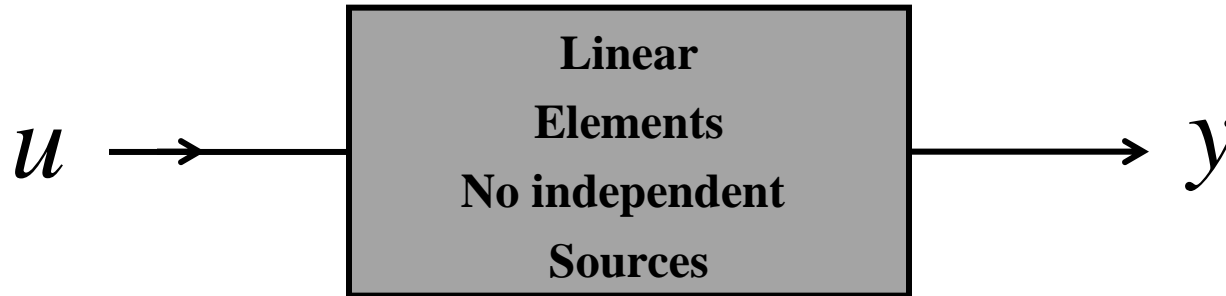

$$u(t) = |U| \cos(\omega t + \angle U)$$



$$U = |U| e^{j\angle U}$$

$$y(t) = |Y| \cos(\omega t + \angle Y)$$




$$Y = |Y| e^{j\angle Y}$$


Definition

$$H(j\omega) \triangleq \frac{Y(j\omega)}{U(j\omega)}$$


is called a **Network Function**.

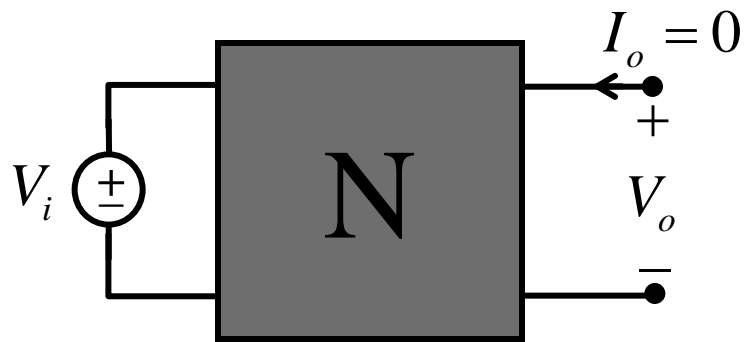

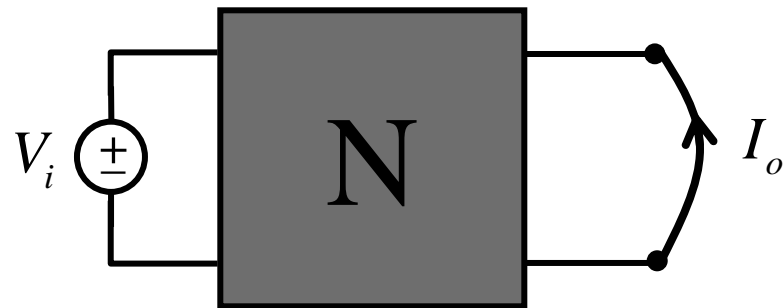
$$H(j\omega) \triangleq \frac{V_o(j\omega)}{V_i(j\omega)}$$


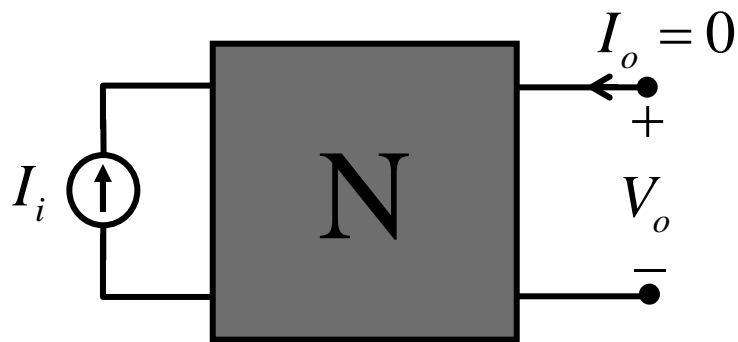
$$H(j\omega) \triangleq \frac{I_o(j\omega)}{V_i(j\omega)}$$




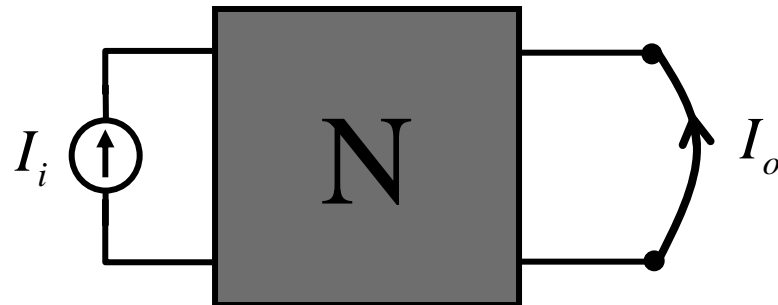
$$H(j\omega) \triangleq \frac{V_o(j\omega)}{I_i(j\omega)}$$



$$H(j\omega) \triangleq \frac{I_o(j\omega)}{I_i(j\omega)}$$

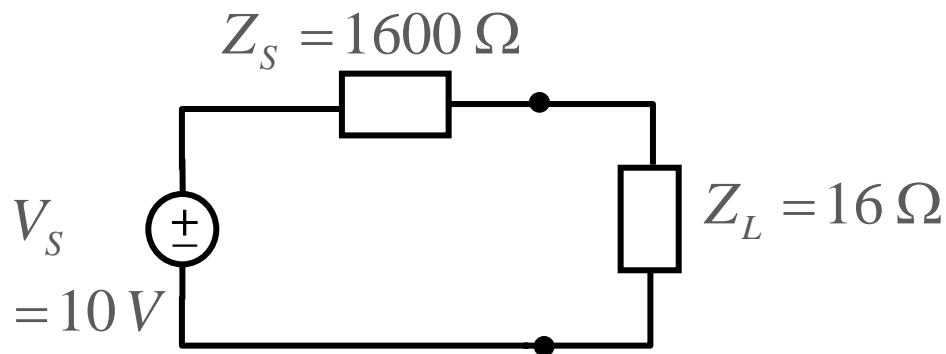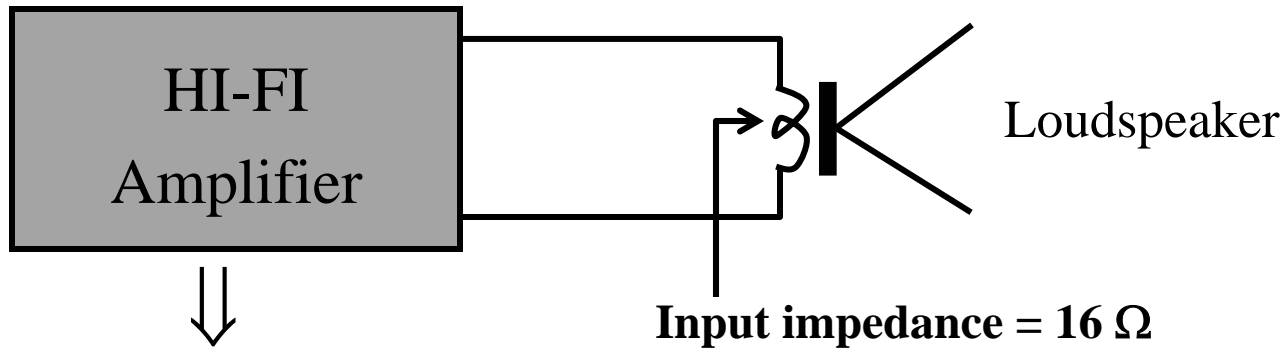Typical Application of Max. Power Theorem



Let P_o = average power delivered to loudspeaker

$$P_o = \frac{1}{2} |V_S|^2 \frac{\text{Re } Z_L}{|Z_S + Z_L|^2} = \frac{1}{2} (10)^2 \left(\frac{16}{1600 + 16} \right) \approx 50 (10^{-2}) = 0.5 W$$



For maximum power transfer, make $Z_L = 1600 \Omega$.

$$P_o = \frac{1}{2} (10)^2 \left(\frac{1600}{1600 + 1600} \right) = 25 W$$

For maximum power transfer, make $Z_L = 1600 \Omega$.


$$P_o = \frac{1}{2} (10)^2 \left(\frac{1600}{1600 + 1600} \right) = 25 \text{ W}$$

Use a transformer :

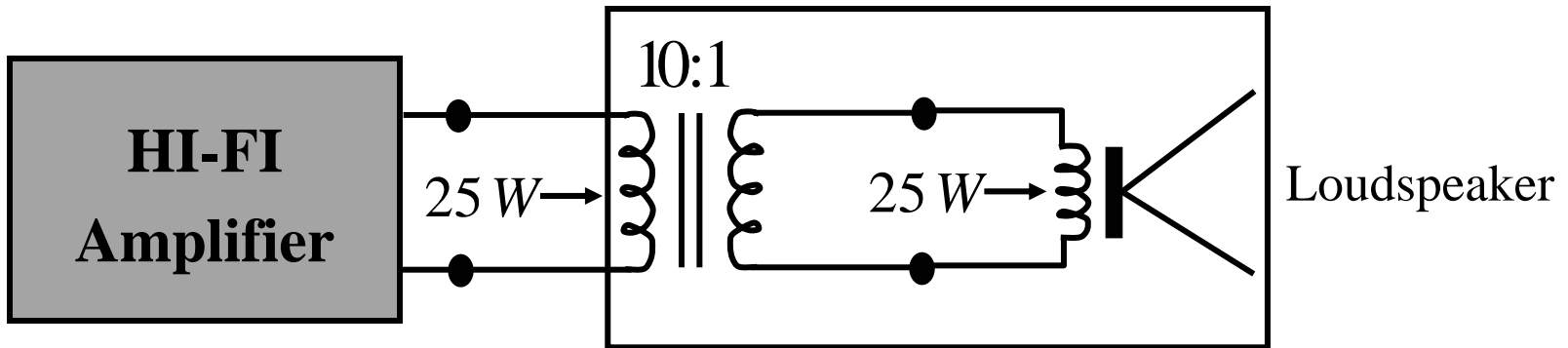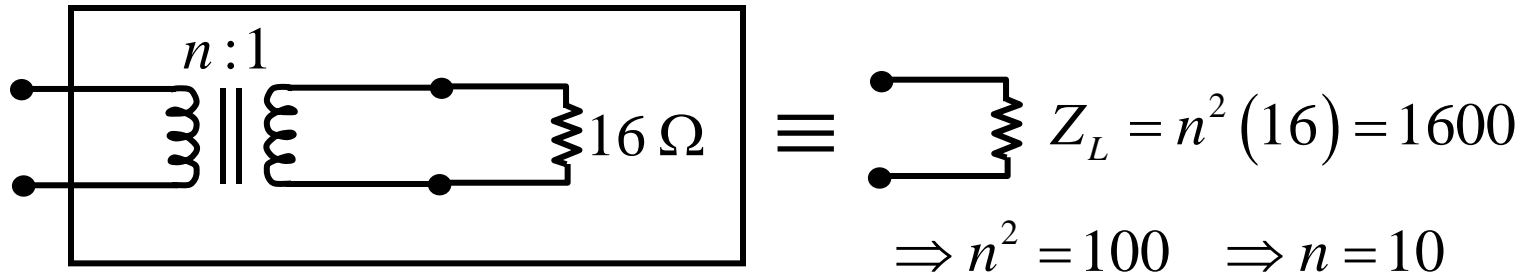

transformer is non-energetic \Rightarrow 25 Watts of power is delivered to loudspeaker.

FREQUENCY RESPONSE

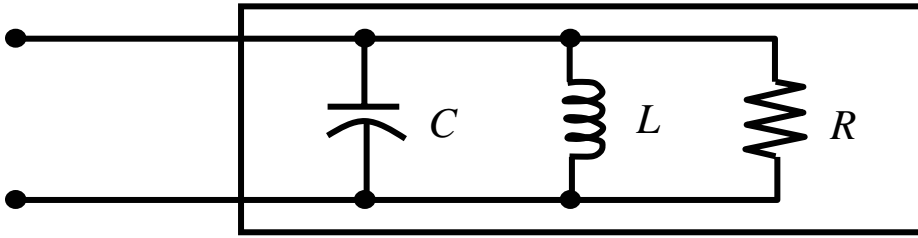




$$Z(j\omega) = \underbrace{\frac{1/R}{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}}_{\text{Resistance function}} + j \underbrace{\frac{-\left(\omega C - \frac{1}{\omega L}\right)}{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2}}_{\text{Reactance function}}$$

Resistance function $\rightarrow R(j\omega)$


$X(j\omega)$

\leftarrow Reactance function
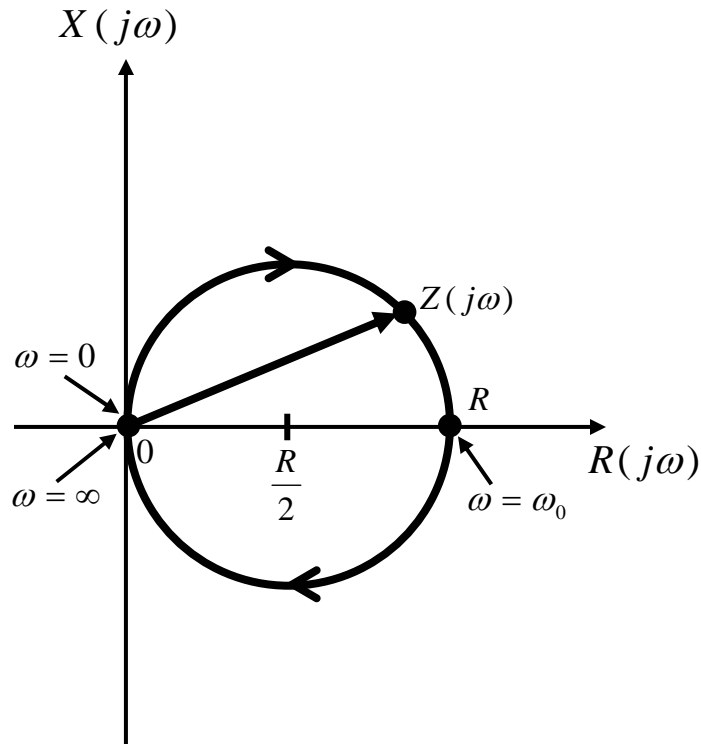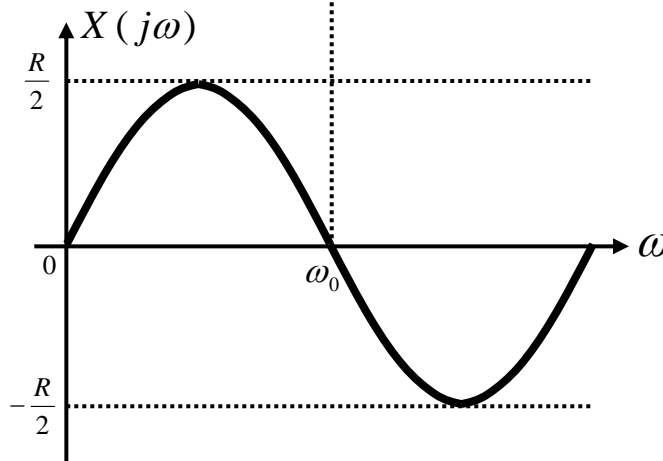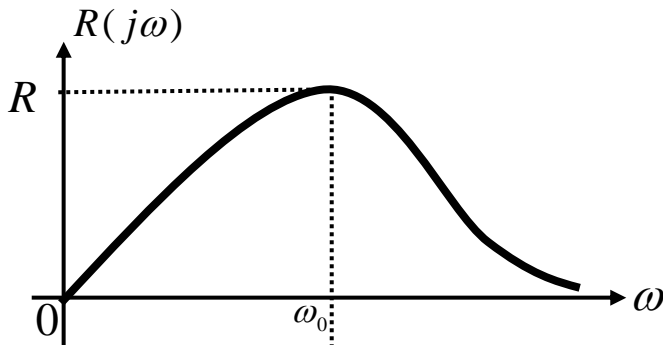
$$\omega C = \frac{1}{\omega L} \Rightarrow \omega = \frac{1}{\sqrt{LC}} \triangleq \omega_0 \leftarrow \text{Resonant frequency}$$



FREQUENCY RESPONSE



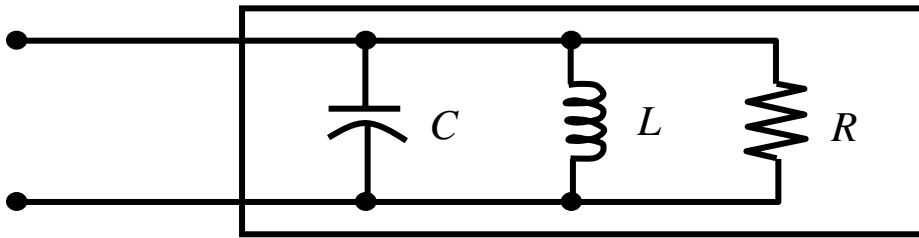


$$|Z(j\omega)| = \sqrt{\left(\frac{1/R}{\left(1/R\right)^2 + \left(\omega C - 1/\omega L\right)^2} \right)^2 + \left(\frac{\omega C - 1/\omega L}{\left(1/R\right)^2 + \left(\omega C - 1/\omega L\right)^2} \right)^2}$$


$$\angle Z(j\omega) = \tan^{-1} \left(\frac{-\left(\omega C - 1/\omega L\right)}{1/R} \right)$$

$$\omega C = 1/\omega L \Rightarrow \omega = 1/\sqrt{LC} \triangleq \omega_0 \leftarrow$$

Resonant frequency

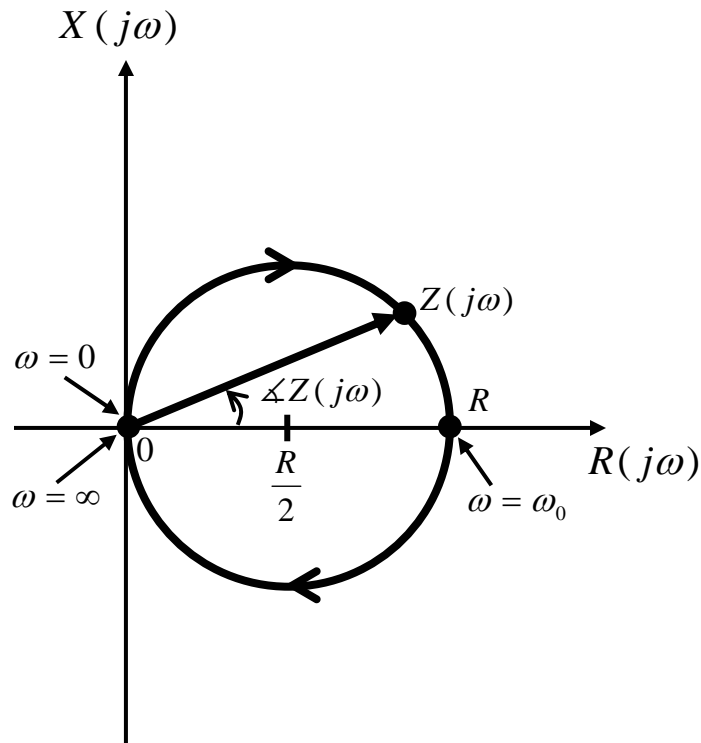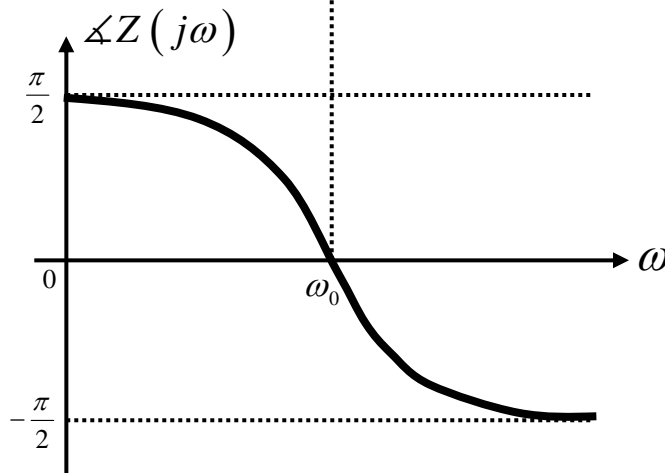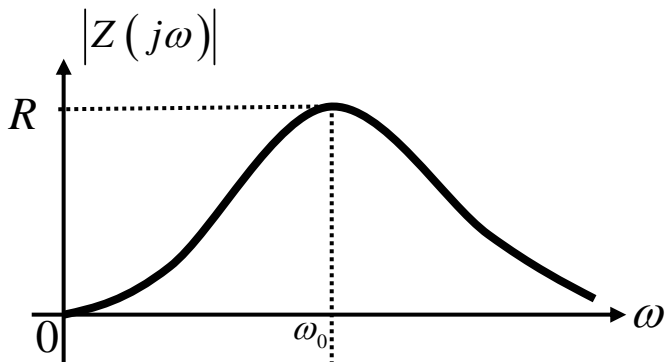

FREQUENCY RESPONSE

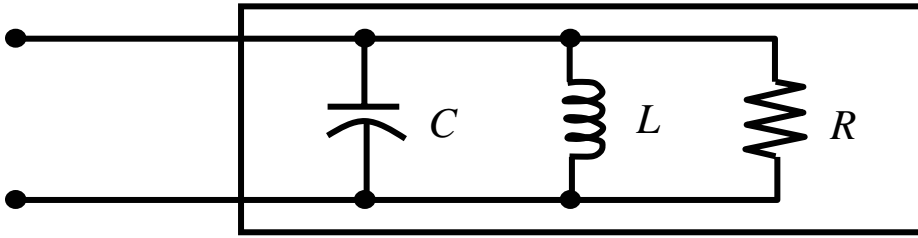

$$Y(j\omega) = \underbrace{\frac{1}{R}}_{G(j\omega)} + j \underbrace{\left(\omega C - \frac{1}{\omega L}\right)}_{B(j\omega)}$$




$G(j\omega)$

$B(j\omega) \leftarrow$ Susceptance function


↑
Conductance function

$$\omega C = \frac{1}{\omega L} \Rightarrow \omega = \frac{1}{\sqrt{LC}} \triangleq \omega_0 \leftarrow$$

Resonant frequency

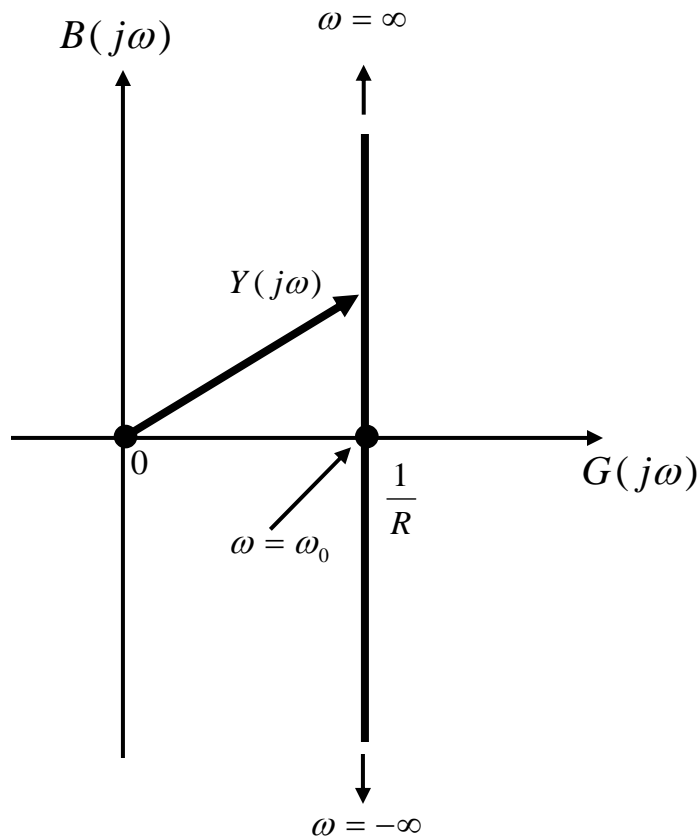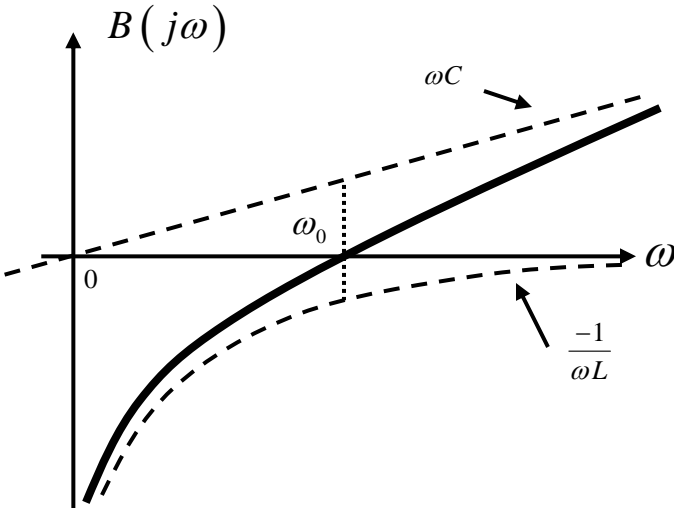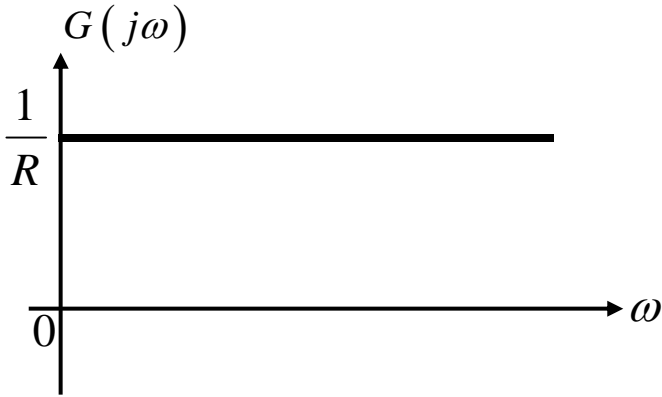




FREQUENCY RESPONSE

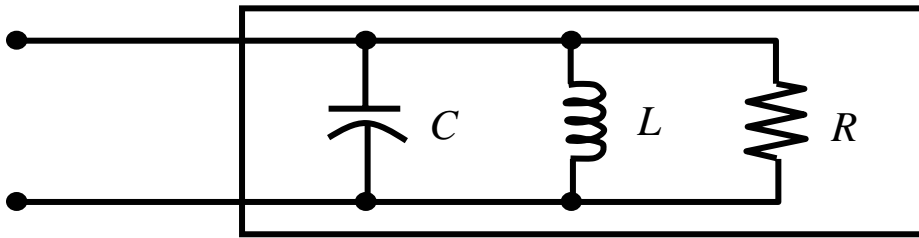



$$|Y(j\omega)| = \sqrt{\left(\frac{1}{R}\right)^2 + \left(\omega C - \frac{1}{\omega L}\right)^2} \quad \leftarrow \text{Magnitude function}$$

$$\angle Y(j\omega) = \tan^{-1} \left(\frac{\omega C - \frac{1}{\omega L}}{\frac{1}{R}} \right) \quad \leftarrow \text{Phase function}$$
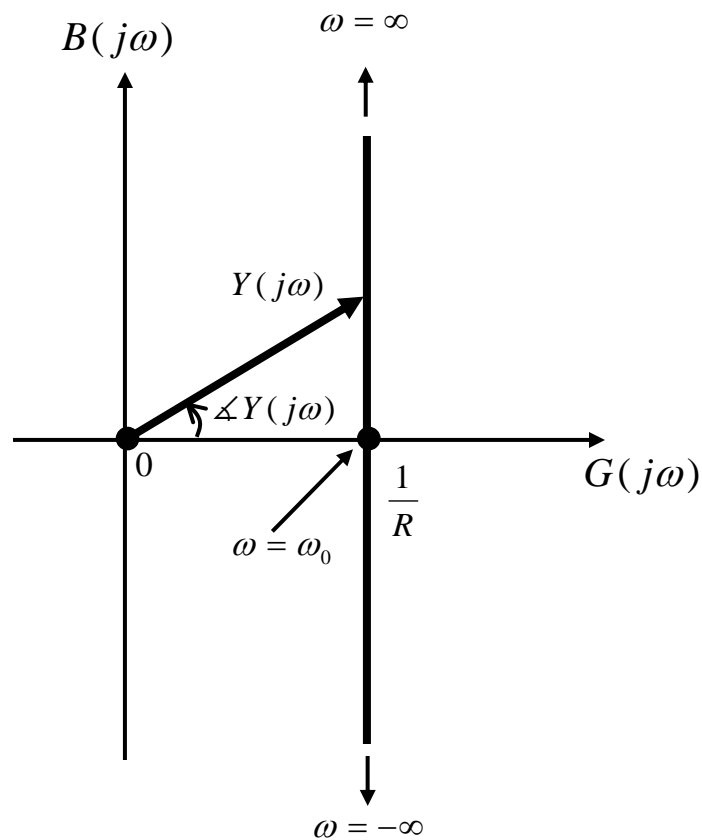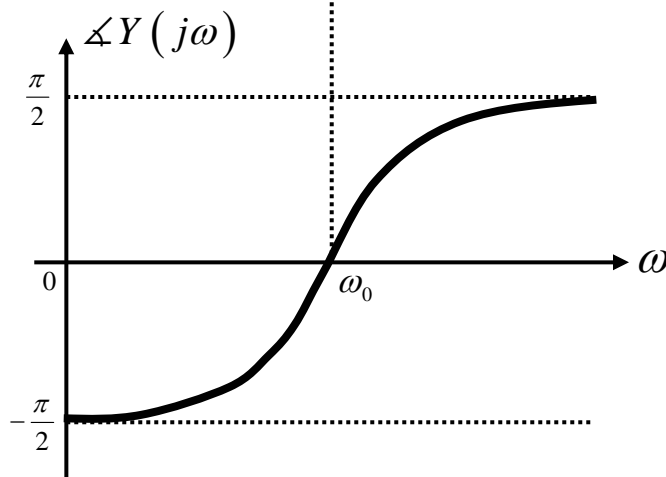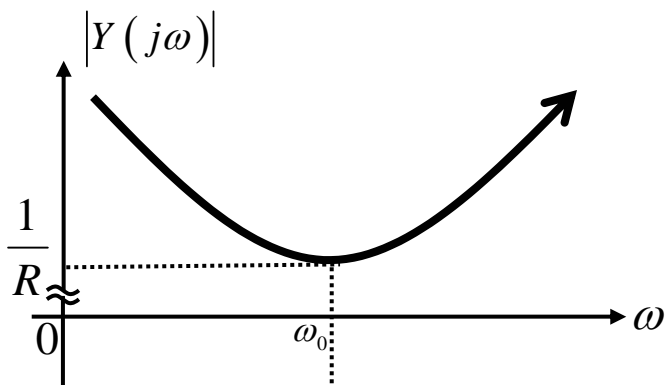
$$\omega C = \frac{1}{\omega L} \Rightarrow \omega = \frac{1}{\sqrt{LC}} \triangleq \omega_0 \quad \leftarrow \text{Resonant frequency}$$




Resonance

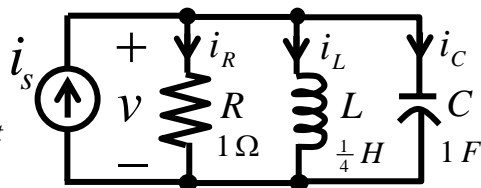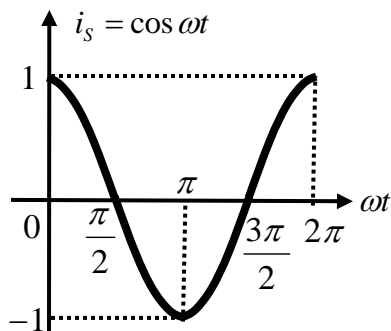

$$\omega = 2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$I = 1e^{i0^\circ}$$

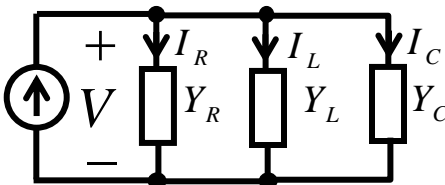


$$Y(j2) = 1 \quad , Z(j2) = 1$$

$$V(j2) = Z(j2)I(j2) = 1$$


$$I_R(j2) = Y_R(j2)V(j2) = 1$$

$$I_L(j2) = Y_L(j2)V(j2) = 2 \angle -90^\circ$$
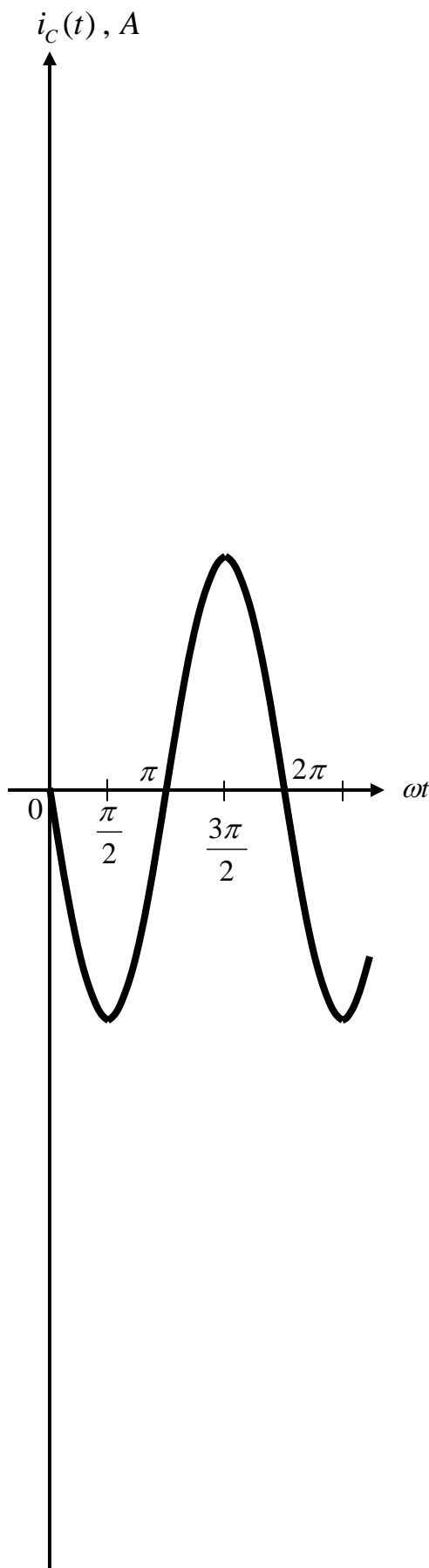
$$I_C(j2) = Y_C(j2)V(j2) = 2 \angle 90^\circ$$





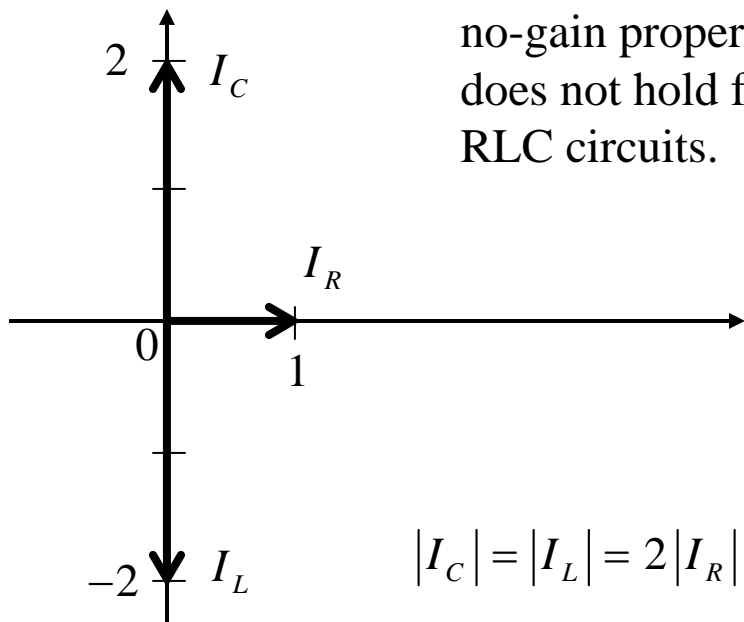no-gain property
does not hold for
RLC circuits.



$$|I_C| = |I_L| = 2 |I_R|$$


Resonance

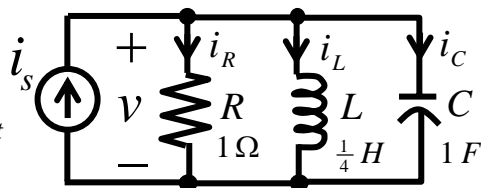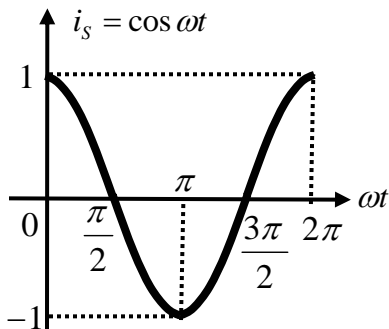

$$\omega = 1$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$I = 1e^{i0^\circ}$$

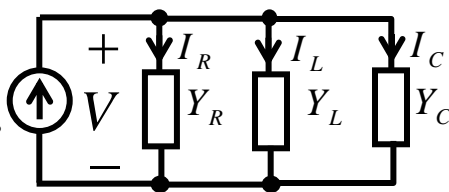



$$Y(j1) = \sqrt{10} \angle -71.6^\circ, \quad Z(j1) = \frac{1}{\sqrt{10}} \angle 71.6^\circ$$

$$V(j1) = Z(j1)I(j1) = \frac{1}{\sqrt{10}} \angle 71.6^\circ$$



$$I_R(j1) = Y_R(j1)V(j1) = \frac{1}{\sqrt{10}} \angle 71.6^\circ$$

$$I_L(j1) = Y_L(j1)V(j1) = \frac{4}{\sqrt{10}} \angle -18.4^\circ$$
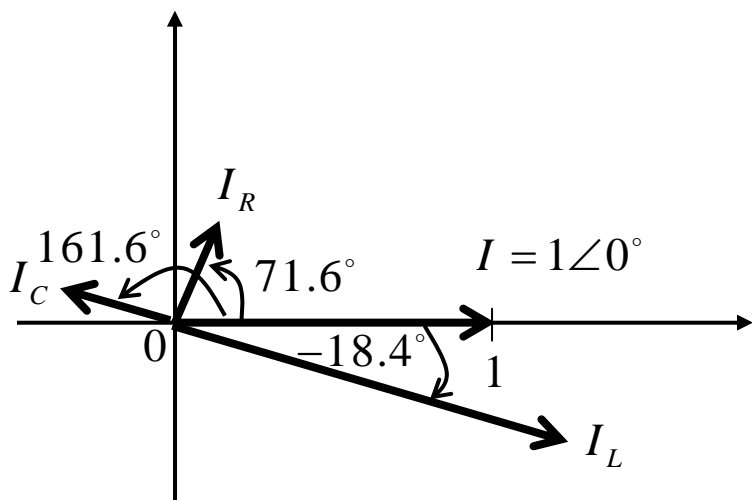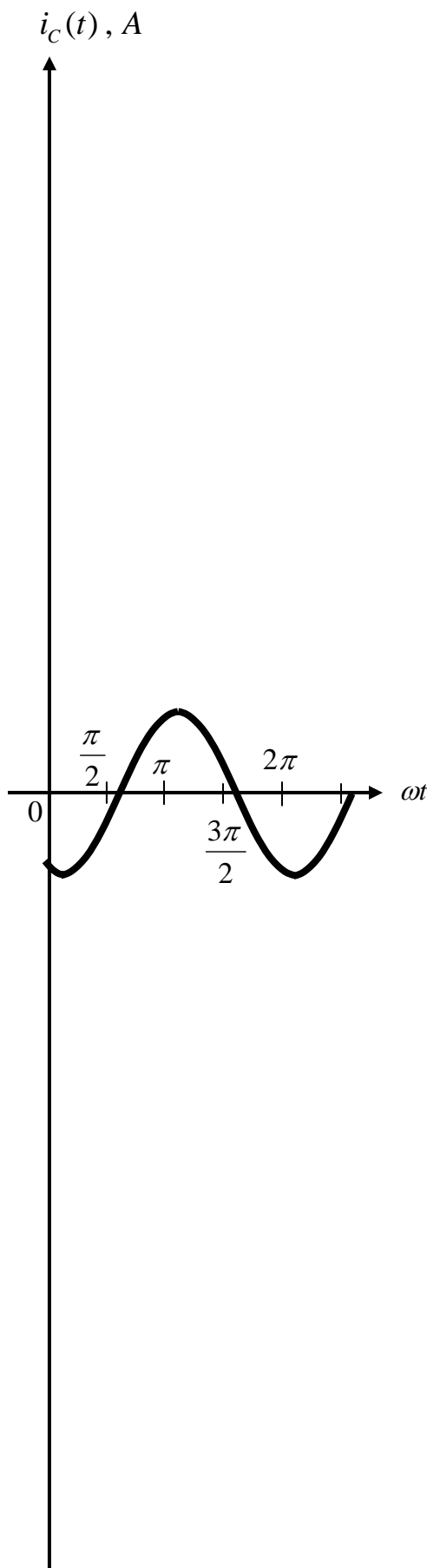
$$I_C(j1) = Y_C(j1)V(j1) = \frac{1}{\sqrt{10}} \angle 161.6^\circ$$




Resonance

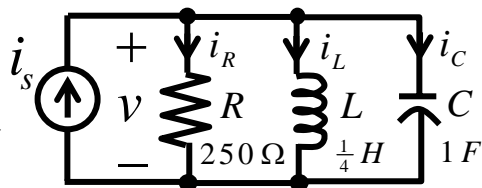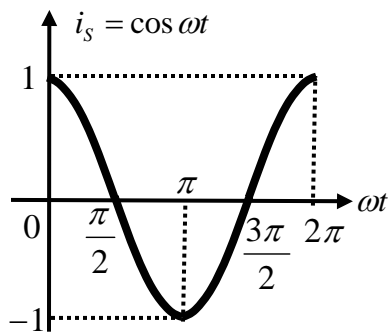

$$\omega = 2$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$I = 1e^{i0^\circ}$$

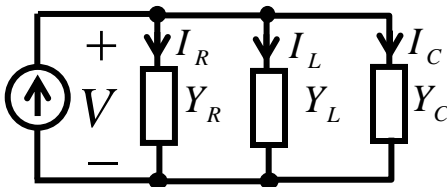



$$Y(j2) = 4 \times 10^{-3} \text{ S}, Z(j2) = 250 \Omega$$

$$V(j2) = Z(j2)I(j2) = 250 \text{ V}$$


$$I_R(j2) = Y_R(j2)V(j2) = 1 \text{ A}$$

$$I_L(j2) = Y_L(j2)V(j2) = 500 \angle -90^\circ \text{ A}$$
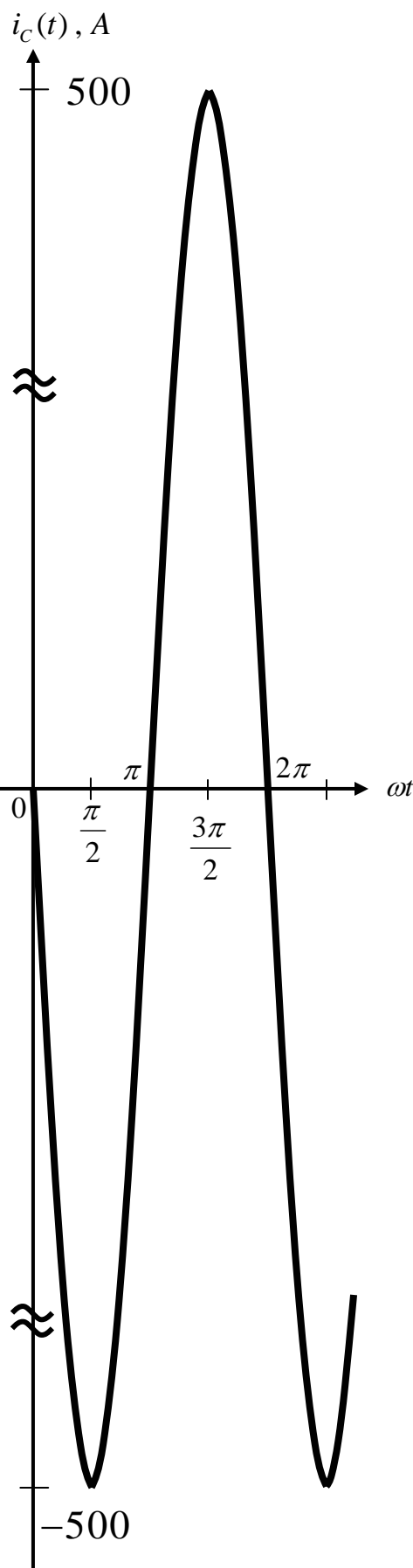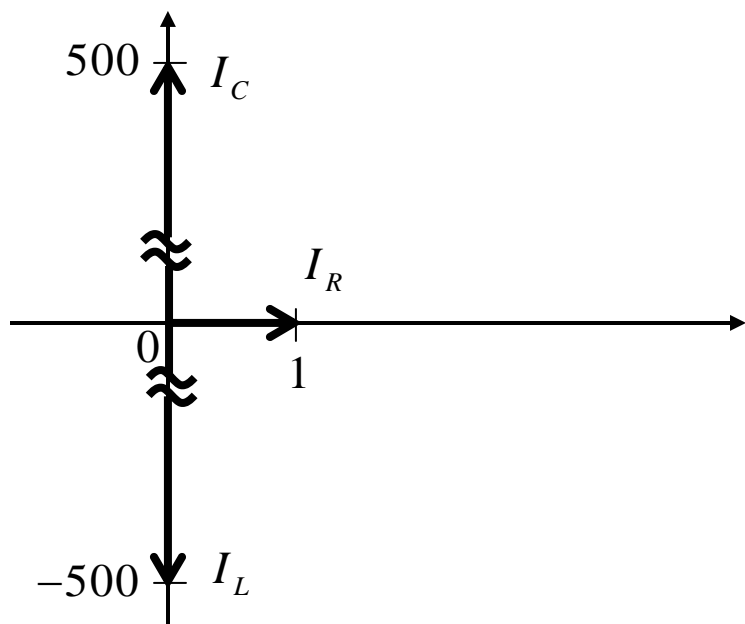
$$I_C(j2) = Y_C(j2)V(j2) = 500 \angle 90^\circ \text{ A}$$



Instantaneous, Average, Complex Power

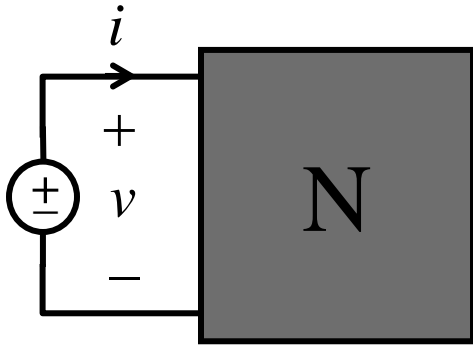

$$v(t) = |V| \cos(\omega t + \angle V)$$

$$i(t) = |I| \cos(\omega t + \angle I)$$


Instantaneous Power

$$p(t) = v(t)i(t) = |V||I| \cos(\omega t + \angle V) \cos(\omega t + \angle I)$$

$$= \underbrace{\frac{1}{2}|V||I| \cos(\angle V - \angle I)}_{\text{constant}} + \underbrace{\frac{1}{2}|V||I| \cos(2\omega t + \angle V + \angle I)}_{\text{Sinusoid of twice the frequency}}$$

constant

Sinusoid of twice the frequency

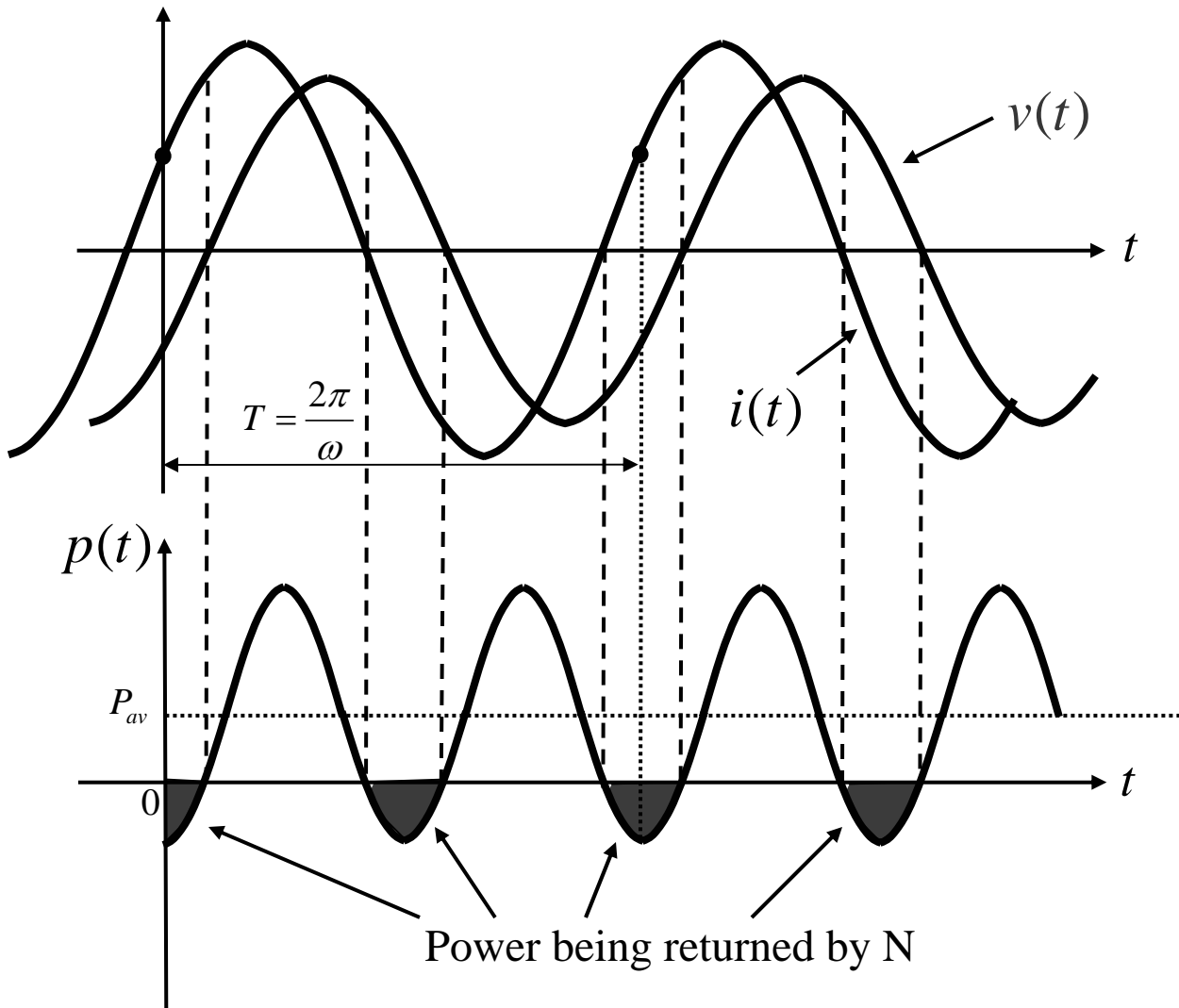


Average Power

$$P_{av} \triangleq \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} |V| |I| \cos(\angle V - \angle I)$$

$$V = Z I$$

$$\begin{aligned} |V| e^{j\angle V} &= |Z| e^{j\angle Z} \cdot |I| e^{j\angle I} \\ &= |Z| |I| e^{j(\angle Z + \angle I)} \end{aligned}$$

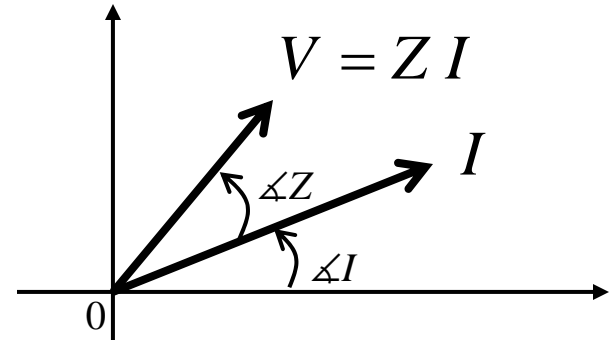

$$\therefore \angle V = \angle Z + \angle I \quad \Rightarrow \quad \angle Z = \angle V - \angle I$$

$$\text{Average Power } P_{av} = \frac{1}{2} |V| |I| \cos \angle Z$$

Remarks:

$$1. \quad P_{av} = 0 \quad \text{in } \begin{cases} \text{INDUCTOR} \\ \text{CAPACITOR} \end{cases}$$

2. If N contains only passive elements, then

$$P_{av} \geq 0 \quad \Rightarrow \quad \cos \angle Z \geq 0$$

$$\therefore \quad -90^\circ \leq \angle Z \leq 90^\circ \quad \text{for passive N}$$

Complex Power $P \triangleq \frac{1}{2} V \bar{I}$

$$P = \frac{1}{2} |V| e^{j\angle V} \cdot |I| e^{-j\angle I} = \frac{1}{2} |V| |I| e^{j(\angle V - \angle I)}$$

$$P = \underbrace{\left(\frac{1}{2} |V| |I| \cos \angle Z \right)}_{P_{av} \triangleq \text{Re } P} + j \underbrace{\left(\frac{1}{2} |V| |I| \sin \angle Z \right)}_{Q \triangleq \text{Im } P}$$

$$P_{av} \triangleq \text{Re } P$$

Active power

$$Q \triangleq \text{Im } P$$

Reactive power

\therefore

$$P_{av} = \text{Re} \left(\frac{1}{2} V \bar{I} \right) = \text{Average (Active) power}$$

$$Q = \text{Im} \left(\frac{1}{2} V \bar{I} \right) = \text{Reactive power}$$



in Watts

Effective (RMS) Value

Definition : Given any **periodic** waveform $x(t)$ of period T ,
the **RMS** (root-mean-square) or effective value of $x(t)$
is defined as

$$X_{RMS} \triangleq \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

Interpretation

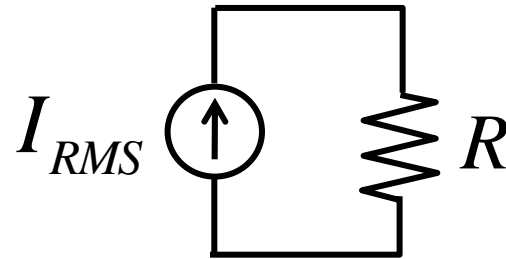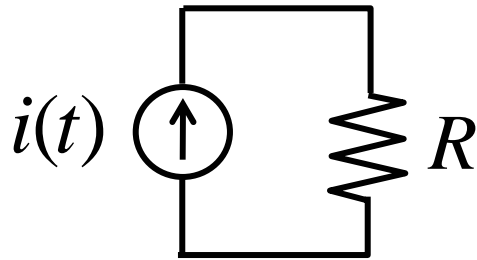

Let $W_R =$ average power dissipated in Resistor

$$W_R = \frac{1}{T} \int_0^T (Ri(t))(i(t)) dt = R \underbrace{\left(\frac{1}{T} \int_0^T i^2(t) dt \right)}_{I_{RMS}^2} = R I_{RMS}^2$$

\therefore The same average power is dissipated if the resistor is driven by a dc current source of value I_{RMS} ; hence I_{RMS} is called the effective value of $i(t)$.

Sinusoidal waveforms: $x(t) = |X| \cos(\omega t + \angle X)$

$$X_{RMS} = \frac{|X|}{\sqrt{2}}$$

Note:

1. Since most instruments measure RMS values; hence our 60Hz-sinusoidal voltages are rated in RMS values.

Example: Line voltage = 110V \Rightarrow magnitude = $\sqrt{2}(110)V$.

2.
$$P_{av} = \frac{|V|}{\sqrt{2}} \cdot \frac{|I|}{\sqrt{2}} \cos \angle Z = V_{RMS} I_{RMS} \cos \angle Z$$

Significance of Complex Power

Most electrical machines are designed to withstand a maximum voltage magnitude $|V|$ and a maximum current magnitude $|I|$. Hence, electrical machines are rated in maximum $|P| = \frac{1}{2} |V| |I|$ in *KVA*, and not in maximum average power dissipation P_{av} .

$$\text{Power factor } PF \triangleq \frac{P_{av}}{\frac{1}{2} |V| |I|} = \frac{|V| |I| \cos \angle Z}{|V| |I|}$$

$$\therefore \boxed{PF = \cos \angle Z}$$

$$PF = \begin{cases} 1 & \text{for Resistors} \\ 0 & \text{for INDUCTORS and CAPACITORS} \end{cases}$$

Note:

1. For power generation companies, it is important to keep the PF of the load (customers) be as close to unity as possible.
2. The *Watt-hour meter* measures P_{av} , **not** $|P|$.

Example: If a factory dissipates $10KW$ of power with 50% PF , then the power company must generate $20 KVA$ of power.

\therefore A penalty is usually levied for low PF customers.