

$$\text{Mesh 1: } 6\hat{i}_1 - 2\hat{i}_3 = 2 \quad (1)$$

$$\text{Mesh 2: } 14\hat{i}_2 - 8\hat{i}_3 = -2 \quad (2)$$

$$\text{Mesh 3: } -2\hat{i}_1 - 8\hat{i}_2 + 10\hat{i}_3 = 5 \quad (3)$$

$$\text{Solving } \hat{i}_1 \text{ from (1)} \Rightarrow \hat{i}_1 = \frac{1}{3}\hat{i}_3 - \frac{2}{3} \quad (4)$$


$$\text{Solving } \hat{i}_2 \text{ from (2)} \Rightarrow \hat{i}_2 = \frac{4}{7}\hat{i}_3 - \frac{1}{7} \quad (5)$$

Substituting (4) and (5) into (3) \Rightarrow

$$\hat{i}_3 = \frac{19}{12} \text{ A} \quad (6)$$

$$(5) \text{ and (6)} \Rightarrow \hat{i}_2 = \frac{8}{20} \text{ A} \quad (7)$$
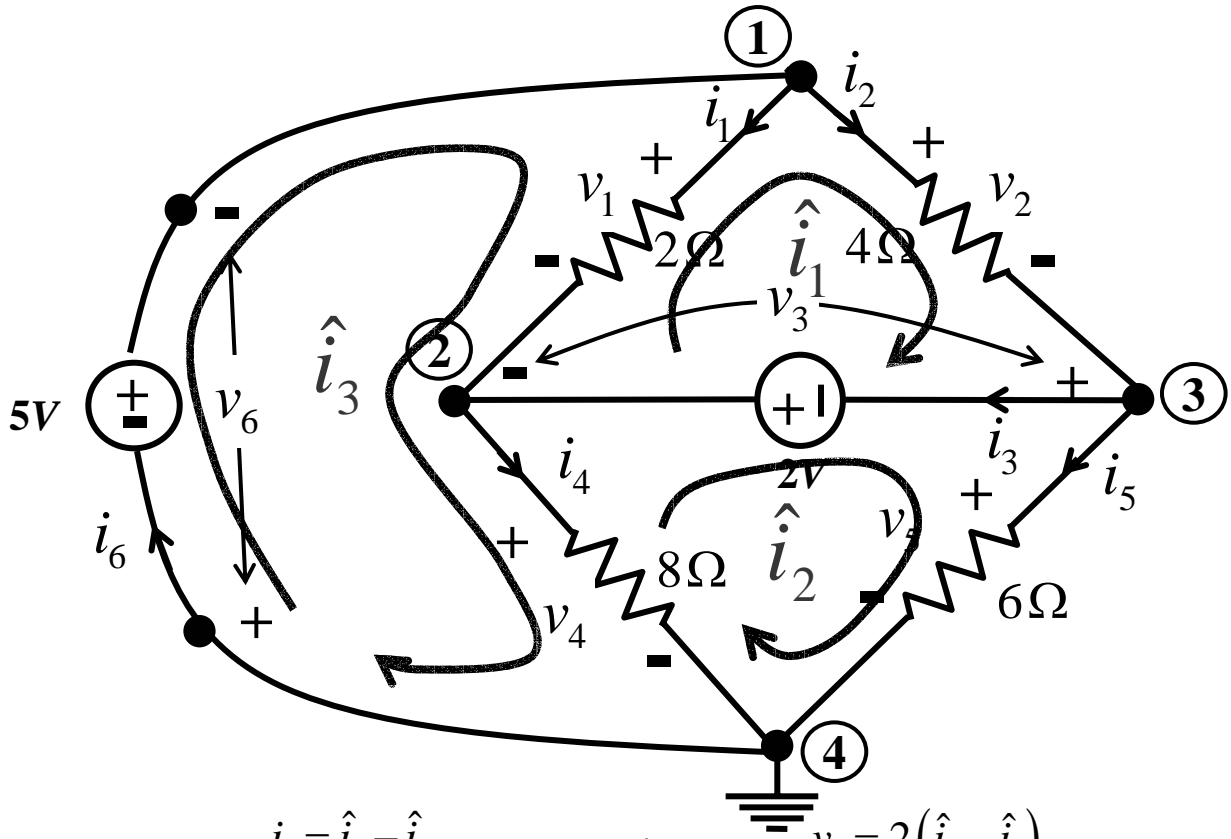
$$(4) \text{ and (6)} \Rightarrow \hat{i}_1 = \frac{13}{20} \text{ A} \quad (8)$$



$$\begin{array}{ll}
 i_1 = \hat{i}_3 - \hat{i}_1 & , \quad v_1 = 2(\hat{i}_3 - \hat{i}_1) \\
 i_2 = \hat{i}_1 & , \quad v_2 = 4\hat{i}_1 \\
 i_3 = \hat{i}_1 - \hat{i}_2 & , \quad v_3 = -2 \\
 i_4 = \hat{i}_3 - \hat{i}_2 & , \quad v_4 = 8(\hat{i}_3 - \hat{i}_2) \\
 i_5 = \hat{i}_2 & , \quad v_5 = 6\hat{i}_2 \\
 i_6 = \hat{i}_3 & , \quad v_6 = -5
 \end{array}$$

Loop equation around mesh 1:


$$\begin{aligned}
 -v_1 + v_2 + v_3 = 0 & \Rightarrow -2(\hat{i}_3 - \hat{i}_1) + 4\hat{i}_1 - 2 = 0 \\
 & \Rightarrow 6\hat{i}_1 - 2\hat{i}_3 = 2
 \end{aligned} \tag{1}$$

Loop equation around mesh 2:


$$\begin{aligned}
 -v_3 + v_5 - v_4 = 0 & \Rightarrow -(-2) + 6\hat{i}_2 - 8(\hat{i}_3 - \hat{i}_2) = 0 \\
 & \Rightarrow 14\hat{i}_2 - 8\hat{i}_3 = -2
 \end{aligned} \tag{2}$$

Loop equation around mesh 3:
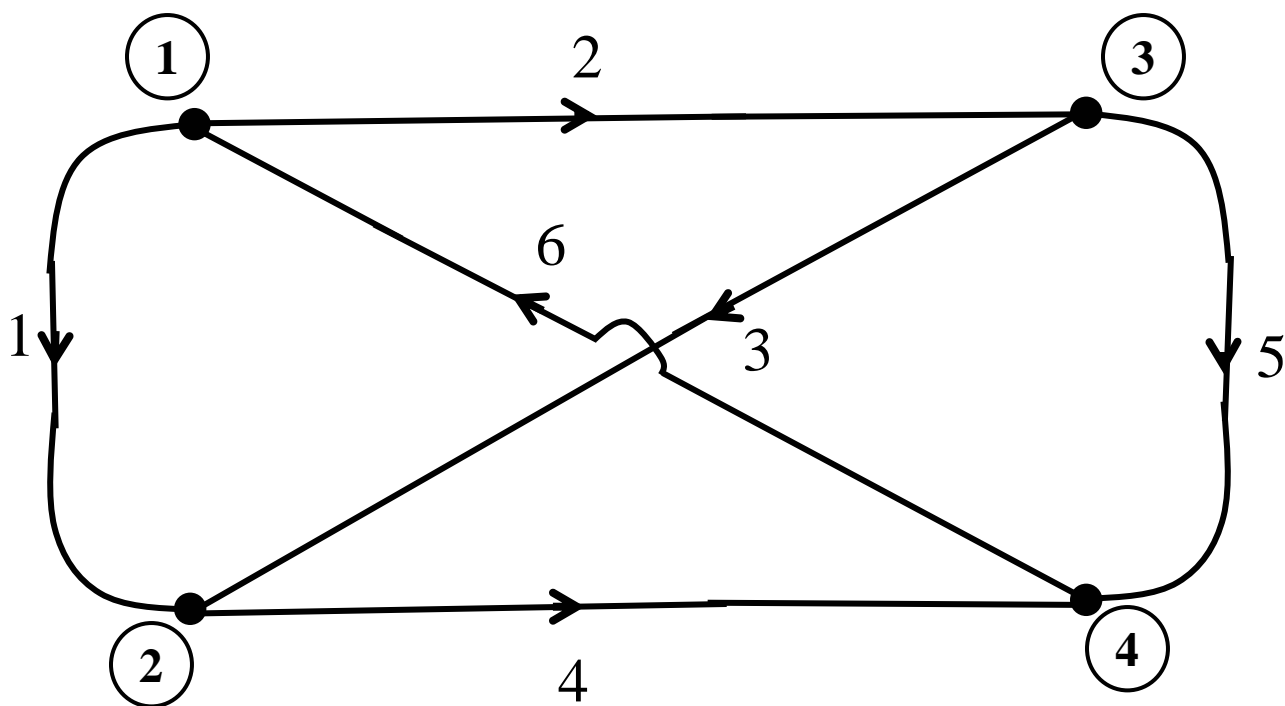
$$\begin{aligned}
 v_6 + v_1 + v_4 = 0 & \Rightarrow -5 + 2(\hat{i}_3 - \hat{i}_1) + 8(\hat{i}_3 - \hat{i}_2) = 0 \\
 & \Rightarrow -2\hat{i}_1 - 8\hat{i}_2 + 10\hat{i}_3 = 5
 \end{aligned} \tag{3}$$



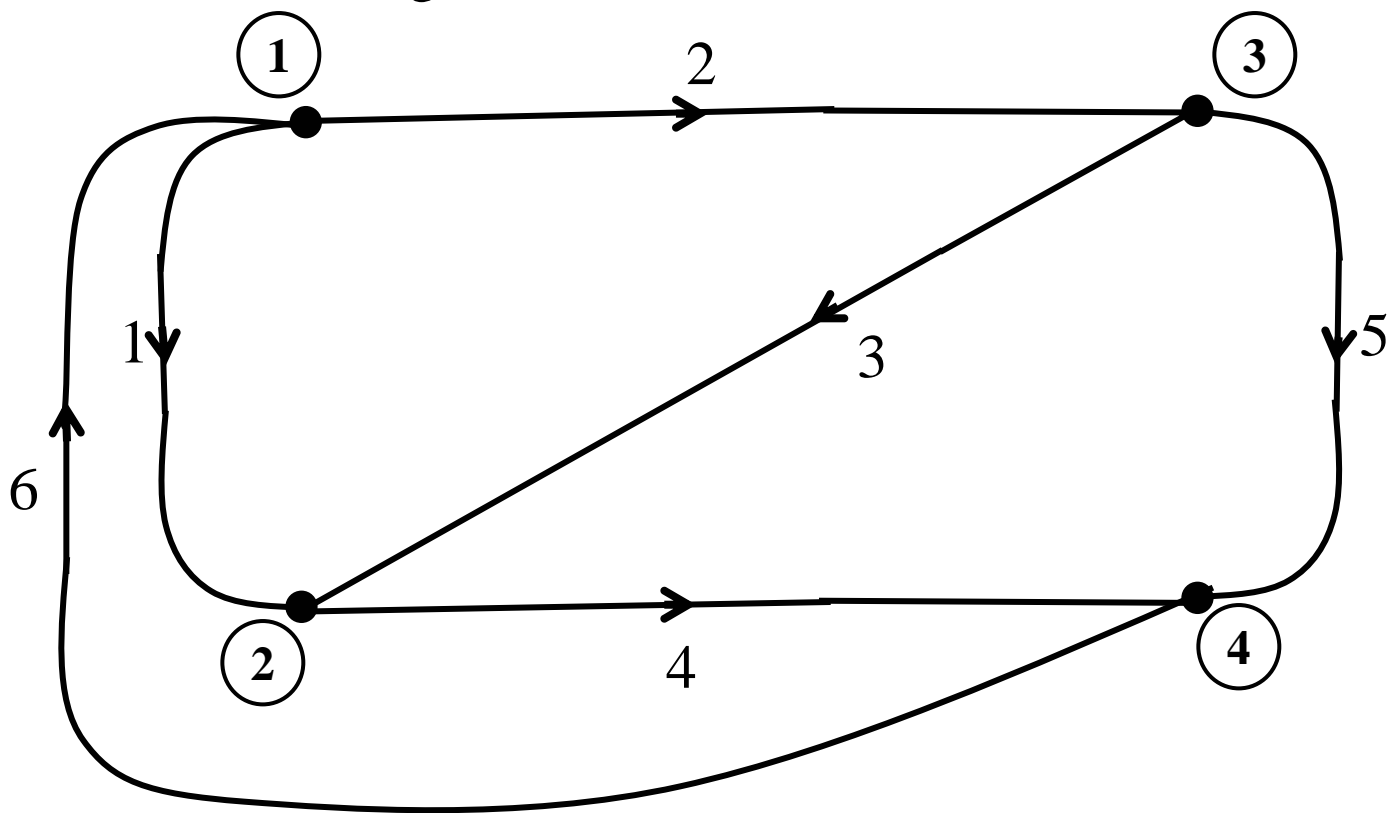We can redraw this digraph so that there are no intersecting branches.



Hence the above digraph is **planar**.

Writing Node-Admittance Matrix \mathbf{Y}_n By Inspection

Node – Voltage Equation :

$$\underbrace{\begin{bmatrix} Y_{11} & Y_{12} & \cdots & Y_{1,n-1} \\ Y_{21} & Y_{22} & \cdots & Y_{2,n-1} \\ \vdots & \vdots & \cdots & \vdots \\ Y_{n-1,1} & Y_{n-1,2} & \cdots & Y_{n-1,n-1} \end{bmatrix}}_{\mathbf{Y}_n} \underbrace{\begin{bmatrix} e_1 \\ e_2 \\ \vdots \\ e_{n-1} \end{bmatrix}}_{\mathbf{e}} = \underbrace{\begin{bmatrix} i_{s_1} \\ i_{s_2} \\ \vdots \\ i_{s_{n-1}} \end{bmatrix}}_{\mathbf{i}_s} \quad (8)$$

where

$i_{s_j} = -$ (algebraic sum of all current sources leaving node (j))

Diagonal Elements of \mathbf{Y}_n

Y_{mm} = sum of admittances $Y_j \triangleq \frac{1}{R_j}$ of all resistors connected to node (m) , $m = 1, 2, \dots, n-1$, where n is the total number of nodes.

\mathbf{Y}_n is called the node-admittance matrix.

\mathbf{e} is the node-to-datum voltage vector.

\mathbf{i}_s is called the node current source vector.

Off-Diagonal Elements of \mathbf{Y}_n

$Y_{jk} = -$ (sum of admittances $Y_j \triangleq \frac{1}{R_j}$ of all resistors connected across node (j) and node (k))

Symmetry Property:

\mathbf{Y}_n is a symmetric matrix, i.e.,

$$\boxed{Y_{jk} = Y_{kj}}$$

Proof :

Since \mathbf{Y}_b in (1) is a diagonal matrix,

$$\mathbf{Y}_b = \mathbf{Y}_b^T$$

$$\begin{aligned}\mathbf{Y}_n^T &= \left(\mathbf{A} \mathbf{Y}_b \mathbf{A}^T \right)^T \\ &= \mathbf{A} \mathbf{Y}_b^T \mathbf{A}^T \\ &= \mathbf{A} \mathbf{Y}_b \mathbf{A}^T \\ &= \mathbf{Y}_n \quad \blacksquare\end{aligned}$$

Writing Mesh-Impedance Matrix \mathbf{Z}_m By Inspection

Let m be the total number of meshes of a planar digraph G , including the exterior mesh formed by traversing the outer boundary branches (i.e., those branches having only one circulating current \hat{i}_j passing through them). Hence,

$$m = \text{number of interior meshes (windows)} + 1$$

Mesh-Current Equation :

$$\underbrace{\begin{bmatrix} Z_{11} & Z_{12} & \cdots & Z_{1,m-1} \\ Z_{21} & Z_{22} & \cdots & Z_{2,m-1} \\ \vdots & \vdots & \cdots & \vdots \\ Z_{m-1,1} & Z_{m-1,2} & \cdots & Z_{m-1,m-1} \end{bmatrix}}_{\mathbf{Z}_m} \underbrace{\begin{bmatrix} \hat{i}_1 \\ \hat{i}_2 \\ \vdots \\ \hat{i}_{m-1} \end{bmatrix}}_{\hat{\mathbf{i}}} = \underbrace{\begin{bmatrix} v_{s_1} \\ v_{s_2} \\ \vdots \\ v_{s_{m-1}} \end{bmatrix}}_{\mathbf{v}_s} \quad (1)$$

where

$$v_{s_j} = - (\text{clockwise algebraic sum of all voltage sources around mesh } j)$$

Diagonal Elements of \mathbf{Z}_m

$$Z_{kk} = \text{sum of impedances } Z_j \triangleq R_j \text{ of all resistors located along mesh "k", } k=1, 2, \dots, m-1, \text{ where } m \text{ is the total number of (interior and exterior) meshes.} \quad (2)$$

\mathbf{Z}_m is called the mesh-impedance matrix.

$\hat{\mathbf{i}}$ is called the mesh-current vector.

\mathbf{v}_s is called the mesh-voltage source vector.


Off-Diagonal Elements of \mathbf{Z}_m

$$Z_{jk} = - (\text{sum of impedances } Z_j \triangleq R_j \text{ of all resistors along both mesh } j \text{ and mesh } k) \quad (3)$$

Symmetry Property:

$$\mathbf{Z}_m \text{ is a symmetric matrix, i.e., } Z_{jk} = Z_{kj} \quad (4)$$

Extended Mesh Current Method

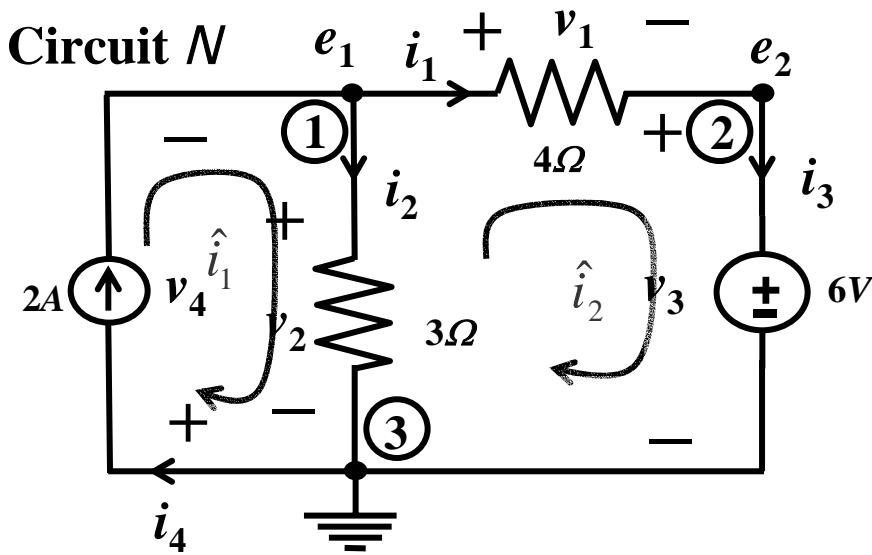

$$v_1 = 4\hat{i}_2$$

$$v_2 = 3(\hat{i}_1 - \hat{i}_2)$$

Step 1.

When the circuit contains " β " current sources $i_{s_1}, i_{s_2}, \dots, i_{s_\beta}$, use their associated voltages $v_{s_1}, v_{s_2}, \dots, v_{s_\beta}$ when applying KVL.

$$\text{KVL around mesh 1:} \quad 3(\hat{i}_1 - \hat{i}_2) + v_4 = 0 \quad (1)$$

$$\text{KVL around mesh 2:} \quad -3(\hat{i}_1 - \hat{i}_2) + 4\hat{i}_2 = -6 \quad (2)$$

Step 2.

For each current source i_{s_j} , add an equation $i_{s_j}^+ - i_{s_j}^- = i_{s_j}$.

$$\hat{i}_1 = 2 \quad (3)$$

Step 3.

Solve the $(m-1) + \beta$ equations for $\hat{i}_1, \hat{i}_2, \dots, \hat{i}_{m-1}, v_{s_1}, v_{s_2}, \dots, v_{s_\beta}$.
Substituting (3) into (2), we obtain :

$$-3(2 - \hat{i}_2) + 4\hat{i}_2 = -6 \Rightarrow \boxed{\hat{i}_2 = 0} \quad (4)$$

Substituting (3) and (4) into (1), we obtain :

$$3(2 - 0) + v_4 = 0 \Rightarrow \boxed{v_4 = -6V} \quad (5)$$

Note:

The unknown variables in the extended mesh current method consist of the usual $m-1$ mesh currents, plus the unknown voltages associated with the current sources.

Hence, if there are “ β ” current sources, the extended mesh current method would consist of $(m-1)+\beta$ independent linear equations involving $(m-1)+\beta$ unknown variables

$$\left\{ \underbrace{\hat{i}_1, \hat{i}_2, \dots, \hat{i}_{m-1}}_{(m-1) \text{ mesh current variables}}, \underbrace{V_{s_1}, V_{s_2}, \dots, V_{s_\beta}}_{\beta \text{ voltage variables}} \right\}.$$

$(m-1)$ mesh
current variables

β voltage
variables

All branch voltages and currents can be trivially calculated from \hat{i}_2 and v_4 .

$$i_1 = \hat{i}_2 = 0 \text{ A} , \quad v_1 = 4 i_1 = 0 \text{ V}$$

$$i_2 = \hat{i}_2 - \hat{i}_1 = 2 \text{ A} , \quad v_2 = 3 i_2 = 6 \text{ V}$$


$$i_3 = \hat{i}_2 = 0 \text{ A} , \quad v_3 = 6 \text{ V}$$

$$i_4 = \hat{i}_1 = 2 \text{ A} , \quad v_4 = -6 \text{ V}$$

Verification of Solution by Tellegen's Theorem :

$$\begin{aligned} \sum_{j=1}^4 v_j i_j &= (v_1 i_1) + (v_2 i_2) + (v_3 i_3) + (v_4 i_4) \\ &= (0)(0) + (6)(2) + (6)(0) + (-6)(2) \\ & \quad ? \\ &= 0 \end{aligned}$$

Extended Node Voltage Method

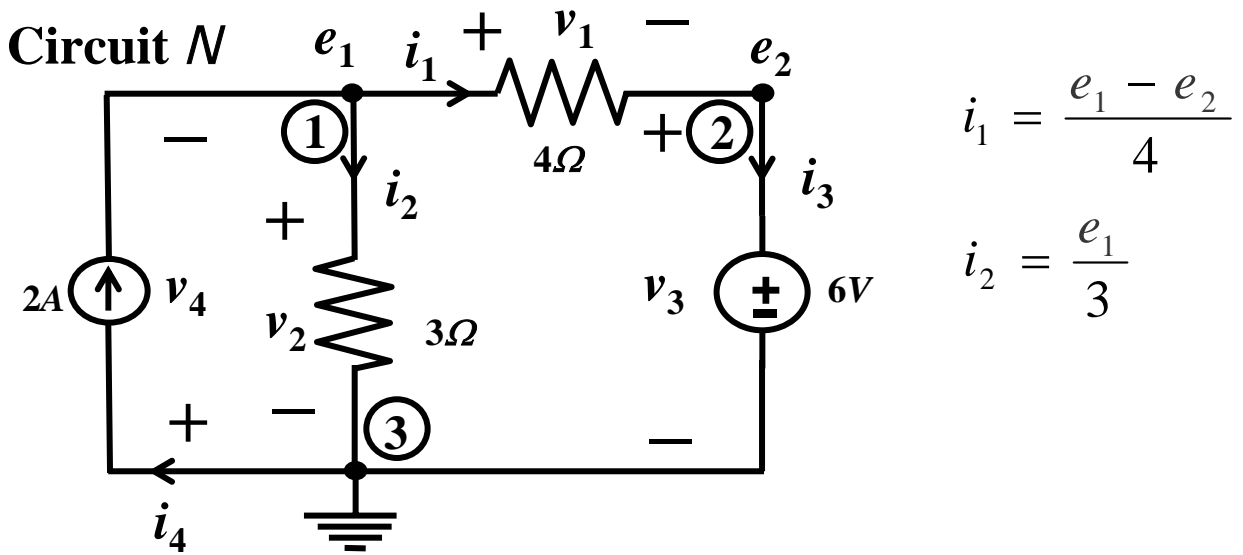

Step 1.

When the circuit contains " α " voltages $v_{s_1}, v_{s_2}, \dots, v_{s_\alpha}$, use their associated currents $i_{s_1}, i_{s_2}, \dots, i_{s_\alpha}$ when applying KCL.

$$\text{KCL at } \textcircled{1} : \quad \frac{e_1}{3} + \frac{(e_1 - e_2)}{4} = 2 \quad (1)$$

$$\text{KCL at } \textcircled{2} : \quad -\frac{(e_1 - e_2)}{4} + i_3 = 0 \quad (2)$$

Step 2.

For each voltage source v_{s_j} , add an equation $e_j^+ - e_j^- = v_{s_j}$.

$$e_2 = 6 \quad (3)$$

Step 3.

Solve the $(n-1) + \alpha$ equations for $e_1, e_2, \dots, e_{n-1}, i_{s_1}, i_{s_2}, \dots, i_{s_\alpha}$.

Substituting (3) into (1), we obtain :

$$\frac{e_1}{3} + \frac{(e_1 - 6)}{4} = 2 \Rightarrow \boxed{e_1 = 6V} \quad (4)$$

Substituting (4) into (2), we obtain :

$$\boxed{i_3 = 0} \quad (5)$$

Note:

The unknown variables in the extended node voltage method consist of the usual $n-1$ node-to-datum voltages, plus the unknown currents associated with the voltage sources.

Hence, if there are “ α ” voltage sources, the modified node voltage method would consist of $(n-1)+\alpha$ independent linear equations involving $(n-1)+\alpha$ unknown variables

$$\left\{ \underbrace{e_1, e_2, \dots, e_{n-1}}_{(n-1) \text{ node-to-datum voltage variables}}, \underbrace{i_{s_1}, i_{s_2}, \dots, i_{s_\alpha}}_{\alpha \text{ current variables}} \right\}.$$

$(n-1)$ node-to-datum
voltage variables

α current
variables

Sufficient Condition for G to be Planar

If G has less than 9 branches, it is planar.


Proof.

The 2 basic nonplanar graphs have 9 and 10 branches, respectively.

Mapping a planar digraph on a sphere

A digraph G is **planar** if, and only if, it can be drawn on the surface of a sphere such that G can be partitioned into contiguous regions and colored (as in a map of countries) such that no two regions have overlapping colors.


Mapping a planar digraph on a sphere

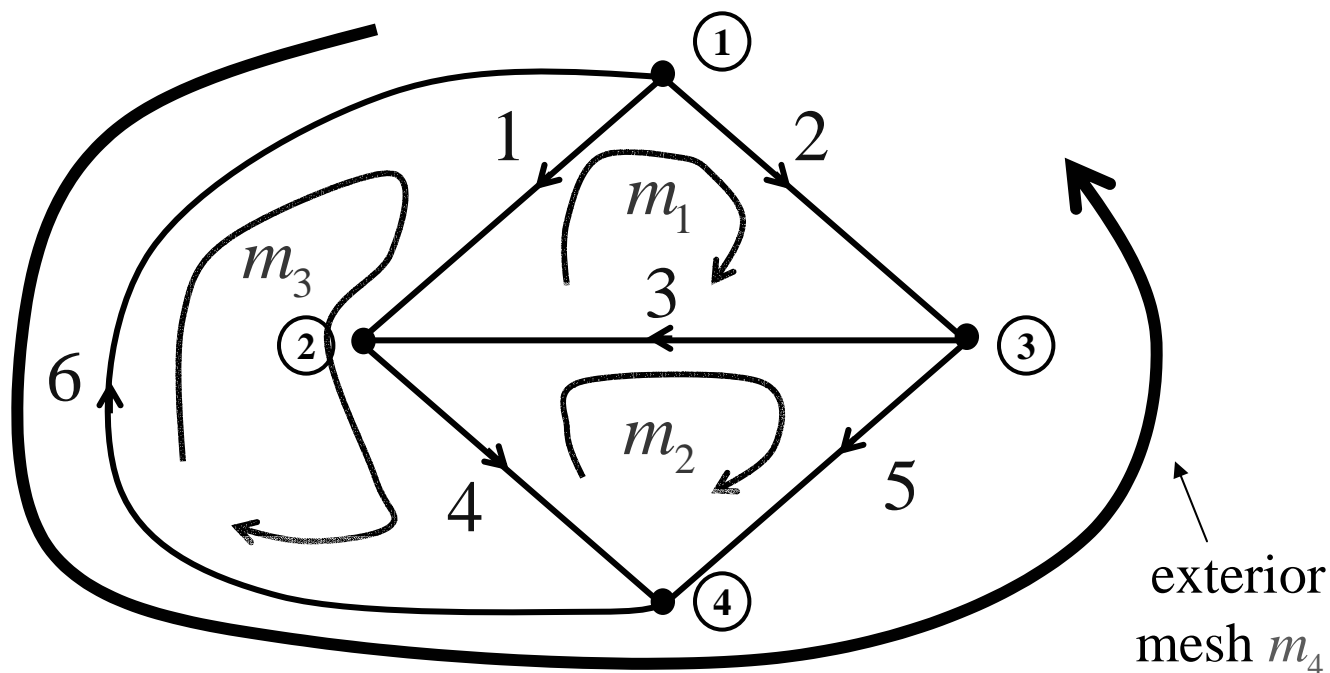

m_1 , m_2 , and m_3 are **interior clockwise meshes**.



We can always redraw a **planar** digraph on the surface of a **sphere** without interior branches and vice-versa, as illustrated below.

- Although mesh m_3 (formed by tracing along branches {1, 4, 6} in the above planar digraph in a clockwise direction) appears to be **counterclockwise** on the sphere, it actually moves in a clockwise direction when viewed from behind.
- Although the counterclockwise loop m_4 formed by **exterior** branches (i.e, boundary branches with only 1 circulating current) {6, 5, 2} does not look like a mesh on the planar digraph, it is in fact a **clockwise** mesh when the digraph is mapped on the surface of a sphere.

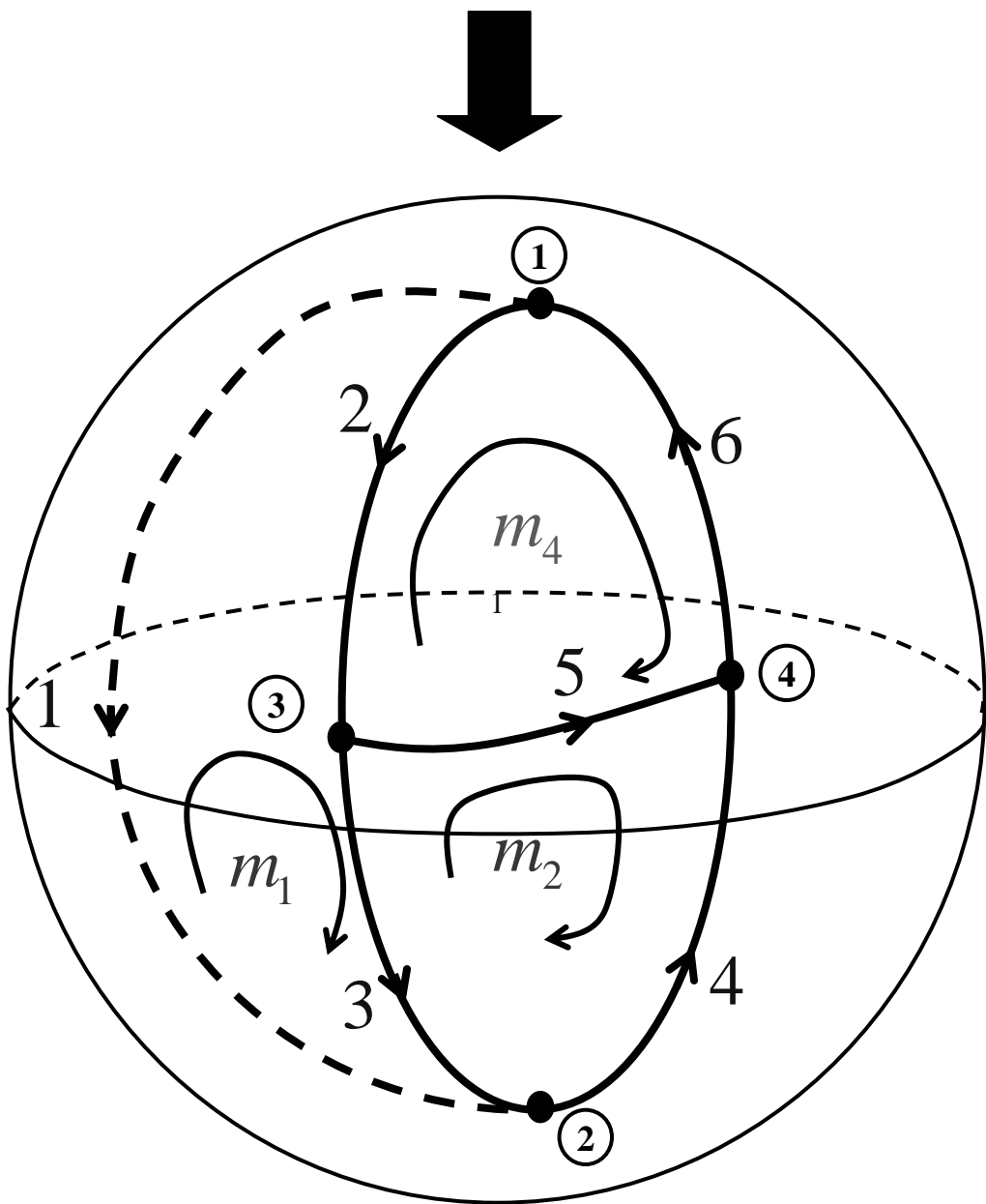

Just as all countries on a **globe** can be mapped onto a flat plane of paper, any **planar** digraph drawn on a **sphere** can always be redrawn as a **planar** digraph on a plane.

Mapping a planar digraph on a sphere

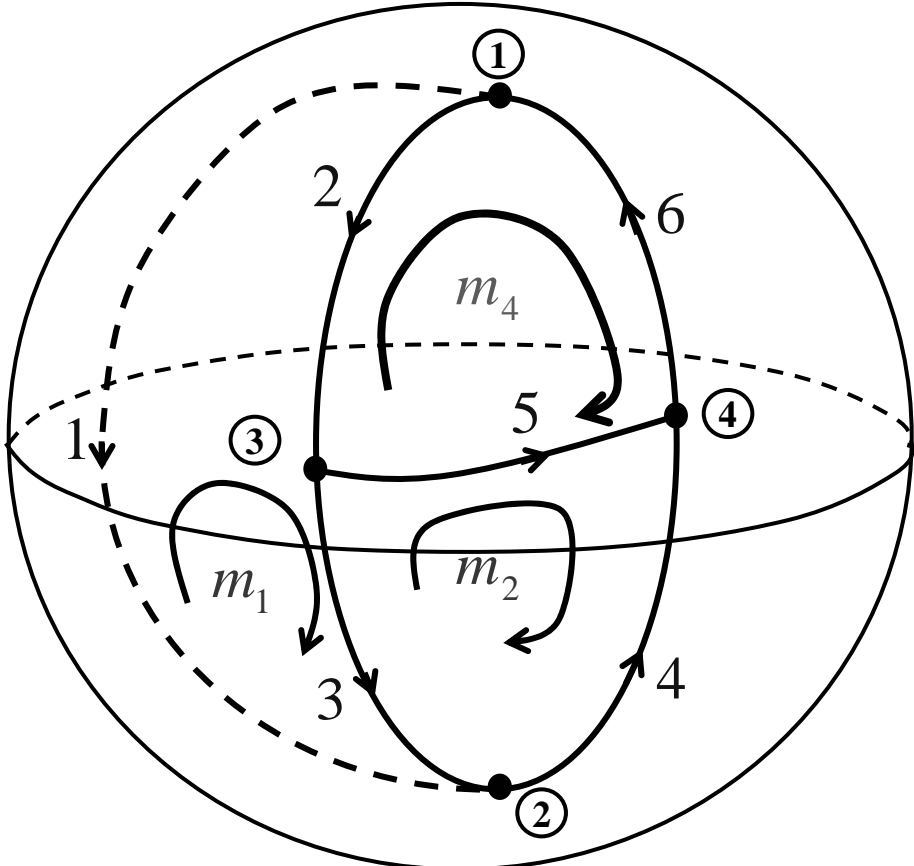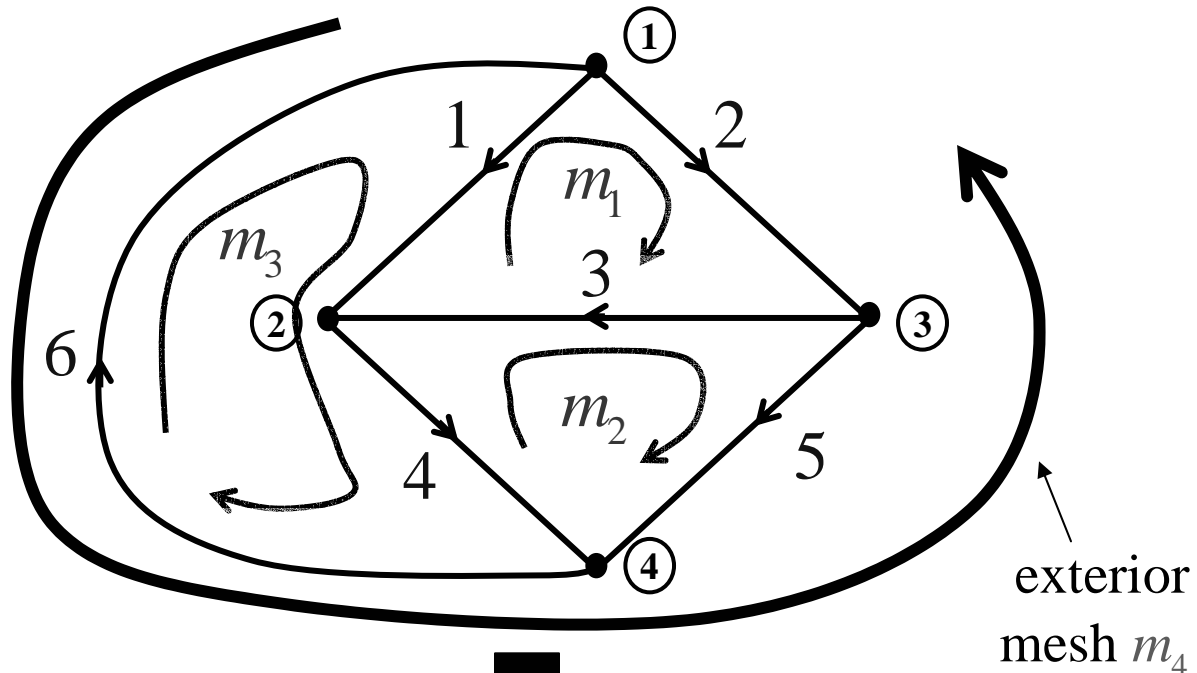


Duality Principle

There are many physical variables, concepts, properties, and theorems in electrical circuit theory which appear in pairs, henceforth called **dual pairs**, such that for each circuit theorem, property, concept, etc., there is a **dual theorem**, **dual property**, and **dual concept**, respectively. This duality principle is extremely useful since we only need to learn and memorize half of them!

Variable, concept, property	Dual variable, concept, property
<p style="text-align: center;"> KVL KCL Voltage Current Series Parallel Resistance (Ohms) Impedance Admittance Node (non-datum) Node voltage Datum node </p>	<p style="text-align: center;"> KCL KVL Current Voltage Parallel Series Conductance (Siemens) Admittance Impedance Mesh (interior) Mesh current Exterior mesh </p>

Example of Duality

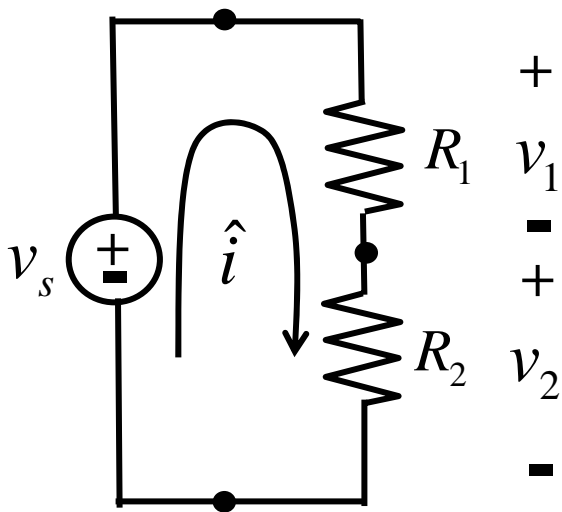


series circuit

$$\text{KVL} : (R_1 + R_2) \hat{i} = v_s$$

voltage divider:
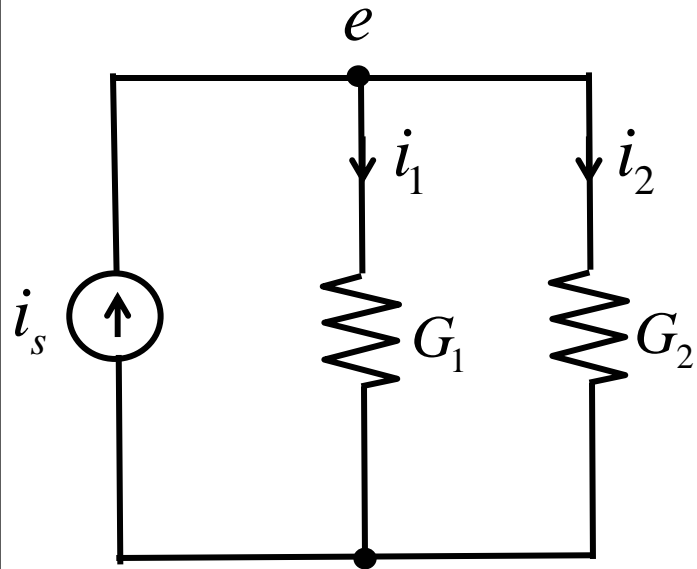
$$v_2 = \left(\frac{R_2}{R_1 + R_2} \right) v_s$$



parallel circuit

$$\text{KCL} : (G_1 + G_2) e = i_s$$

current divider:

$$i_2 = \left(\frac{G_2}{G_1 + G_2} \right) i_s$$

Duality Theorem

For planar circuits, the **node-voltage method** and the **mesh-current method**, as well as their extended versions, are dual sets of equations which can be derived from each other via their **dual** variables.

Node-voltage Equation $\mathbf{Y}_n \mathbf{e} = \mathbf{i}_s$	Mesh-current equation $\mathbf{Z}_m \hat{\mathbf{i}} = \mathbf{v}_s$
Node-Admittance matrix \mathbf{Y}_n	Mesh-Impedance matrix \mathbf{Z}_m